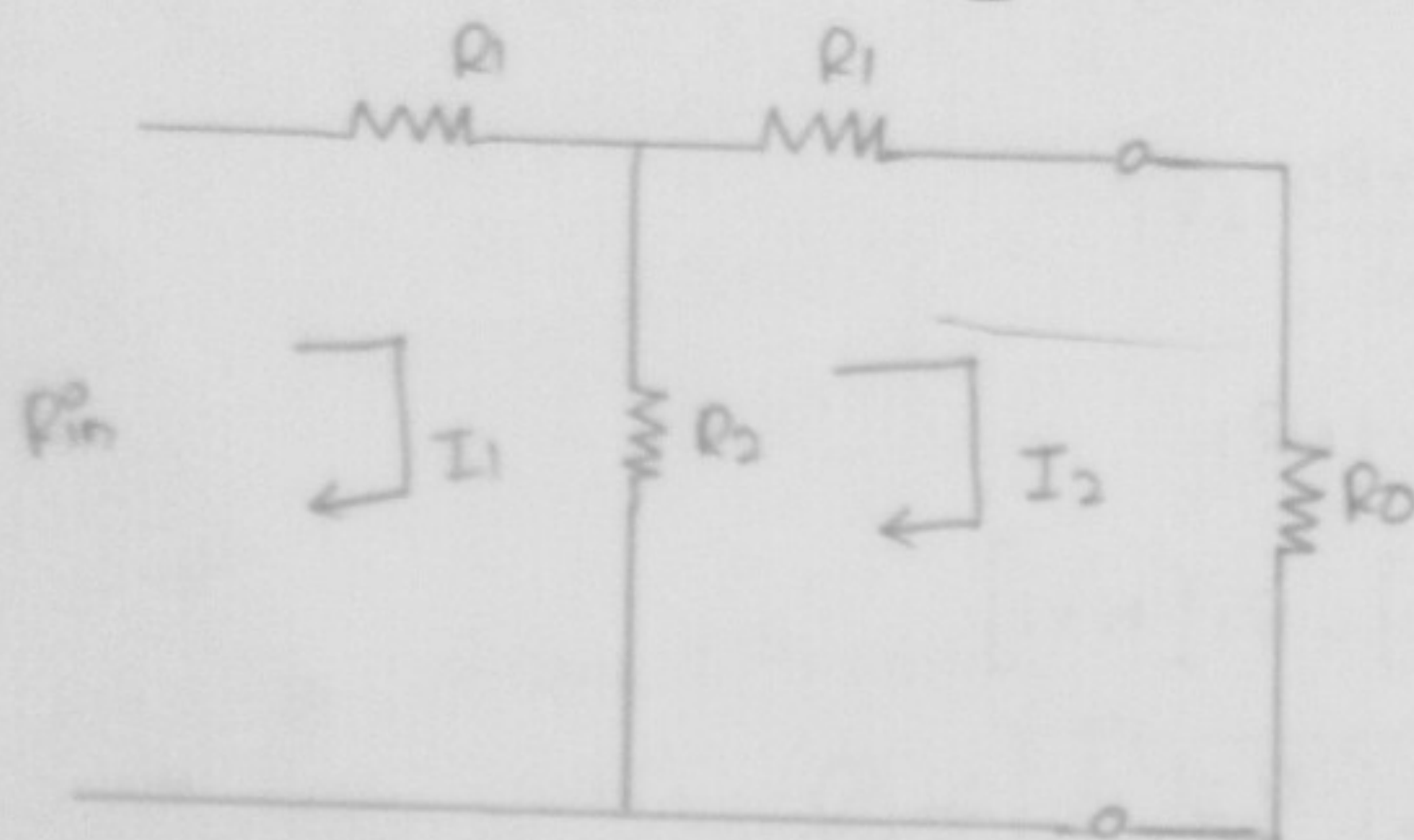


- 1 explain a T-type attenuator and also design a T-type attenuator to give an attenuation of 60 dB and to work in a line of 500Ω impedance.

Symmetrical T-type attenuator



It is an attenuator whose structure look like a T symbol with equal series arm resistance. The symmetrical T attenuator is shown in above fig.

Let R_0 be the characteristic resistance of the attenuator

we have $\frac{I_1}{I_2} = N$

Apply KVL to loop 2 we have

$$R_1 I_2 + R_0 I_2 + R_2 [I_2 - I_1] = 0$$

$$I_2 [R_1 + R_0 + R_2] = R_2 I_1$$

$$\frac{I_1}{I_2} = \frac{R_1 + R_0 + R_2}{R_2} = N \quad \text{--- ①}$$

$$R_{in} = [R_1 + R_0] \parallel R_2 + R_1$$

(2)

$$\Rightarrow \frac{[R_1 + R_0] R_2}{R_1 + R_0 + R_2} + R_1$$

For a symmetrical attenuator $R_{in} = R_0$

$$R_0 = \frac{[R_1 + R_0] R_2}{R_1 + R_0 + R_2} + R_1$$

$$R_0 = \frac{R_1 + R_0}{N} + R_1$$

$$NR_0 = R_1 + R_0 + NR_1$$

$$R_0[N-1] = R_1[N+1]$$

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right] \quad \text{--- (3)}$$

From (1)

$$R_1 + R_2 + R_0 = NR_2$$

$$R_2[N-1] = R_1 + R_0$$

$$R_2[N-1] = R_0 \left[\frac{N-1}{N+1} \right] + R_0$$

$$\Rightarrow R_0 \left[\frac{N-1}{N+1} + \frac{N+1}{N+1} \right]$$

$$R_2[N-1] = R_0 \left[\frac{2N}{N+1} \right]$$

$$R_2 = R_0 \left[\frac{2N}{N^2-1} \right]$$

Given data

attenuation in dB = 60

2

$$R_0 = 500 \Omega$$

$$N = \text{antilog} \left[\frac{\text{dB}}{20} \right]$$

$$N = 10^{\left[\frac{\text{dB}}{20} \right]}$$
$$= 10^{\left[\frac{60}{20} \right]}$$

$$N = 10^3 = 1000$$

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right]$$

$$= 500 \left[\frac{1000-1}{1000+1} \right]$$

$$= 500 \times 0.998001$$

$$= 499.000999$$


$$R_2 = R_0 \left[\frac{2N}{N^2-1} \right]$$

$$= 500 \left[\frac{2 \times 1000}{(1000)^2-1} \right]$$


$$R_2 = 1.00 \Omega$$

$$499.000999 \Omega$$

$$499.000999 \Omega$$

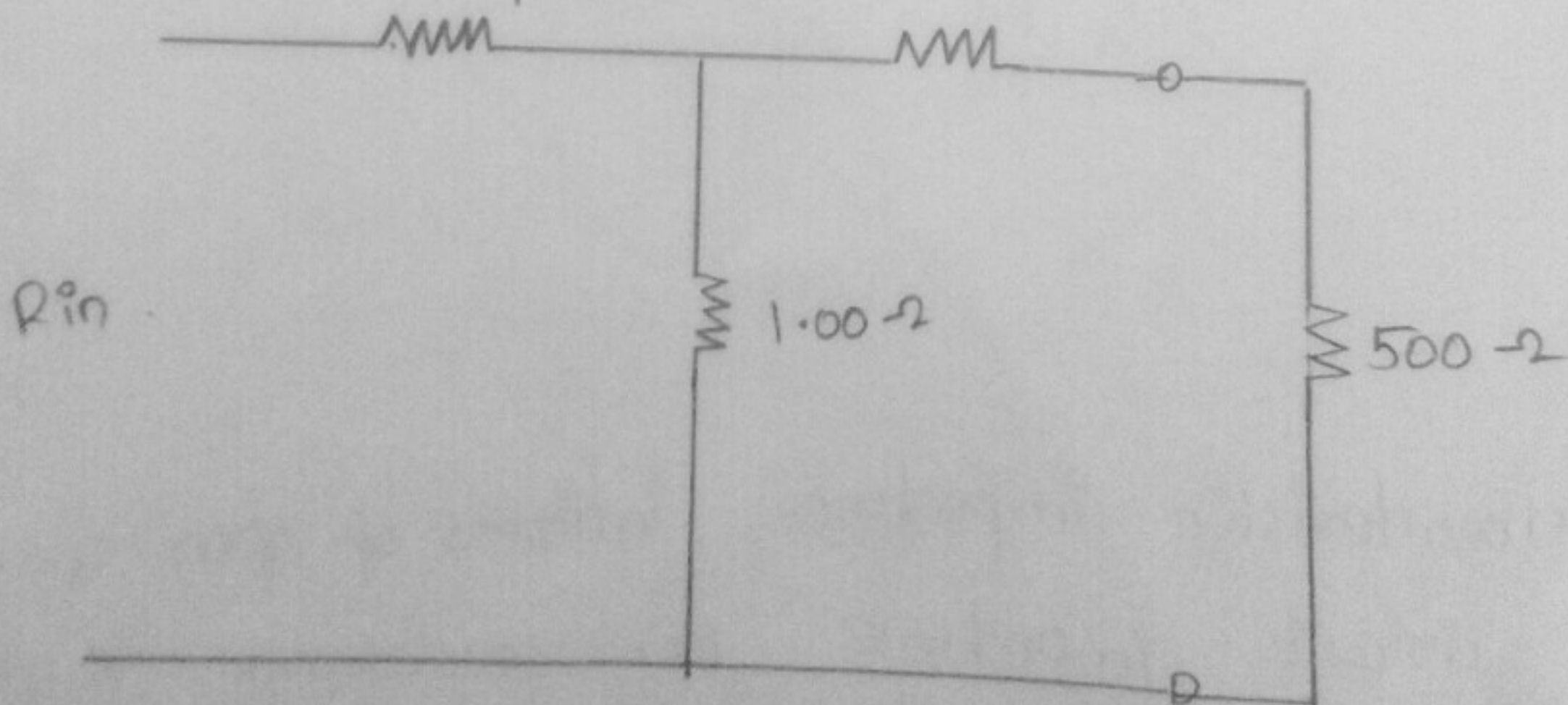

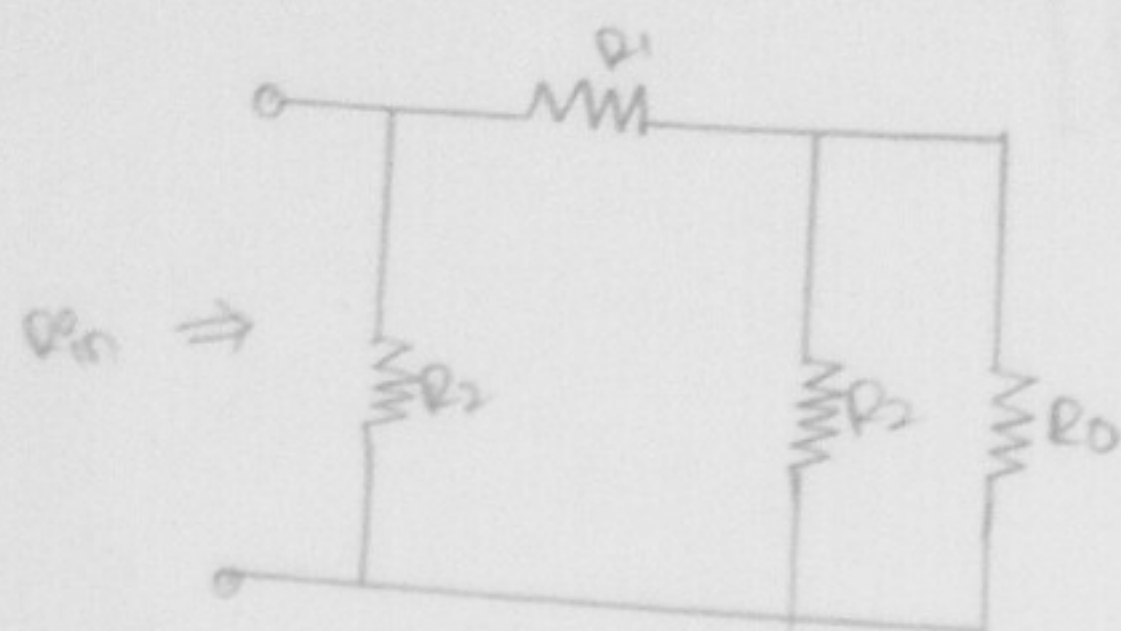- 3) explain π -type attenuator and also design it to gain 20 dB attenuation and to have characteristic impedance of 100Ω



It is an attenuator whose structure look like π -symbol with equal shunt arm resistance R_2 . A symmetrical π -configuration is shown in above fig.

From the propagation constant we have

$$\gamma = \alpha + j\beta = \ln \left[\frac{I_1}{I_2} \right]$$

From the above eqn we have

$$\frac{I_1}{I_2} = e^{\gamma} = N$$

As attenuator is purely resistive we have $\gamma = \alpha$

$$e^{\gamma} = e^{\alpha}$$

From the basics we have R_1 and R_2

$$R_1 = R_0 \sinh \alpha \quad \text{---(1)}$$

$$R_2 = R_0 \coth \frac{\alpha}{2} \quad \text{---(2)}$$

$$R_1 = R_0 \left[\frac{e^{\alpha} - e^{-\alpha}}{2} \right]$$

$$\Rightarrow R_0 \left[\frac{e^{2\alpha} - 1}{2e^{\alpha}} \right]$$

$$R_1 = R_0 \left[\frac{N^2 - 1}{2N} \right]$$

$$R_2 = R_0 \left[\frac{\cosh \alpha/2}{\sinh \alpha/2} \right]$$

$$= R_0 \left[\frac{e^{\alpha/2} + e^{-\alpha/2}}{e^{\alpha/2} - e^{-\alpha/2}} \right]$$

$$= R_0 \left[\frac{e^{\alpha} + 1}{e^{\alpha} - 1} \right]$$

$$\boxed{R_2 = R_0 \left[\frac{N+1}{N-1} \right]}$$

(5)

Given data

$$\text{dB} = 20$$

$$R_0 = 100 \, \Omega$$

$$N = 10 \left[\frac{\text{dB}}{20} \right]$$

$$= 10 \left[\frac{20}{20} \right]$$

$$N = 10$$

$$R_1 = R_0 \left[\frac{N^2 - 1}{2N} \right]$$

$$= 100 \left[\frac{10^2 - 1}{20} \right]$$


$$= 100 \left[\frac{99}{20} \right] = 495 \, \Omega$$

$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$

$$= 100 \left[\frac{10+1}{10-1} \right]$$


$$= 100 \left[\frac{11}{9} \right]$$

$$= 122.22 \, \Omega$$

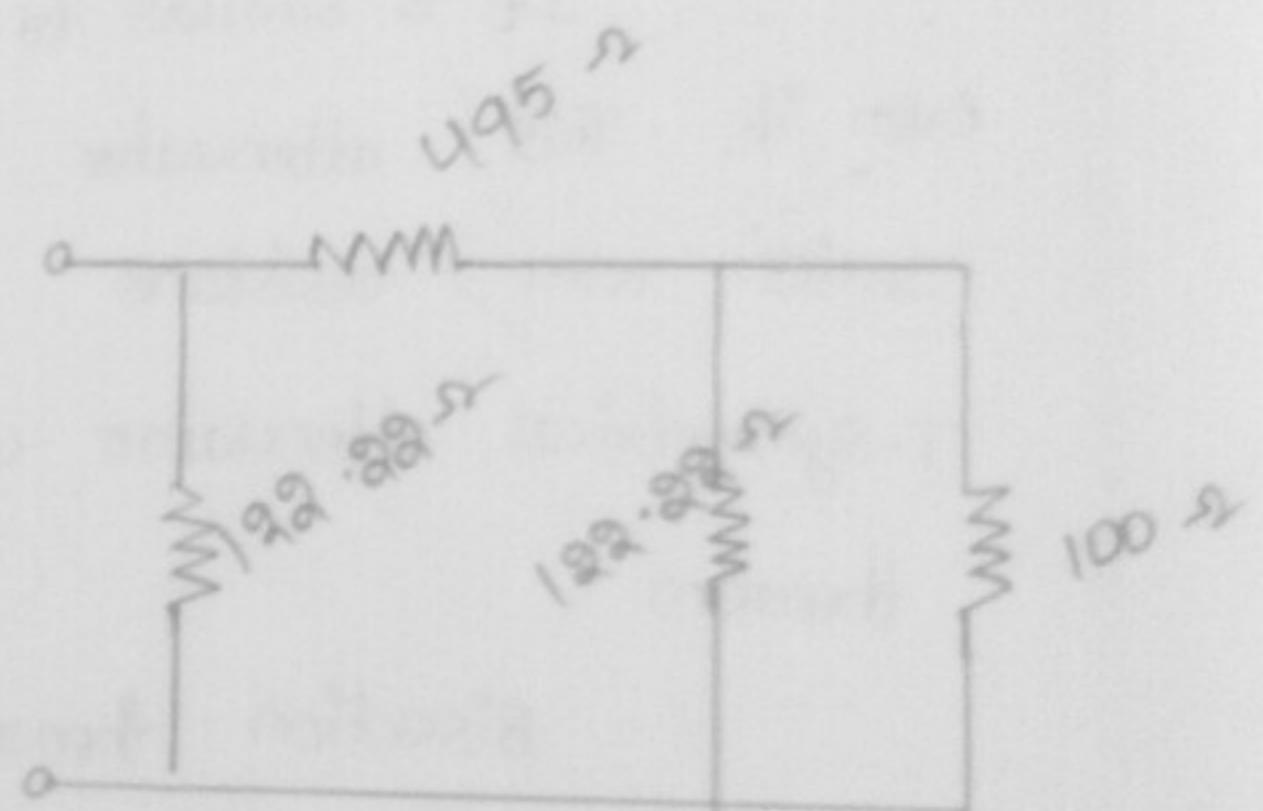


2) Explain the lattice attenuator and also design a lattice attenuator to have a characteristic impedance of $800\ \Omega$ and attenuation of 20dB .

(b)

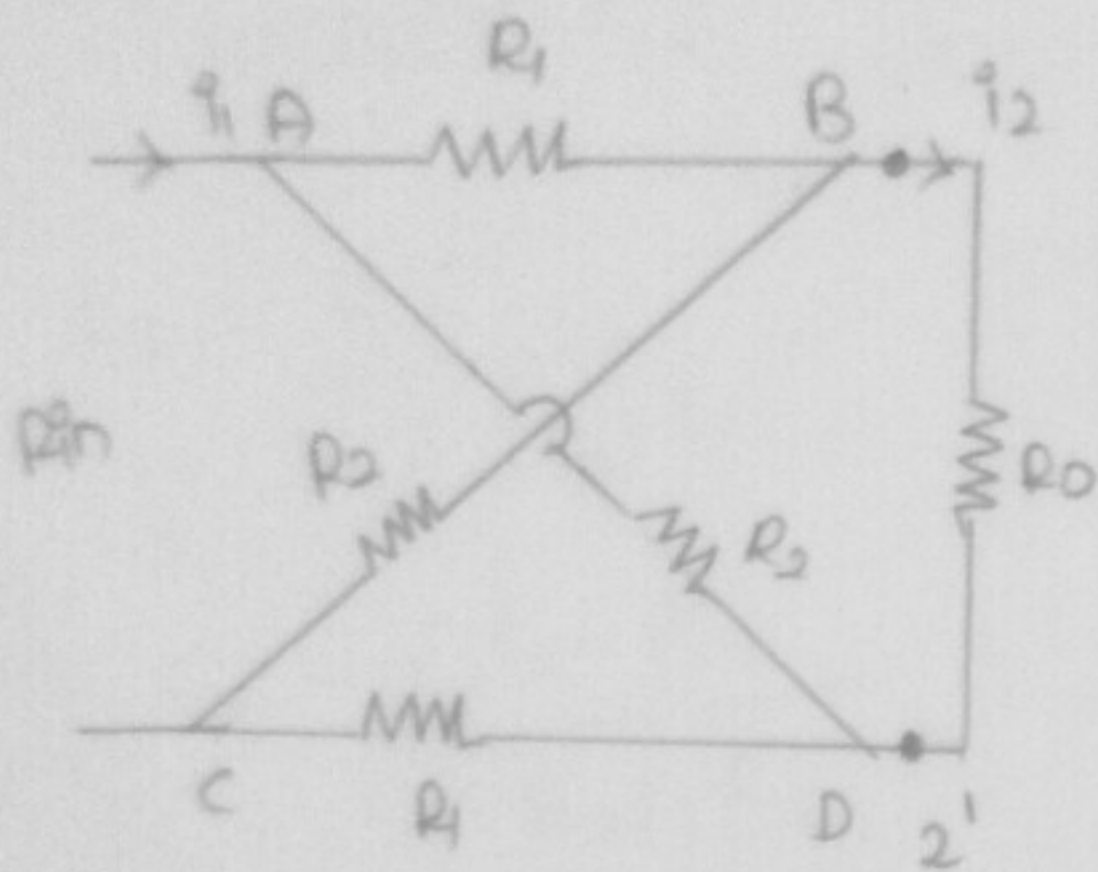

A attenuator is said to be a lattice attenuator if it consists of two series arm impedance two diagonal arm impedance. A lattice attenuator is said to be symmetrical lattice attenuator when its series arm impedance are equal and diagonal arm impedance are equal. A lattice attenuator is as shown in figure.

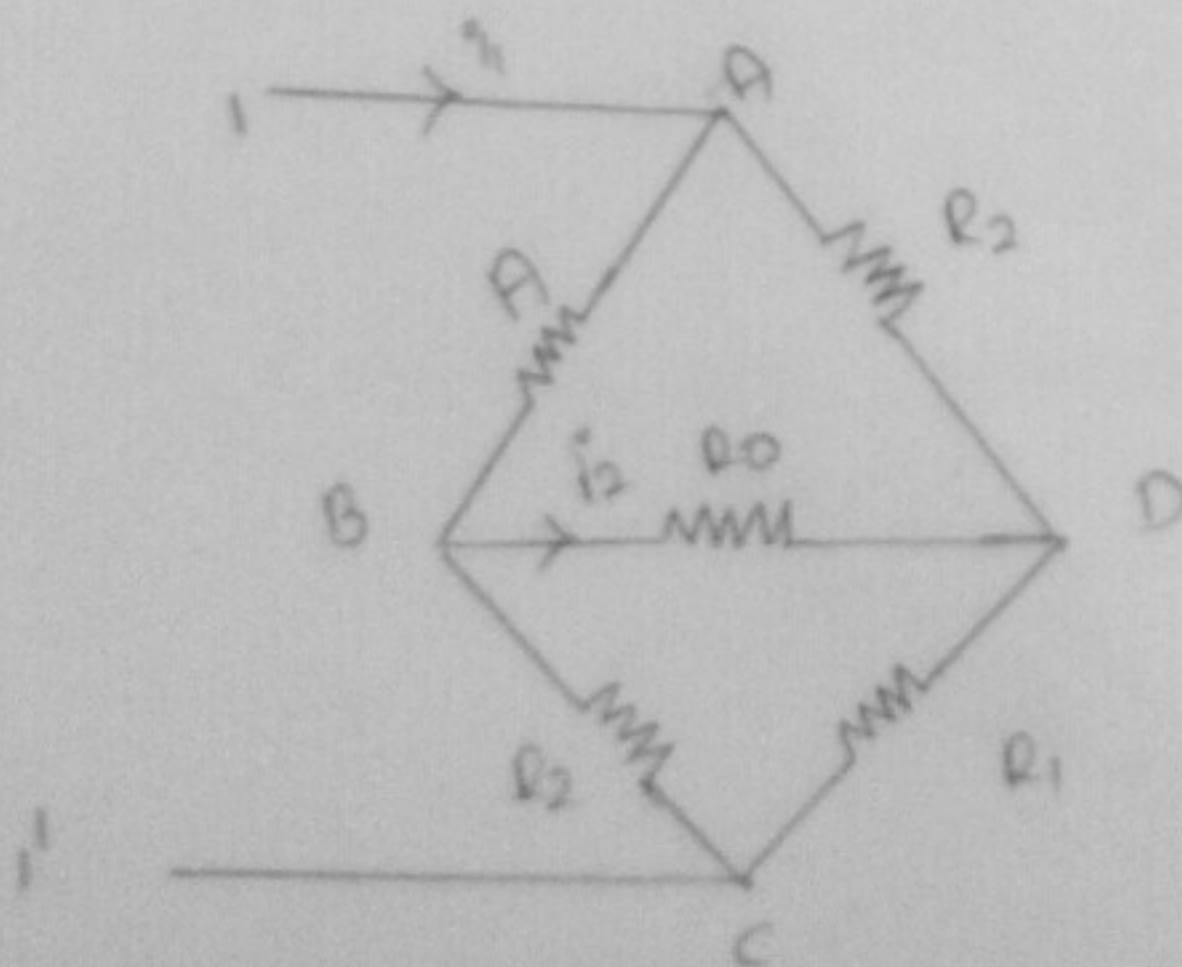The above n/w is redrawn as shown in figure



The characteristic impedance in terms of open circuit and short circuit impedance or resistance is given as


$$Z_0 = \sqrt{Z_{oc} \cdot Z_{sc}}$$

$$R_0 = \sqrt{R_{oc} \cdot R_{sc}} \quad - (a)$$

where R_{oc} is the equivalent resistance at Port 1-1' when the port 2-2' is open circuited.

R_{sc} is the equivalent resistance at port 1-1' when port 2 terminals are short circuited.


(7)

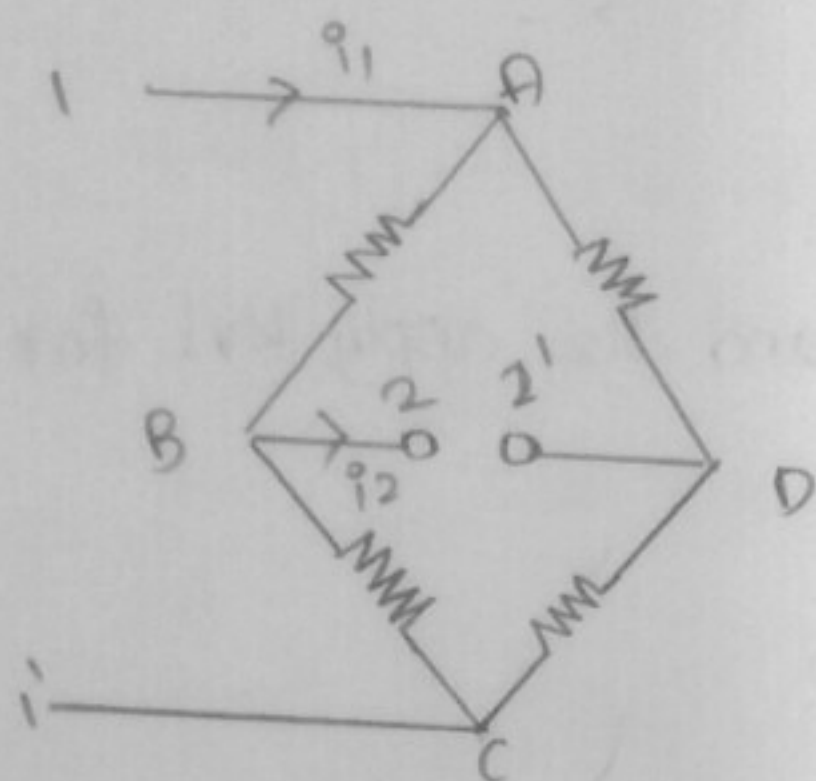

$$R_{oc} = (R_1 + R_2) \parallel R_1 + R_2$$

$$= \frac{(R_1 + R_2)(R_1 + R_2)}{2(R_1 + R_2)}$$
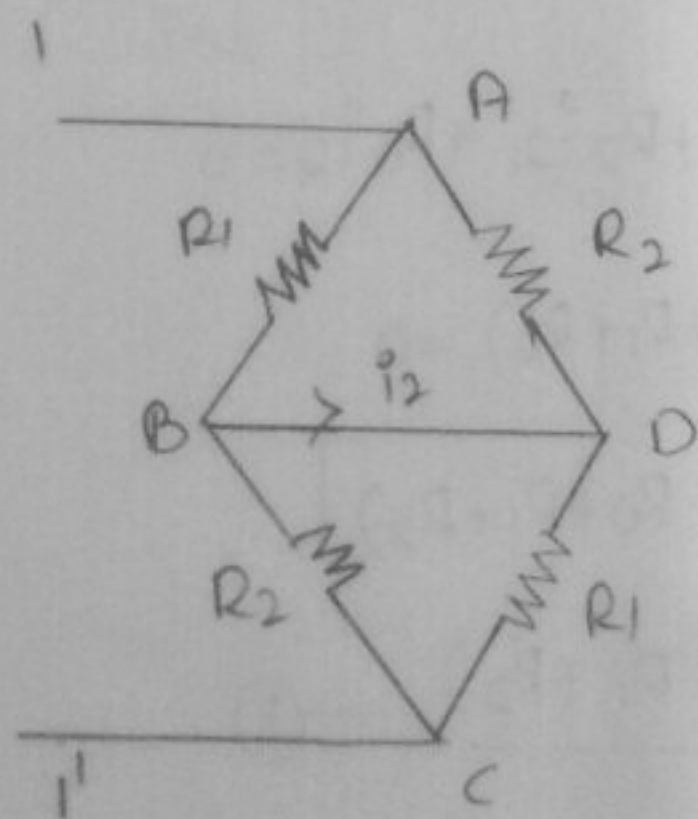
$$R_{oc} = \frac{R_1 + R_2}{2} \quad - (1)$$



$$R_{sc} = [R_1 \parallel R_2] + [R_1 \parallel R_2]$$

$$\frac{R_1 R_2}{R_1 + R_2} + \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{sc} = \frac{2R_1R_2}{R_1+R_2} \quad \text{--- (2)}$$

Substitute (1) and (2) in eq (1)

$$R_0 = \sqrt{\left(\frac{R_1+R_2}{2}\right) \left(\frac{2R_1R_2}{R_1+R_2}\right)}$$

$$R_0 = \sqrt{R_1R_2}$$

$$\sqrt{R_2} = \frac{R_0}{\sqrt{R_1}}$$

In order to find R_1 and R_2 apply KVL for upper loop we have

$$R_2(i_1 - i) - R_0 i_2 - R_1 i = 0$$

$$-i[R_2 + R_1] = R_0 i_2 - R_2 i_1$$

$$i = \frac{R_2 i_1 - R_0 i_2}{R_2 + R_1}$$

Apply KVL to 2nd loop

$$R_1(i_1 - i + i_2) - R_2(i - i_2) + R_0 i_2 = 0$$

$$-i(R_1 + R_2) + R_1 i_1 + R_1 i_2 + R_2 i_2 + R_0 i_2 = 0$$

$$-i(R_1 + R_2) + R_1 i_1 + i_2(R_0 + R_1 + R_2) = 0$$

$$-i(R_1 + R_2) = -[R_1 i_1 + i_2(R_0 + R_1 + R_2)]$$

$$i = \frac{R_1 i_1 + i_2(R_0 + R_1 + R_2)}{R_1 + R_2} \quad \text{--- (3)}$$

equating (3) & (4)

$$\frac{R_2 i_1 - R_0 i_2}{R_1 + R_2} = \frac{R_1 i_1 + i_2(R_0 + R_1 + R_2)}{R_1 + R_2}$$

Given attenuation in dB = 20

(2)

$$R_0 = 800 \Omega$$

$$\begin{aligned} N &= \text{antilog} \left[\frac{\text{dB}}{20} \right] \\ &= 10^{\left[\frac{\text{dB}}{20} \right]} \\ &= 10^{\left[\frac{20}{20} \right]} \end{aligned}$$

10

$$N = 10$$

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right]$$

$$= 800 \left[\frac{10-1}{10+1} \right]$$


$$= 800 \left[\frac{9}{11} \right]$$

$$= 654.5454 \Omega$$

$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$

$$= 800 \left[\frac{10+1}{10-1} \right]$$
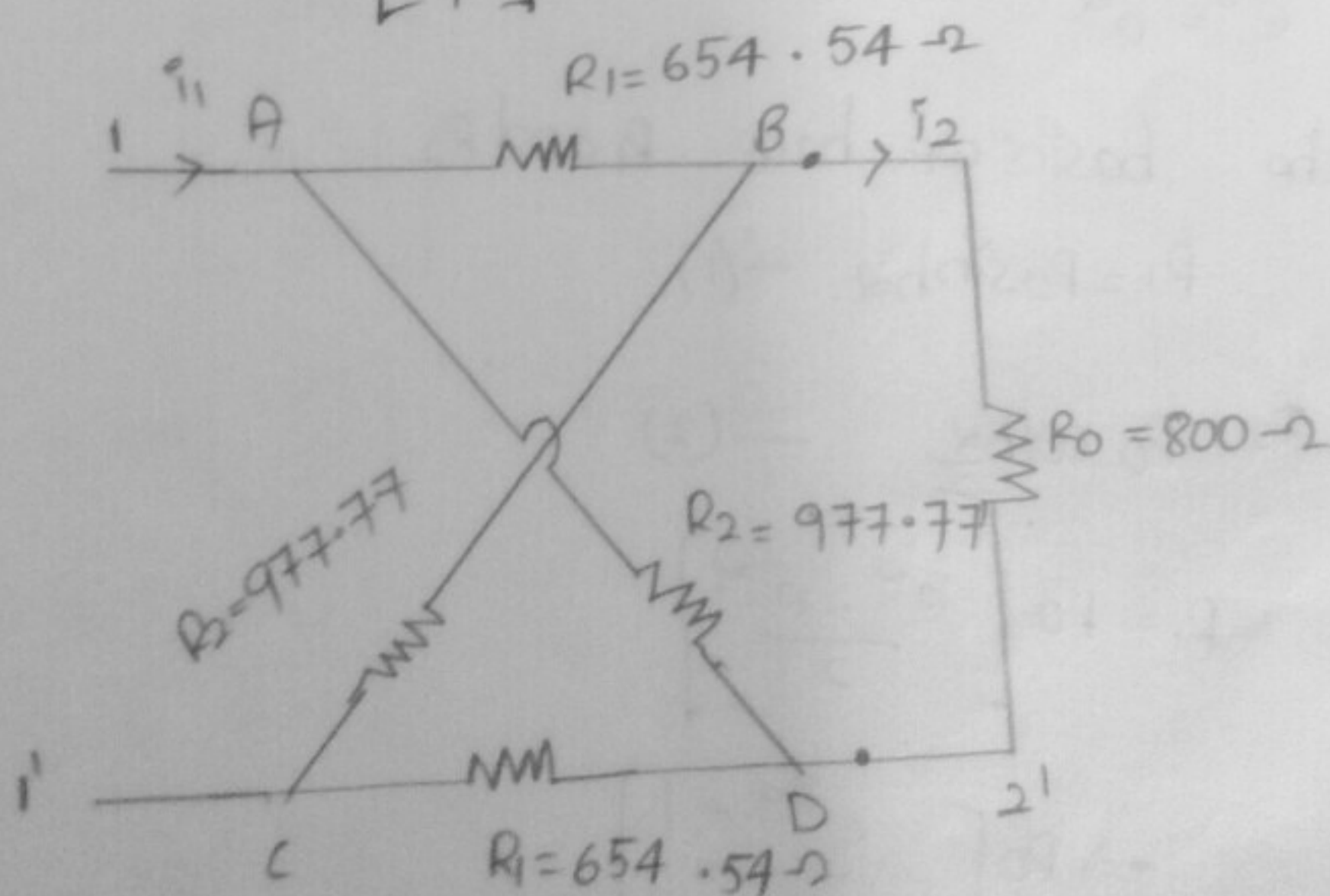
$$= 800 \left[\frac{11}{9} \right] = 977.777 \Omega$$



$$i_1 (R_2 - R_1) - i_2 (2R_0 + R_1 + R_2) = 0$$

$$i_1 (R_2 - R_1) = i_2 (2R_0 + R_1 + R_2)$$

$$\frac{i_1}{i_2} = \frac{2R_0 + R_1 + R_2}{R_2 - R_1} = N$$

$$\frac{i_1}{i_2} = N = e^{\frac{2}{N}} \rightarrow e^2$$

$$(R_2 - R_1) N = R_1 + R_2 + 2\sqrt{R_1 R_2}$$

$$N(R_2 - R_1) = (\sqrt{R_1})^2 + (\sqrt{R_2})^2 + 2\sqrt{R_1 R_2}$$

$$N(\sqrt{R_2} + \sqrt{R_1})(\sqrt{R_2} - \sqrt{R_1}) = (\sqrt{R_1} + \sqrt{R_2})^2$$

$$N(\sqrt{R_2} - \sqrt{R_1}) = \sqrt{R_1} + \sqrt{R_2}$$

$$\text{Sub } \sqrt{R_2} = \frac{R_0}{\sqrt{R_1}}$$

$$N\left(\frac{R_0}{\sqrt{R_1}} - \sqrt{R_1}\right) = \sqrt{R_1} + \frac{R_0}{\sqrt{R_1}}$$

$$N\left(\frac{R_0 - R_1}{\sqrt{R_1}}\right) = \frac{R_1 + R_0}{\sqrt{R_1}}$$

$$R_1 - R_0 \left[\frac{N-1}{N+1} \right]$$


$$\text{Sub } \sqrt{R_1} = \frac{R_0}{\sqrt{R_2}}$$

$$N\left(\sqrt{R_2} - \frac{R_0}{\sqrt{R_2}}\right) = \frac{R_0}{\sqrt{R_2}} + \sqrt{R_2}$$

$$N\left(\frac{R_2 - R_0}{\sqrt{R_2}}\right) = \frac{R_0 + R_2}{\sqrt{R_2}}$$



$$NR_2 - NR_0 = R_2 + R_0$$
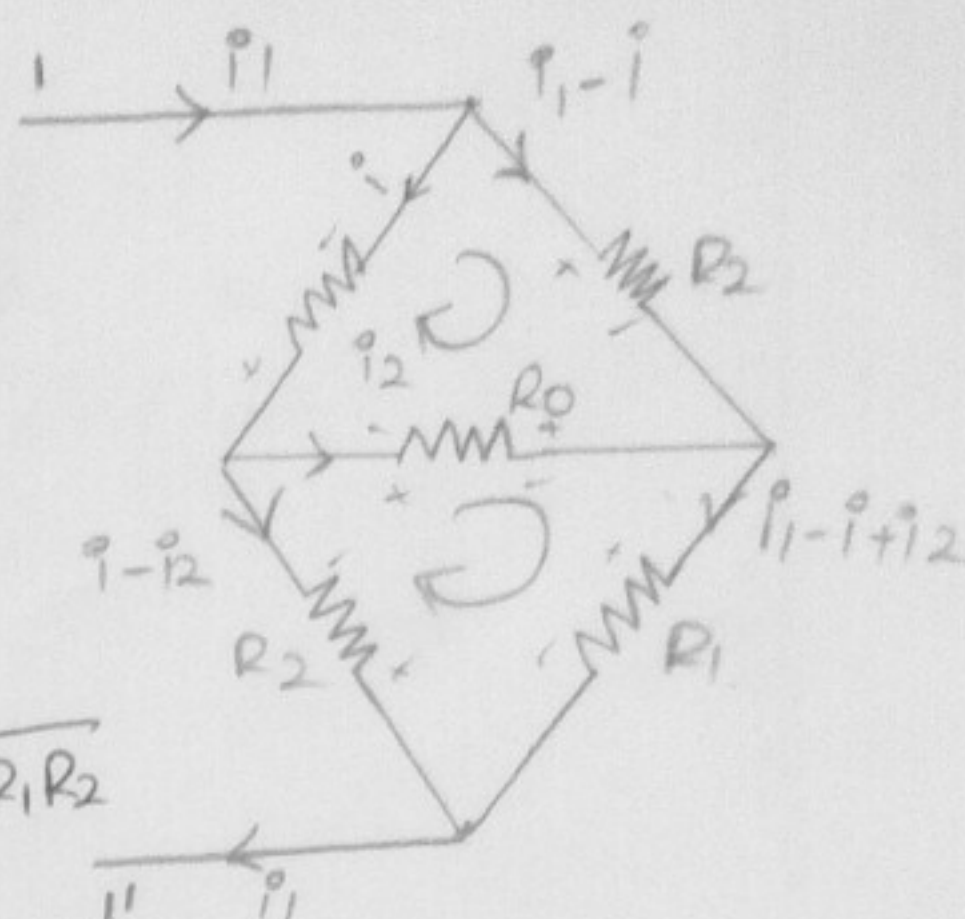
$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$



(9)

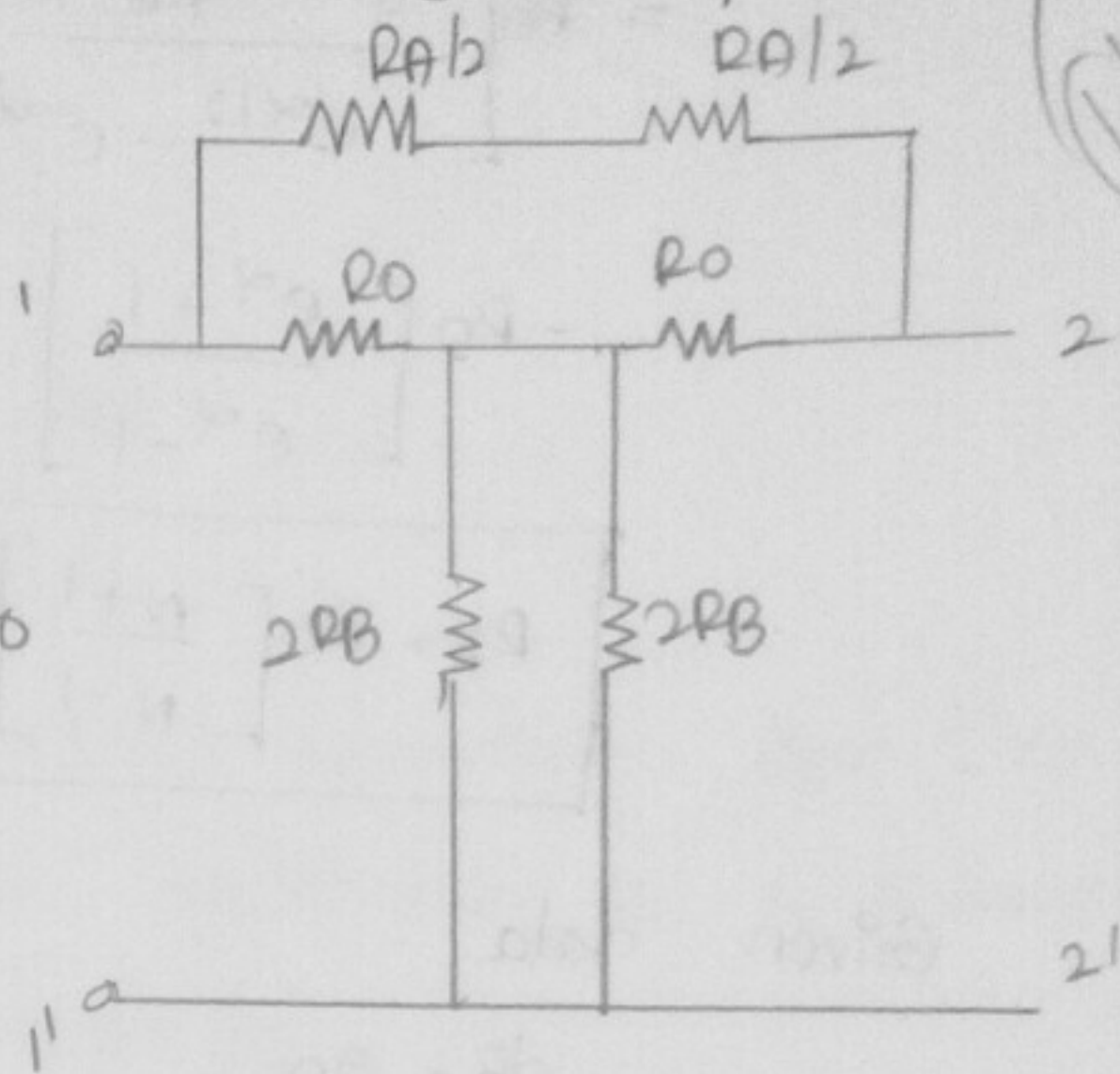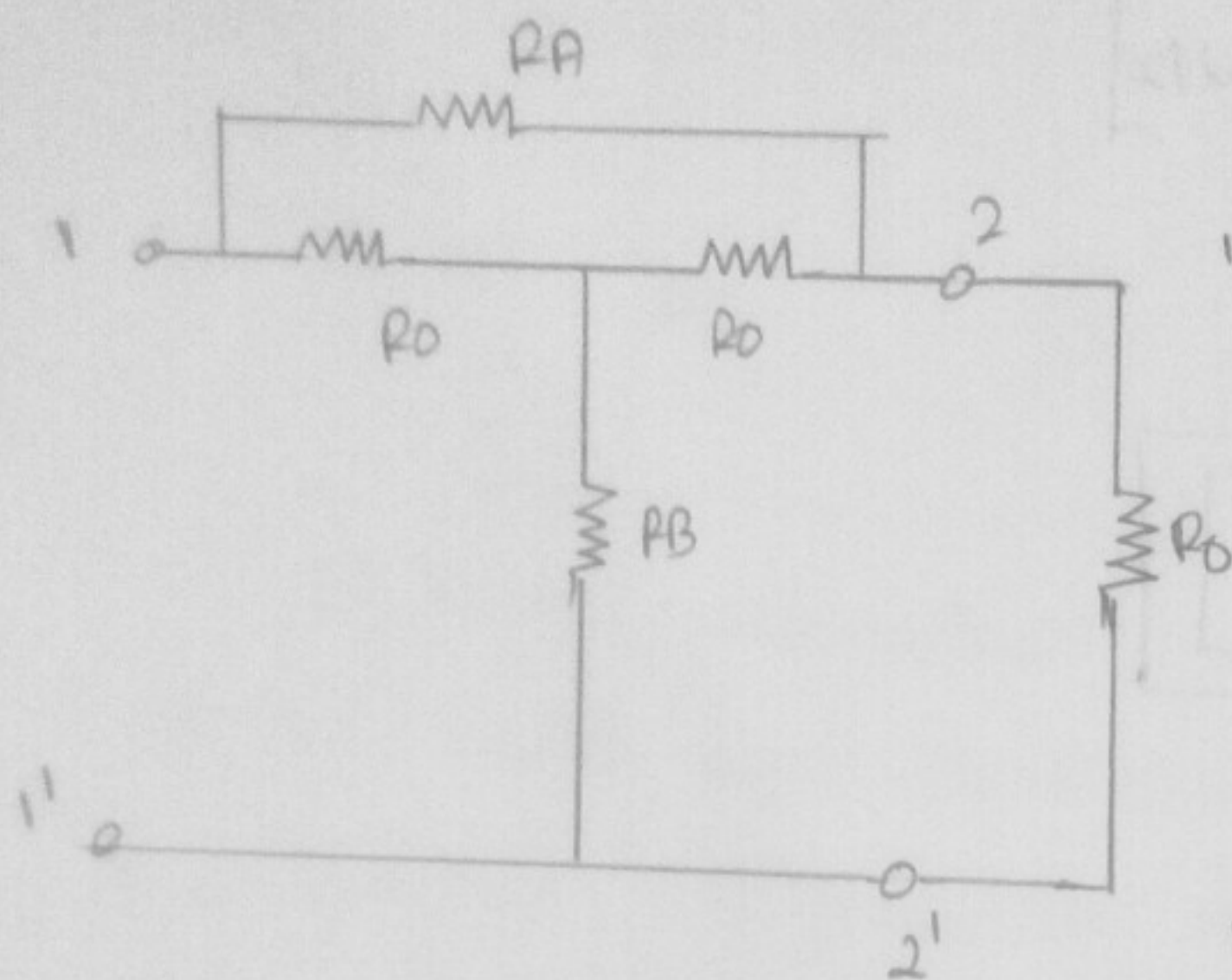- 4) Explain bridged T-attenuator and also design it with an attenuation of 20 dB and terminated in a load of $500\ \Omega$



It is similar to the T-attenuator with extra bridge over it. This attenuator is said to be symmetrical when its series arm resistance is equal. The design of the bridged T-symmetrical attenuator will be carried through bisection theorem.

Bisection theorem states that the n/w with mirror image symmetry can be converted into equivalent lattice structure where the series arm impedance of the equivalent lattice structure is equal to short circuited i/p impedance of the bisected n/w where as diagonal arm impedance is equal open circuited impedance of the bisected n/w.

The above can be redrawn as shown in figure from the bisection theorem $R_1 = R_{sc}$.

$$(R_A + 2R_0) \left[\frac{N-1}{N+1} \right] = R_A$$

$$R_A \left[\frac{N-1}{N+1} \right] + 2R_0 \left[\frac{N-1}{N+1} \right] = R_A$$

(3)

$$2R_0 \left[\frac{N-1}{N+1} \right] = R_A \left[1 - \frac{N-1}{N+1} \right]$$

$$2R_0 \left[\frac{N-1}{N+1} \right] = R_0 \left[\frac{N+1 - N+1}{N+1} \right]$$

$$\frac{2R_0 \left[\frac{N-1}{N+1} \right]}{\frac{2}{N+1}} = R_A$$

$$R_A = R_0 [N-1]$$

$$R_2 = R_0 \left[\frac{N+1}{N-1} \right] \quad \text{--- (4)}$$

equating (3) and (4)

$$R_0 + 2R_B = R_0 \left[\frac{N+1}{N-1} \right]$$


$$2R_B = R_0 \left[\frac{N+1}{N-1} - 1 \right]$$

$$2R_B = R_0 \left[\frac{N+1 - N+1}{N-1} \right]$$

$$R_B = \frac{R_0}{N-1}$$

The bridged T-network is said to be symmetrical when the bridge arm and shunt arm satisfies

$$R_A = R_B = R_0^2$$

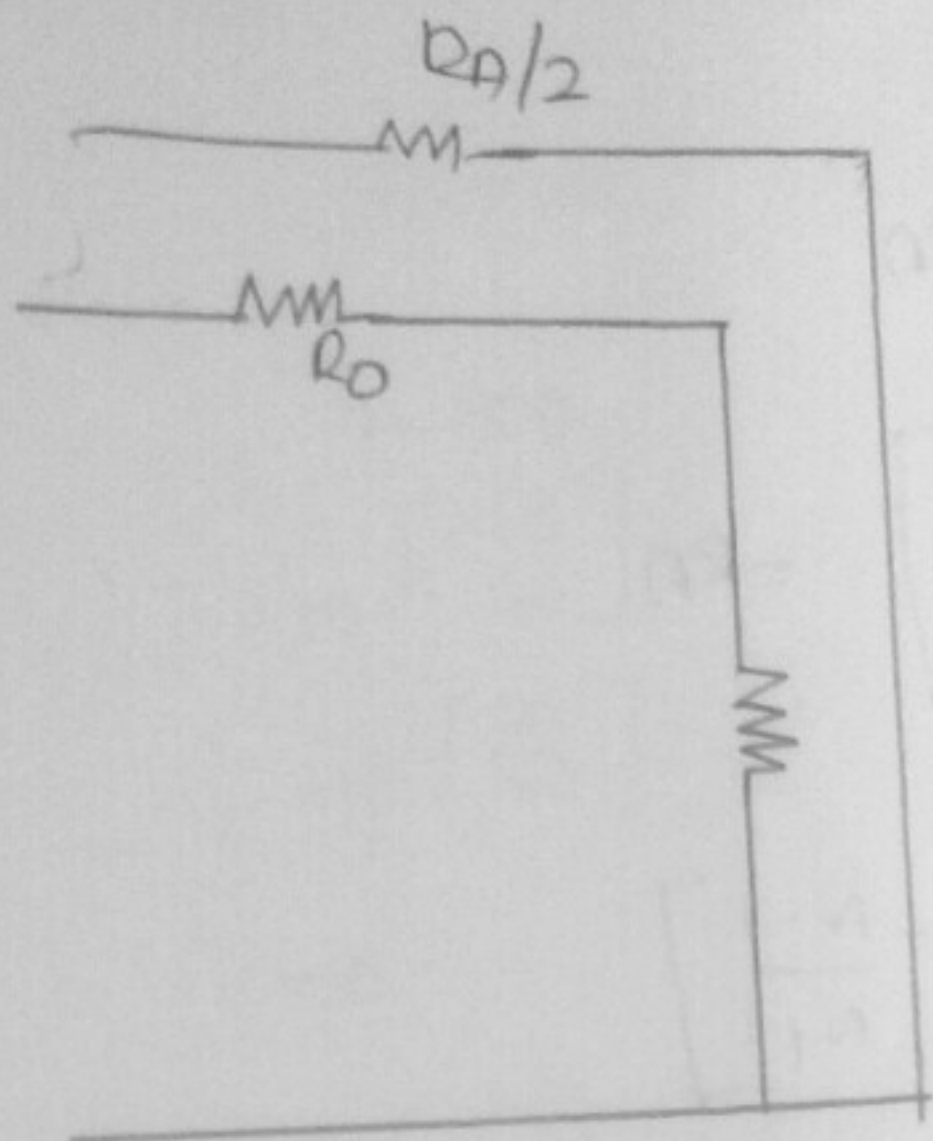


$$R_{SC} = R_A/2 \parallel R_0$$

$$R_{SC} = \frac{\frac{R_A}{2} \cdot R_0}{\frac{R_A}{2} + R_0} = \frac{R_0 R_A}{R_A + 2R_0}$$

$$(\because R_{SC} = R_1)$$

$$R_1 = \frac{R_0 R_A}{R_A + 2R_0} \quad \text{--- ①}$$

$$R_2 = R_{OC}$$

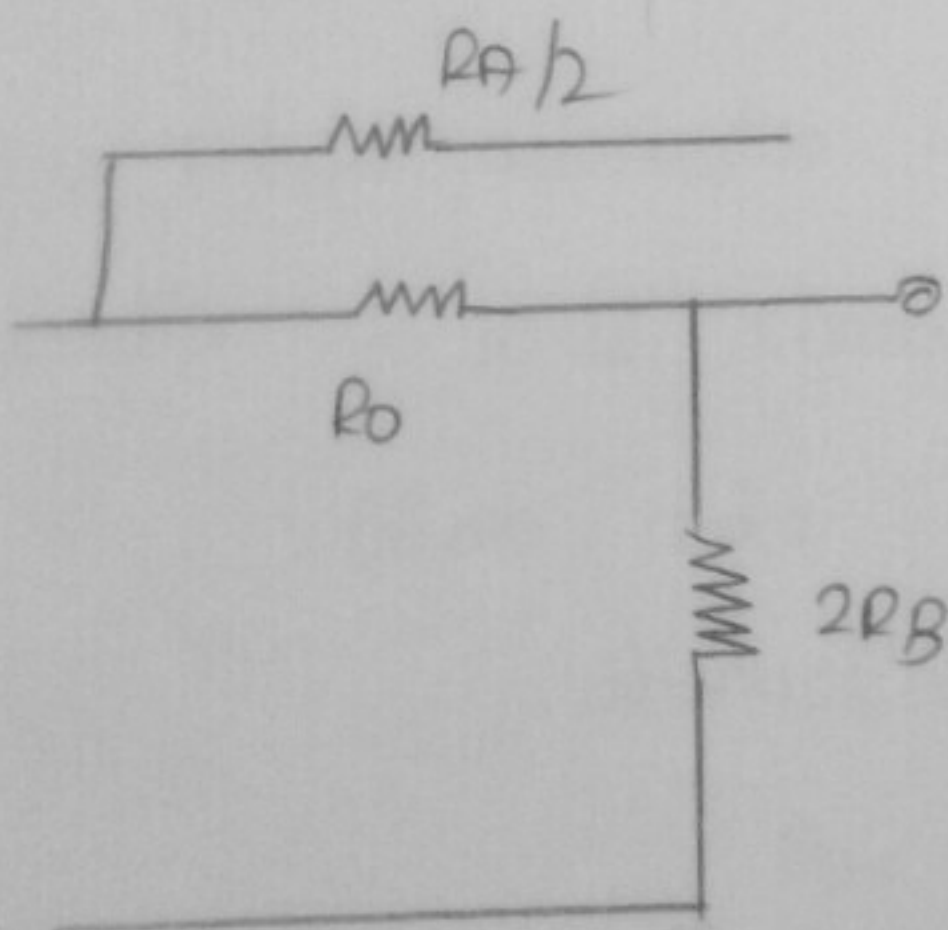

$$R_{OC} = R_0 + 2R_B \quad \text{--- ②}$$

From the lattice attenuator we know that

$$R_1 = R_0 \left[\frac{N-1}{N+1} \right] \quad \text{--- ③}$$

equating eq ① and ③

$$R_0 \left[\frac{N-1}{N+1} \right] = \frac{R_0 R_A}{R_A + 2R_0}$$

Given

$$dB = 20$$

$$R_0 = 500$$

$$N = 10 \left[\frac{dB}{20} \right]$$

$$= 10 \left[\frac{20}{20} \right]$$

$$N = 10$$

$$R_A = R_0 [N - 1]$$


$$= 500 [10 - 1]$$

$$= 4500$$

$$= 4.5 \text{ k}\Omega$$

$$R_B = \frac{R_0}{N - 1}$$

$$= \frac{500}{9} = 55.55 \Omega$$

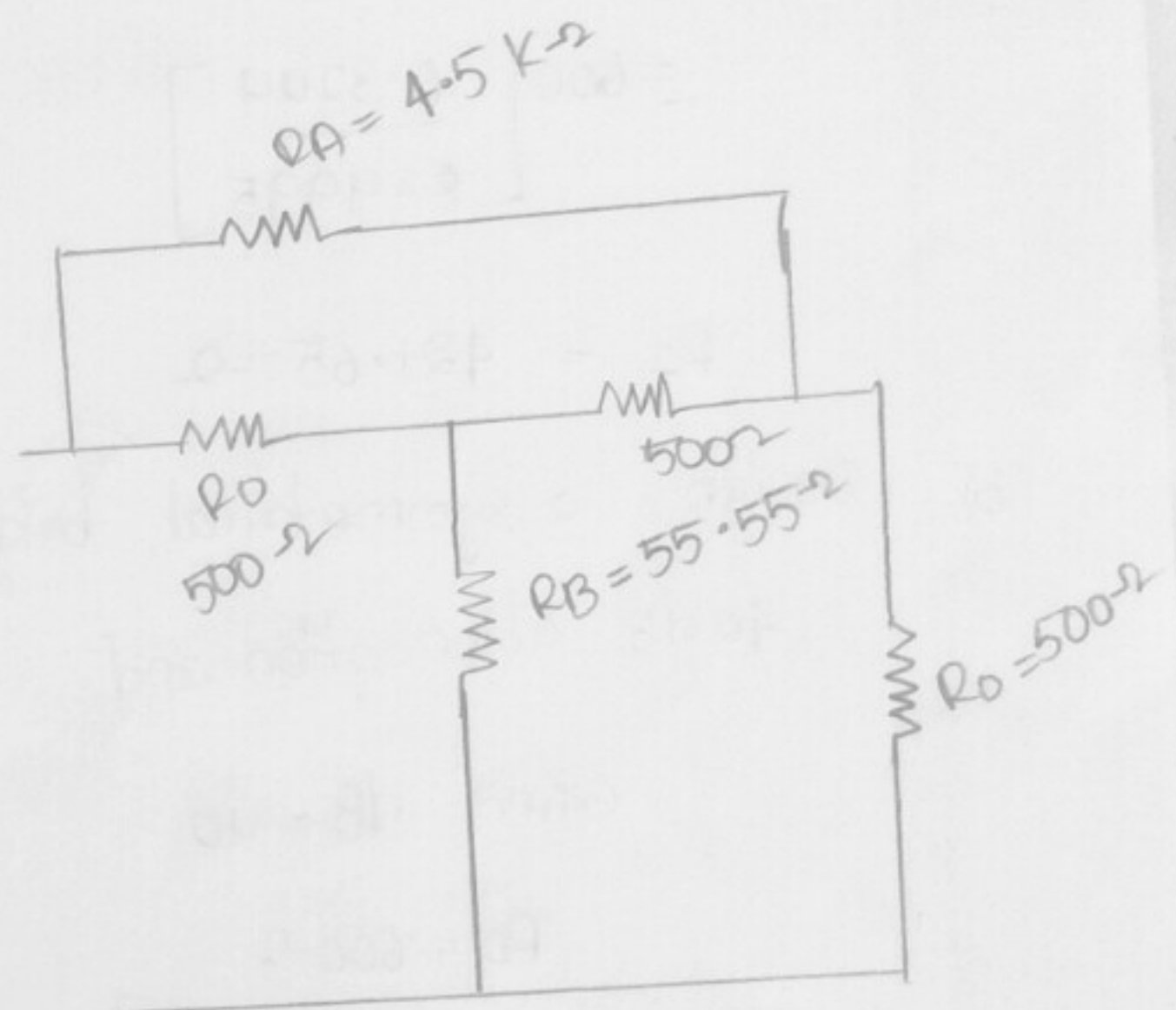

5 a) design a T-type attenuator with the following specification
attenuation = 10 dB, characteristic impedance = 600 Ω

Given data

$$\text{attenuation} = 10 \text{ dB}$$

$$R_0 = 600 \Omega$$

$$N = 10 \left[\frac{dB}{20} \right]$$

$$= 10 \left[\frac{10}{20} \right] = 3.1622$$

$$R_1 = R_0 \left[\frac{N - 1}{N + 1} \right]$$

$$= 600 \left[\frac{3.1622 - 1}{3.1622 + 1} \right] = 600 \left[\frac{2.1622}{4.1622} \right]$$


$$= 311.69 \Omega$$

$$P_2 = P_0 \left[\frac{2N}{N^2 - 1} \right]$$

$$= 600 \left[\frac{2 \left[3.1622 \right]}{(3.1622)^2 - 1} \right]$$

$$= 600 \left[\frac{6.3244}{8.9995} \right]$$

$$P_2 = 421.65 \Omega$$

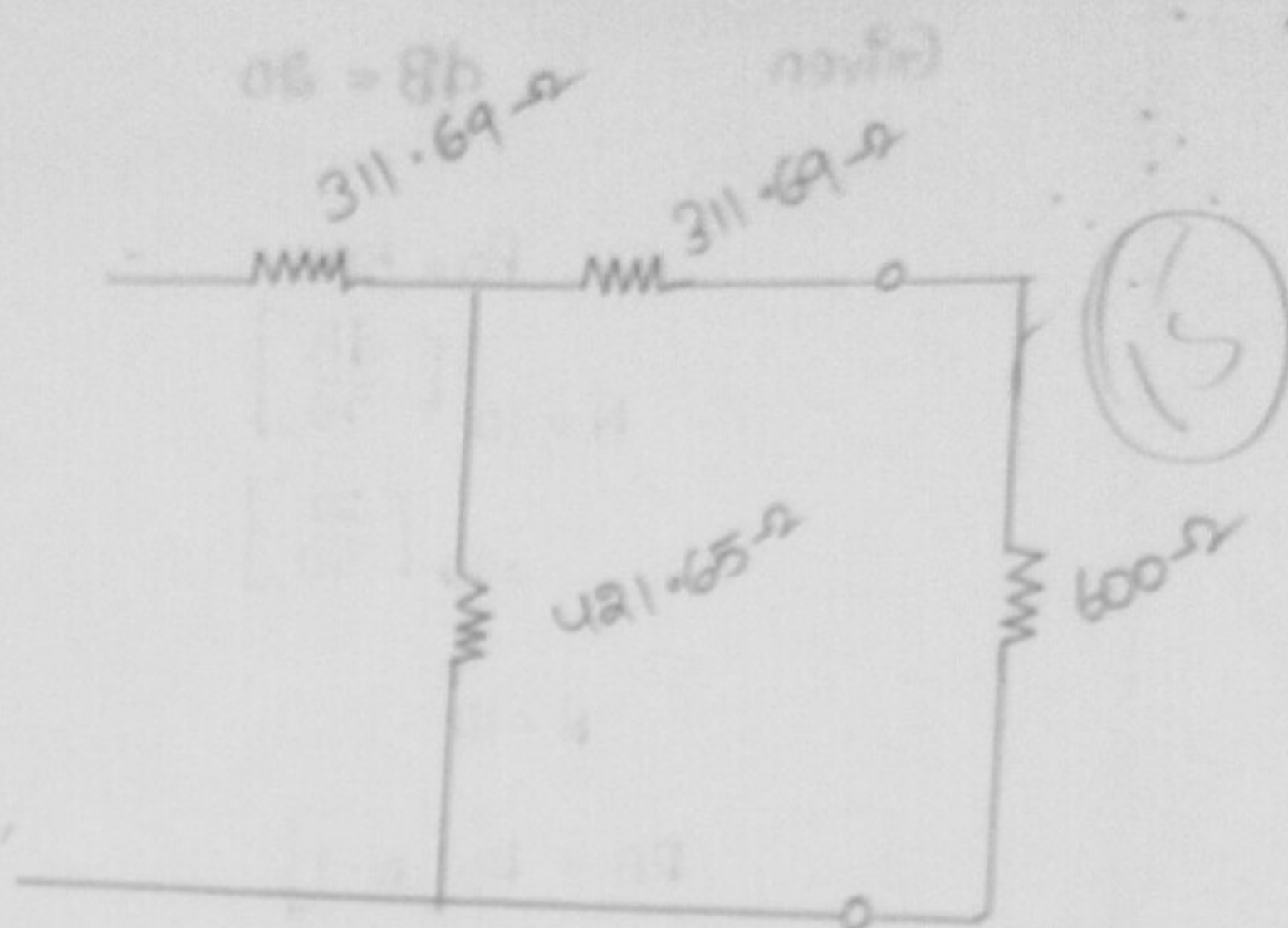

- b) Design a symmetrical bridged T-type attenuator with 40 dB attenuation and design impedance of 600 Ω

$$\text{Given } dB = 40$$

$$P_0 = 600 \Omega$$

$$N = 10 \left[\frac{40}{20} \right]$$

$$N = 100$$

$$P_A = P_0 [N - 1]$$


$$= 600 [100 - 1]$$

$$= 600 [99] = 59.4 \text{ k}\Omega$$

$$P_B = \frac{P_0}{N - 1}$$

$$= \frac{600}{99}$$

$$P_B = 6.0606 \Omega$$

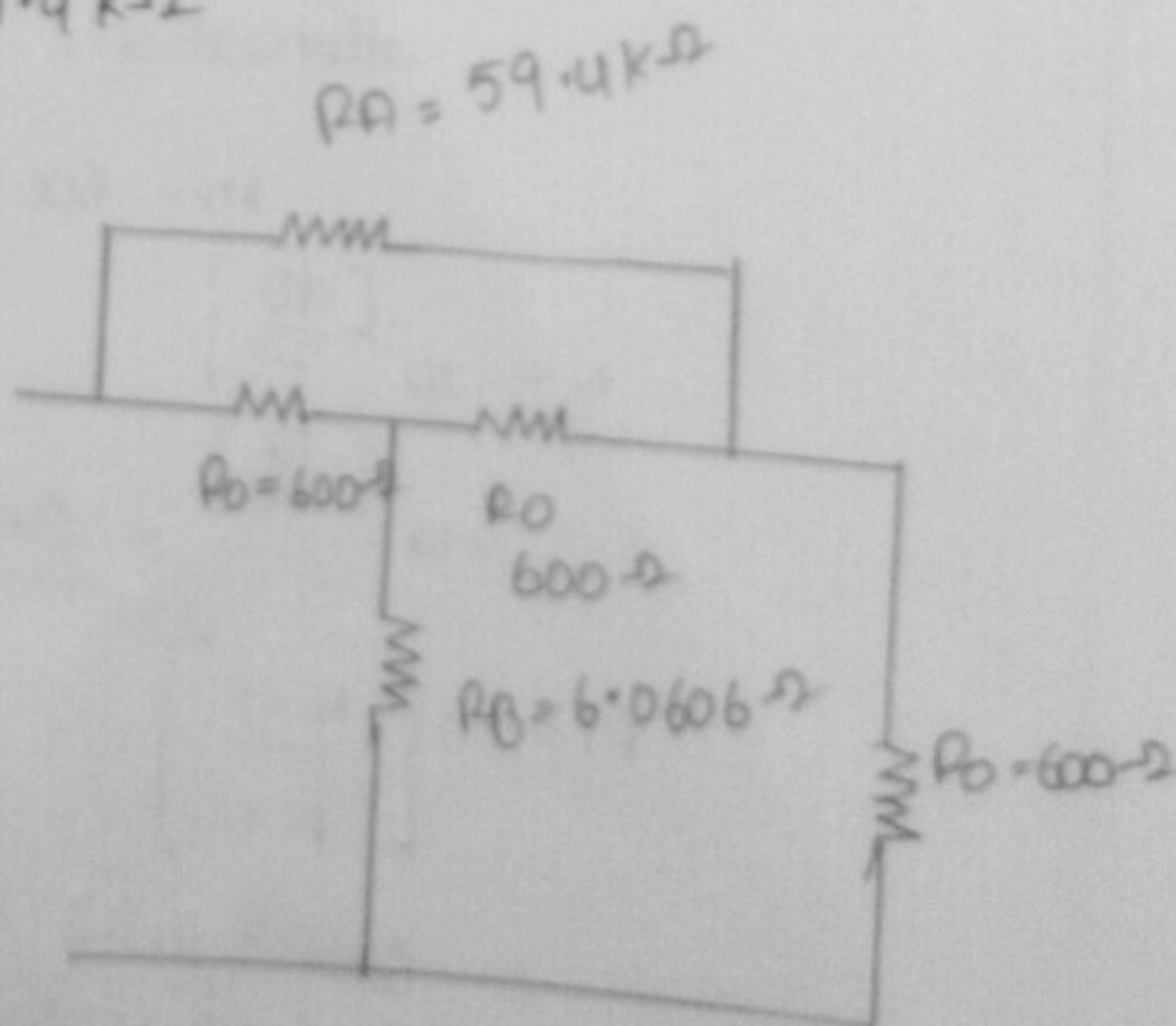

a) Design a symmetrical lattice attenuator with 20dB attenuation and characteristic impedance of 600Ω .

Given data

$$dB = 20$$

$$R_0 = 600$$

$$N = 10^{\left[\frac{dB}{20}\right]} = 10^{\left[\frac{20}{20}\right]}$$

$$N = 10$$


$$R_1 = R_0 \left[\frac{N-1}{N+1} \right]$$

$$= 600 \left[\frac{10-1}{10+1} \right]$$

$$= 600 \left[\frac{9}{11} \right] = 490.90\Omega$$

$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$
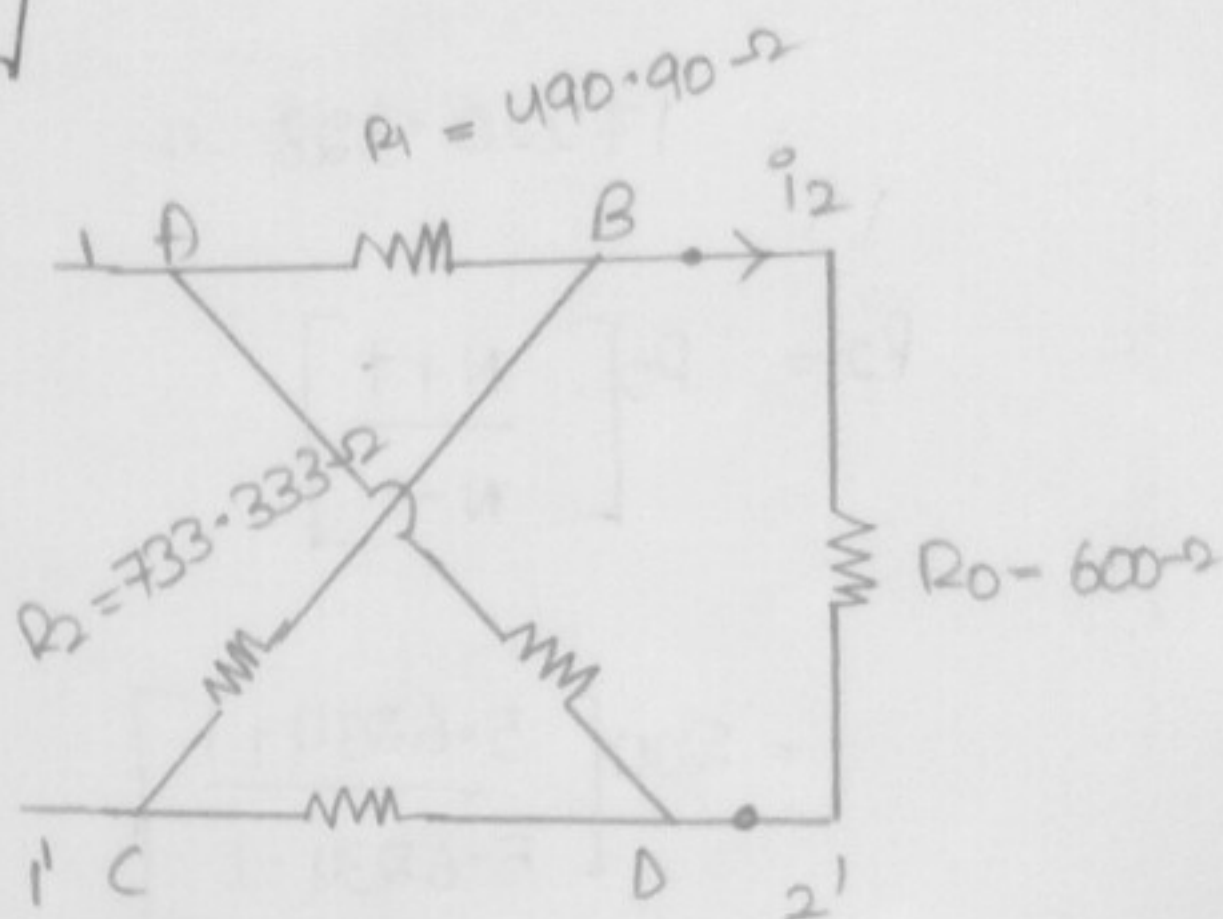
$$= 600 \left[\frac{11}{9} \right] = 733.333\Omega$$



b) Design a π type attenuator to provide an attenuation of 15dB. characteristic impedance = 200Ω

Given data

$$dB = 15$$

$$R_0 = 200\Omega$$

$$N = 10^{\left[\frac{dB}{20}\right]}$$

$$= 10^{\left[\frac{15}{20}\right]}$$

$$N = 5.6234$$

$$R_1 = R_0 \left[\frac{N^2 - 1}{2N} \right]$$

$$= 200 \left[\frac{(5.6234)^2 - 1}{2(5.6234)} \right]$$

$$= 200 [86.1016]$$


$$= 17220.328 \, \Omega$$

$$R_2 = R_0 \left[\frac{N+1}{N-1} \right]$$

$$= 200 \left[\frac{5.6234+1}{5.6234-1} \right]$$

$$= 200 \left[\frac{6.6234}{4.6234} \right]$$

$$= 286.5164 \, \Omega$$

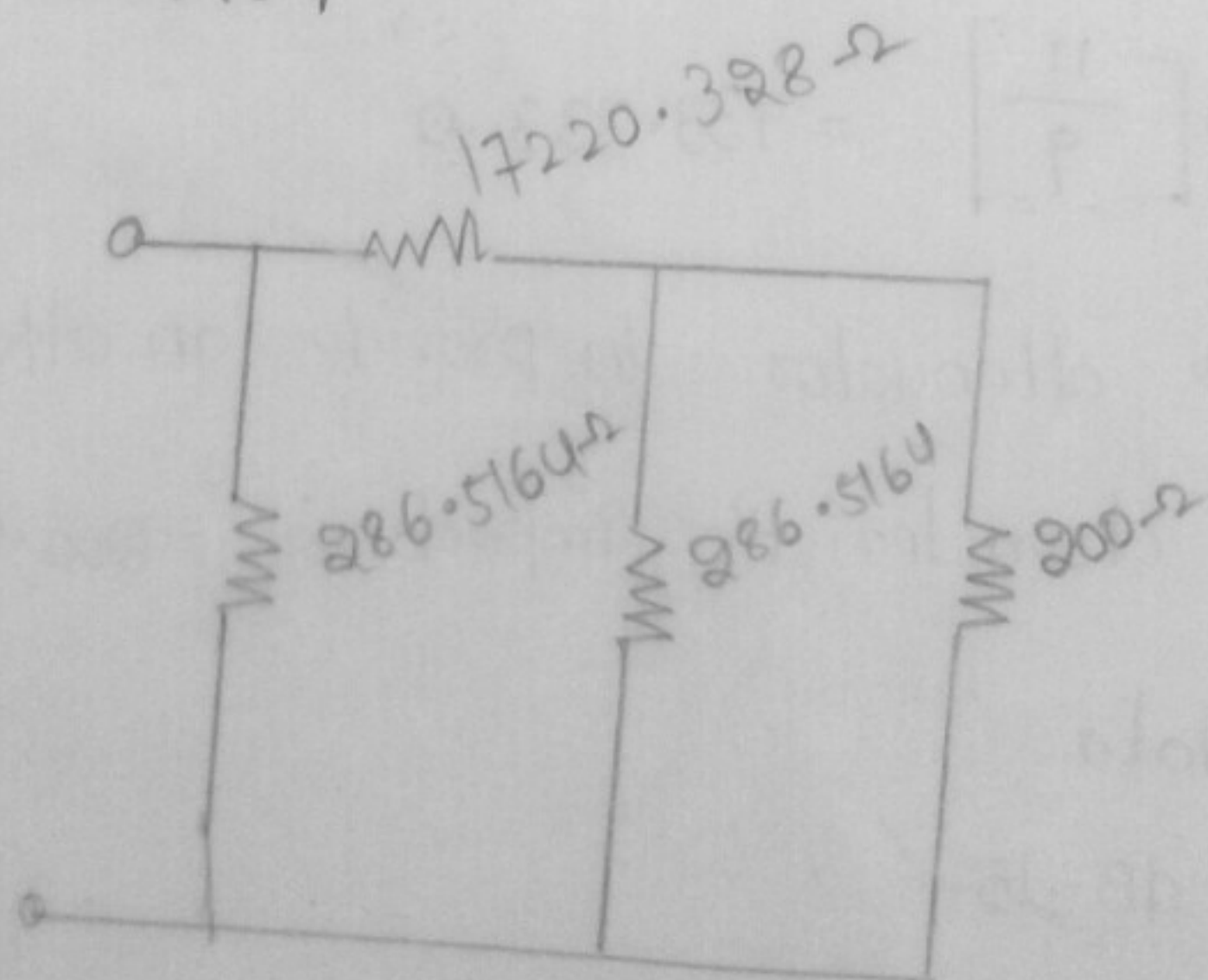

$$\Rightarrow Z_1 e^{\gamma} = Z_2 (e^{\gamma} - 2 + e^{-\gamma}) e^{\gamma}$$

$$\Rightarrow Z_1 = Z_2 (e^{\gamma} - 2 + e^{-\gamma})$$

$$\Rightarrow Z_1 = Z_2 (e^{\gamma} + e^{-\gamma}) - 2Z_2$$

$$\Rightarrow \frac{Z_1 + 2Z_2}{Z_2} = e^{\gamma} + e^{-\gamma}$$

$$\Rightarrow \frac{Z_1 + 2Z_2}{2Z_2} = \frac{e^{\gamma} + e^{-\gamma}}{2}$$

$$\Rightarrow 1 + \frac{Z_1}{2Z_2} = \cosh \gamma$$

$\Rightarrow$ From the hyperbolic relations, we know that

$$\Rightarrow \cosh 2\gamma = 1 + 2\sinh^2 \gamma$$

$$Z_2 = \frac{R_A R_B}{R_A + R_B}$$

$$\Rightarrow \cosh \gamma = 1 + \frac{Z_1}{2Z_2}$$

$$\Rightarrow \cosh 2 \cdot \frac{\gamma}{2} = 1 + 2\sinh^2 \frac{\gamma}{2} = 1 + \frac{Z_1}{2Z_2}$$

$$\Rightarrow 2\sinh^2 \frac{\gamma}{2} = \frac{Z_1}{2Z_2}$$

$$\Rightarrow \sinh \frac{\gamma}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$\Rightarrow$ we know that the propagation constant $\gamma = \alpha + j\beta$

where α is attenuation &

β is phase shift.

$$\Rightarrow \sinh \frac{\gamma}{2} = \sinh \left(\frac{\alpha + j\beta}{2} \right) = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\Rightarrow \sinh \left(\frac{\alpha}{2} + j\frac{\beta}{2} \right) = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\Rightarrow \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \sin \frac{\beta}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

Characteristic Impedance and classification of

pass and stop band:-

$\Rightarrow$ Characteristic impedance of symmetrical T-nlw:

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

3(7) 15

$$\Rightarrow Z_{OT} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4 Z_2}}}$$

$$\Rightarrow \sinh \frac{\alpha}{2} = \sqrt{\frac{Z_1}{4 Z_2}}$$

$$\Rightarrow \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \sin \frac{\beta}{2} = \sqrt{\frac{Z_1}{4 Z_2}}$$

Case (i):- When Z_1 and Z_2 are of same reactances, Then

$$\Rightarrow \left| \frac{Z_1}{4 Z_2} \right| > 0 \Rightarrow \left| \frac{Z_1}{4 Z_2} \right| > 0 \quad \text{i.e., } \sqrt{\frac{Z_1}{4 Z_2}} = x + j \cdot 0 \text{ [real value]}$$

$\Rightarrow$ But, we know that

$$\Rightarrow \sinh \frac{\alpha}{2} = x + j(0)$$

$$\Rightarrow \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \sin \frac{\beta}{2} = x + j(0)$$

$\Rightarrow$ comparing real and imaginary parts on both sides

$$\Rightarrow \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} = x \rightarrow \textcircled{1}$$

$$\cosh \frac{\alpha}{2} \sin \frac{\beta}{2} = 0 \rightarrow \textcircled{2}$$

$\Rightarrow$ eq. ① & ② will be satisfy when $\beta = 0$, hence from eq ①

$$\Rightarrow \sinh \frac{\alpha}{2} = x$$

$$\Rightarrow \alpha = 2 \sinh^{-1} \left(\sqrt{\frac{Z_1}{4 Z_2}} \right) \Rightarrow \alpha = 2 \sinh^{-1} \left(\sqrt{\frac{Z_1}{4 Z_2}} \right) \neq 0$$

$\Rightarrow$ When both the reactances are of same ^{type} reactance there exist attenuation band (or) stop band (since $\alpha \neq 0$ stop band)

Case (ii):- When Z_1 and Z_2 are of opposite reactances,

$$\Rightarrow \frac{Z_1}{4 Z_2} < 0 \Rightarrow \frac{Z_1}{4 Z_2} < 0$$

$$\text{i.e., } \Rightarrow \sqrt{\frac{Z_1}{4 Z_2}} = 0 + j \cdot x \text{ (imaginary value)}$$

$$\Rightarrow \sinh \frac{\alpha}{2} \cos \beta/2 + j \cosh \frac{\alpha}{2} \sin \beta/2 = 0 + jx$$

$$\Rightarrow \sinh \frac{\alpha}{2} \cos \beta/2 = 0 \longrightarrow \textcircled{A}$$

$$\cosh \frac{\alpha}{2} \sin \beta/2 = x \longrightarrow \textcircled{B}$$

$\Rightarrow$ eq. $\textcircled{A}$ will be satisfied when $\alpha = 0$ (pass band) and

$$\beta = 2n\pi \text{ or } \pi$$

$$\beta = (2n+1)\pi \text{ where } n \text{ is integer}$$

$\Rightarrow$ case (A) :- When $\alpha = 0$ there exists a pass band since the attenuation is zero.

$\Rightarrow$ case (B) :- When $\beta = \pi$,

$$\text{from eq. } \textcircled{B} \Rightarrow \cosh \frac{\alpha}{2} = x$$

$$\alpha = 2 \cosh^{-1}(x) \neq 0$$

$\Rightarrow$ Hence there exists a stop band.

Filter

Condition for pass band and stop band with the value of characteristic impedance:-

We know that from propagation constant,

$$\sinh \frac{\alpha}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

$$\Rightarrow \sinh \frac{\alpha}{2} \cos \beta/2 + j \cosh \frac{\alpha}{2} \sin \beta/2 = \sqrt{\frac{Z_1}{4Z_2}}$$

condition

$\rightarrow$ When both impedances are of same type, the

value of $\frac{Z_1}{4Z_2} > 0$ (which is a real value)

$\rightarrow$ Under this condition, the value of $\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}} \neq 0$

Hence there exists a stop band i.e., the condition

for stop band is that $\frac{Z_1}{4Z_2} > 0$

case 2:-

When Z_1 and Z_2 are of opposite reactances $\sqrt{\frac{Z_1}{4Z_2}}$ is an imaginary value, which gives two sets of equations 76
3(8)

$$\sinh \alpha_2 \cos \beta_2 = 0 \longrightarrow (1)$$

$$\cosh \alpha_2 \sin \beta_2 = x \longrightarrow (2)$$

→ When $\beta = \pi$, eq. (1) = 0

from eq. (2) $\cosh \alpha_2 = x$

$$\alpha = 2 \cosh^{-1}(x) = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}} \neq 0$$

→ Again there exists a stop band.

→ And the condition for stop band here is when $\frac{Z_1}{4Z_2} < -1$

→ When $\alpha = 0$,

eq. (1) = 0 and there is a pass band (exists)

from eq. (2) $\sin \beta_2 = x = \sqrt{\frac{Z_1}{4Z_2}}$

$$\beta = 2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}}$$

→ As we know the limits of $\sin$ exists between -1 to 1 (-1 to 1)
Hence the value of $\frac{Z_1}{4Z_2}$ will also lie between -1 to 1 .

→ But we know that when $\frac{Z_1}{4Z_2} > 0$, it will enter into the attenuation band. Hence to have pass band, the value of

$\frac{Z_1}{4Z_2}$ should be between -1 to 0 .

$$-1 < \frac{Z_1}{4Z_2} < 0$$

$$-1 < \frac{Z_1}{4Z_2} \rightarrow \frac{Z_1}{4Z_2} < 0$$

→ The value of frequency at which the filter changes its state from stop band to pass band and vice versa is termed as cutoff frequency (or) nominal frequency.

→ From the pass band condition, we have

$$-1 \leq \frac{Z_1}{4Z_2} \leq 0$$

from the lower limit

$$\frac{Z_1}{4Z_2} = -1 \Rightarrow Z_1 + 4Z_2 = 0$$

→ from the upper limit

$$\Rightarrow \frac{Z_1}{4Z_2} = 0 \Rightarrow Z_1 = 0$$

→ From symmetrical network, we know the characteristic impedance is,

$$Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2}$$

(opposite type of reactances)

→ Under stop band condition i.e., when $\frac{Z_1}{4Z_2} > 0$ (or) $\frac{Z_1}{4Z_2} < -1$
(same type of reactances)

→ The value of characteristic impedance

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$

case (i):-

Let $Z_1 = jX_1$, $Z_2 = jX_2$ and $\frac{Z_1}{4Z_2} > 0$

$$\Rightarrow Z_{OT} = \sqrt{j^2 X_1 X_2 \left(1 + \frac{X_1}{4X_2}\right)}$$

$$\Rightarrow Z_{OT} = \sqrt{-1} (K) = jK \text{ (imaginary)}$$

→ Under stop band condition, is ^{always} imaginary.

→ Hence the characteristic impedance under attenuation band is always imaginary

case (ii):- Under pass band

$$-1 < \frac{Z_1}{4Z_2} < 0 \text{ (opposite reactances)}$$

$$Z_1 = jX_1$$

$$Z_2 = -jX_2$$

$$\Rightarrow Z_{OT} = \sqrt{-j^2 X_1 X_2 \left(1 + \frac{jX_1}{-4jX_2}\right)} = \sqrt{X_1 X_2 \left(1 - \frac{X_1}{4X_2}\right)} = K$$

$$1 - \frac{X_1}{4X_2} > 0 \text{ (since from pass band condition)}$$

→ Hence under pass band condition, the characteristic impedance will be always real.

Characteristic of filters:-

3(9) 17

1. Under pass band condition, the characteristic impedance of the filter is real always
2. Under stop band condition, the characteristic network of the filter is imaginary always

$$\Rightarrow Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)} \quad \text{and} \quad Z_{O\pi} = \sqrt{\frac{Z_1 Z_2}{4Z_2}} = \sqrt{\frac{Z_1}{4}}$$

Relation between Z_{OT} and $Z_{O\pi}$:-

$$\Rightarrow Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}, \quad Z_{O\pi} = \sqrt{\frac{Z_1 Z_2}{4Z_2}}$$

$$\Rightarrow Z_{OT} = \sqrt{Z_1 Z_2 Z_{O\pi}}$$

$$\Rightarrow Z_{OT}^2 = Z_1^2 Z_2^2 Z_{O\pi}^2 \Rightarrow Z_{O\pi} = \frac{Z_1 Z_2}{Z_{OT}}$$

$$\Rightarrow \text{Under stop band } Z_{O\pi} = jK = \frac{jx_1 jx_2}{jK} = j \frac{x_1 x_2}{K}$$

$$Z_{O\pi} = jA \text{ (imaginary)}$$

$$\Rightarrow \text{Under pass band } Z_{O\pi} = \frac{(jx_1)(-jx_2)}{\frac{K'}{L}K} = -\frac{x_1 x_2}{K} = B$$

$\Rightarrow$ So impedance is real.

8/11/13

Type of filters:-

The filters are primarily classified into 2 types basically

1. Active filters (constructed with operational amplifier)
2. Passive filters (constructed with L, C, elements)

$\rightarrow$ The passive filters are again classified into two types

1. constant K (or) prototype filters
2. m-derived filters

1. Constant-K Filters:-

→ A filter is said to be constant-k when its elements satisfy the relationship that

$$Z_1 Z_2 = k^2$$

Where Z_1 = series arm impedance

Z_2 = shunt arm impedance

k = Nominal (or) design impedance

→ Constant k-filters are classified in 2 types.

1. constant-k low pass filter.

2. constant-k high pass filter.

1. constant-k low pass filter:-

→ When the series arm impedance is inductance & the shunt arm impedance is capacitance, then that filter exhibits the characteristics of a LPF.

⇒ Let $Z_1 = j\omega L$ and $Z_2 = \frac{1}{j\omega C} = -jX_C$.

$$\text{then } Z_1 Z_2 = j\omega L \cdot \frac{1}{j\omega C} = \frac{L}{C} = k^2$$

$$\frac{L}{C} = k^2$$

$$\therefore k^2 = \frac{L}{C}$$

∴ Hence it is a constant k-filter (since it is satisfying the filter $Z_1 Z_2 = k^2$)

⇒ From the pass band condition,

$$\Rightarrow -1 < \frac{Z_1}{4Z_2} < 0$$

$$\Rightarrow -1 < \frac{j\omega L}{4 \cdot \frac{1}{j\omega C}} < 0$$

$$\Rightarrow -1 < \frac{j^2 \omega^2 L C}{4} < 0$$

$$\Rightarrow -1 < -\frac{(2\pi f)^2 LC}{4} < 0$$

$$\Rightarrow -1 < -\frac{4\pi^2 f^2 LC}{4} < 0$$

$$\Rightarrow -1 < -\pi^2 f^2 LC < 0$$

$$\Rightarrow -1 < -\frac{f^2}{\left(\frac{1}{\pi^2 LC}\right)} < 0 \longrightarrow \textcircled{1}$$

from the condition of cut-off frequencies

$$\Rightarrow \frac{Z_1}{4Z_2} = 0 \quad \text{and} \quad Z_1 = -4Z_2$$

$$\Rightarrow Z_1 = 0$$

$$j\omega L = -\frac{4}{j\omega C}$$

$$\Rightarrow j\omega L = 0$$

$$j^2 \omega^2 = -\frac{4}{LC}$$

$$\Rightarrow f = 0$$

$$\omega^2 = \frac{4}{LC} \Rightarrow f_c^2 = \frac{1}{\pi^2 LC}$$

$$f_c = \frac{1}{\pi \sqrt{LC}} \checkmark$$

Where f_c is known as cut-off frequency or nominal
(Which separates stop band & transmission band)

substituting f_c in eq. ①

$$\Rightarrow -1 < -\frac{f^2}{f_c^2} < 0$$

$$\Rightarrow -1 < -\left(\frac{f}{f_c}\right)^2 < 0$$

from lower limit

$$\Rightarrow -1 < -\left(\frac{f}{f_c}\right)^2$$

$$\Rightarrow -\left(\frac{f}{f_c}\right)^2 > -1$$

$$\Rightarrow \left(\frac{f}{f_c}\right)^2 < 1$$

$$\Rightarrow f < f_c$$

Upper limit

$$-\left(\frac{f}{f_c}\right)^2 < 0$$

$$\left(\frac{f}{f_c}\right)^2 > 0$$

$$f > (f_c \times 0)$$

$$f > 0$$

The range of frequencies that the filter can transmit is $0 < f < f_c$.

$$\frac{1}{j\omega C} = -\frac{j}{\omega C}$$

$$\frac{1}{4} = \omega^2 LC$$

$$\Rightarrow \frac{1}{4f_c^2 LC} = \frac{1}{4}$$


$$\Rightarrow f_c^2 = \frac{1}{16\pi^2 LC}$$

$$\Rightarrow f_c = \frac{1}{4\pi \sqrt{LC}}$$

→ As the filter allows the frequencies below a cut off frequencies it is a Low pass filter.

$$0 < f < f_c$$

Attenuation(α)

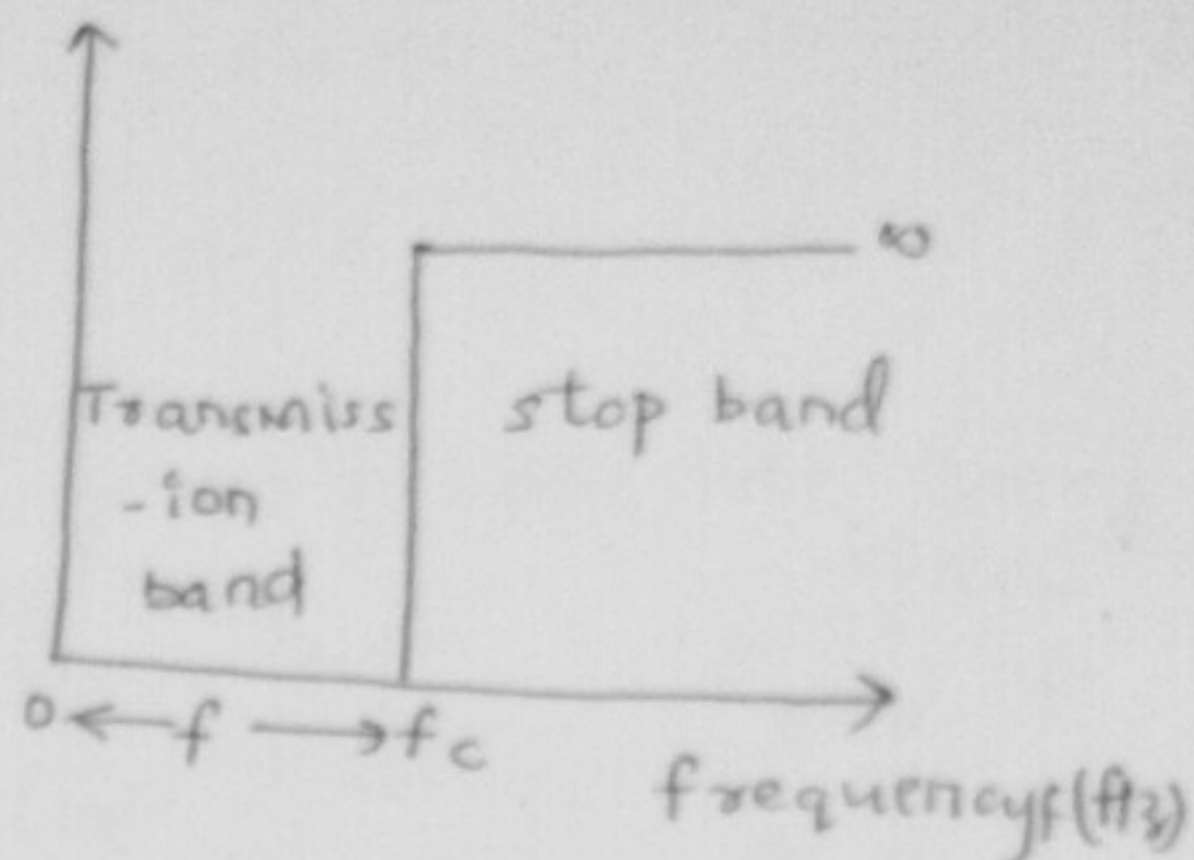

Symmetrical T-filter:-

→ We know that the configuration of symmetrical T-filter is,


here,

$$Z_1 = j\omega L$$

$$Z_2 = -jX_c$$

$$\text{i.e., } \frac{Z_1}{2Z_2} = \frac{j\omega L}{2} = j\omega\left(\frac{L}{2}\right)$$

$$Z_2 = \frac{1}{j\omega C}$$

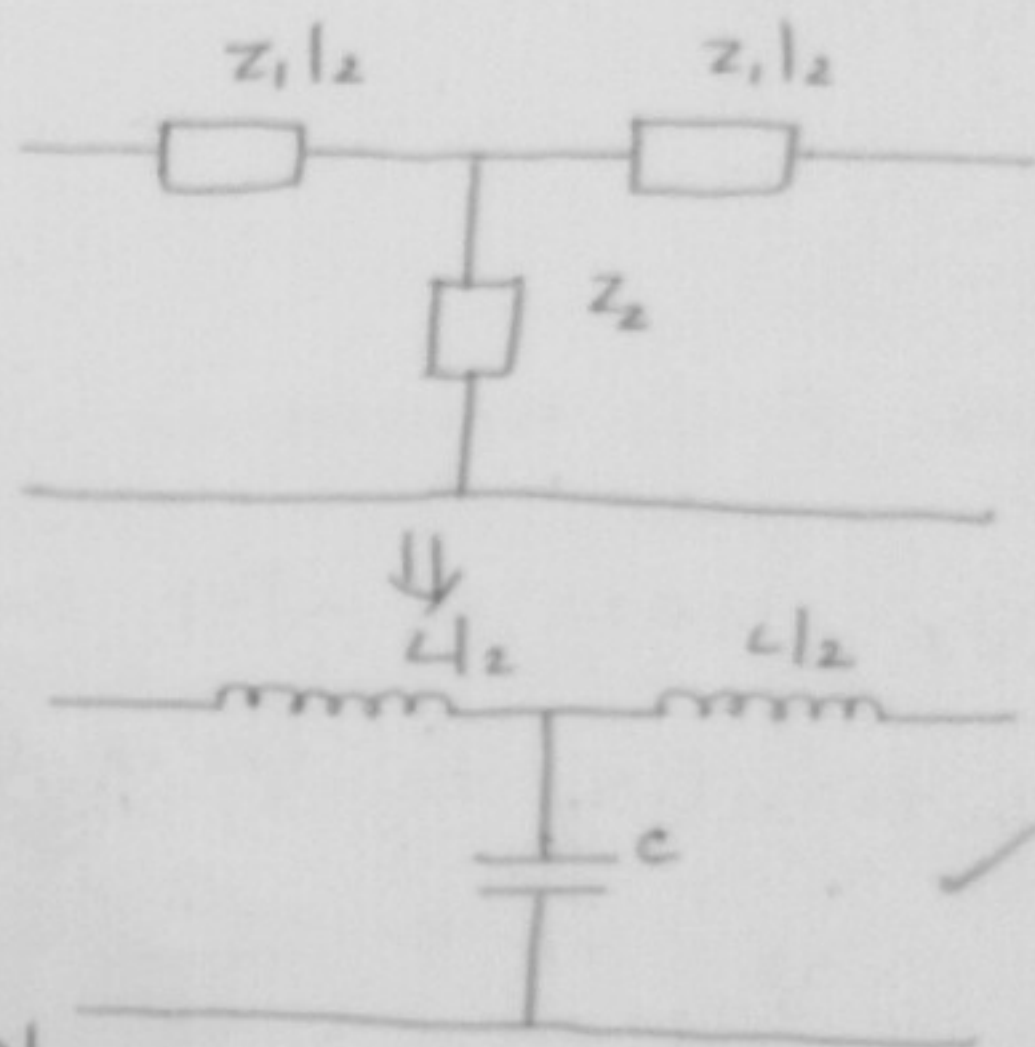

→ The characteristic impedance of symmetrical T-network, is

$$\downarrow Z_{OT} = \sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$

$$\Rightarrow \frac{Z_1}{4Z_2} = -\left(\frac{f}{f_c}\right)^2 = \sqrt{K^2 \left(1 - \left(\frac{f}{f_c}\right)^2\right)}$$

$$Z_1 Z_2 = K^2$$

1. When $f=0 \Rightarrow Z_{OT} = K = \text{real}$



2. When $f < f_c \Rightarrow \frac{f}{f_c} < 1 \Rightarrow \left(\frac{f}{f_c}\right)^2 < 1 \Rightarrow 1 - \left(\frac{f}{f_c}\right)^2 > 0$

$\Rightarrow Z_{OT} > 0$ (real value)

3. When $f = f_c \Rightarrow Z_{OT} = 0$

4. When $f > f_c \Rightarrow \left(\frac{f}{f_c}\right) > 1 \Rightarrow \left(\frac{f}{f_c}\right)^2 > 1 \Rightarrow 1 - \left(\frac{f}{f_c}\right)^2 < 0$ 3(ii)

Impedance diagram

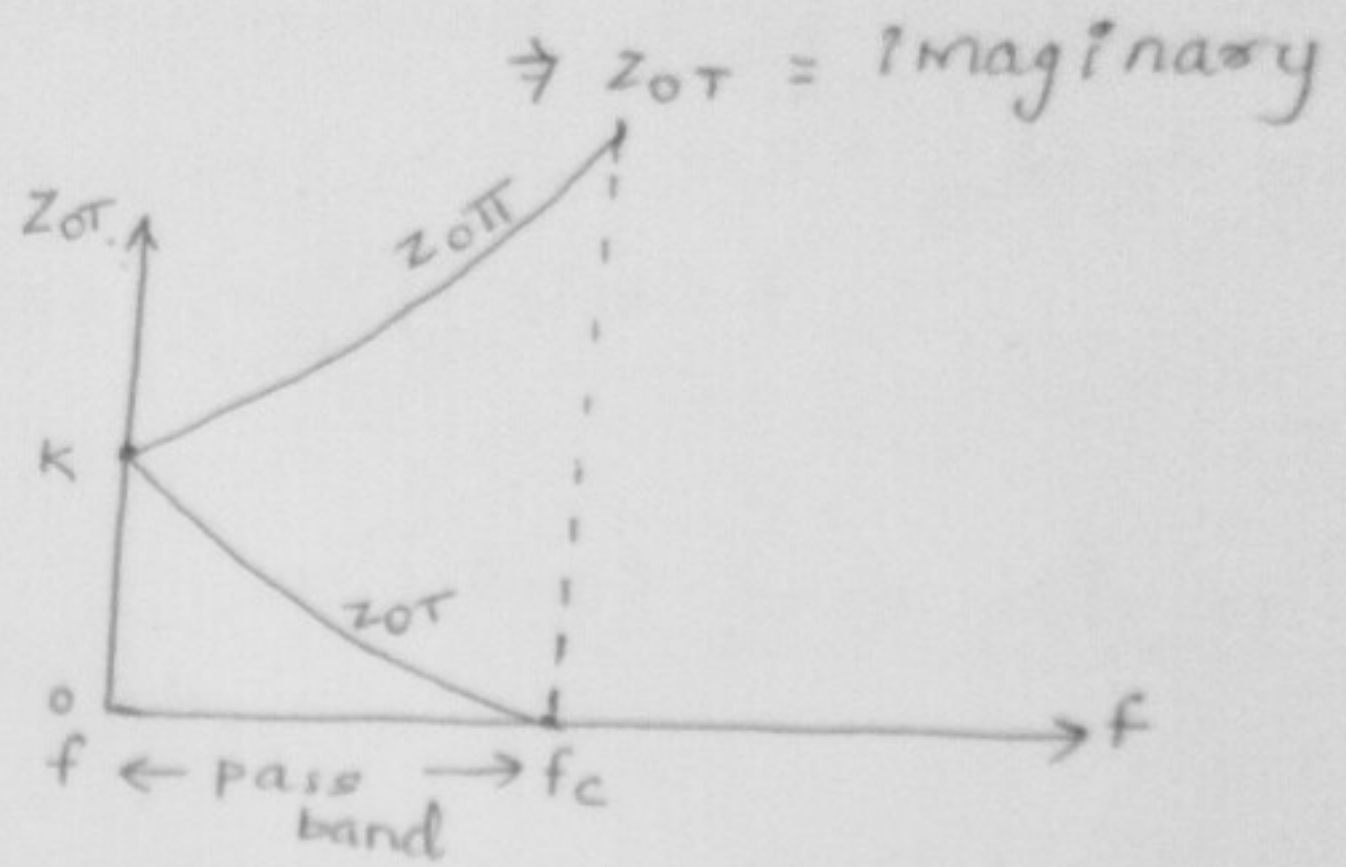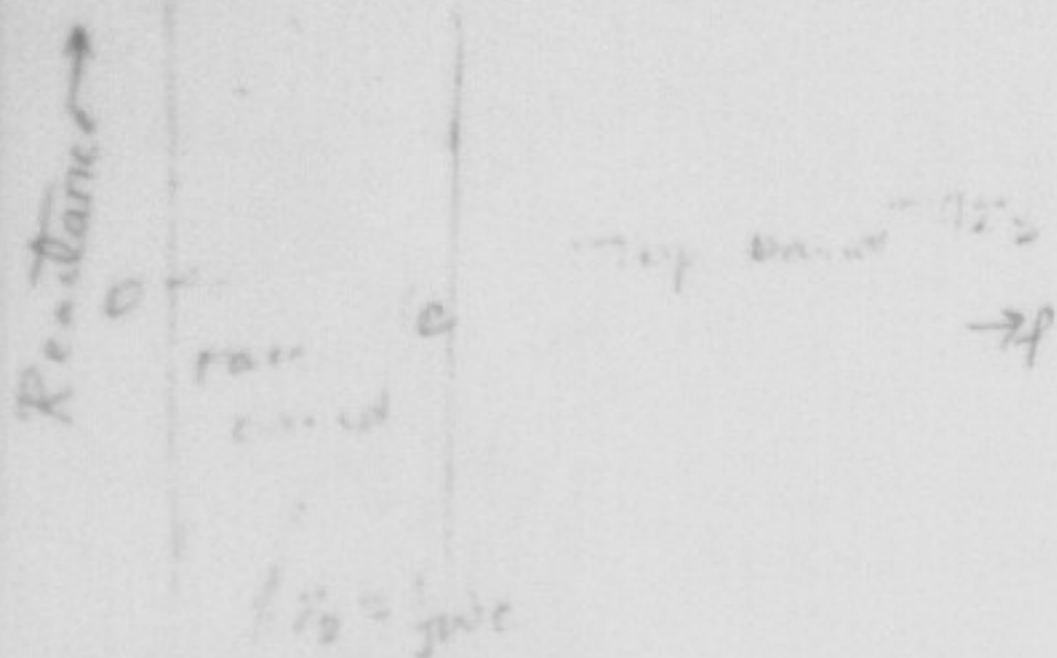


Symmetrical π -filter:-

$\Rightarrow$ we know that symmetrical π -configuration is,

$$\Rightarrow Z_1 = j\omega L$$

$$Z_2 = \frac{1}{j\omega C}$$
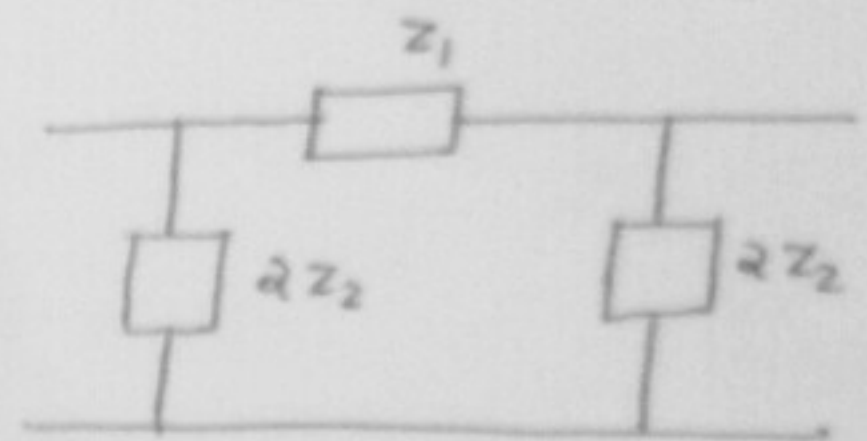
$$\Rightarrow 2Z_2 = \frac{2}{j\omega C} = \frac{1}{j\omega\left(\frac{C}{2}\right)}$$




$\Rightarrow$ The characteristic impedance of symmetrical π -network is,

$$\Rightarrow Z_{OT} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}}$$

$$\Rightarrow Z_{OT} = \sqrt{\frac{k^2}{1 + \left(\frac{f}{f_c}\right)^2}} = \sqrt{\frac{k^2}{1 - \left(\frac{f}{f_c}\right)^2}}$$
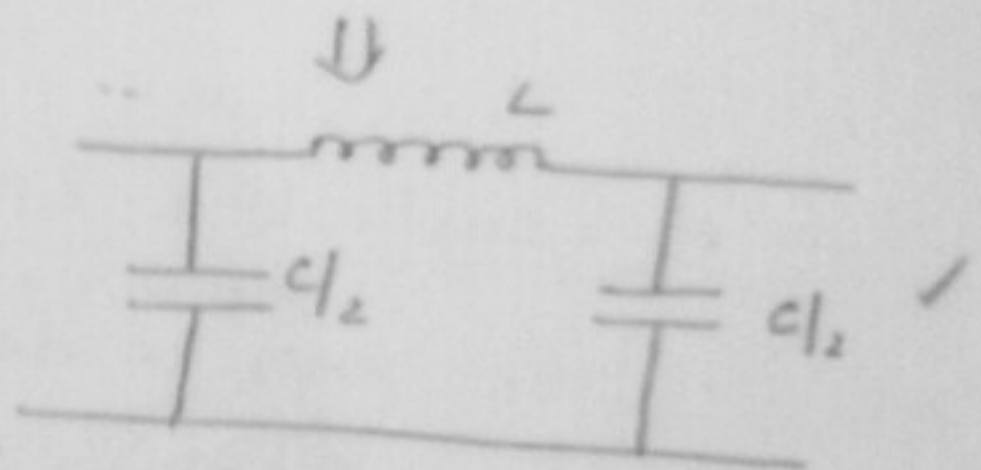
$$\Rightarrow Z_{OT} = \frac{k}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$



1. When $f=0 \Rightarrow Z_{OT} = k$ (real)

2. When $f < f_c \Rightarrow \frac{f}{f_c} < 1 \Rightarrow 1 - \left(\frac{f}{f_c}\right)^2 > 0 \Rightarrow Z_{OT} = \text{real}(\uparrow)$

3. When $f > f_c \Rightarrow Z_{OT} = \text{imaginary.}$

4. When $f = f_c \Rightarrow Z_{OT} = \infty$

Variation of α, β with frequency :-

Under condition :-
 $\Rightarrow$ Pass Band $\alpha = 0$

$$\beta = 2 \sin^{-1} \left(\sqrt{\frac{Z_1}{4Z_2}} \right) = 2 \sin^{-1} \left(j \frac{f}{f_c} \right)$$

$$\cosh^{-1} \left(\frac{5}{4} \right) = 0.69$$


$$\cosh^{-1} \left(\frac{8}{4} \right) = 1.31$$

$$\cosh^{-1} \left(\frac{10}{4} \right) = 1.56$$

Under stop band condition;

$$\alpha = 2 \cosh^{-1} \left(\sqrt{\frac{Z_1}{4Z_2}} \right) = 2 \cosh^{-1} \left(j \frac{f}{f_c} \right)$$

$$\beta = \pi$$

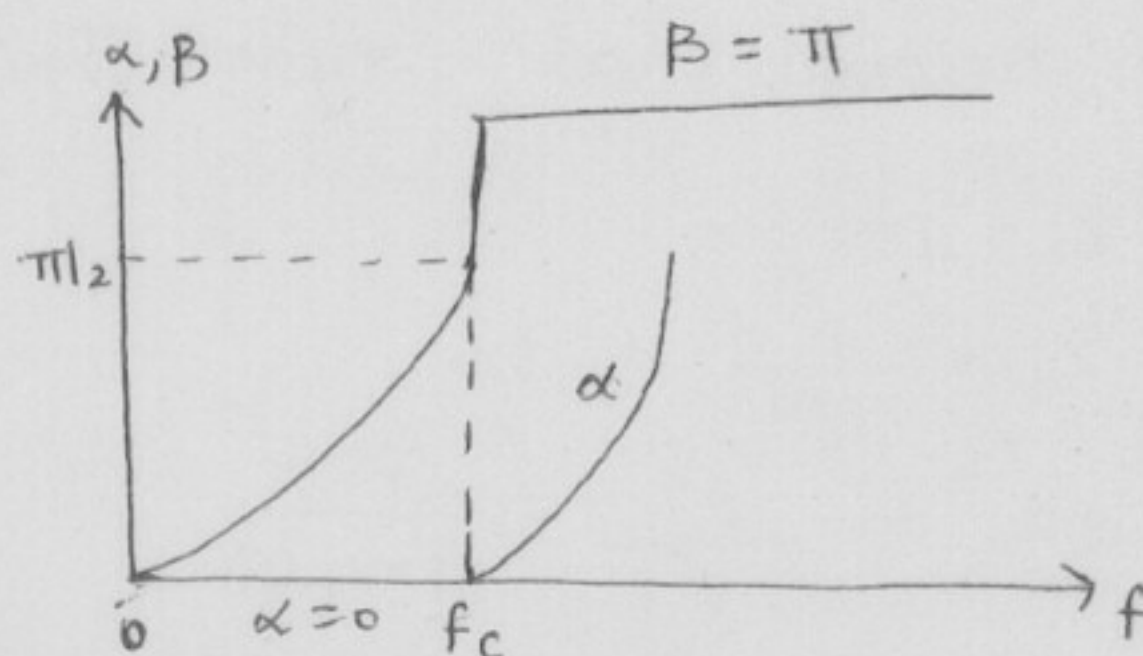

Design of constant-k LPF :-

$\Rightarrow$ Any filter can be designed for a specified values of cut-off frequency and nominal impedance i.e., always

a designer will be provided with k and f_c value.

$\Rightarrow$ from the basics $\Rightarrow k^2 = \frac{L}{C} \Rightarrow L = k^2 C \rightarrow \text{①}$

of constant-k

Low pass filter, $\Rightarrow k = \sqrt{\frac{L}{C}}$

We know that

$$f_c = \frac{1}{\pi \sqrt{LC}}$$

$$\Rightarrow f_c^2 = \frac{1}{\pi^2 LC}$$

$$\Rightarrow f_c^2 \pi^2 LC = 1 \quad \text{from eq. ①}$$

$$\Rightarrow f_c^2 \pi^2 k^2 C \cdot C = 1$$

$$\Rightarrow C^2 = \frac{1}{f_c^2 \pi^2 k^2}$$

$$\Rightarrow C = \frac{1}{\pi k f_c} \quad \text{farads}$$

$$L = k^2 C$$

$$L = k^2 \frac{1}{\pi k f_c}$$

$$L = \frac{k}{\pi f_c} \quad \text{Henrys}$$

2. Constant-k High pass filter:- A

3(12)

→ Where the series arm impedance is capacitance and the shunt arm impedance is inductance, then that filter exhibits the characteristics of a HPF,

→ Let $z_1 = \frac{1}{j\omega C}$ and $z_2 = j\omega L$

→ then $z_1 z_2 = \frac{1}{j\omega C} \cdot j\omega L = \frac{L}{C} = k^2 \Rightarrow k^2 = \frac{L}{C}$

→ From the pass-band condition,

$\Rightarrow -1 < \frac{z_1}{4z_2} < 0 \Rightarrow -1 < \frac{1}{4j^2\omega^2 LC} < 0.$

$\Rightarrow -1 < \frac{-1}{4(4\pi^2 f^2)LC} < 0 \Rightarrow -1 < \frac{-1}{16\pi^2 f^2 LC} < 0.$

$\Rightarrow -1 < \frac{-\left(\frac{1}{16\pi^2 LC}\right)}{f^2} < 0 \rightarrow \textcircled{1}$

→ from the condition of cut-off frequencies,

Upper boundary

$\Rightarrow \frac{z_1}{4z_2} = 0$

$\Rightarrow z_1 = 0 \Rightarrow \frac{1}{j\omega C} = 0 \Rightarrow \frac{1}{f} = 0$

$\Rightarrow f = \infty$

Lower limit

$z_1 = -4z_2$

$\Rightarrow \frac{1}{j\omega C} = -4j\omega L \Rightarrow \omega^2 LC = \frac{1}{4}$

$\Rightarrow 4\pi^2 f_c^2 LC = \frac{1}{4}$

$\Rightarrow f_c^2 = \frac{1}{16\pi^2 LC}$

$\Rightarrow \therefore f_c = \frac{1}{4\pi\sqrt{LC}}$ is known as

cut-off frequency (or) nominal frequency.

→ substituting f_c in eq. ①.

$\Rightarrow -1 < -\left(\frac{f_c^2}{f^2}\right) < 0 \Rightarrow -1 < -\left(\frac{f_c}{f}\right)^2 < 0.$

→ Lower limit

$\Rightarrow -1 < -\left(\frac{f_c}{f}\right)^2$

$\Rightarrow -\left(\frac{f_c}{f}\right)^2 > -1$

$\Rightarrow \left(\frac{f_c}{f}\right)^2 < 1$

$\Rightarrow f_c < f$

$\Rightarrow \boxed{f > f_c}$

Upper limit


$\Rightarrow -\left(\frac{f_c}{f}\right)^2 < 0$

$\Rightarrow \left(\frac{f_c}{f}\right)^2 > 0 \Rightarrow \left(\frac{f}{f_c}\right)^2 < \frac{1}{0}$

$\Rightarrow f_c > 0 \Rightarrow \boxed{f < \infty}$

$\Rightarrow$ The range of frequencies that the filter can transmit is for $f > f_c$ and $f < \infty$. $\Rightarrow f_c < f < \infty$
 stop band $\Rightarrow 0 < f < f_c$ $\alpha \neq 0$
 pass band $\Rightarrow f_c < f < \infty$ $\alpha = 0$
 $\rightarrow$ HPF is one which allows the frequencies above the cut-off frequencies it is a High pass filter.

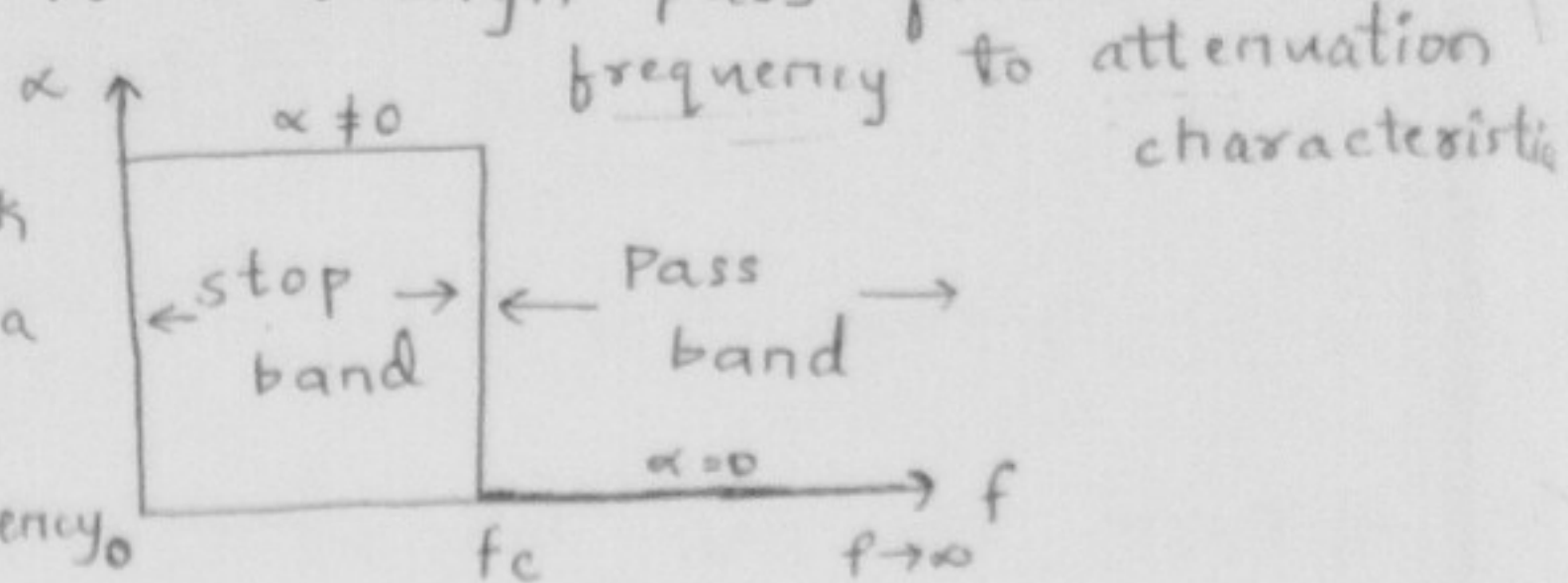Note:- The constructed constant-k filter has a pass band above a cut off frequency and stop below the cut-off frequency.
 Hence it is a HPF




Symmetrical T-filter:-

$\Rightarrow$ We know that the configuration of symmetrical T-filter


is, $z_1 = \frac{1}{j\omega C}$ and $z_2 = j\omega L$

$\Rightarrow$ i.e., $\frac{z_1}{2} = \frac{1}{j\omega C/2} = \left(\frac{1}{j\omega C}\right) = \frac{1}{j\omega(z_c)}$

$\frac{z_1}{2} = z_c$

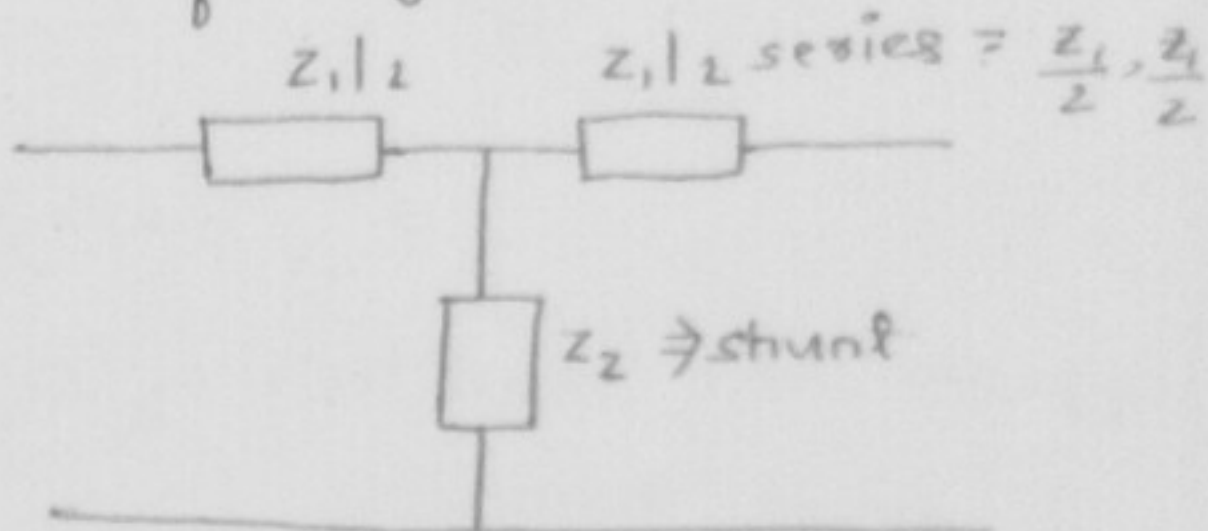

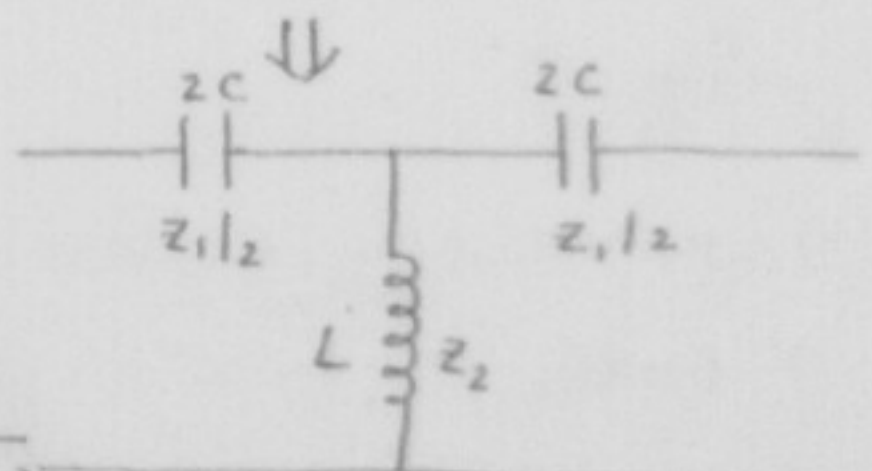$\Rightarrow$ The characteristic impedance of symmetrical T-network is



$\Rightarrow Z_{or} = \sqrt{\frac{z_1^2}{4} + z_1 z_2} = \sqrt{z_1 z_2 \left(1 + \frac{z_1}{4z_2}\right)}$

$Z_{or} = \sqrt{k^2 \left(1 - \left(\frac{f_c}{f}\right)^2\right)}$ (since $\frac{z_1}{4z_2} = -\left(\frac{f_c}{f}\right)^2$ and $z_1 z_2 = k^2$)

1. When $f = 0 \Rightarrow Z_{or} = (-ve \text{ value})$ imaginary.
2. When $f < f_c \Rightarrow \frac{f}{f_c} < 1 \Rightarrow f_c > f \Rightarrow \frac{f_c}{f} > 1 \Rightarrow \left(\frac{f_c}{f}\right)^2 > 1 \Rightarrow 1 - \left(\frac{f_c}{f}\right)^2 < 0$ (imaginary)
3. When $f = f_c \Rightarrow Z_{or} = 0$.
4. When $f > f_c \Rightarrow f_c < f \Rightarrow \left(\frac{f_c}{f}\right)^2 < 1 \Rightarrow 1 - \left(\frac{f_c}{f}\right)^2 > 0 \Rightarrow Z_{or} > 0$ (real value)

$f < f_c \Rightarrow f_c > f$
 $\Rightarrow \left(\frac{f_c}{f}\right)^2 > 1$
 $\Rightarrow 1 - \left(\frac{f_c}{f}\right)^2 < 0$

Symmetrical π -filter:-

→ We know that the configuration of symmetrical π -filter




→ $Z_1 = \frac{1}{j\omega C}$ and $Z_2 = j\omega L$

→ i.e., $2Z_2 = \frac{2}{1/j\omega L} \Rightarrow 2j\omega L \Rightarrow j\omega(2L)$

→ The characteristic impedance of symmetrical π -network is,

$$\Rightarrow Z_{0\pi} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}} = \sqrt{\frac{K^2}{1 - (\frac{f_c}{f})^2}}$$
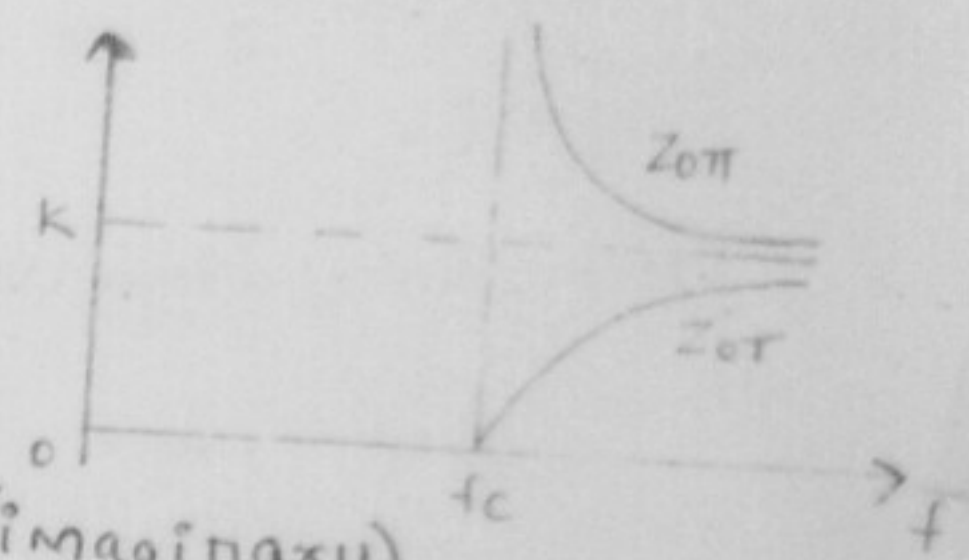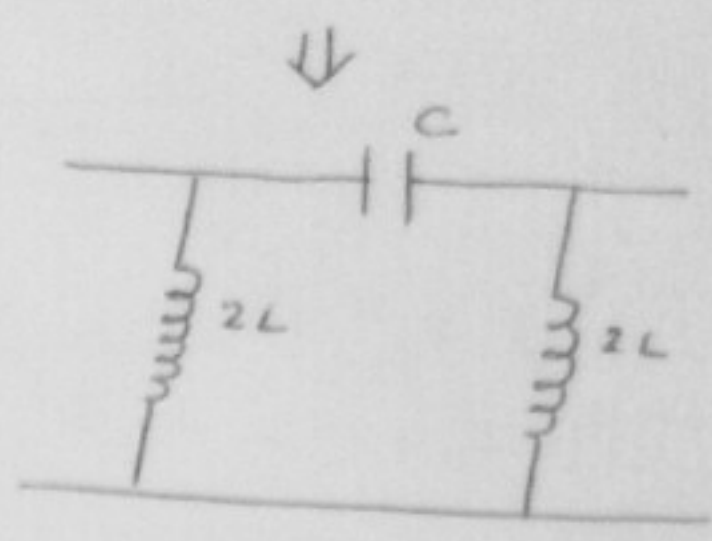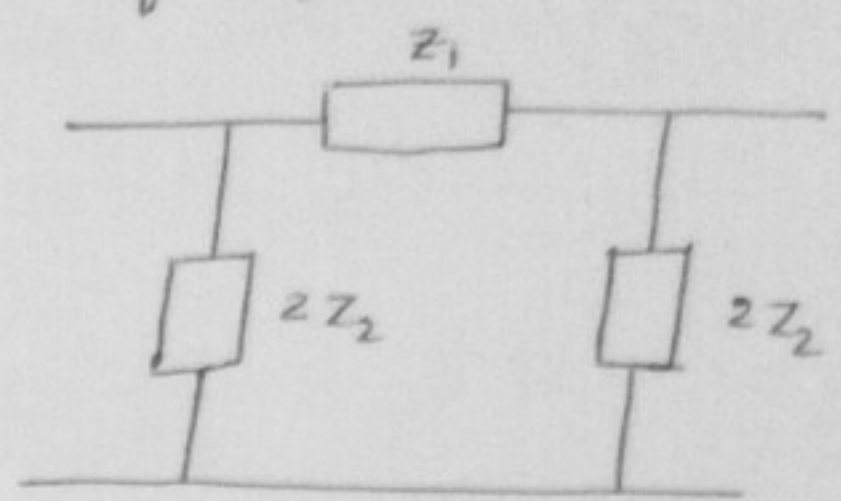
$$\Rightarrow Z_{0\pi} = \frac{K}{\sqrt{1 - (\frac{f_c}{f})^2}}$$



1. When $f=0 \Rightarrow Z_{0\pi} = \frac{0}{1-\infty} = 0$.
2. When $f < f_c \Rightarrow f_c > f \Rightarrow 1 - (\frac{f_c}{f})^2 < 0$ (imaginary)
3. When $f = f_c \Rightarrow f_c = f \Rightarrow Z_{0\pi} = \infty$
4. When $f > f_c \Rightarrow f_c < f \Rightarrow (\frac{f_c}{f})^2 < 1 \Rightarrow 1 - (\frac{f_c}{f})^2 > 0$ (real value)

Variation of α, β with frequency:-

1. Under pass band condition:- $\alpha = 0$

$$\beta = 2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}} = 2 \sin^{-1} \left(\sqrt{\frac{Z_1}{4Z_2}} \right)$$

$$\beta = 2 \sin^{-1} j \left(\frac{f_c}{f} \right) = 2 \sin^{-1} \left(j \frac{f_c}{f} \right)$$

2. Under stop band condition:-


$$\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}} = 2 \cosh^{-1} \left(j \frac{f_c}{f} \right) = 2 \cos^{-1} \left(\frac{f_c}{f} \right)$$

$$\beta = -\pi$$

$$\Rightarrow 2 \cos^{-1} \left(\frac{4}{5} \right) = 1.28$$

$$\Rightarrow 2 \cos^{-1} \left(\frac{4}{8} \right) = 2.09$$
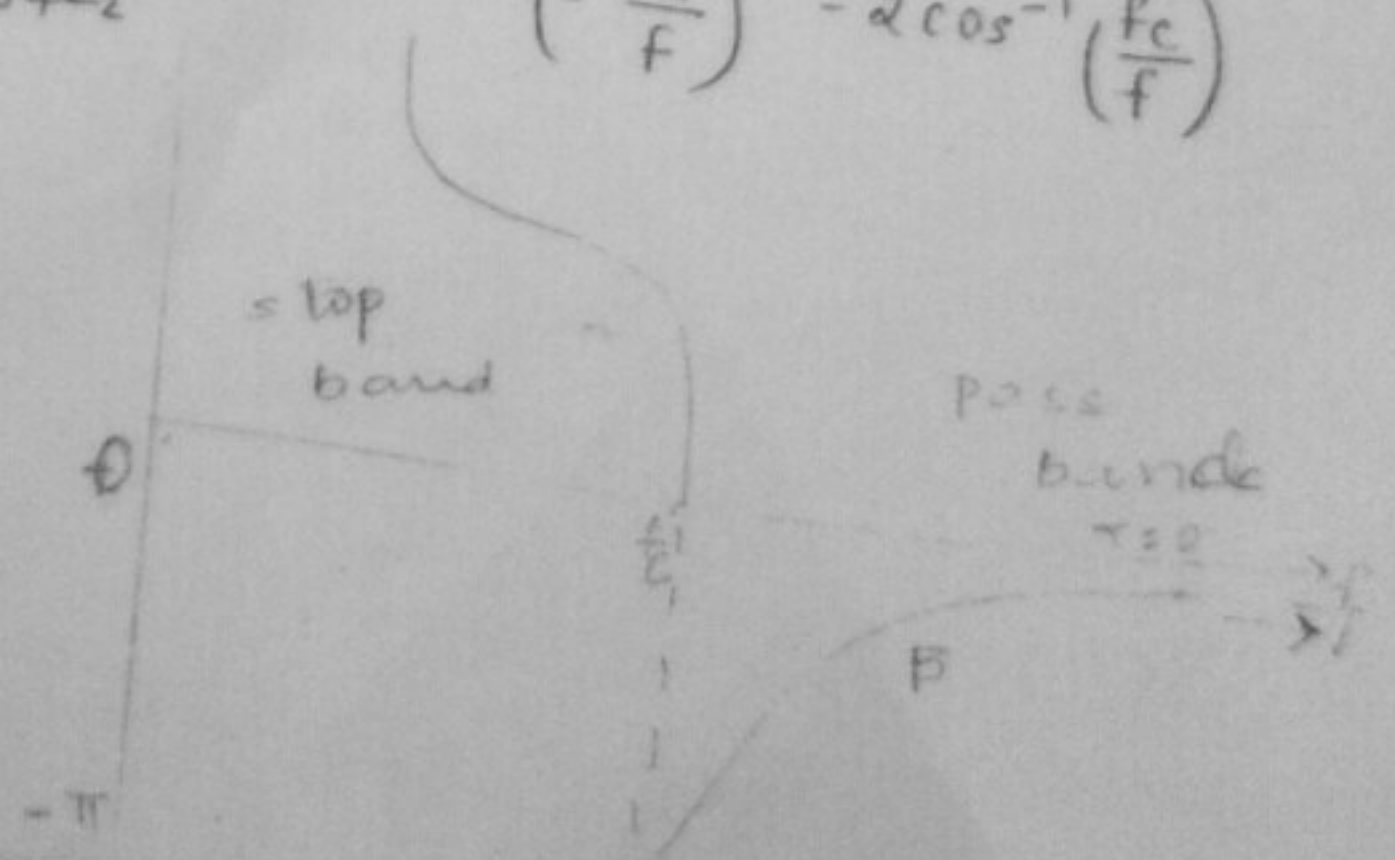
$$\Rightarrow 2 \cos^{-1} \left(\frac{4}{10} \right) = 2.31$$



1. When $f = \infty \Rightarrow Z_{0T} = k$


2. When $f = f_c \Rightarrow Z_{0T} = \infty$

(and it is real always)

Variation in characteristic impedance with respect to frequency:-

$$\Rightarrow f > f_c \Rightarrow \frac{f_c}{f} < 1 \Rightarrow \left(\frac{f_c}{f}\right)^2 < 1$$
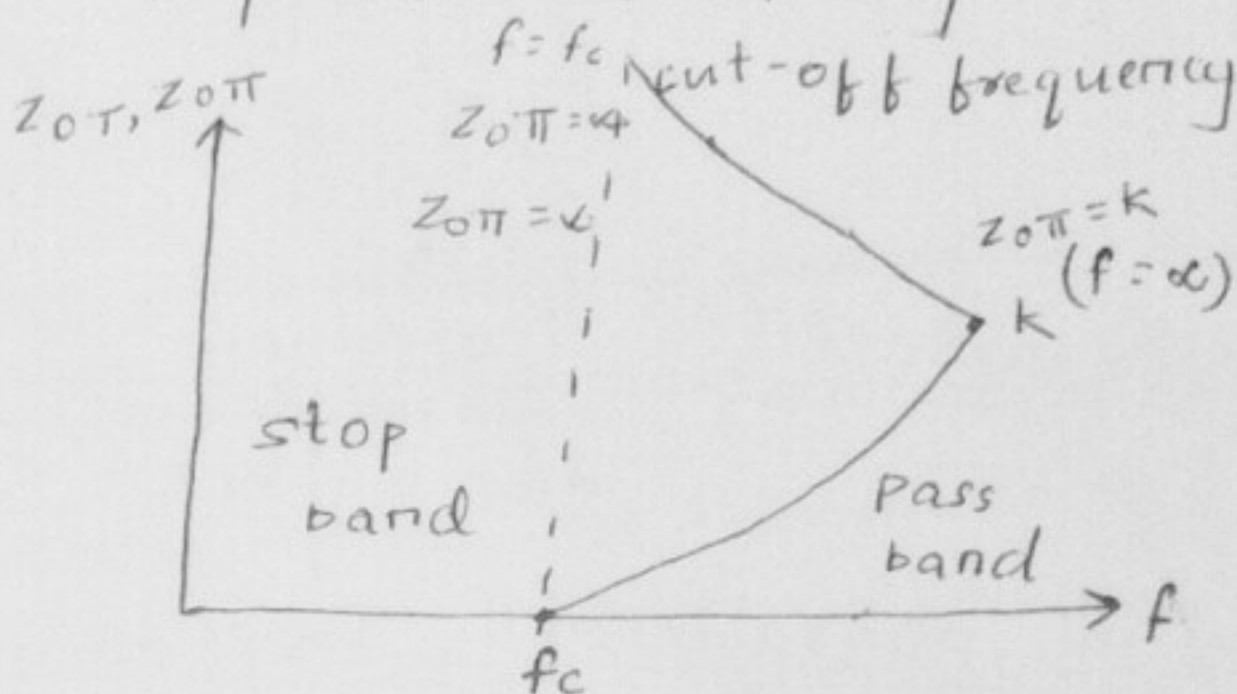
$$\Rightarrow \left(1 - \frac{(f_c)^2}{f^2}\right) > 0 \uparrow \uparrow$$



16/1/13

M-derived filters :- As the attenuation in the stop band for a prototype filter is not infinite (∞) is not sharp there is a need for us to go for a new filter which will produce sharp attenuation in the stop band. This can be achieved in 2 ways,

1. By cascading no. of prototype filters which has same characteristic impedance, same pass band & same stop band. However this is disadvantageous since the elements are not pure. (practically L, C will have some internal resistance).
2. Sharp attenuation will be achieved by deriving a new filter from the prototype which are usually known as M-derived filter. The condition for deriving a filter is the characteristic impedance should be same i.e., $Z_0 = Z_0'$ Where Z_0 is characteristic impedance of prototype filter.



Z_0' is characteristic impedance of derived filter

M-derived T-Section filter:-

→ We know that the basic T-section filter is,

⇒ and m-derived T-section

will be,

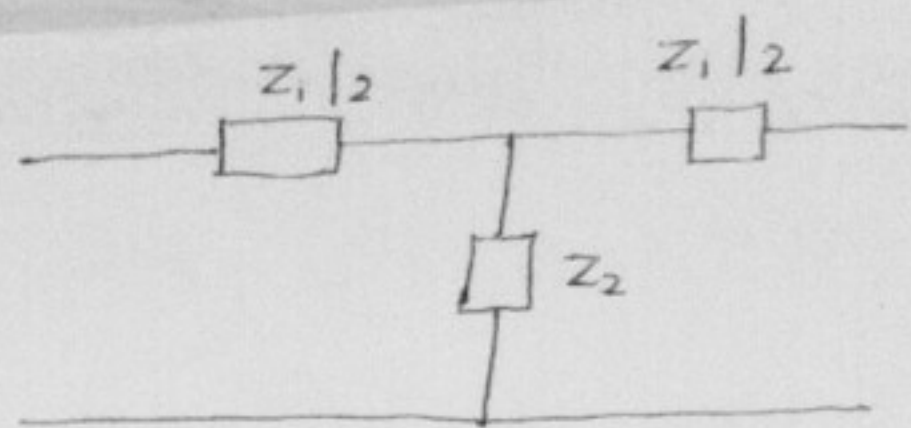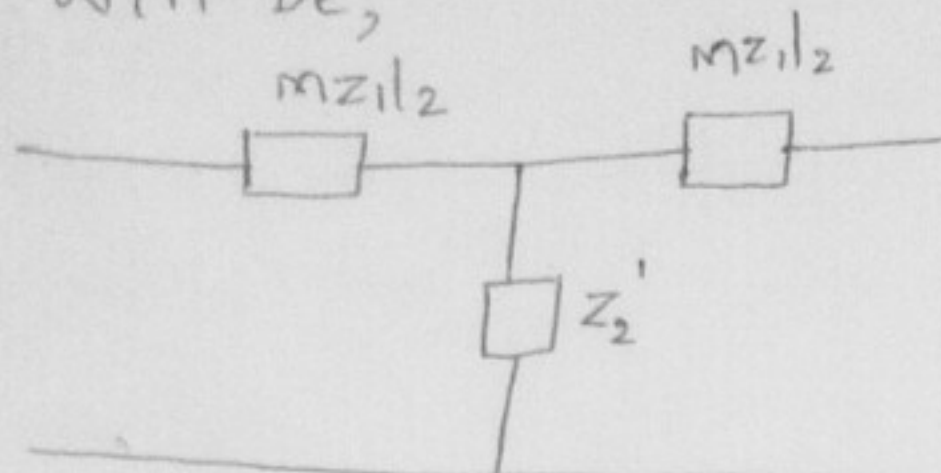

⇒ Characteristic Impedance of prototype T-filter is:-

$$Z_{OT} = \sqrt{Z_1 Z_2 + \frac{Z_1^2}{4}}$$

⇒ The characteristic Impedance of m-derived T-section filter,
is

$$\Rightarrow Z_{in} = \left(Z_0 + \frac{mZ_1}{2} \right) \parallel Z_2' + \frac{mZ_1}{2}$$

$$\Rightarrow Z_{in} = \frac{mZ_1}{2} + \left(Z_2' \parallel Z_0 + \frac{mZ_1}{2} \right)$$

$$\Rightarrow Z_{in} = \frac{mZ_1}{2} + \frac{Z_2' \cdot \left(Z_0 + \frac{mZ_1}{2} \right)}{Z_2' + Z_0 + \frac{mZ_1}{2}}$$

Symmetrical $Z_{in} = Z_0$

$$\Rightarrow Z_0 = \frac{mZ_1}{2} \left(\frac{Z_2' + Z_0 + \frac{mZ_1}{2}}{Z_2' + Z_0 + \frac{mZ_1}{2}} \right) + \frac{Z_2' Z_0 + Z_2' \frac{mZ_1}{2}}{Z_2' + Z_0 + \frac{mZ_1}{2}}$$

$$\Rightarrow \cancel{Z_2' Z_0} + Z_0^2 + \frac{mZ_1}{2} Z_0 = \cancel{Z_2' \frac{mZ_1}{2}} + \frac{mZ_1}{2} Z_0 + \frac{m^2 Z_1^2}{4} + \cancel{Z_2' Z_0} + \frac{mZ_1 Z_2'}{2}$$

$$\Rightarrow Z_0^2 = mZ_1 \cdot Z_2' + \frac{m^2 Z_1^2}{4}$$




$$\Rightarrow Z_0 = \sqrt{\frac{m^2 Z_1^2}{4} + mZ_1 Z_2'} = Z_{OT}$$

⇒ From, the condition of derivation, we have

$$\Rightarrow \boxed{Z_{OT} = Z_{OT}'}$$

$$\Rightarrow Z_1 Z_2 + \frac{Z_1^2}{4} = m^2 \frac{Z_1^2}{4} + mZ_1 Z_2'$$
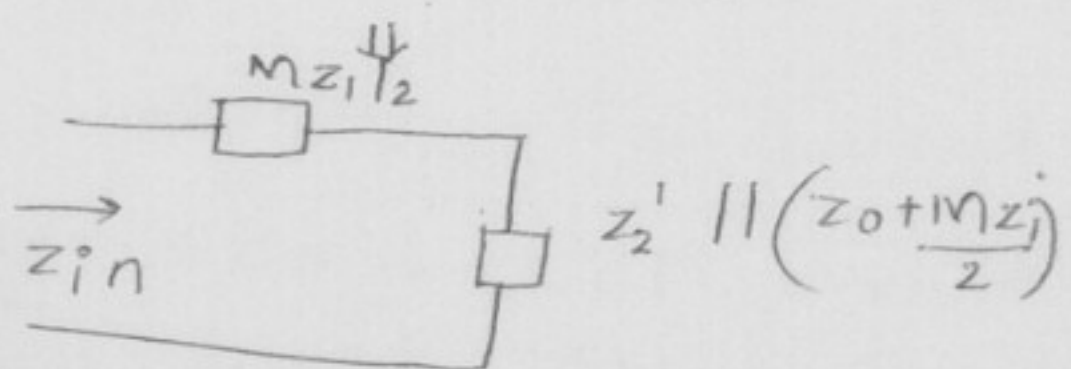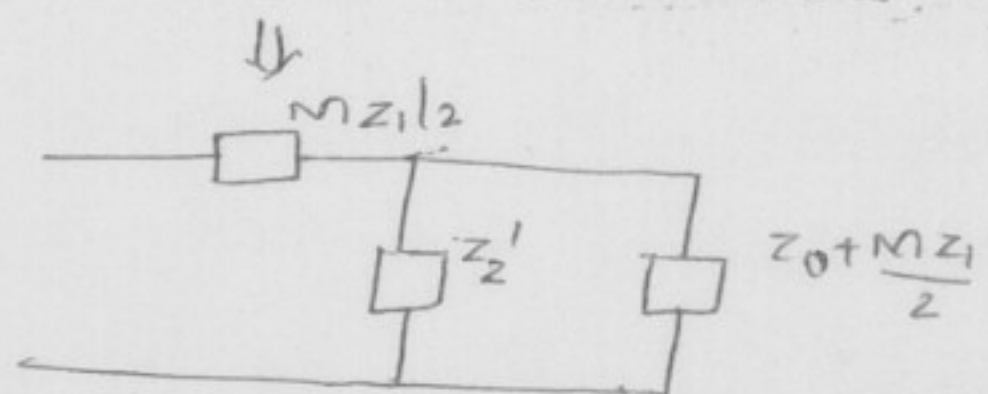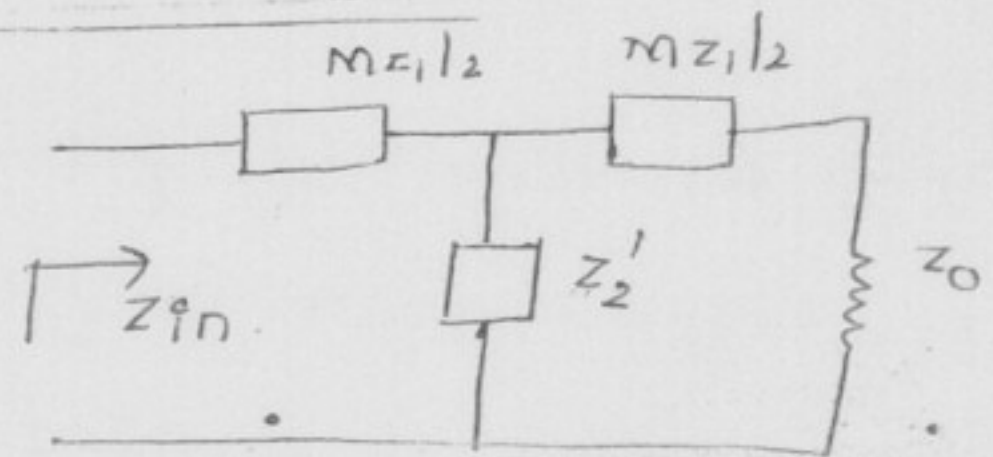
$$\Rightarrow Z_1 Z_2 - mZ_1 Z_2' = (m^2 - 1) \frac{Z_1^2}{4}$$




$$\Rightarrow M Z_1 Z_2' = (1 - M^2) \frac{Z_1^2}{4} + Z_1 Z_2$$

$$\Rightarrow Z_2' = (1 - M^2) \frac{Z_1}{4M} + \frac{Z_2}{M}$$

$$\Rightarrow Z_2' = \left(\frac{1 - M^2}{4M} \right) Z_1 + \frac{Z_2}{M}$$

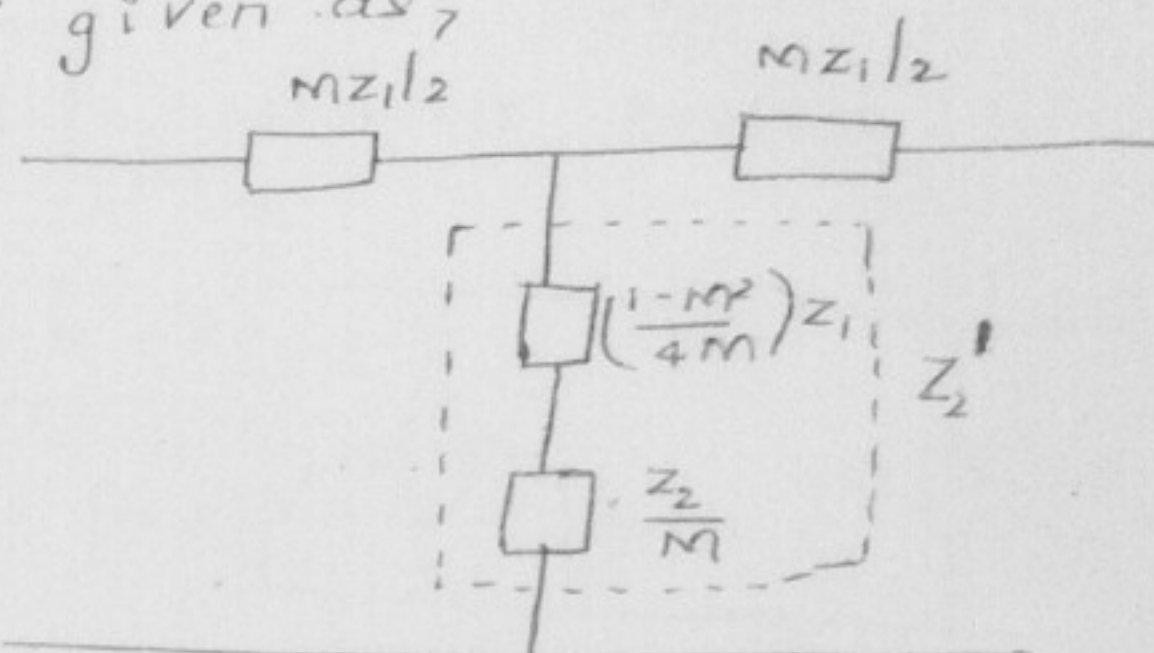$\Rightarrow$ Hence for an m -derived T -section filter, the shunt impedance is not a single impedance it is the series combination of two impedances. And the symmetrical m -derived T -section is given as,



m -derived Low pass filter of T -section:-

$$\Rightarrow \text{series} \Rightarrow \frac{1}{j\omega C} = Z_2$$

$$\text{shunt} \Rightarrow j\omega L = Z_1$$

$$\Rightarrow \frac{M Z_1}{2} = \frac{M(j\omega L)}{2} = j\omega \left(\frac{ML}{2} \right)$$

$$\Rightarrow \left(\frac{1 - M^2}{4M} \right) Z_1 = \left(\frac{1 - M^2}{4M} \right) (j\omega L) = j\omega \left(\frac{1 - M^2}{4M} \right) L$$

$$\Rightarrow \frac{Z_2}{M} = \frac{1}{j\omega(MC)} = \frac{-j}{\omega(MC)}$$


m -derived High pass filter of T -section:-

$$Z_1 = \frac{1}{j\omega C}, Z_2 = j\omega L$$

$$\Rightarrow \frac{M Z_1}{2} = \frac{M}{2j\omega C} = \frac{1}{j\omega} \left(\frac{M}{2C} \right) = \frac{-j}{\omega} \left(\frac{M}{2C} \right)$$

$$\Rightarrow \left(\frac{1 - M^2}{4M} \right) Z_1 = \frac{1}{j\omega} \left(\frac{1 - M^2}{4M} \right) \frac{1}{C} = \frac{-j}{\omega} \left(\frac{1 - M^2}{4M} \right) \frac{1}{C}$$

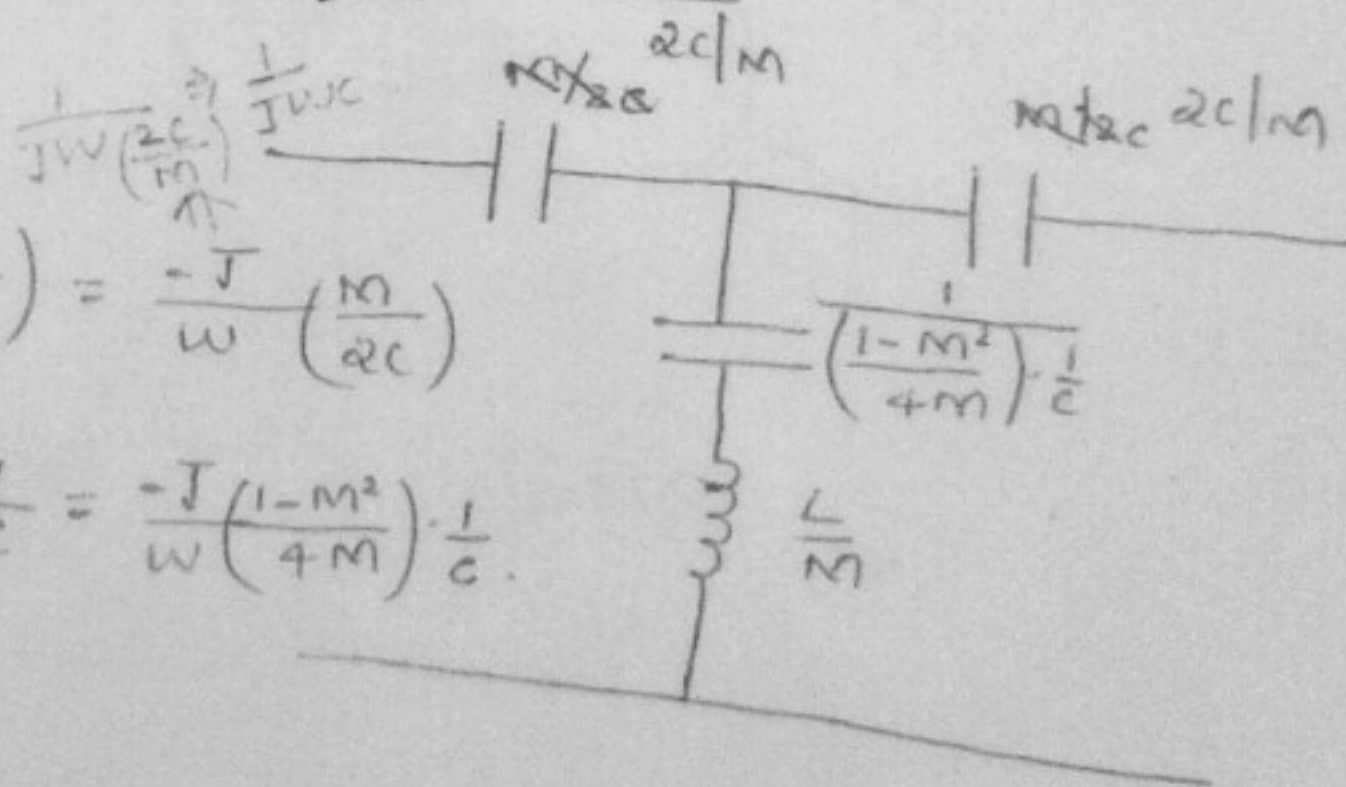
$$\Rightarrow \frac{Z_2}{M} = \frac{j\omega L}{M} = j\omega \left(\frac{L}{M} \right)$$



$$\Rightarrow \left(\frac{1-M^2}{4M}\right) Z_1 = \left(\frac{1-M^2}{4M}\right) \left(\frac{1}{j\omega C}\right)$$




$$= \frac{1}{j\omega} \left(\frac{1-M^2}{4Mc}\right)$$
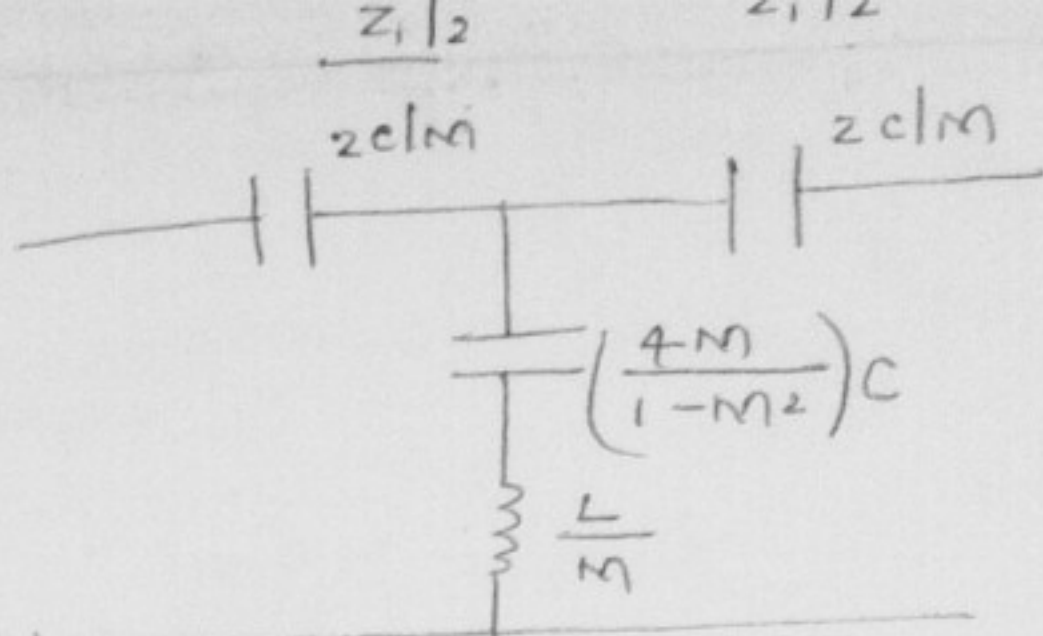
$$= \frac{1}{j\omega} \left(\frac{4Mc}{1-M^2}\right) = \frac{1}{j\omega C}$$



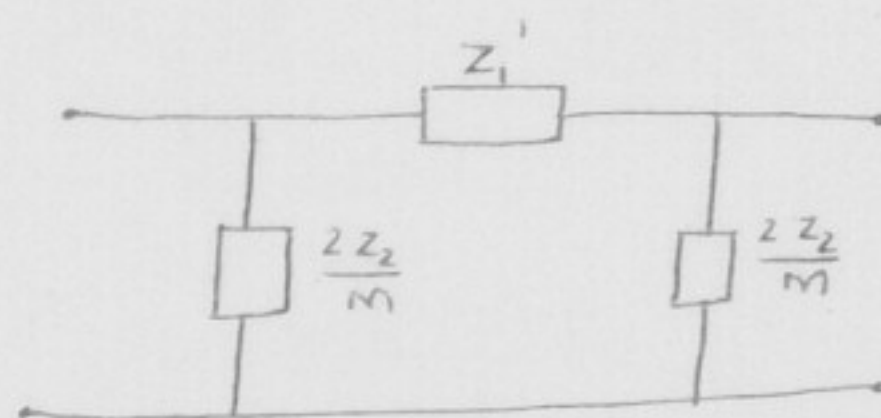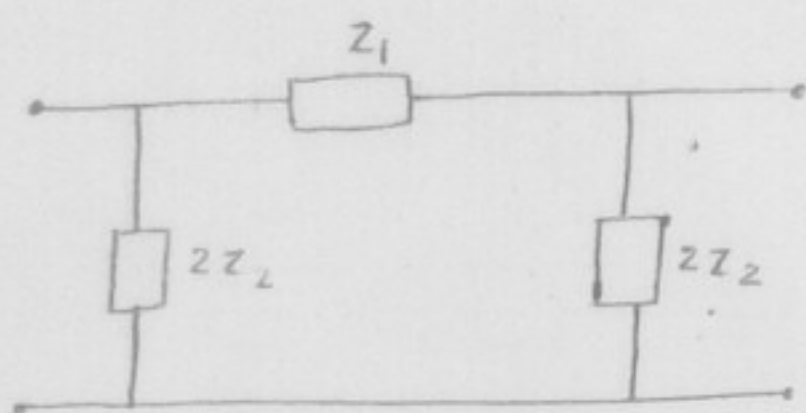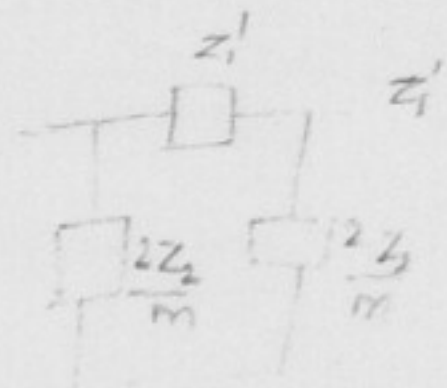2. M-derived π -section filter:-

→ we know the basic π -section filter and the m-derived π -section filter,




→ characteristic impedance of prototype π -filter is

$$Z_{0\pi} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}}$$


→ The characteristic impedance of m-derived π -section filter is,

$$\Rightarrow Z_{in} = \frac{2Z_2}{m} \parallel \left(Z_1' + \frac{Z_0 \frac{2Z_2}{m}}{Z_0 + \frac{2Z_2}{m}} \right)$$

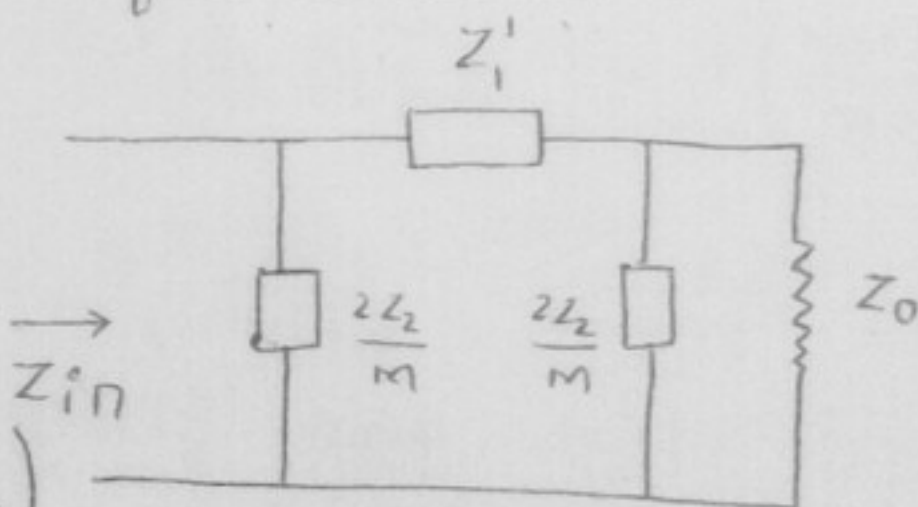
$$\Rightarrow Z_{in} = \frac{2Z_2}{m} \parallel \left(\frac{Z_1' (Z_0 + \frac{2Z_2}{m}) + Z_0 \frac{2Z_2}{m}}{Z_0 + \frac{2Z_2}{m}} \right)$$


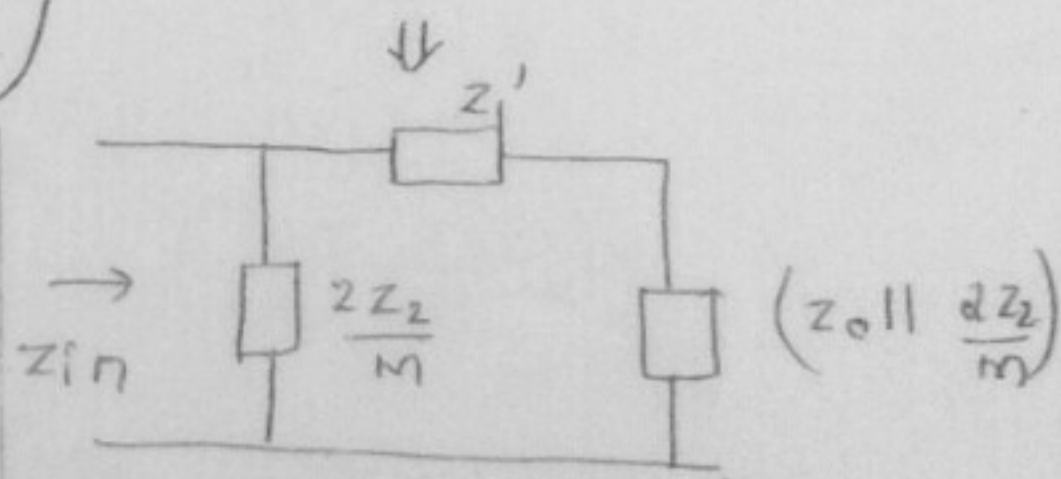
$$\Rightarrow Z_{in} = \frac{2Z_2}{m} \left(\frac{Z_1' Z_0 + \frac{2Z_2}{m} Z_1' + Z_0 \frac{2Z_2}{m}}{\frac{2Z_2}{m} + Z_0 + \frac{2Z_2}{m}} \right)$$


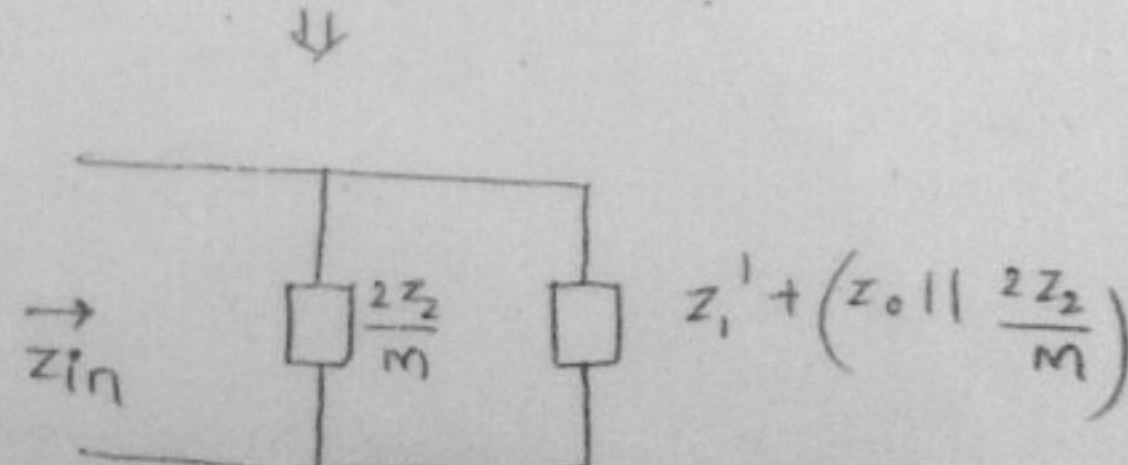
$$\Rightarrow Z_{in} = \frac{2Z_2}{m} \frac{Z_1' Z_0 + \frac{4Z_2^2}{m^2} Z_1' + \frac{4Z_2^2}{m^2} Z_0}{\frac{4Z_2}{m} + Z_0}$$



condition:-
 $\Rightarrow$ symmetrical $Z_{in} = Z_0$

3(16)

$$\Rightarrow Z_0 = \frac{\frac{2Z_2}{M} Z_1' Z_0 + \frac{4Z_2^2}{M^2} Z_1' + \frac{4Z_2^2}{M^2} Z_0}{\frac{4Z_2}{M} + Z_0}$$

$$\Rightarrow Z_0^2 + \frac{4Z_2}{M} Z_0 = \frac{2Z_2}{M} Z_1' Z_0 + \frac{4Z_2^2}{M^2} Z_1' + \frac{4Z_2^2}{M^2} Z_0$$

$$\Rightarrow Z_{in} = \frac{\frac{2Z_2}{M} \left(\frac{Z_1' Z_0 + \frac{2Z_2}{M} Z_1' + Z_0 \frac{2Z_2}{M}}{Z_0 + \frac{2Z_2}{M}} \right)}{\frac{2Z_2}{M} + \frac{2Z_2}{M} Z_1' + \frac{2Z_2}{M} Z_0 + Z_1' Z_0}$$

$$\Rightarrow Z_{in} = \frac{\frac{2Z_2}{M} \left(Z_1' Z_0 + \frac{2Z_2}{M} Z_1' + \frac{2Z_2}{M} Z_0 \right)}{\frac{2Z_2}{M} Z_0 + \left(\frac{2Z_2}{M} \right)^2 + \frac{2Z_2}{M} Z_1' + Z_1' Z_0 + \frac{2Z_2}{M} Z_0}$$

$\Rightarrow$ symmetrical $Z_{in} = Z_0$

$$\Rightarrow Z_0 = \frac{\frac{2Z_2}{M} \left(Z_1' Z_0 + \frac{2Z_2}{M} Z_1' + \frac{2Z_2}{M} Z_0 \right)}{\frac{2Z_2}{M} \left(Z_0 + \frac{2Z_2}{M} + Z_1' + Z_1' Z_0 \frac{M}{2Z_2} + Z_0 \right)}$$

$$\Rightarrow Z_0^2 + \frac{2Z_2}{M} Z_0 + Z_0 Z_1' + Z_1' Z_0^2 \frac{M}{2Z_2} + Z_0^2 = Z_1' Z_0 + \frac{2Z_2}{M} Z_1' + \frac{2Z_2}{M} Z_0$$

$$\Rightarrow 2Z_0^2 = \frac{2Z_2}{M} Z_1' - Z_1' Z_0^2 \frac{M}{2Z_2} \Rightarrow 2Z_0^2 + Z_0^2 Z_1' \frac{M}{2Z_2} = \frac{2Z_2}{M} Z_1'$$

$$\Rightarrow Z_0^2 \left(2 + Z_1' \frac{M}{2Z_2} \right) = \frac{2Z_2}{M} Z_1'$$

$$\Rightarrow Z_0^2 = \frac{\frac{2Z_2}{M} Z_1'}{2 + Z_1' \left(\frac{M}{2Z_2} \right)} = \frac{\frac{Z_2}{M} Z_1'}{1 + Z_1' \left(\frac{M}{4Z_2} \right)}$$

$$\Rightarrow Z_0^2 = \sqrt{\frac{\frac{Z_2}{M} Z_1'}{1 + Z_1' \frac{1}{4 \left(\frac{Z_2}{M} \right)}}} = Z_{0\pi}$$

⇒ From, the condition of derivation, we have

$$\Rightarrow Z_{0\pi} = Z_{0T}'$$

$$\Rightarrow \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}} = \sqrt{\frac{\frac{Z_1' Z_2}{M}}{1 + \frac{Z_1'}{4\left(\frac{Z_2}{M}\right)}}$$

$$\Rightarrow \frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}} = \frac{\frac{Z_2 Z_1'}{M}}{1 + \frac{Z_1' M}{4Z_2}}$$

$$\Rightarrow Z_1 Z_2 + \frac{Z_1' Z_1 M}{4} = \frac{Z_1' Z_2}{M} + \frac{Z_1 Z_1'}{4M}$$

$$\Rightarrow Z_1' \left(\frac{Z_1 M}{4} + \frac{Z_2}{M} - \frac{Z_1}{4M} \right) = -Z_1 Z_2$$

$$\Rightarrow Z_1' = \frac{Z_1 Z_2}{\frac{Z_1}{4M} + \frac{Z_2}{M} - \frac{M Z_1}{4}} = \frac{Z_1 Z_2}{\frac{Z_2}{M} + \frac{Z_1}{4M} (1 - M^2)}$$

⇒ Multiplying and


dividing by

$$\left(\frac{4M^2}{1-M^2} \right) \Rightarrow Z_1' = \frac{Z_1 Z_2 \times \left(\frac{4M^2}{1-M^2} \right)}{\left(\frac{Z_2}{M} + \frac{Z_1}{4M} (1-M^2) \right) \left(\frac{4M^2}{1-M^2} \right)} = \frac{Z_1 Z_2 \left(\frac{4M^2}{1-M^2} \right)}{\frac{Z_2 4M}{1-M^2} + \frac{Z_1 M^2}{M}}$$

$$\Rightarrow Z_1' = \frac{(M Z_1) \left(\frac{4M}{1-M^2} Z_2 \right)}{M Z_1 + \frac{4M}{1-M^2} Z_2}$$

∴ Hence for a m-derived π-section filter, the series arm impedance is a parallel combination of MZ_1 and $\frac{4M}{1-M^2} Z_2$.

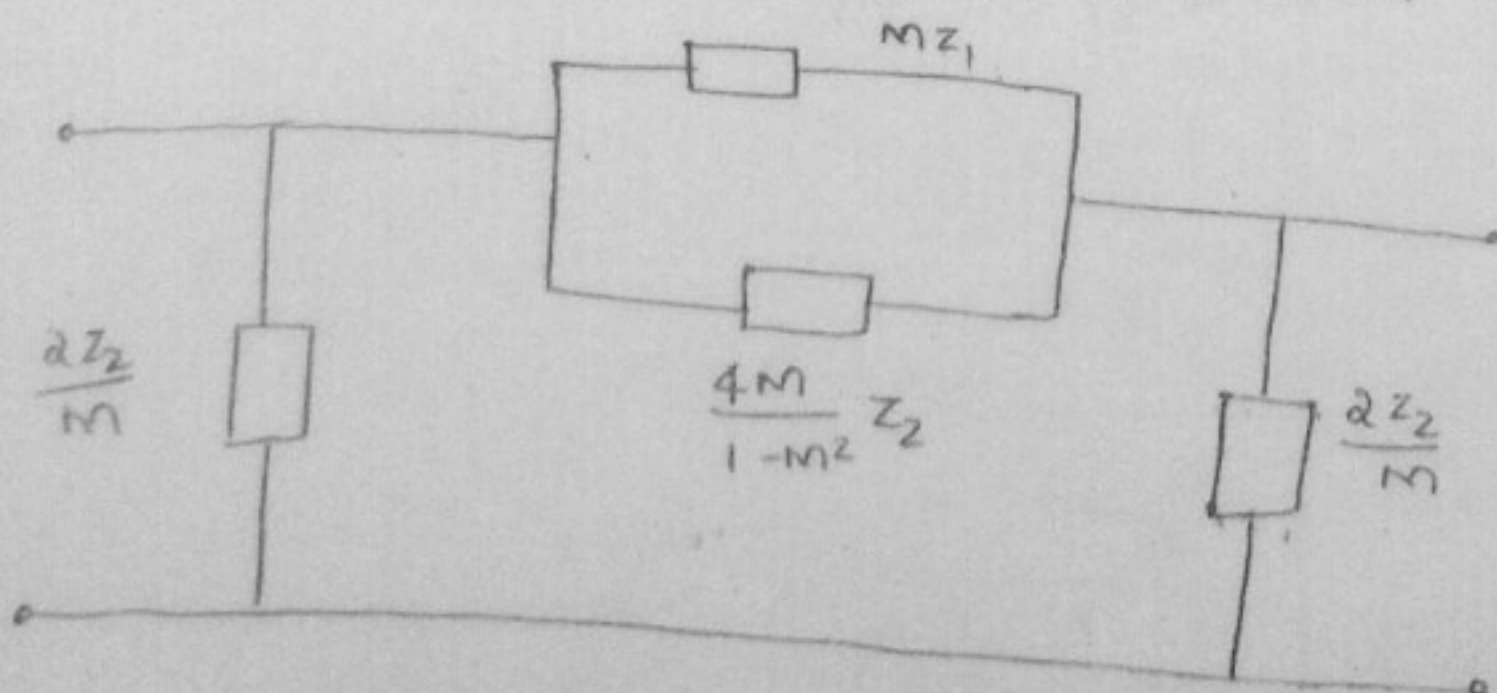And the symmetrical m-derived π-section is given as,



$$Z_1 = \frac{1}{j\omega C}$$

$$Z_2 = j\omega L$$

$$mZ_1 = \frac{1}{j\omega C(m)}$$

m-derived LPF of π -section filter:-


$$\Rightarrow Z_1 = j\omega L \text{ and } Z_2 = \frac{1}{j\omega C}$$

$$\Rightarrow mZ_1 = j\omega(mL)$$

$$\Rightarrow \frac{4m}{1-m^2}(Z_2) = \frac{4m}{(1-m^2)(j\omega C)} = \frac{1}{C \cdot j\omega \left(\frac{1-m^2}{4m} \right)}$$

$$= \frac{1}{j\omega \left(\frac{1-m^2}{4m} \right) C}$$
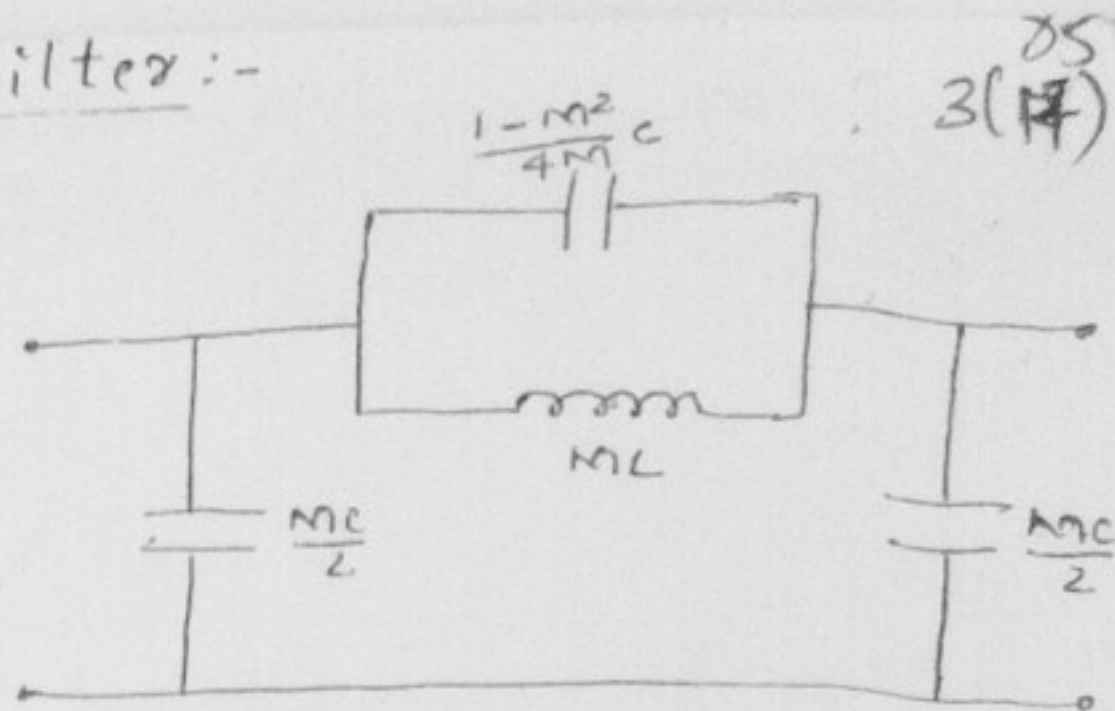
$$\Rightarrow \frac{2Z_2}{m} = \frac{2}{j\omega(mC)} = \frac{1}{j\omega \left(\frac{mC}{2} \right)}$$




m-derived HPF of π -filter:-

$$\Rightarrow Z_1 = \frac{1}{j\omega C} \text{ f } Z_2 = j\omega L$$

$$\Rightarrow mZ_1 = \frac{m}{j\omega C} = \frac{1}{j\omega \left(\frac{C}{m} \right)}$$

$$\Rightarrow \frac{4m}{1-m^2} Z_2 = j\omega \left(\frac{4m}{1-m^2} \right) L$$

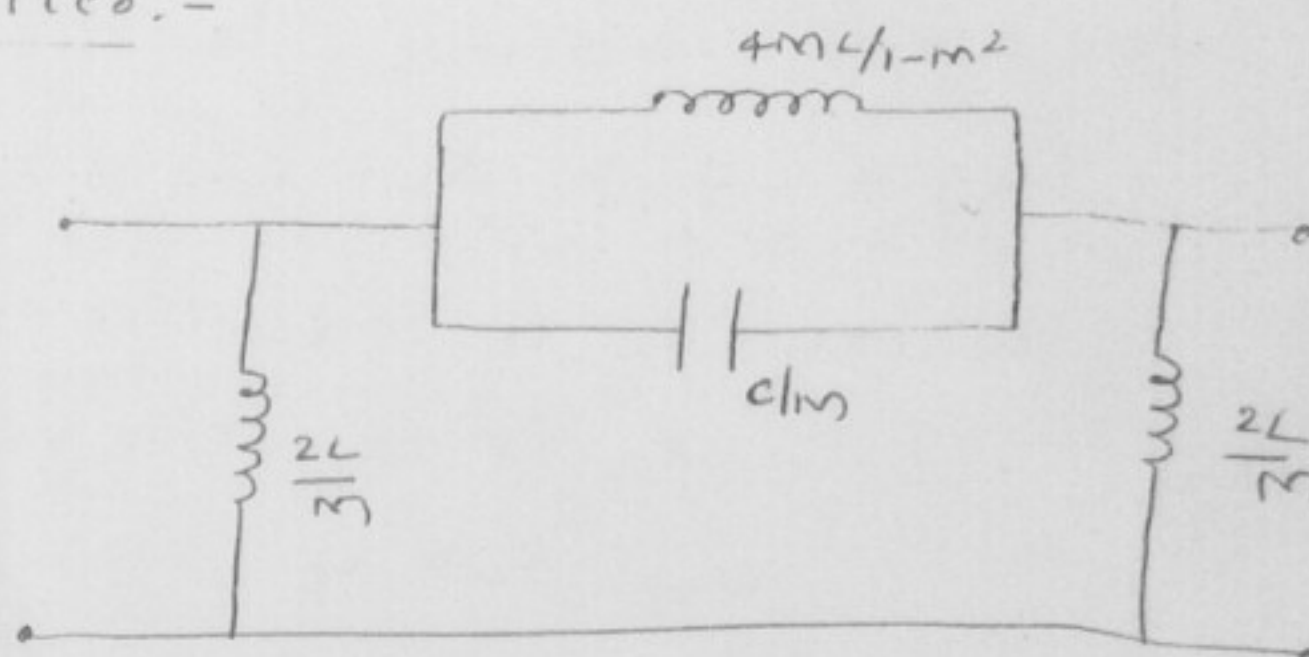
$$\Rightarrow \frac{2Z_2}{m} = j\omega \left(\frac{2L}{m} \right)$$




17/11/13
m-derived low pass Filter:-

→ It is the filter which is derived from basic LPF which will produce infinite attenuation in the stop band at a desired frequency.

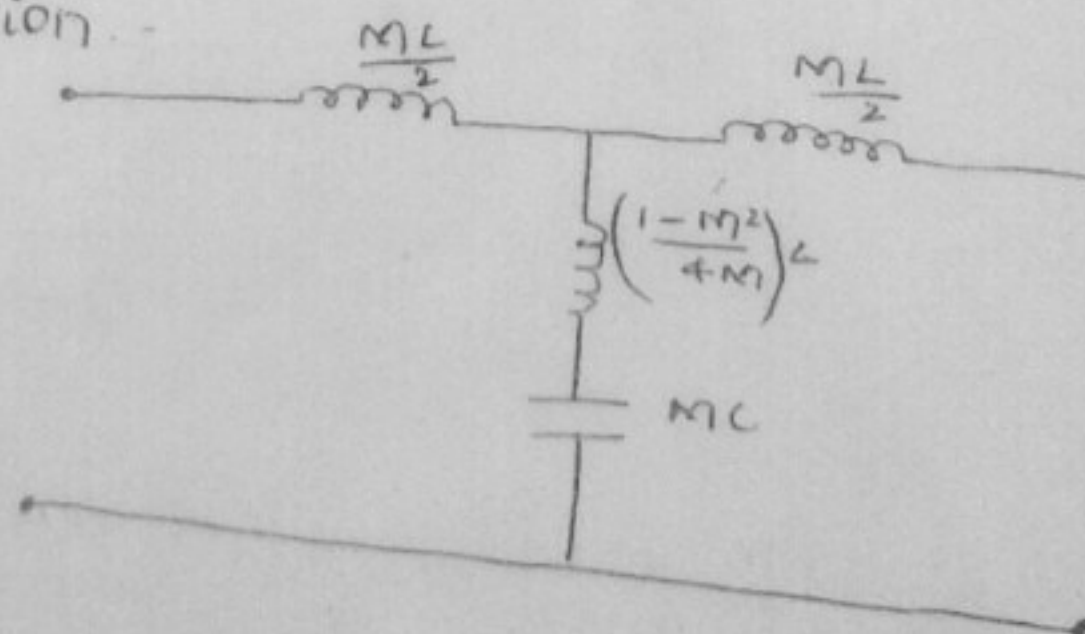→ From the basic symmetrical T and π section, we can derive the LPF as m-derived T-section.



M-derived π -section:-

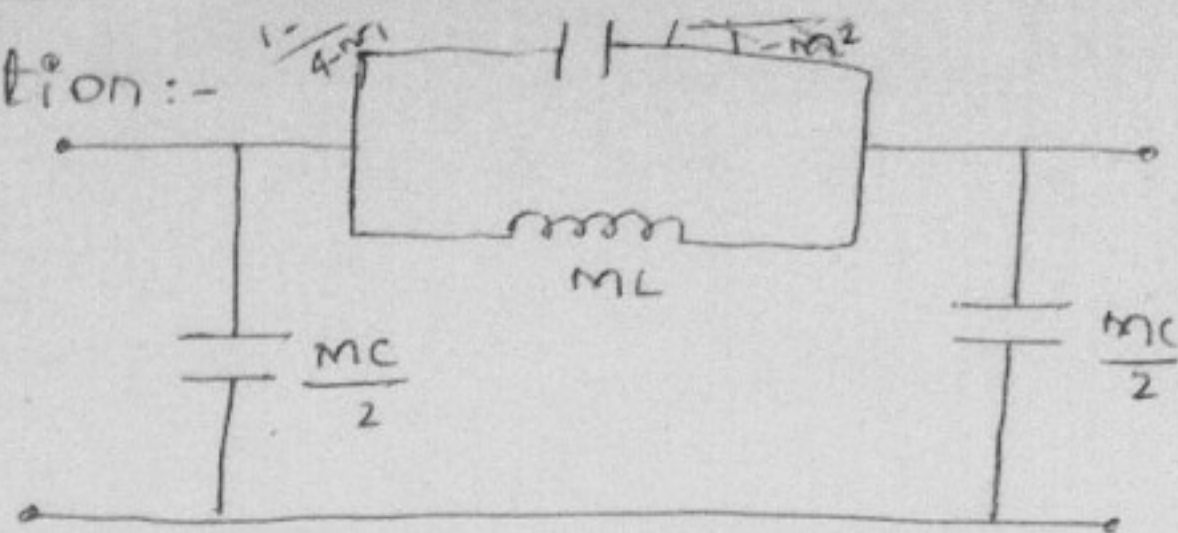

(i)

→ From the symmetrical T-section filter, infinite attenuation will be achieved at a frequency when the shunt arm resonates. The shunt arm of symmetrical T-filter consists of two elements in series.

→ From the basics of resonance, we know that the condition for series resonance is net reactance of circuit = 0.

$$\text{i.e., } X = 0 \Rightarrow X_L - X_C = 0 \Rightarrow X_L = X_C \text{ at } f = f_r$$

Where X_L is inductive reactance of the coil (ωL)

X_C is capacitive reactance

$$\Rightarrow X_L = X_C$$

$$\Rightarrow \omega_r L = \frac{1}{\omega_r C}$$

$$\Rightarrow \omega_r^2 = \frac{1}{LC_1} \Rightarrow \text{from diagram } L_1 = \left(\frac{1-M^2}{4M} \right) L$$

$$C_1 = MC$$

$$\Rightarrow \omega_r^2 = \frac{1}{\left(\frac{1-M^2}{4M} \right) L (MC)}$$

$$\Rightarrow \omega_r^2 = \frac{4}{(1-M^2) LC}$$

$$\omega_r = \text{radians/sec}$$

$$\therefore \omega_r = 2\pi f_r$$

$$\Rightarrow 4\pi^2 f_r^2 = \frac{4}{(1-M^2) LC}$$

$$\Rightarrow f_r^2 = \frac{4}{4\pi^2 (1-M^2) LC} = \frac{1}{\pi^2 (1-M^2) LC}$$

$$\Rightarrow f_r = \frac{1}{\pi \sqrt{(1-M^2) LC}} \quad f_r \text{ is the frequency at which infinite attenuation occurs.}$$


→ But from LPF configuration, we know that the cut off frequency $f_c = \frac{1}{\pi \sqrt{LC}}$

$$\Rightarrow f_{\infty} = \frac{f_c}{\sqrt{1-M^2}} \Rightarrow \sqrt{1-M^2} = \frac{f_c}{f_{\infty}}$$

3(18) 86

$$\Rightarrow 1-M^2 = \left(\frac{f_c}{f_{\infty}}\right)^2 \Rightarrow 1 - \left(\frac{f_c}{f_{\infty}}\right)^2 = M^2$$
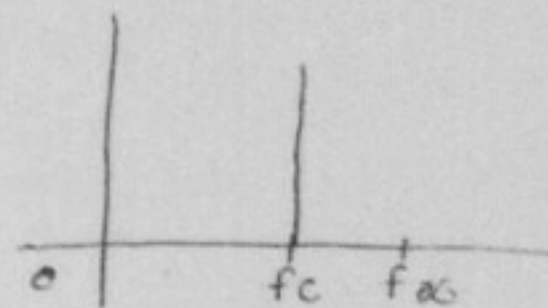
$$\Rightarrow M = \sqrt{1 - \left(\frac{f_c}{f_{\infty}}\right)^2}$$



$\Rightarrow$ As f_{∞} will be always greater than cut off frequency, the value of M will be less than 1.

$$1. f_{\infty} > f_c \Rightarrow \frac{f_c}{f_{\infty}} < 1 \Rightarrow 1 - \left(\frac{f_c}{f_{\infty}}\right)^2 > 0 \Rightarrow M > 0.$$

2. Minimum value^(M) at $f_{\infty} = f_c \Rightarrow$ then $M = 0$.

3. Maximum value of M f_{∞} is infinite $\Rightarrow M = 1$

$\Rightarrow$ The value of M is between 0 & 1.

$$0 \leq M < 1$$

(ii) From the symmetrical π -configuration infinite attenuator will be achieved when the series arm resonates. The series arm consists of L and C elements in parallel whose resonant condition is given by net susceptance is equal to zero i.e., $B = 0$.

$$Y = JB \quad (Y = G + JB)$$

$\Rightarrow$ When $B = 0$ then $Y = 0$

$$Z = \frac{1}{0} = \infty$$

for the series branch,

$$I = 0$$

$$\Rightarrow Y_T = Y_1 + Y_2 = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$= \frac{1}{j\omega ML} + \frac{1}{\left(\frac{1}{j\omega \left(\frac{1-M^2}{4M}\right) C}\right)}$$

$$= \frac{1}{j\omega ML} + j \frac{(1-M^2)\omega C}{4M}$$

$$= \frac{-j}{\omega ML} + j \frac{(1-M^2)\omega C}{4M} = 0 + j \left[\left(\frac{1-M^2}{4M}\right)\omega C - \frac{1}{\omega ML} \right]$$

$$Y_T = G + jB$$

(since Impedance is infinite admittance is zero)

→ At resonant frequency $\omega = \omega_r$ then $B = 0$

$$\Rightarrow \frac{1-m^2}{4m} \omega_r C = \frac{1}{\omega_r m L}$$

$$\Rightarrow \omega_r^2 = \frac{4}{(1-m^2)LC}$$

$$\Rightarrow (2\pi f_r)^2 = \frac{4}{(1-m^2)LC}$$

$$\Rightarrow f_r^2 = \frac{1}{\pi^2 LC (1-m^2)}$$

$$\Rightarrow f_r = \frac{1}{\pi \sqrt{LC} \sqrt{1-m^2}}$$

$$f_c = \frac{1}{\pi \sqrt{LC}} \Rightarrow f_\infty = \frac{1}{f_c \sqrt{1-m^2}}$$


$$\Rightarrow m = \sqrt{1 - \left(\frac{f_c}{f_\infty}\right)^2}$$

19/1/13

2M-derived High pass filter:-

A m-derived HPF is the one in which ^{we} one can achieve infinite attenuation at a desired frequency below cut-off frequency.


i) m-derived T-section HPF :-

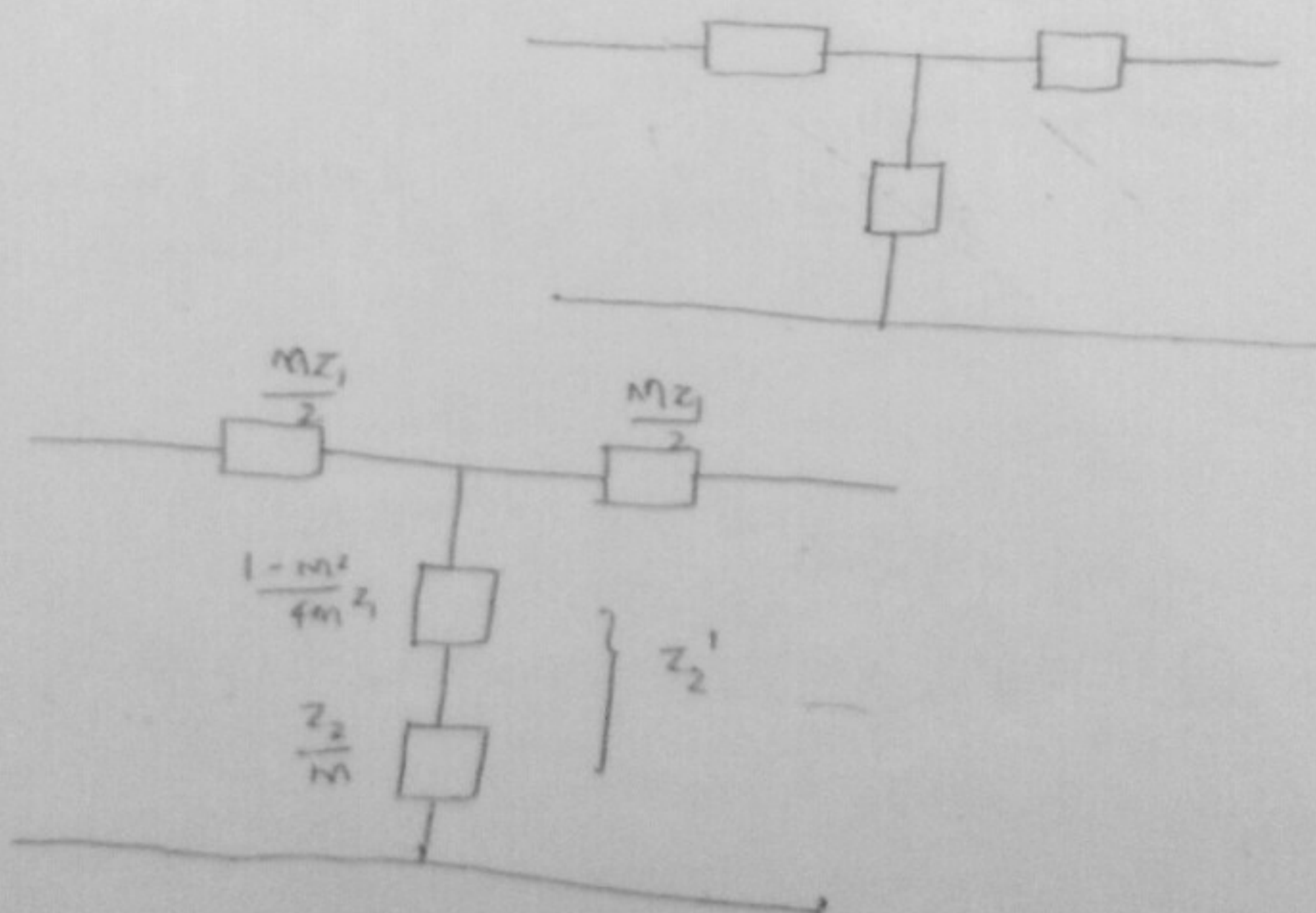

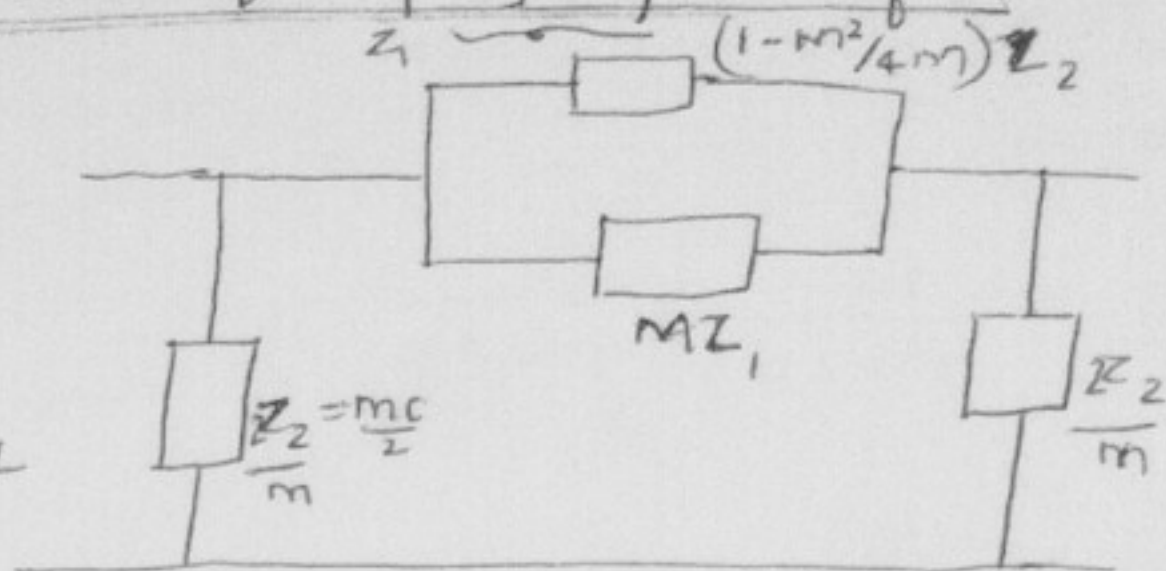
(ii) Symmetrical π -filter for high pass filter:-

Where $\frac{1}{Z_1} = \frac{1}{j\omega L}$, $\frac{1}{Z_2} = j\omega C$

$$Z_1 = \frac{1}{j\omega C}, Z_2 = j\omega L$$



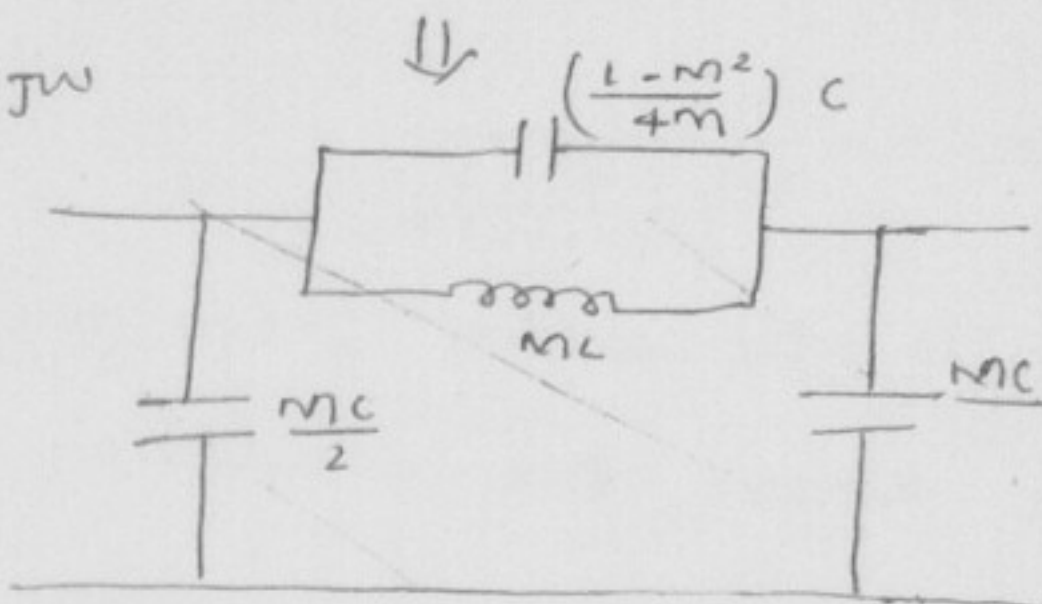
$$\Rightarrow \left(\frac{1-m^2}{4m} \right) Z_2 = \left(\frac{1-m^2}{4m} \right) L \cdot j\omega$$



$$\Rightarrow \frac{Z_2}{m} = \frac{j\omega L}{j\omega \left(\frac{mC}{2} \right)}$$

$$\Rightarrow mZ_1 = \frac{1}{j\omega \left(\frac{C}{m} \right)}$$
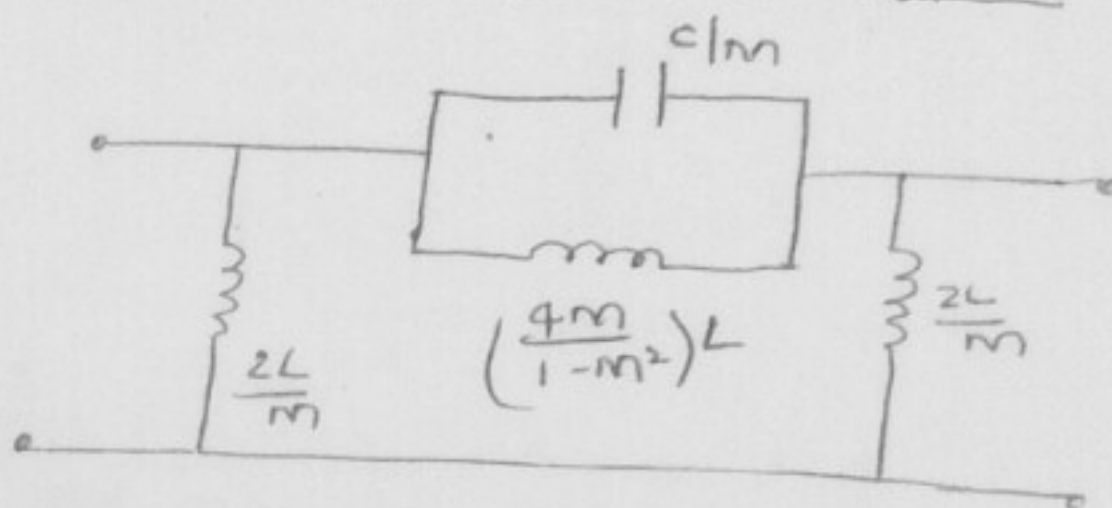
$$\Rightarrow \frac{Z_2}{m} = j\omega \left(\frac{2L}{m} \right)$$



$$\Rightarrow Y = G + jB$$

$$B = 0$$

$$\Rightarrow Y_T = \frac{1}{Z_x} + \frac{1}{Z_y} = \frac{1}{j\omega \left(\frac{C}{m} \right)} + \frac{1}{j\omega \frac{4mC}{1-m^2}}$$

$$= 0 + \left(j\omega \frac{C}{m} + \frac{1-m^2}{j4\omega mL} \right)$$

$$= 0 + j \left(\frac{\omega C}{m} - \frac{1-m^2}{4\omega mL} \right)$$

$$Y_T = G + jB$$

$$\Rightarrow \text{At } f_c \Rightarrow B = 0 \Rightarrow (\omega = \omega_c \text{ at } f_c)$$

$$\Rightarrow \frac{\omega_c C}{m} = \frac{1-m^2}{4\omega_c mL}$$

$$\Rightarrow \omega_c C = \frac{1-m^2}{4\omega_c L}$$

$$\Rightarrow \omega_c^2 = \frac{1-m^2}{4LC} = \frac{1-m^2}{4LC}$$

$$\Rightarrow 4\pi^2 f_c^2 = \frac{1-m^2}{4LC}$$

$$\Rightarrow f_c = \frac{\sqrt{1-m^2}}{4\pi\sqrt{LC}}$$


→ The above is said to be High pass when $Z_1 = \frac{1}{j\omega C}$, $Z_2 = j\omega L$

$$\Rightarrow Z_1 = \frac{1}{j\omega C}$$

$$\Rightarrow \frac{MZ_1}{2} = \frac{M}{j\omega 2C} = \frac{1}{j\omega \left(\frac{2C}{M}\right)}$$

$$\Rightarrow \frac{Z_2}{M} = j\omega \left(\frac{L}{M}\right)$$
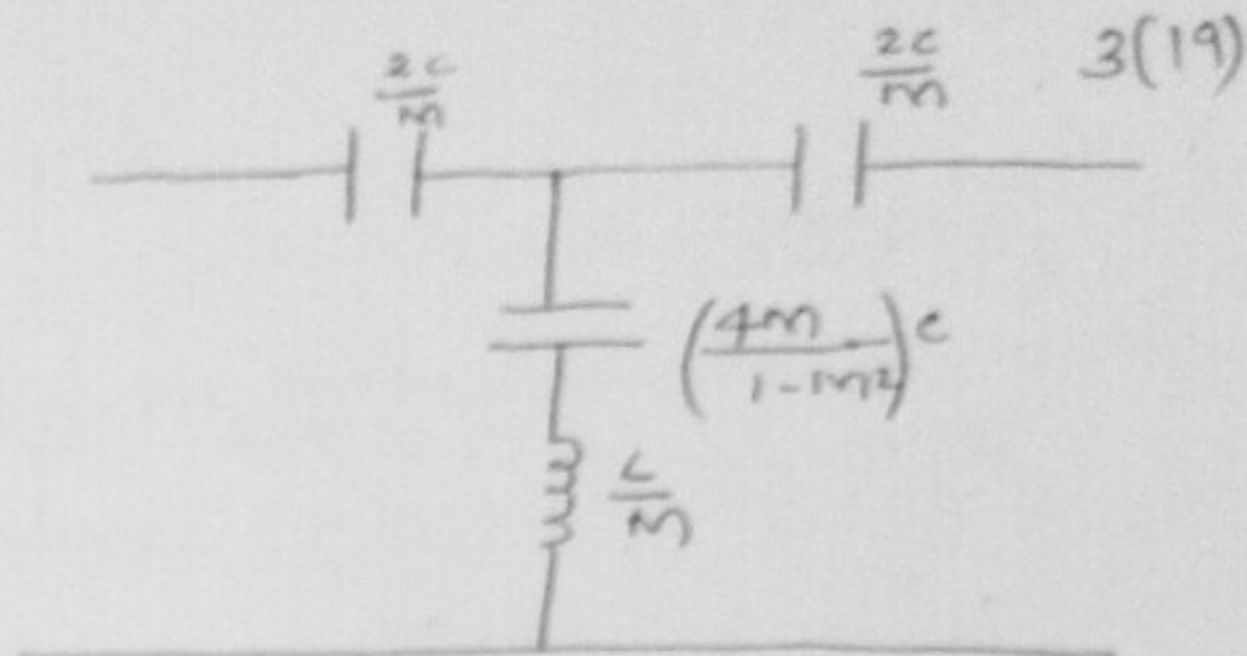
$$\Rightarrow \frac{1-M^2}{4M} Z_1 = \frac{1}{j\omega \left(\frac{4M}{1-M^2}\right)C}$$



→ At infinite attenuation frequency, the shunt branch will resonate where the condition is $X_L = X_C$.

$$\Rightarrow \omega_r L = \frac{1}{\omega_r C}$$

$$\Rightarrow \omega_r^2 = \frac{1}{LC}$$

$$\Rightarrow 4\pi^2 f_r^2 = \frac{1}{LC}$$

$$\Rightarrow \pi^2 4 f_r^2 = \frac{1}{\frac{L}{M} \left(\frac{4M}{1-M^2}\right)C} \Rightarrow f_r^2 = \frac{1-M^2}{16\pi^2 LC}$$

$$\Rightarrow f_r = \frac{\sqrt{1-M^2}}{4\pi\sqrt{LC}} = f_\infty \quad \text{where } f_\infty \text{ indicates the frequency of infinite attenuation.}$$

To find m:-

→ From the characteristics of HPF, we know that the value of cut-off frequency,

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

$$\Rightarrow f_\infty = \frac{\sqrt{1-M^2}}{1/f_c}$$

$$\Rightarrow f_\infty = f_c \sqrt{1-M^2}$$

$$\Rightarrow \frac{f_\infty}{f_c} = \sqrt{1-M^2} \Rightarrow 1-M^2 = \left(\frac{f_\infty}{f_c}\right)^2$$

$$\Rightarrow M = \sqrt{1 - \left(\frac{f_\infty}{f_c}\right)^2}$$

1. When $f_\infty = f_c \Rightarrow M = 0$

1. When $f_\infty = 0 \Rightarrow M = 1$

$\Rightarrow M$ lies between 0 and 1 $\Rightarrow 0 < M < 1$

$$\Rightarrow f_{\infty} = f_c \sqrt{1-m^2}$$

$$\Rightarrow m = \sqrt{1 - \left(\frac{f_{\infty}}{f_c}\right)^2}$$

Q:- Design an m-derived LPF with a cut-off frequency of 10kHz and a characteristic impedance of 400Ω . The frequency of infinite attenuation is given as 20kHz .

sol:- Given data,

$\Rightarrow$ given that it is m-derived LPF

$\Rightarrow$ cut-off frequency $f_c = 10\text{kHz}$

$\Rightarrow$ characteristic impedance (or) Design $K = 400\Omega$ impedance.

$\Rightarrow f_{\infty} = 20\text{kHz}$

For a LPF, $Z_1 = j\omega L$, $Z_2 = \frac{1}{j\omega C}$ Where $L = \frac{K}{\pi f_c}$

$$\Rightarrow L = \frac{400}{\pi \times 10000 \times 10} \text{ and } C = \frac{1}{\pi K f_c}$$

$$C = \frac{1}{\pi K f_c}$$

$$\Rightarrow L = 0.012 \text{ Henry}$$



$$C = 0.0795 \mu\text{F}$$

$$\Rightarrow L = 12\text{mH}$$


The value of m is,

$$m = \sqrt{1 - \left(\frac{f_c}{f_{\infty}}\right)^2} = \frac{\sqrt{3}}{2} = 0.866$$

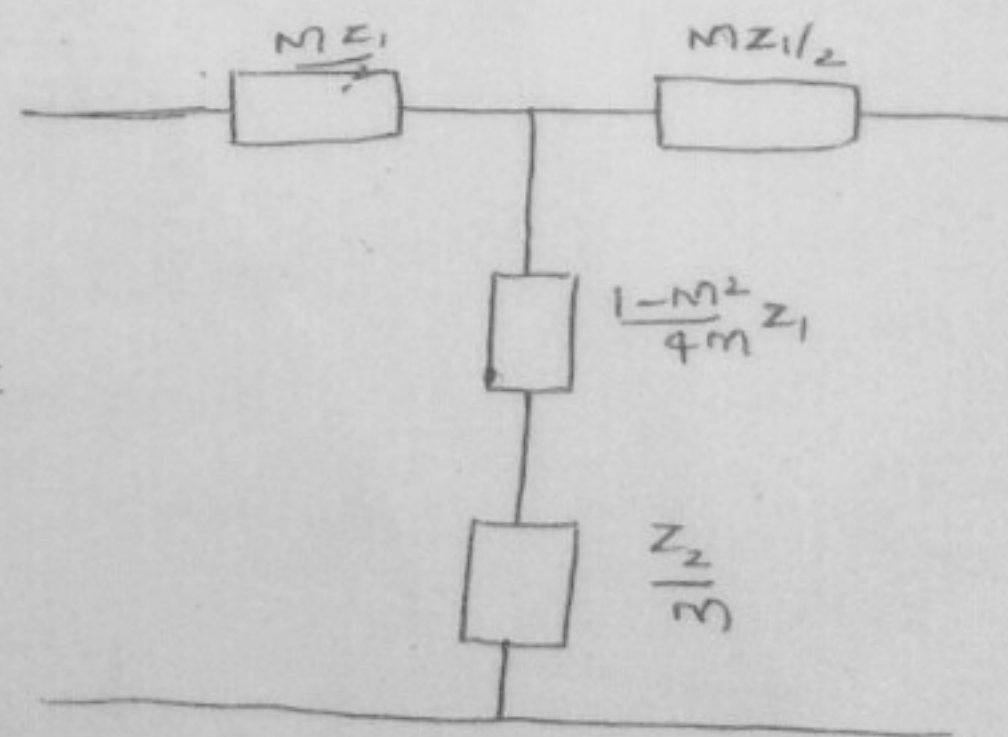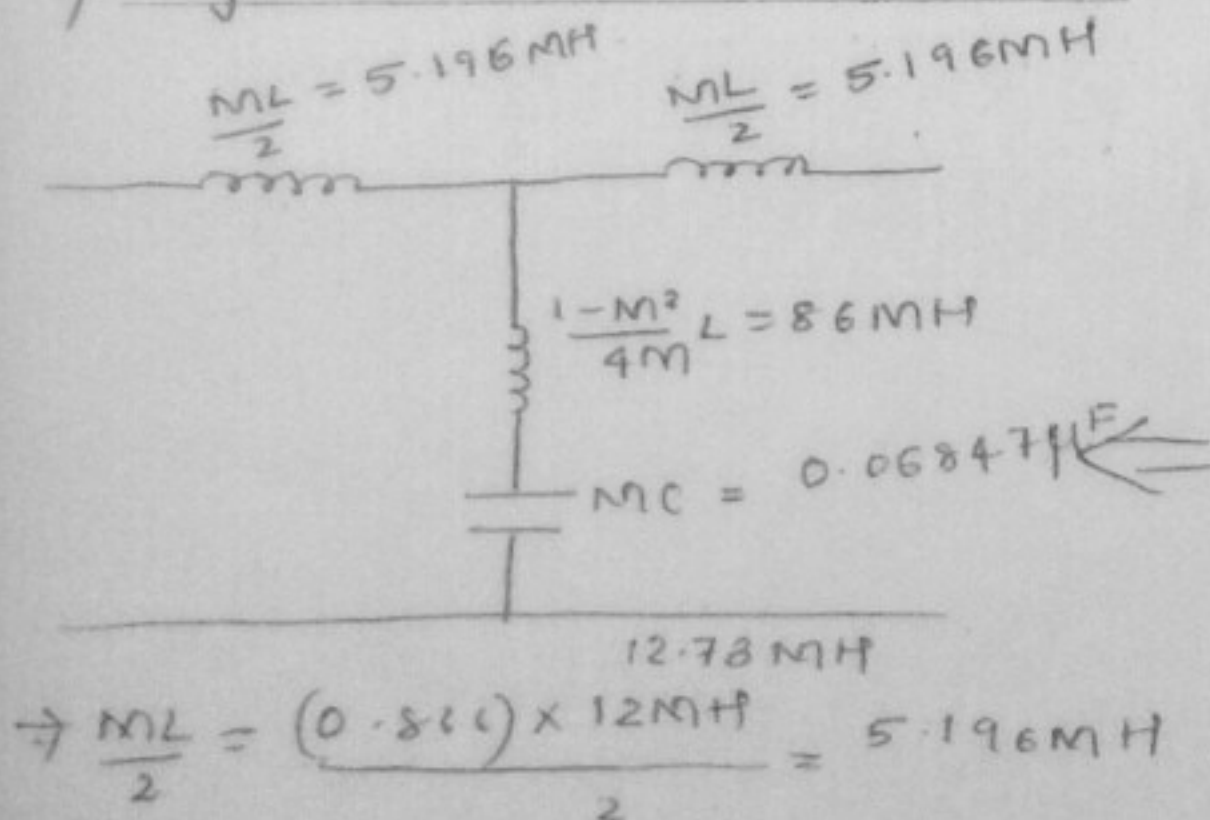$\Rightarrow$ Symmetrical T-section filter, (Low Pass)



Symmetrical Π -section LPF:-

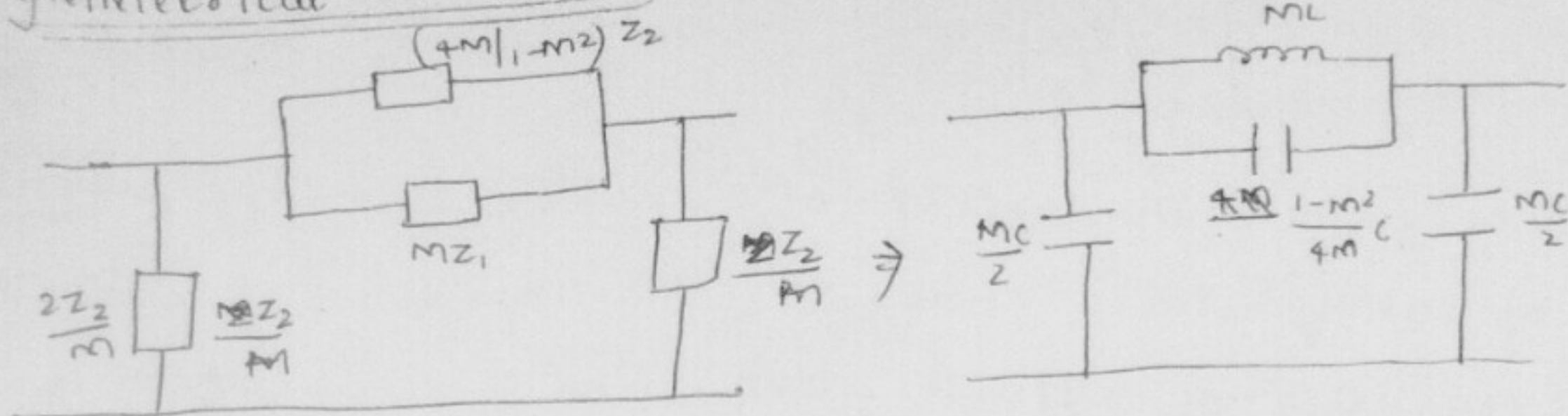

Q:- Design an m -derived HPF for a nominal impedance of 500Ω with a cut-off frequency of $f_c = 25\text{kHz}$ to attain infinite attenuation at a frequency of $f_\infty = 12.5\text{kHz}$.

sol:- Given, $k = 500\Omega$

$$f_c = 25\text{kHz}$$

$$f_\infty = 12.5\text{kHz}$$

→ For a HPF $Z_1 = \frac{1}{j\omega C}$ and $Z_2 = j\omega L$

$$\text{Where } L = \frac{k}{4\pi f_c} \text{ \& } C = \frac{1}{4\pi k f_c}$$

$$\Rightarrow L = \frac{500}{4\pi \times 25 \times 10^3} = 1.59\text{mH}$$

$$C = \frac{1}{4\pi \times 500 \times 25} \text{ MF} = 6.366 \times 10^{-9} \text{ F}$$


$$C = 0.00636 \mu\text{F}$$

$$\therefore \text{The value of } m \text{ is } m = \sqrt{1 - \left(\frac{f_\infty}{f_c}\right)^2} = \sqrt{1 - \left(\frac{12.5}{25}\right)^2} = \frac{\sqrt{3}}{2}$$

$$m = 0.86602$$

$$m = 0.866$$

Symmetrical T-section HPF:-

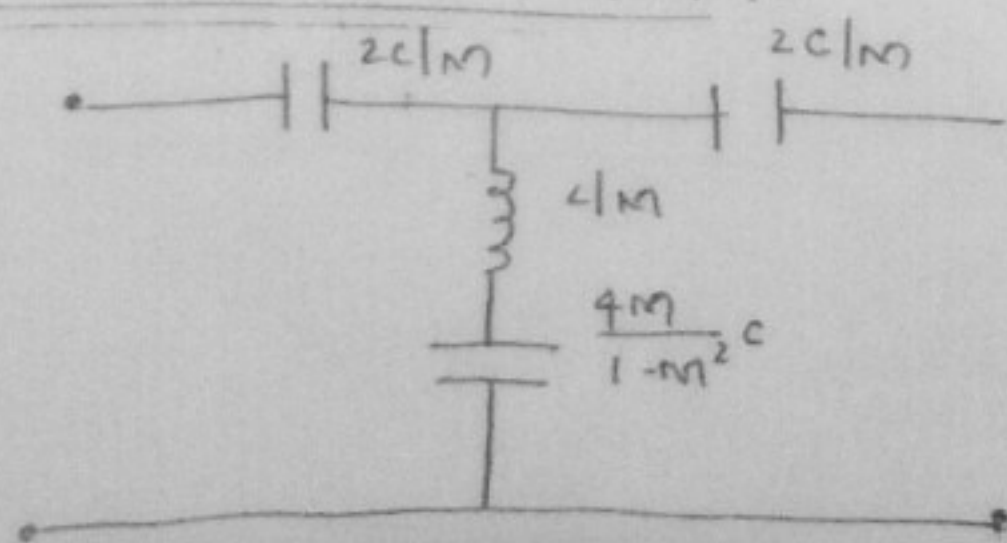


$$\frac{2C}{m} = 0.0147 \mu\text{F}$$

$$\frac{L}{m} = 1.8371 \text{ mH}$$

$$\frac{4m}{1-m^2} C = 0.8819 \mu\text{F}$$

Symmetrical π -section HPF:-

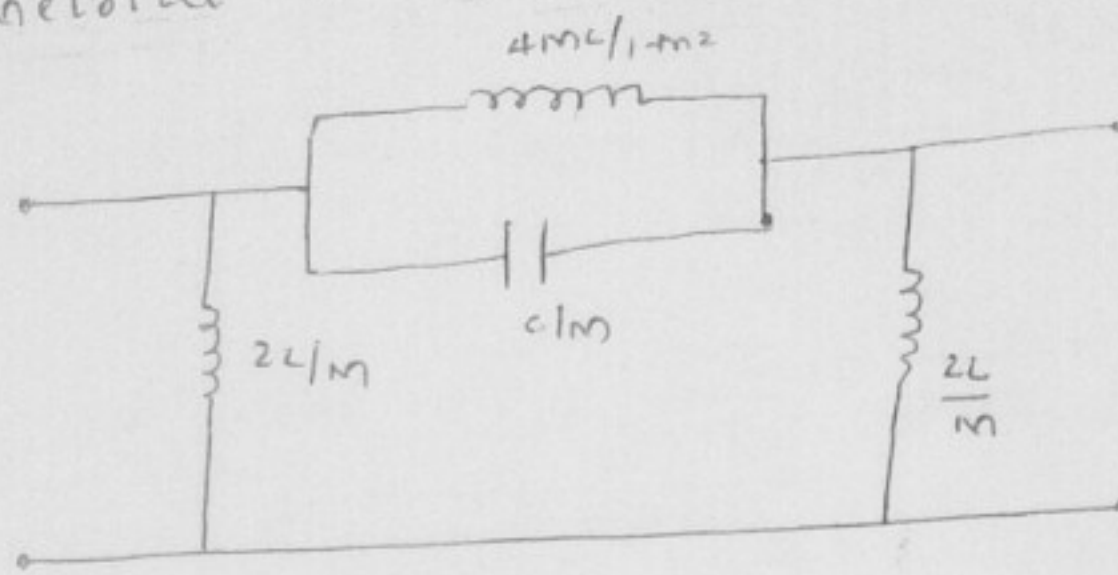

$$\frac{4ML}{1-M^2} = 2204 \text{ MH}$$


$$\frac{C}{M} = 7.351 \times 10^{-3} \text{ pF}$$

$$\frac{2L}{M} = 3.674 \text{ MH}$$

21/1/13


Band pass filter:- A BPF is a one which transmits a certain band of frequencies and eliminates the remaining.

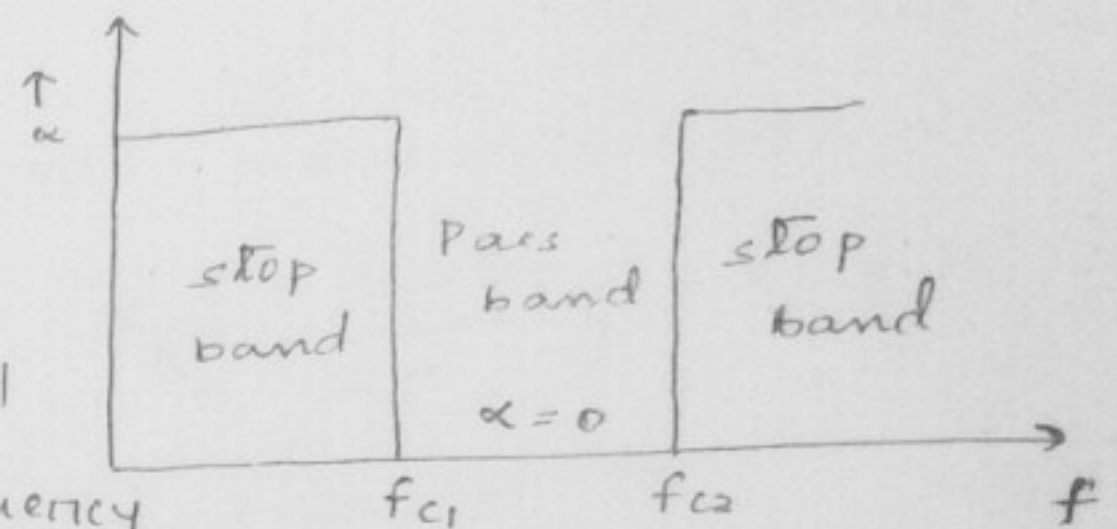→ The Band pass Filter can be constructed by joining a HPF with a LPF where the LPF cut off frequency will be the upper cut off frequency





if the cut-off frequency of HPF will be the lower cut off frequency. But it is an uneconomical to join two prototype filters of different characteristics.

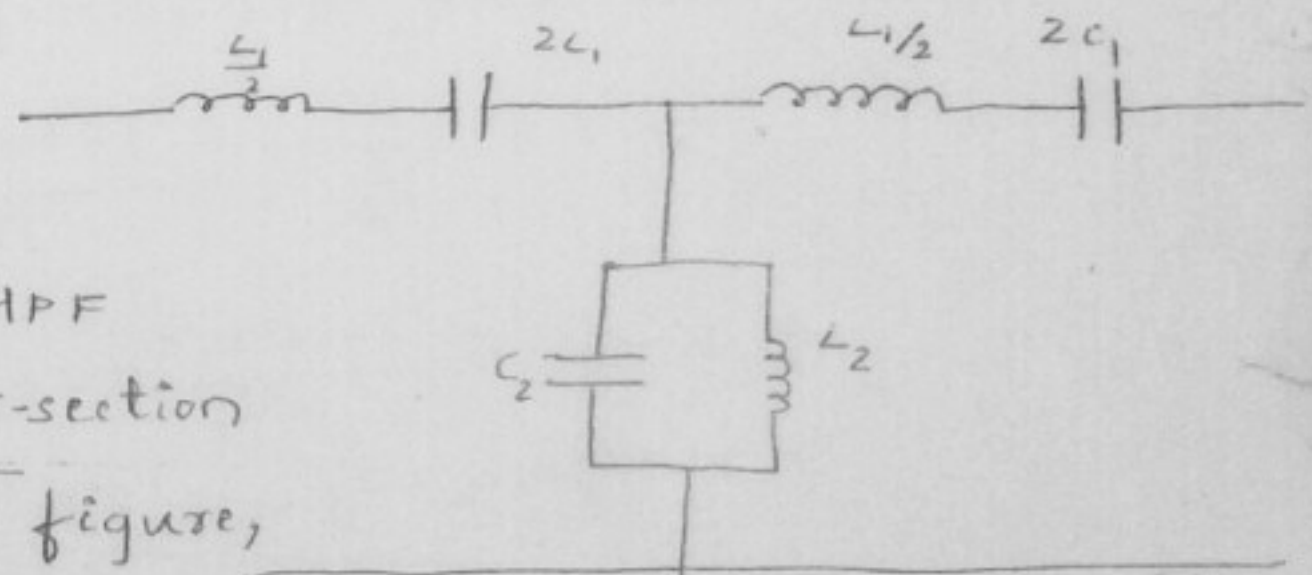→ Hence the BPF will be constructed by joining the elements of LPF and HPF together. A symmetrical T-section BPF will be as shown in figure,



Symmetrical π -section filter:-

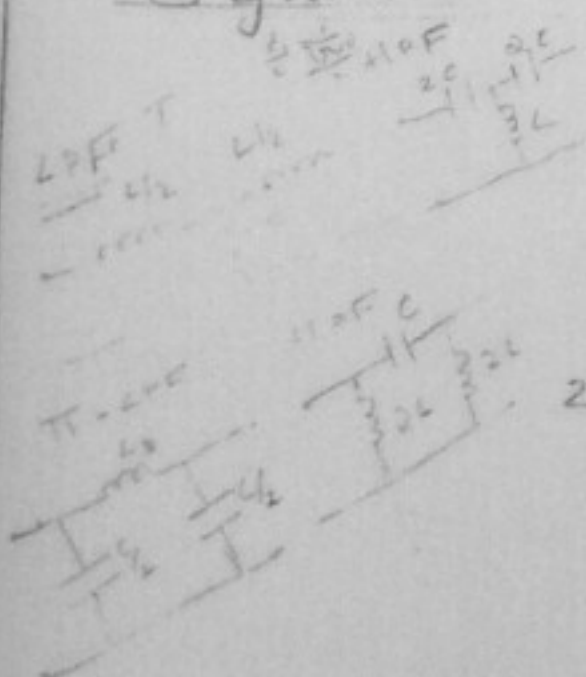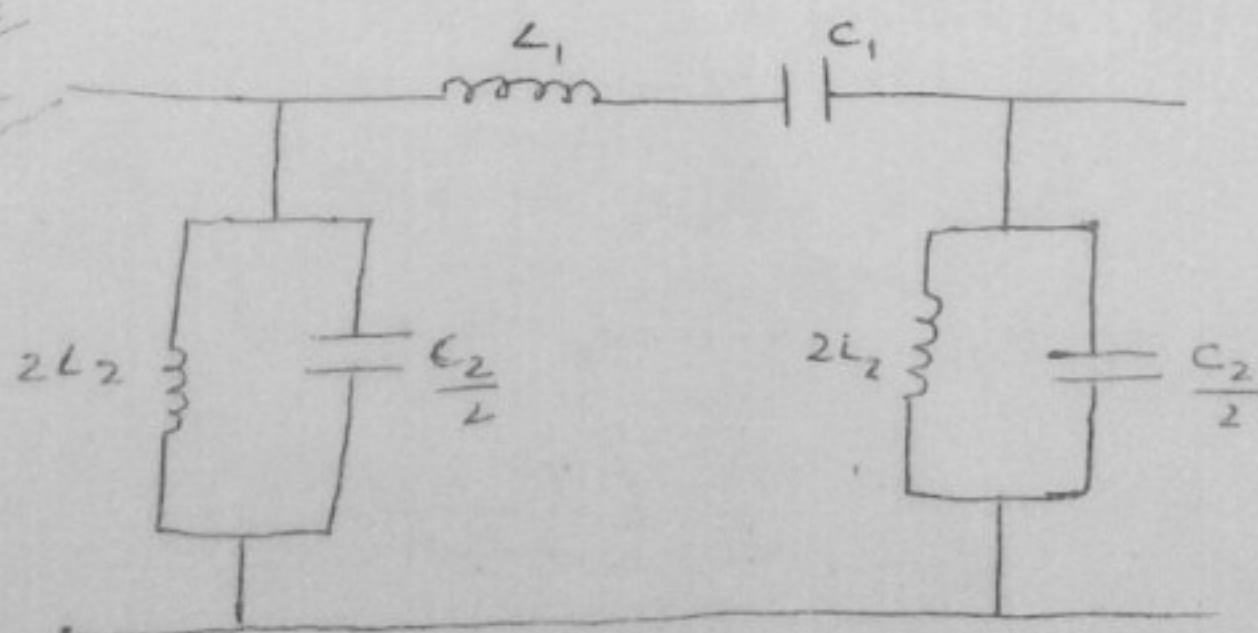

⇒ The series arm impedance is,

$$Z_1 = j\omega L_1 + \frac{1}{j\omega C_1} = j \left(\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right) \rightarrow (1) \quad Y_1 = Y_1^*$$

$$Z_2 = L_2 \parallel C_2 = j\omega L_2 \parallel \frac{1}{j\omega C_2} = \frac{j\omega L_2}{\frac{j\omega L_2 + \frac{1}{j\omega C_2}}{j\omega C_2}} = \frac{L_2(j\omega C_2)}{C_2(1 - \omega^2 L_2 C_2)}$$

$$Z_2 = \frac{j\omega L_2}{1 - \omega^2 L_2 C_2} \rightarrow (2)$$

The condition to have transmission band for a BPF is the series arm and shunt arms should resonate at the same frequency.

→ For the series arm, the resonant condition is net reactance = 0

$$\text{i.e., } 0 + j \left(\frac{\omega^2 L_1 C_1 - 1}{\omega C_1} \right) = 0.$$

$$\Rightarrow \omega^2 L_1 C_1 - 1 = (\omega C_1) \cdot 0$$

$$\Rightarrow \omega^2 L_1 C_1 = (\omega C_1)^0 + 1$$

$$\Rightarrow \omega^2 = \frac{1}{L_1 C_1} \rightarrow (3)$$

→ For the shunt arm, net susceptance = 0 ($\because$ $\parallel$ el LC resonant ckt)

$$\Rightarrow Y = \frac{1}{Z_2} = \frac{1 - \omega^2 L_2 C_2}{j\omega L_2} = \frac{-j(1 - \omega^2 L_2 C_2)}{\omega L_2} = G + jB$$

$$\Rightarrow B = 0 \Rightarrow \frac{1 - \omega^2 L_2 C_2}{\omega L_2} = 0$$

$$\Rightarrow 1 - \omega^2 L_2 C_2 = 0$$

$$\Rightarrow \omega^2 = \frac{1}{L_2 C_2} \rightarrow (4)$$

From eq.s (3) & (4), $\frac{1}{L_1 C_1} = \frac{1}{L_2 C_2}$

$$\Rightarrow L_1 C_1 = L_2 C_2 \rightarrow (5)$$

→ For a constant k-type filter, $Z_1 Z_2 = k^2$, for the given BPF

$$\Rightarrow Z_1 Z_2 = j^2 \frac{\omega L_2}{\omega C_1} \left(\frac{\omega^2 L_1 C_1 - 1}{1 - \omega^2 L_2 C_2} \right)$$

$$\Rightarrow Z_1 Z_2 = \frac{L_2}{C_1} \left(\frac{1 - \omega^2 L_1 C_1}{1 - \omega^2 L_2 C_2} \right)$$

from eq. (5) $\Rightarrow Z_1 Z_2 = \frac{L_2}{C_1} \left(\frac{1 - \omega^2 L_2 C_2}{1 - \omega^2 L_2 C_2} \right) = \frac{L_2}{C_1}$

$L_1 C_1 = L_2 C_2$

$\Rightarrow Z_1 Z_2 = \frac{L_2}{C_1} = k^2$ Which is a constant - k filter.

* Relation between Resonating frequencies & cut-off frequencies:

→ From the condition of pass band, we have $-1 < \frac{Z_1}{4Z_2} < 0$

$\Rightarrow \frac{Z_1}{4Z_2} = -1$

$\Rightarrow Z_1 = -4Z_2$ Multiply Z_1 on both sides

$\Rightarrow Z_1^2 = -4Z_1 Z_2$ $\because Z_1 Z_2 = k^2$

$\Rightarrow Z_1^2 = -4k^2$

$\Rightarrow Z_1 = \pm 2jk$

→ At low cut off frequency $Z_1 = -2jk$ ($\because X_{C1} > X_{L1}$) and at upper cut off frequency $Z_1 = +2jk$ ($X_{L1} > X_{C1}$).

Z_1 at lower cut of frequency at $\omega = \omega_1$

Z_1 at $\omega = \omega_1 = j\omega_1 L_1 + \frac{1}{j\omega_1 C_1} = -2jk$

Z_1 at $\omega = \omega_2 = j\omega_2 L_1 + \frac{1}{j\omega_2 C_1} = +2jk$

$\Rightarrow j\omega_1 L_1 + \frac{1}{j\omega_1 C_1} = - \left(j\omega_2 L_1 + \frac{1}{j\omega_2 C_1} \right)$

$\Rightarrow j\omega_1 L_1 + \frac{1}{j\omega_1 C_1} = -j\omega_2 L_1 - \frac{1}{j\omega_2 C_1}$

$\Rightarrow \frac{j^2 \omega_1^2 L_1 C_1 + 1}{j\omega_1 C_1} = \frac{-j^2 \omega_2^2 L_1 C_1 - 1}{j\omega_2 C_1}$

$\Rightarrow (-\omega_1^2 L_1 C_1 + 1)\omega_2 = -(-\omega_2^2 L_1 C_1 + 1)\omega_1$

$\Rightarrow -\omega_1^2 L_1 C_1 \omega_2 + \omega_2 = -(-\omega_2^2 L_1 C_1 + \omega_1)$

$\Rightarrow L_1 C_1 \omega_1 \omega_2 (\omega_1 + \omega_2) = -(\omega_1 + \omega_2)$

$\Rightarrow \omega_1 \omega_2 = \frac{-1}{L_1 C_1}$ (since $\frac{1}{L_1 C_1} = \omega_c^2$)

$\Rightarrow \frac{1}{\omega_c^2} = \frac{1}{\omega_1 \omega_2} \Rightarrow \omega_c^2 = \omega_1 \omega_2 \Rightarrow \omega_c = \sqrt{\omega_1 \omega_2}$

$\Rightarrow \frac{1}{\omega_c} = \frac{1}{\sqrt{\omega_1 \omega_2}} \Rightarrow \frac{1}{2\pi f_c} = \frac{1}{\sqrt{2\pi f_1 \times 2\pi f_2}} \Rightarrow f_c = \sqrt{f_1 f_2}$

Design of a Band pass Filter:-

$$Z_1 \text{ at } \omega = \omega_1 \Rightarrow -2jk = j\omega_1 L_1 + \frac{1}{j\omega_1 C_1}$$

$$\Rightarrow 1 + j^2 \omega_1^2 L_1 C_1 = -2j^2 k \omega_1 C_1 = 2k \omega_1 C_1$$

$$\Rightarrow \omega_1 L_1 = -2k + 1 - \omega_1^2 L_1 C_1 = 2\omega_1 k C_1$$

$$\Rightarrow \omega_1 = \frac{-2k}{\omega_1} \quad \left(\text{since } L_1 C_1 = \frac{1}{\omega_s^2} \right)$$

$$\Rightarrow 2jk = j\omega_2 L_1 + \frac{1}{j\omega_2 C_1}$$

$$\Rightarrow 2j^2 k \omega_2 C_1 = j^2 \omega_2^2 L_1 C_1 + 1$$

$$\Rightarrow -2k \omega_2 C_1 = 1 - \omega_2^2 L_1 C_1$$

$$\Rightarrow L_1 C_1 = \frac{1}{\omega_s^2} \Rightarrow -2k \omega_2 C_1 = 1 - \omega_2^2 k$$

$$\therefore L_1 C_1 = \frac{1}{\omega_s^2} \Rightarrow -2k \omega_2 C_1 = 1 - \frac{\omega_2^2}{\omega_s^2}$$

$$\Rightarrow -2k \omega_2 C_1 = 1 - \frac{f_2^2}{f_s^2}$$

$$\Rightarrow -2k \omega_2 C_1 = 1 - \frac{f_2}{f_1}$$

$$\Rightarrow -2k(2\pi f_2 f_1) C_1 = f_1 - f_2$$

$$\Rightarrow -4\pi k C_1 f_1 f_2 = f_1 - f_2$$

$$\Rightarrow C_1 = \frac{f_2 - f_1}{4\pi k f_1 f_2}$$

→ It is a constant k - filter, where
Values of shunt arm,

$$\Rightarrow Z_1 Z_2 = k^2 = \frac{L_2}{C_1} = \frac{L_1}{C_2} = k^2$$

$$\Rightarrow L_1 C_1 = L_2 C_2$$

$$\Rightarrow L_2 = C_1 k^2 = \frac{k(f_2 - f_1)}{4\pi f_1 f_2} \text{ Henrys}$$

$$\Rightarrow C_2 = \frac{L_1}{k^2} = \frac{1}{\pi k(f_2 - f_1)} \text{ Farads}$$

$$\Rightarrow 1 - \omega_1^2 L_1 C_1 = 2\omega_1 k C_1$$

$$\Rightarrow 1 - \frac{\omega_1^2}{\omega_s^2} = 2\omega_1 k C_1$$

$$\Rightarrow 1 - \left(\frac{f_1}{f_s} \right)^2 = 4\pi k f_1 C_1$$

$$\text{since } \omega_s = \sqrt{\omega_1 \omega_2}$$

$$f_s = \sqrt{f_1 f_2}$$

$$f_s^2 = f_1 f_2$$

$$\omega_1^2 = 4\pi^2 f_1^2 \text{ (and) } \omega_s^2 = 4\pi^2 f_s^2$$

$$\Rightarrow 1 - \frac{f_1^2}{f_1 f_2} = 4\pi k f_1 C_1$$

$$\Rightarrow 1 - \frac{f_1}{f_2} = 4\pi k f_1 C_1$$

$$\Rightarrow f_2 - f_1 = 4\pi k f_1 f_2 C_1$$

$$\Rightarrow C_1 = \frac{f_2 - f_1}{4\pi k f_1 f_2} \text{ Farads}$$

$$\text{and } L_1 C_1 = \frac{1}{\omega_s^2}$$

$$L_1 = \frac{1}{\omega_s^2 C_1}$$

$$\Rightarrow L_1 = \frac{4\pi k f_1 f_2}{\omega_s^2 (f_2 - f_1)}$$

$$\Rightarrow L_1 = \frac{4\pi k f_1 f_2}{4\pi^2 f_s^2 (f_2 - f_1)}$$

$$\Rightarrow L_1 = \frac{k f_1 f_2}{\pi f_1 f_2 (f_2 - f_1)}$$

$$\Rightarrow L_1 = \frac{k}{\pi (f_2 - f_1)} \text{ Henrys}$$

18:- Design a Band pass filter whose cut off frequencies are $f_1 = 5\text{kHz}$ and $f_2 = 10\text{kHz}$ for a nominal impedance of 600Ω . Determine the value of resonant frequency also. $3(23)$

Sol:- Given data,

$$K = 600\Omega,$$

Lower-cut of frequency $f_1 = 5\text{kHz}$.

Upper-cut of frequency $f_2 = 10\text{kHz}$.

We know that from the design of Band pass filter,

$$\begin{aligned} L_1 &= \frac{K}{\pi(f_2 - f_1)} \text{ Henry} & L_2 &= \frac{K(f_2 - f_1)}{4\pi f_1 f_2} \\ C_1 &= \frac{f_2 - f_1}{4\pi K f_1 f_2} & C_2 &= \frac{1}{\pi K(f_2 - f_1)} \end{aligned}$$

$$f_r = \sqrt{f_1 f_2}$$


$$\Rightarrow L_1 = \frac{K}{\pi(f_2 - f_1)} = \frac{600}{\pi(5\text{K})} = 38.19\text{mH}$$

$$\Rightarrow C_1 = \frac{f_2 - f_1}{4\pi K f_1 f_2} = \frac{5\text{K}}{50\text{K}^2 \times 600 \times 4\pi} = 1.32 \times 10^{-8} = 0.013\mu\text{F}$$


$$\Rightarrow L_2 = \frac{600(5\text{K})}{4\pi \times 50\text{K} \times (10\text{K})^2} = 4.77\text{mH}$$

$$\Rightarrow C_2 = \frac{1}{\pi \times 600 \times (5\text{K})} = 0.106\mu\text{F}$$

Symmetrical T-filter:-

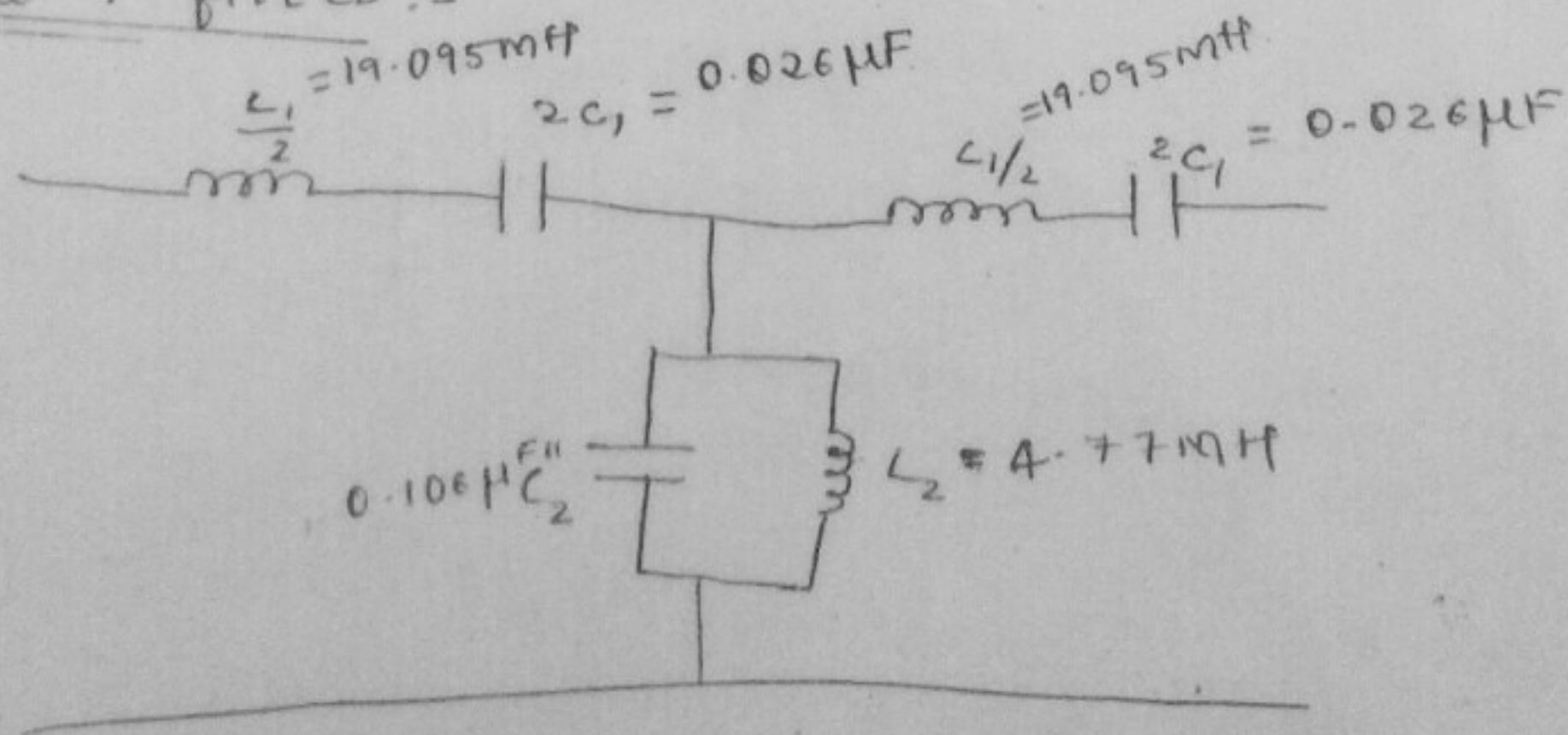

Symmetrical π -filter:- (BPF)

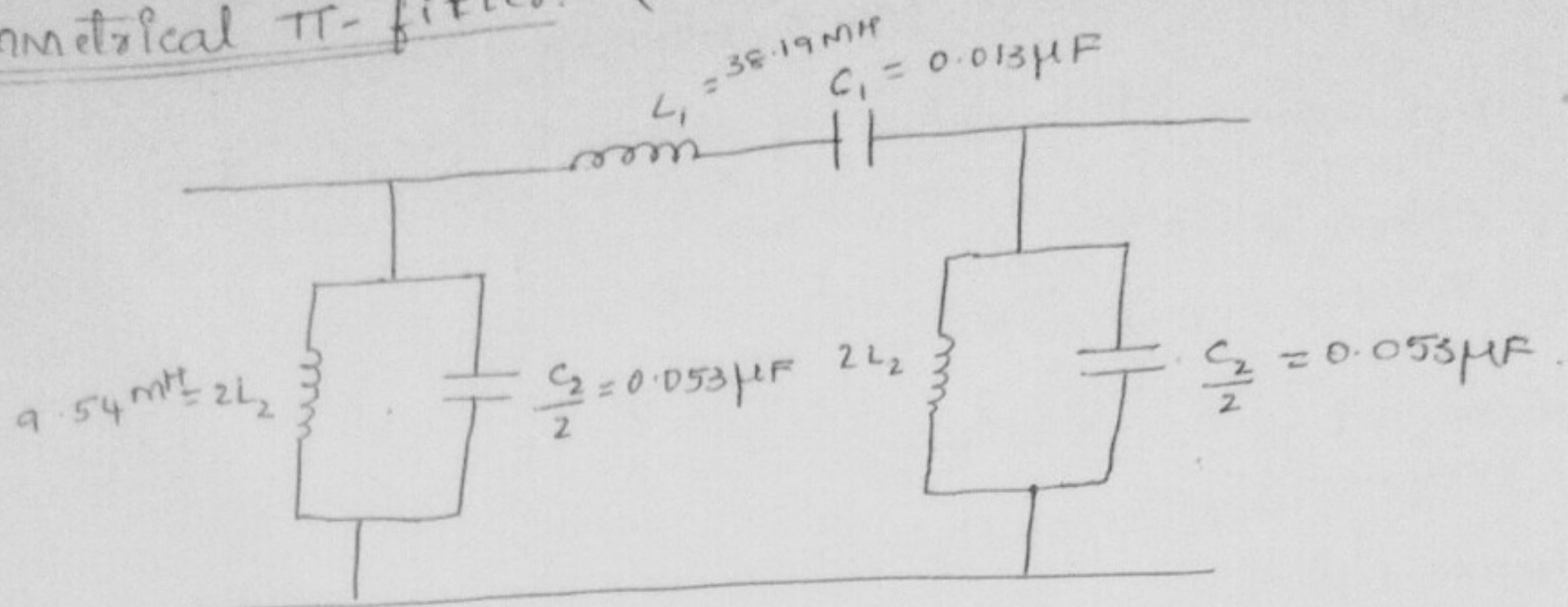

We know that,

$$\Rightarrow f_c = \sqrt{f_1 f_2}$$

$$\Rightarrow f_c = \sqrt{5 \times 10^3} = \sqrt{50} \text{ kHz} = 7.07 \text{ kHz}$$

29:- Design a Band pass filter whose cut off frequencies are 1 kHz and 10 kHz and the nominal impedance is 500Ω . Draw the symmetrical T and π configuration.

Sol:- Given data,

Nominal impedance $K = 500 \Omega$

Lower cut frequency $f_1 = 1 \text{ kHz}$

$f_2 = 10 \text{ kHz}$

We know that,

$$L_1 = \frac{K}{\pi(f_2 - f_1)} \text{ H} \quad \& \quad C_1 = \frac{f_2 - f_1}{4\pi K f_1 f_2} \text{ F}$$

$$L_2 = \frac{K(f_2 - f_1)}{4\pi f_1 f_2} \quad \& \quad C_2 = \frac{1}{\pi K(f_2 - f_1)}$$

$$\Rightarrow L_1 = \frac{500}{\pi \times 9 \text{ k}} = 17.68 \text{ mH}$$


$$\Rightarrow C_1 = \frac{9 \text{ k}}{4\pi(500)10 \text{ k}^2} = 1.432 \times 10^{-7} = 0.14 \mu\text{F}$$

$$\Rightarrow C_2 = \frac{1}{\pi(500)(9 \text{ k})} = 0.707 \mu\text{F} \quad 7.07 \times 10^{-7} = 0.07 \mu\text{F}$$


$$\Rightarrow L_2 = \frac{500 \times 9k}{4\pi \times 10k^2} = 35.80 \text{ mH}$$

3(24)02

Symmetrical T-section BPF:-

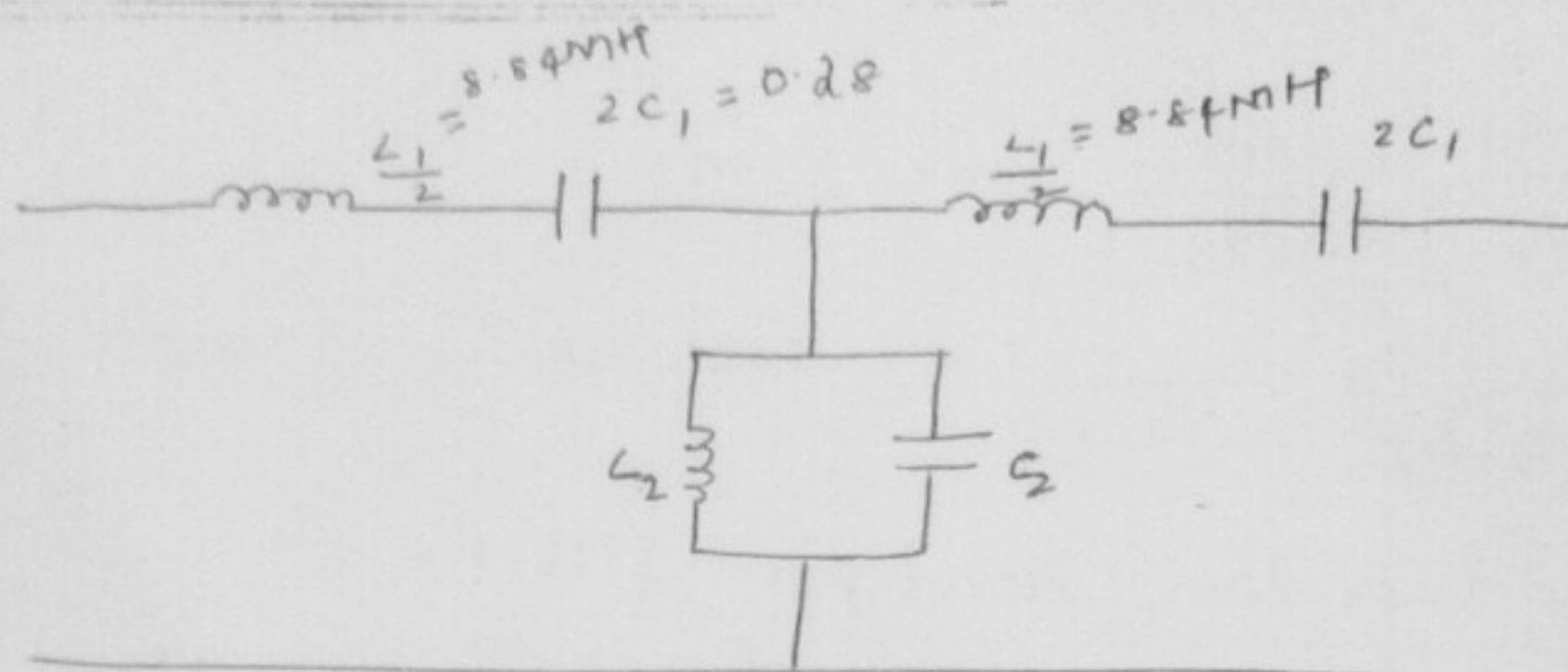

Symmetrical π -section BPF:-

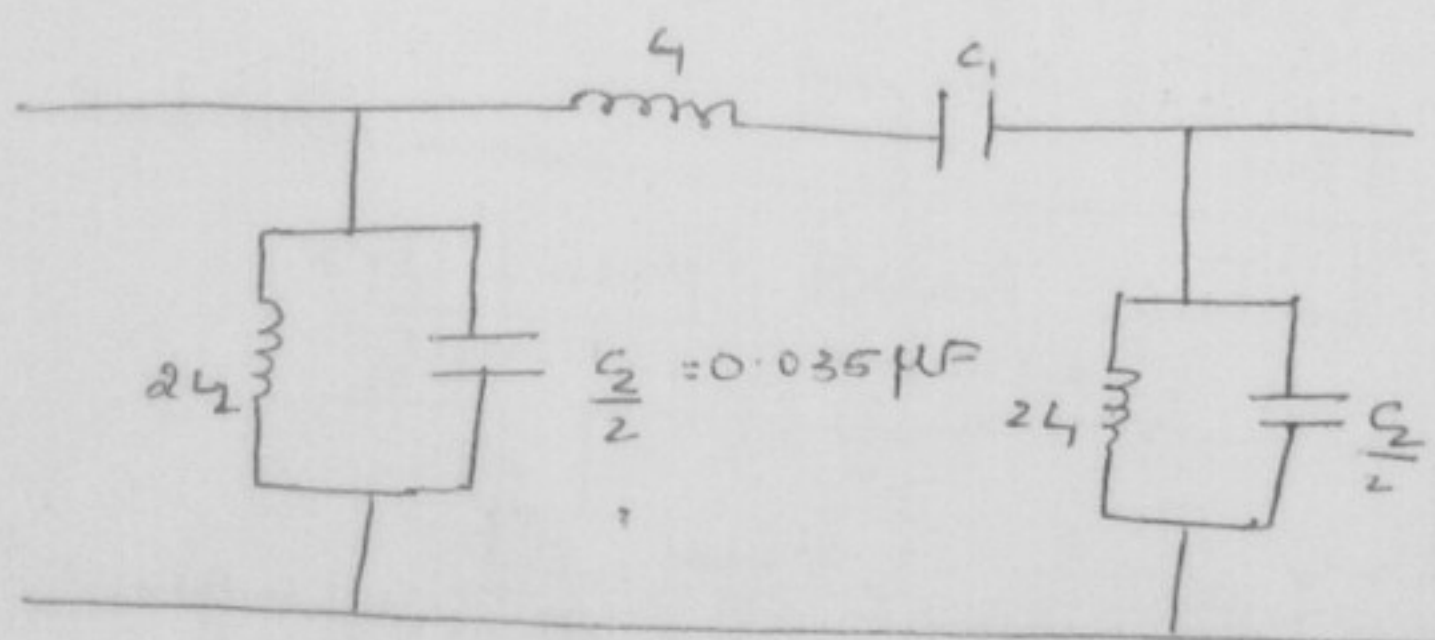

Q:- Design a symmetrical BPF of T & π sections whose cut off frequencies are 6 kHz and 3 kHz, the nominal impedance is given as 600 Ω .

sol:- Given,

Lower cut of frequency = $f_1 = 3 \text{ kHz}$

Upper cut of frequency = $f_2 = 6 \text{ kHz}$

Nominal Impedance $k = 600 \Omega$

We know that,

$$L_1 = \frac{k}{\pi(f_2 - f_1)} \text{ Henry} \quad \& \quad C_1 = \frac{f_2 - f_1}{4\pi k f_1 f_2} \text{ F}$$

$$L_2 = \frac{k(f_2 - f_1)}{4\pi f_1 f_2} \quad \& \quad C_2 = \frac{1}{\pi k(f_2 - f_1)}$$


$$L_1 = \frac{k}{\pi(f_2 - f_1)} = \frac{600}{\pi \times 3k} = 63.66 \text{ mH}$$

$$C_1 = \frac{f_2 - f_1}{4\pi k f_1 f_2} = \frac{3}{4\pi \times 600 \times 18k} = 2.2104 \times 10^{-8} = 0.0221 \mu\text{F}$$


$$L_2 = \frac{k(f_2 - f_1)}{4\pi f_1 f_2} = \frac{600 \times 3}{4\pi \times 18k} = 7.957 \text{ mH}$$

$$C_2 = \frac{1}{\pi k(f_2 - f_1)} = \frac{1}{\pi \times 600 \times 3k} = 1.7683 \times 10^{-7} = 0.17683 \mu\text{F}$$

Symmetrical T-section Band pass filter:-

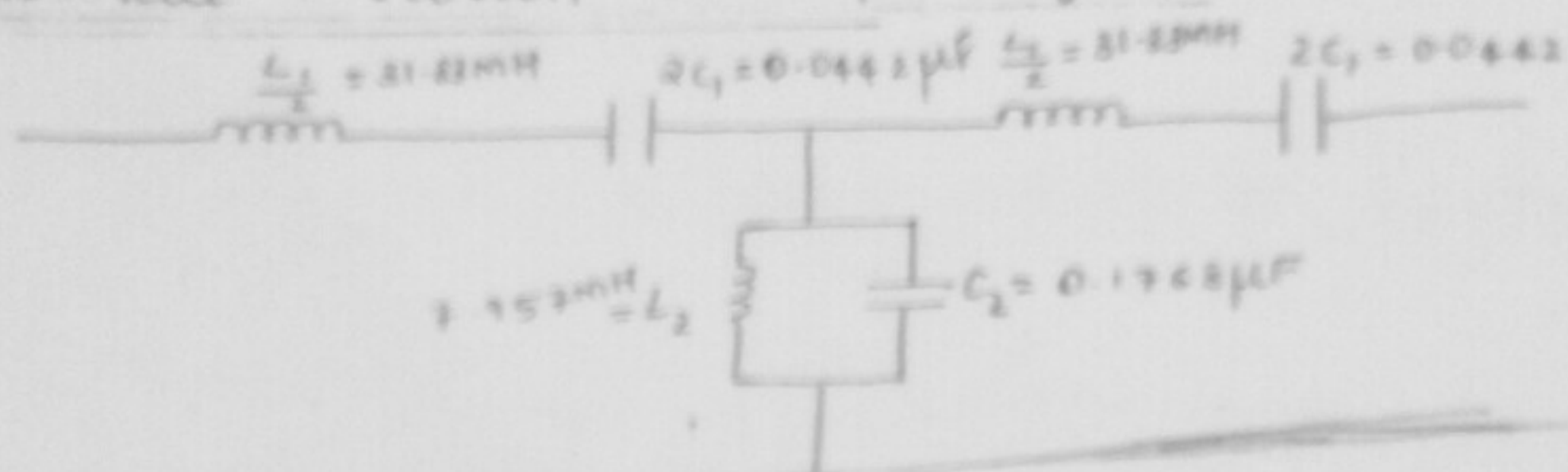

Symmetrical π-section Band pass filter:-

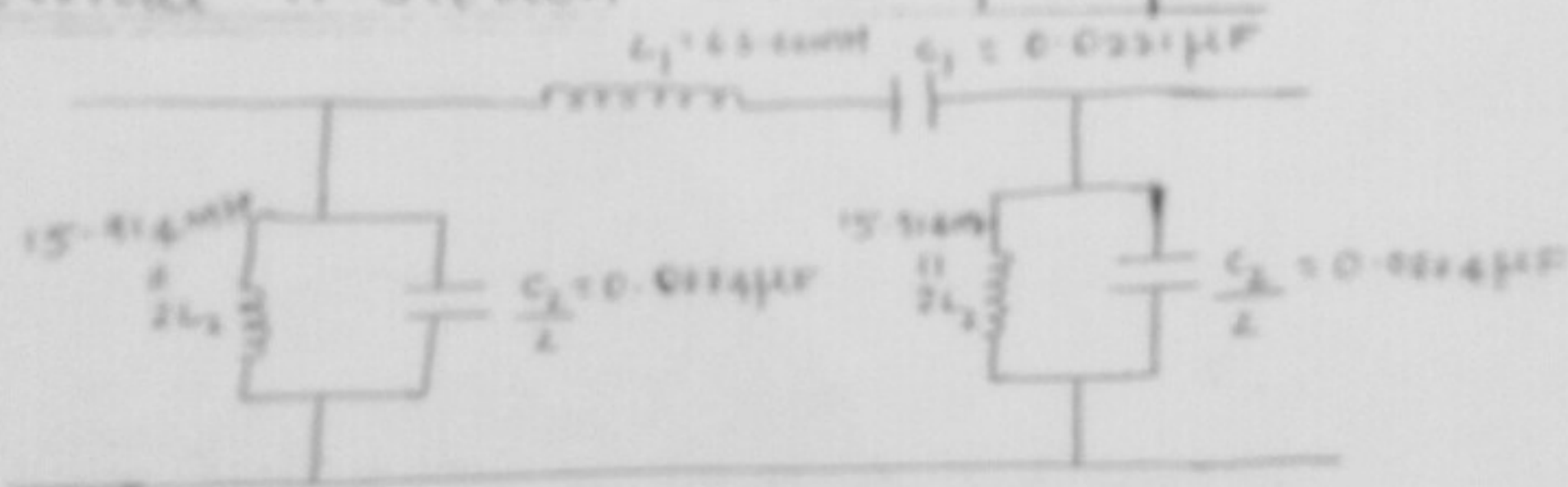

Band Elimination Filter:-

→ A BEF is a one which attenuates a particular band of frequencies and allows the remaining.

→ The frequency to attenuation characteristics are shown

as below,

pass band → $0 \rightarrow f_1$ & $f_2 \rightarrow \infty$


$f_1 \rightarrow \infty$

$(f < f_1)$

$f < f_1$ & $f > f_2$

$f_2 < f < f_1$

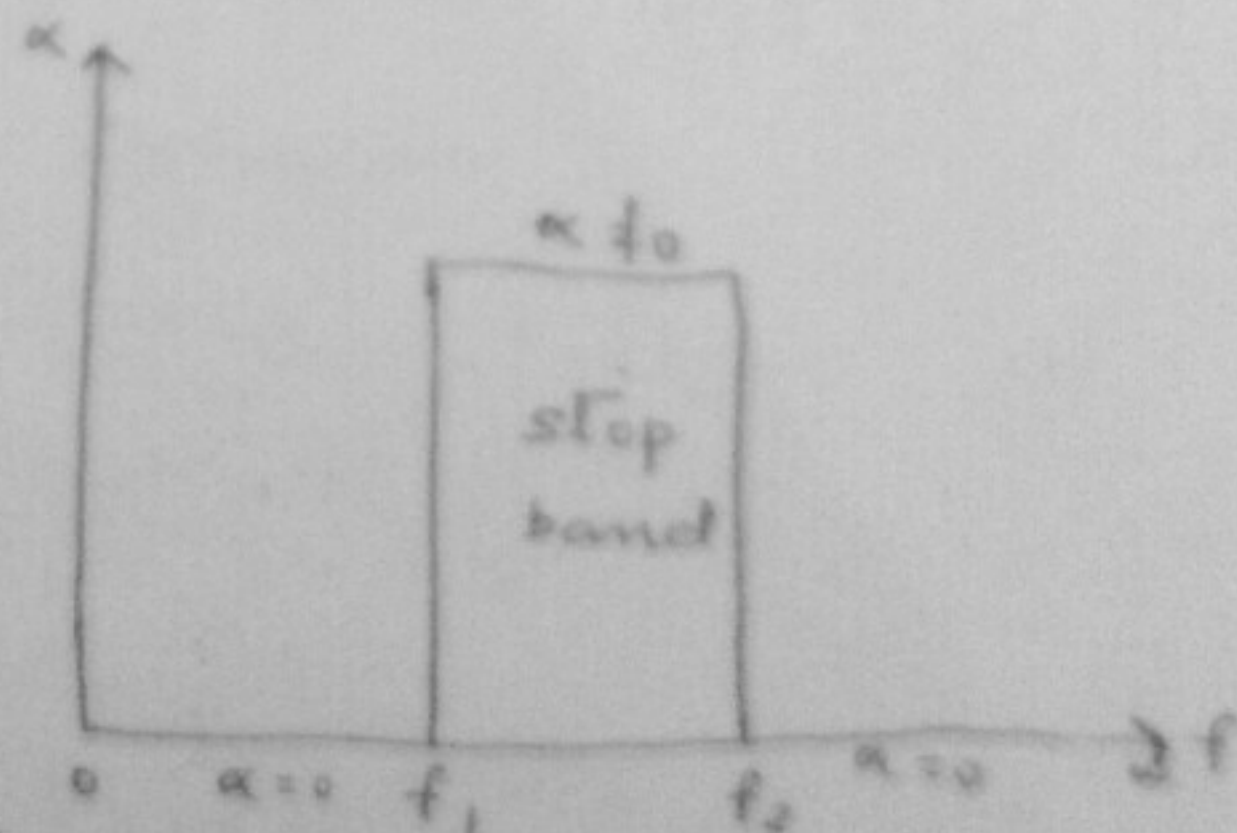stop band $f_1 \rightarrow f_2 \Rightarrow f_1 < f < f_2$




BEF will be constructed by joining a Low pass filter with a High pass filter in parallel


3(25)

Symmetrical T-section Band Elimination Filter:-

$L/2$ and $C/2$

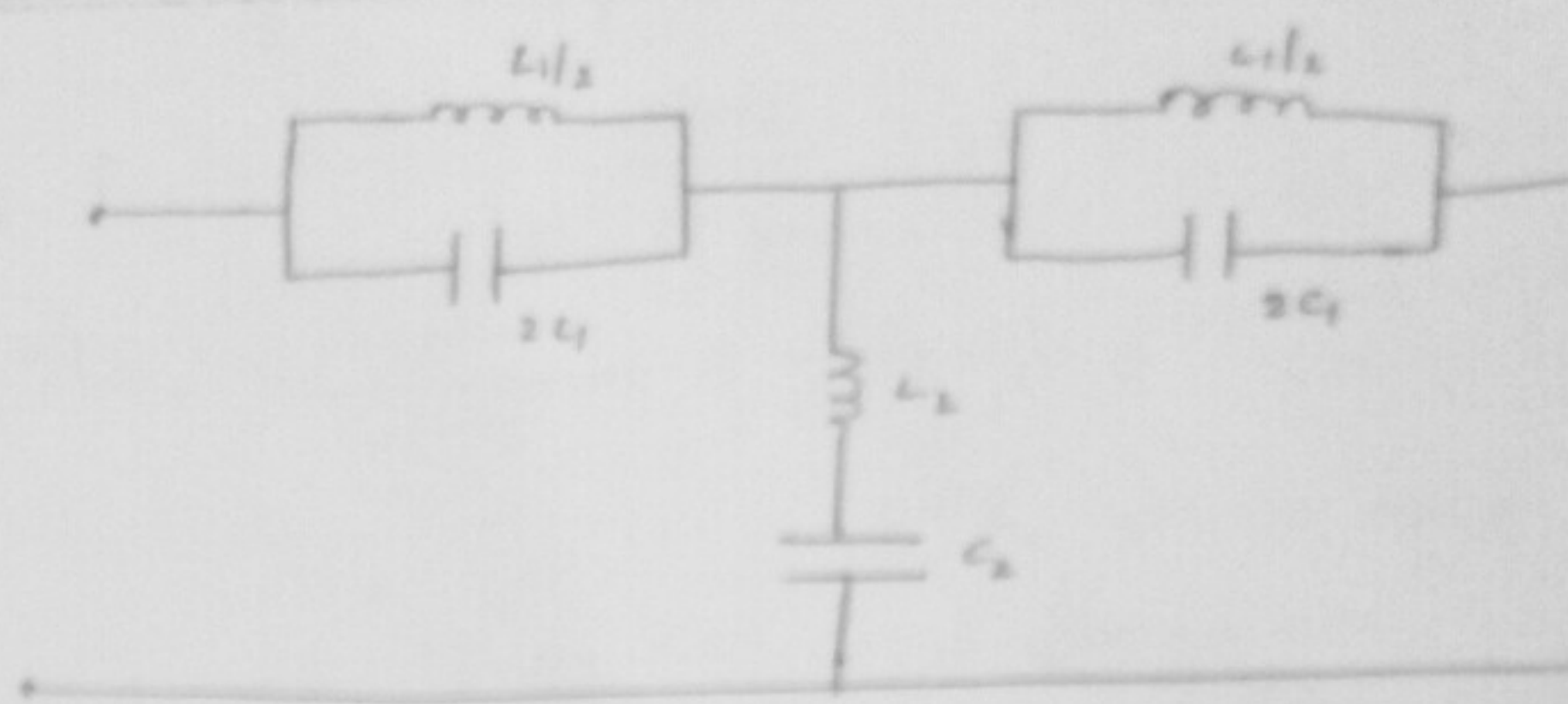

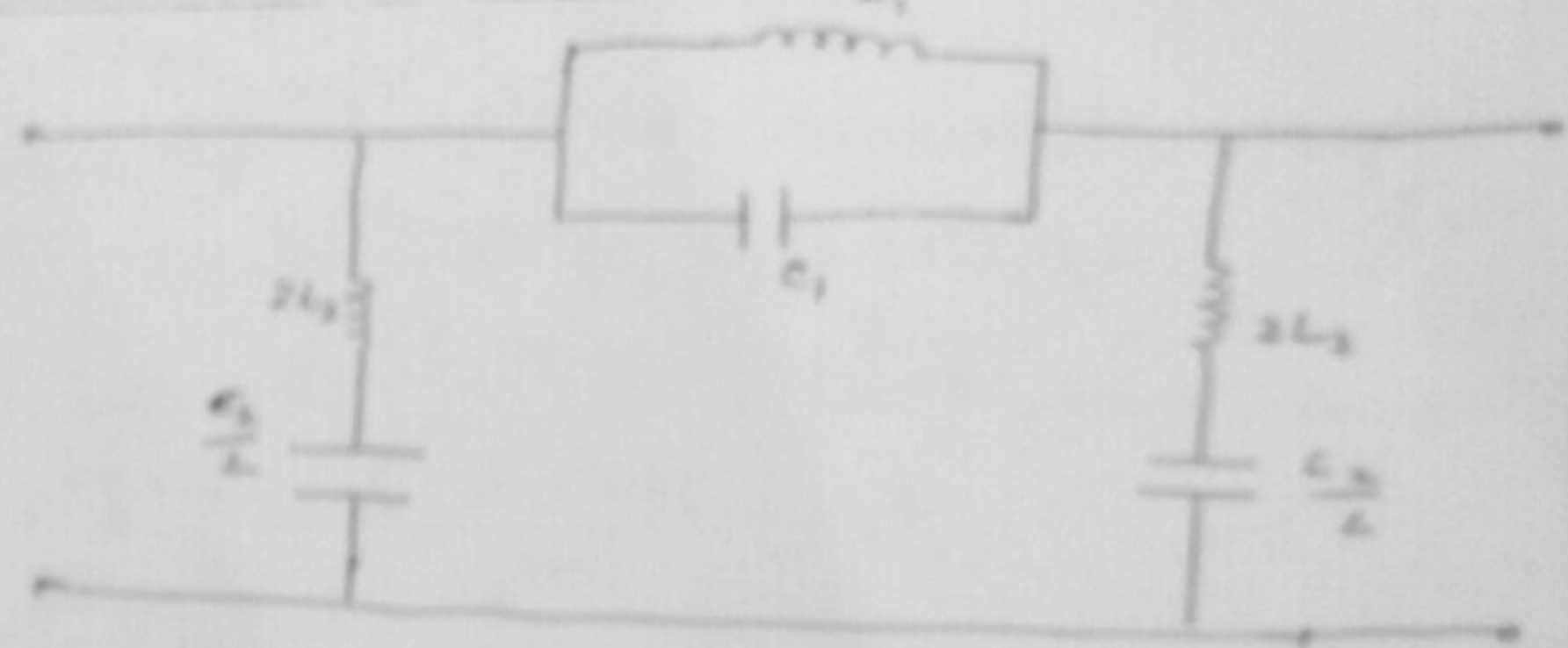Symmetrical π -section Band elimination filter:-



from symmetrical T-section,

$$\Rightarrow Z_1 = \left\{ (j\omega \frac{L_1}{2}) \parallel \left(\frac{1}{j\omega 2C_1} \right) \right\} + \left\{ (j\omega \frac{L_1}{2}) \parallel \left(\frac{1}{j\omega 2C_1} \right) \right\}$$

$$\Rightarrow Z_1 = 2 \times \frac{j\omega \frac{L_1}{2} \times \frac{1}{j\omega 2C_1}}{\frac{j\omega L_1}{2} + \frac{1}{j\omega 2C_1}} = \frac{2 \times \frac{L_1}{4C_1}}{\frac{L_1 - \omega^2 L_1 C_1 + 1}{4C_1}} = \frac{\frac{L_1}{C_1}}{\frac{j\omega L_1 + \frac{1}{j\omega C_1}}{2}} = \frac{\frac{L_1}{C_1}}{\frac{j\omega(L_1 + \frac{1}{\omega^2 C_1})}{2}}$$

$$\Rightarrow Z_1 = \frac{L_1 - j\omega}{1 - \omega^2 L_1 C_1}$$

$$\Rightarrow Z_1 = \frac{j\omega L_1}{1 - \omega^2 L_1 C_1}$$

$$\Rightarrow Z_2 = j\omega L_2 + \frac{1}{j\omega C_2} = \frac{-\omega^2 L_2 C_2 + 1}{j\omega C_2} = \frac{j(\omega^2 L_2 C_2 - 1)}{\omega C_2}$$

→ To obtain Band elimination characteristics the series arm and shunt arm should resonate at same frequency. The series arm consists of parallel

resonant ckt whose resonant condition will be obtained at its net susceptance zero.

→ We know that impedance of the series branch,

$$\Rightarrow Z_1 = \frac{j\omega L_1}{1 - \omega^2 L_1 C_1}$$

$$\Rightarrow Y_1 = \frac{1}{Z_1} = \frac{1 - \omega^2 L_1 C_1}{j\omega L_1} = \frac{j(\omega^2 L_1 C_1 - 1)}{\omega L_1} = 0 + jB$$

→ At $\omega = \omega_r$, $B = 0$

$$\omega_r^2 L_1 C_1 = 1$$

$$\omega_r = \frac{1}{\sqrt{L_1 C_1}} \longrightarrow \textcircled{1}$$

→ The shunt branch consists of a series resonant ckt which will resonate at a frequency where its net reactance = 0

→ We know that,

$$Z_2 = \frac{j(\omega^2 L_2 C_2 - 1)}{\omega C_2} = 0 + jX$$

→ At $\omega = \omega_r$, $X = 0$

$$\Rightarrow \omega_r^2 L_2 C_2 = 1$$

$$\Rightarrow \omega_r = \frac{1}{\sqrt{L_2 C_2}} \longrightarrow \textcircled{2}$$

∴ From eq ① & ②

$$L_1 C_1 = L_2 C_2 \Rightarrow \frac{1}{L_1 C_1} = \frac{1}{L_2 C_2}$$

Taking the product of $Z_1 Z_2$,

$$\Rightarrow Z_1 Z_2 = \frac{j\omega L_1}{(1 - \omega^2 L_1 C_1)} \times \frac{j(1 - \omega^2 L_2 C_2)}{\omega C_2} = \left(\frac{1 - \omega^2 L_2 C_2}{1 - \omega^2 L_1 C_1} \right) \frac{L_1}{C_2}$$

$$\Rightarrow Z_1 Z_2 = \frac{L_1}{C_2} = K^2 \quad \left(\begin{array}{l} \Downarrow \\ \text{from resonant} \\ \text{cond}^n L_1 C_1 = L_2 C_2 \end{array} \right)$$

→ As the filter satisfy the relationship $Z_1 Z_2 = K^2$, it's a constant - K filter.

→ From the condition of pass band, we have

$$-1 < \frac{Z_1}{4Z_2} < 0$$

lowest limit,

3(26)04

$$\Rightarrow \frac{Z_1}{4Z_2} = -1$$

$$\Rightarrow Z_1 = -4Z_2 \quad (\text{multiply on both sides with } Z_2)$$

$$\Rightarrow Z_1 Z_2 = -4Z_2^2$$

$$\Rightarrow k^2 = -4Z_2^2 \Rightarrow Z_2 = \pm \frac{jk}{2} \quad \text{Where the value of } Z_2 \text{ at lower cut-off frequency is opposite to the value of } Z_2 \text{ at upper cut-off frequency.}$$

$$\Rightarrow \text{We have } Z_2 = j\omega L_2 + \frac{1}{j\omega C_2}$$

(i) $\Rightarrow$ At $\omega = \omega_1$, then i.e., at lower cut-off frequency capacitive reactance dominates inductive reactance and hence Z_2 is negative and is given by

$$Z_2 = -\frac{jk}{2} \quad (X_C > X_L) \quad \therefore j\omega L_2 + \frac{1}{j\omega C_2}$$

(ii) At $\omega = \omega_2$, i.e., at upper cut-off frequency, inductive reactance dominates capacitive reactance, and Z_2 is +ve and is given by

$$Z_2 = \frac{+jk}{2}$$

$$\Rightarrow \therefore Z_2 \text{ at } \omega = \omega_2 = -(Z_2 \text{ at } \omega = \omega_1) \text{ i.e., } Z_2 = \left(j\omega_1 L_2 + \frac{1}{j\omega_1 C_2} \right) = -\left(j\omega_2 L_2 + \frac{1}{j\omega_2 C_2} \right)$$

$$\Rightarrow j\omega_1 L_2 + \frac{1}{j\omega_1 C_2} = -j\omega_2 L_2 - \frac{1}{j\omega_2 C_2}$$

$$\Rightarrow jL_2(\omega_1 + \omega_2) = -\frac{1}{j\omega_2 C_2} - \frac{1}{j\omega_1 C_2}$$

$$\Rightarrow jL_2(\omega_1 + \omega_2) = j \left(\frac{1}{\omega_2 C_2} + \frac{1}{\omega_1 C_2} \right)$$

$$\Rightarrow L_2(\omega_1 + \omega_2) = \frac{1}{C_2} \left(\frac{\omega_1 + \omega_2}{\omega_1 \omega_2} \right)$$

$$\Rightarrow L_2 C_2 = \frac{1}{\omega_1 \omega_2}$$

$$\Rightarrow \omega_1 \omega_2 = \frac{1}{L_2 C_2} = \frac{1}{1/\omega_s^2} = \omega_s^2$$

$$\Rightarrow \omega_s = \sqrt{\omega_1 \omega_2}$$

$$\omega_s = \omega_0$$

Design of Band Elimination filter:-

→ The value of x_2 at $\omega = \omega_1 = -\frac{jk}{2}$

$$\Rightarrow j\omega_1 L_2 + \frac{1}{j\omega_1 C_2} = -\frac{jk}{2}$$

$$\Rightarrow j\left(\omega_1 L_2 - \frac{1}{\omega_1 C_2}\right) = -\frac{jk}{2}$$

$$\Rightarrow -\omega_1 L_2 + \frac{1}{\omega_1 C_2} = \frac{k}{2}$$

$$\Rightarrow \frac{1 - \omega_1^2 L_2 C_2}{\omega_1 C_2} = \frac{k}{2} \Rightarrow \frac{1 - \frac{\omega_1^2}{\omega_g^2}}{\omega_1 C_2} = \frac{k}{2}$$

$$\Rightarrow 1 - \left(\frac{\omega_1}{\omega_g}\right)^2 = \omega_1 C_2 \frac{k}{2}$$

$$\Rightarrow 1 - \frac{\omega_1^2}{\omega_1^* \omega_2^*} = \omega_1 C_2 \frac{k}{2} \Rightarrow 1 - \frac{\omega_1}{\omega_2} = \omega_1 C_2 \frac{k}{2} \Rightarrow \frac{\omega_2 - \omega_1}{\omega_2} = \omega_1 C_2 \frac{k}{2}$$

$$\Rightarrow \frac{2\pi(f_2 - f_1)}{2\pi f_2} = 2\pi f_1 C_2 \frac{k}{2} \Rightarrow \frac{f_2 - f_1}{f_2} = \pi f_1 C_2 k$$

$$\Rightarrow C_2 = \frac{f_2 - f_1}{k\pi f_1 f_2} \text{ Farads.}$$

→ we know that,

$$\Rightarrow \omega_g^2 = \frac{1}{L_2 C_2} \Rightarrow C_2 = \frac{1}{\omega_g^2 L_2} = \frac{k\pi f_1 f_2}{\omega_1 \omega_2 (f_2 - f_1)}$$

$$\Rightarrow L_2 = \frac{k\pi f_1 f_2}{4\pi^2 f_1 f_2 (f_2 - f_1)} = \frac{k}{4\pi(f_2 - f_1)}$$

$$L_2 = \frac{k}{4\pi(f_2 - f_1)} \text{ Henrys}$$

we know that

$$\Rightarrow \frac{L_1}{C_2} = k^2 \Rightarrow \frac{L_2}{C_1} = k^2 = \frac{L_1}{C_2}$$

$$\Rightarrow L_1 = k^2 C_2 = \frac{k(f_2 - f_1)}{\pi f_1 f_2} \text{ Henrys.}$$

$$\Rightarrow C_1 = \frac{L_2}{k^2} = \frac{1}{4\pi k(f_2 - f_1)} \text{ Farads.}$$

$$j\omega L_1 + j\omega L_2$$

$$j\omega_1^2 L_1 C_2 + 1 = -\frac{jk}{2} j\omega_1 C_2$$

$$1 - \frac{\omega_1^2}{\omega_g^2} = -jk\pi f_1 C_2$$

$$1 - \frac{f_1}{f_2} = k\pi f_1 C_2$$

$$C_2 = \frac{f_2 - f_1}{k\pi f_1 f_2}$$

29/11/23

Q:- Design a LPF of constant k-type whose cut-off frequency is 20kHz and for a nominal impedance of 400Ω and also determine the values of α, β, Z_0 at a frequency of a) 10kHz b) 30kHz

Ans:- Given data,

It is a low pass filter of constant k-type

cut-off frequency $f_c = 20\text{kHz}$

Nominal Impedance $k = 400\Omega$

Design:-

⇒ We know that, the value of L and C from LPF is


$$L = \frac{k}{\pi f_c} \quad \& \quad C = \frac{1}{k\pi f_c}$$

$$L = \frac{400}{\pi(20\text{k})}$$


$$L = 6.36\text{mH}$$

$$C = \frac{1}{400\pi \times 20\text{k}} = 0.0397\mu\text{F}$$

T-section

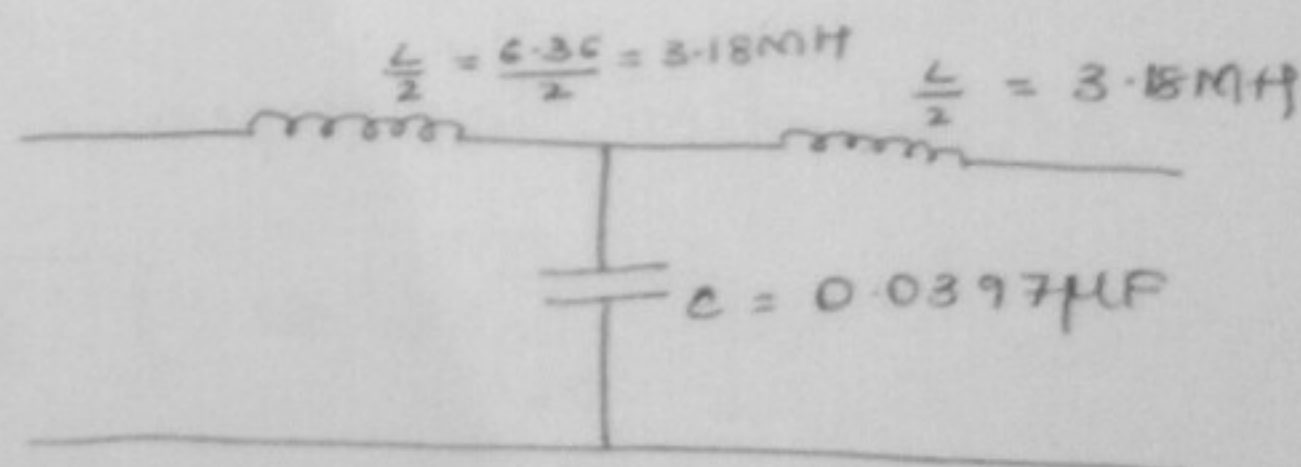

π-section:-

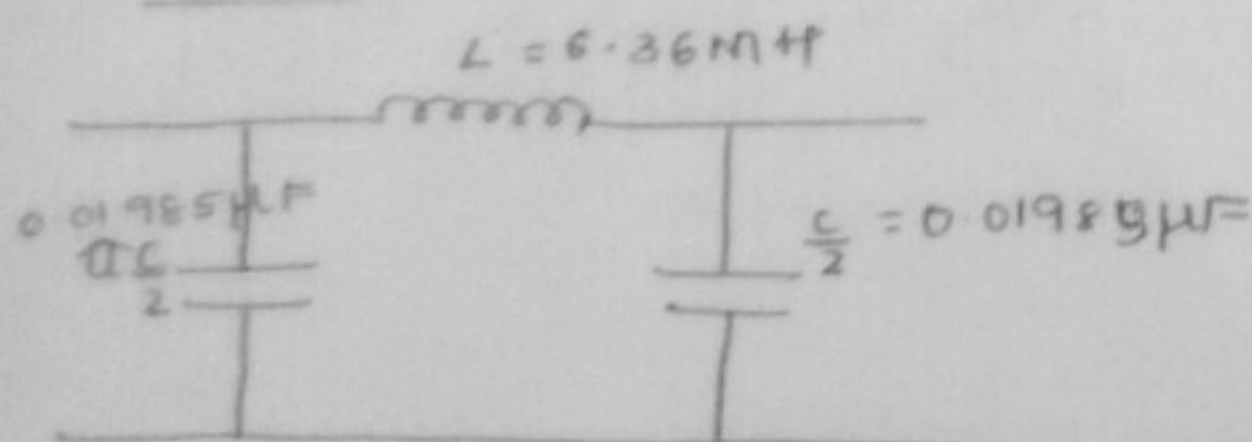

Determination of α, β, Z_0 :-

a) 10kHz , Given that $f = 10\text{kHz}$

$$f = 10\text{kHz} < f_c = 20\text{kHz}$$

Hence it lies in transmission band.

→ According to condⁿ of transmission band,


$$\alpha = 0, \quad \beta = 2\sin^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|}$$

$$\beta = 2\sin^{-1} \left(\frac{f}{f_c} \right) = 2\sin^{-1} \left(\frac{10}{20} \right)$$

$$\beta = 2\sin^{-1}(0.5) = 2 \times 30^\circ = 60^\circ$$

$$\left(\frac{Z_1}{4Z_2} = \frac{f}{f_c} \right)$$
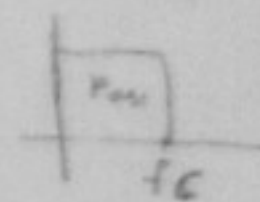
$$\therefore \frac{Z_1}{4Z_2} = \left(\frac{f}{f_c} \right)^2$$



$$Z_{0\pi} = \frac{k}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}} = \frac{400 \times 2}{\sqrt{3}} = 461.88 \Omega$$

b) At a frequency of $f = 30 \text{ kHz}$.

$$\Rightarrow f = 30 \text{ kHz} > f_c = 20 \text{ kHz} \Rightarrow f > f_c$$

$\therefore$ It lies in stop band.

In the stop band,

$$\beta = \pi, \quad \alpha = 2 \cosh^{-1} \left| \sqrt{\frac{Z_1}{4Z_2}} \right| = 2 \cosh^{-1} \left(\frac{f}{f_c} \right)$$

$$\alpha = 2 \cosh^{-1} \left(\frac{30}{20} \right) = 2 \cosh^{-1} (1.5) = 2 \times 0.912$$

$$\alpha = (1.82) \text{ Nepers}$$

Note:-

→ Attenuation is expressed in terms of decibels (or)

Nepers.

$$\rightarrow \text{Attenuation in dB is given by } \alpha = 20 \log \left(\frac{V_1}{V_2} \right) = 20 \log \left(\frac{I_1}{I_2} \right) \\ = 10 \log \left(\frac{P_1}{P_2} \right) \text{ dB.}$$

$$\rightarrow \text{Attenuation in Nepers is given by } \alpha = \ln \left(\frac{V_1}{V_2} \right) = \ln \left(\frac{I_1}{I_2} \right)$$

$$Z_{0T} = k \sqrt{1 - \left(\frac{f}{f_c}\right)^2} = 400 \sqrt{1 - \frac{9}{4}} = j447.213 \Omega$$

$$Z_{0\pi} = \frac{400}{\sqrt{1 - \frac{9}{4}}} = -j447.213357.7 \Omega$$

29:- Design a constant k-HPF whose cut-off frequency

is 25 kHz for a nominal impedance of 600Ω and

also determine the values of α , β , Z_0 at frequencies of

50 kHz and 12.5 kHz

30:- Given data,

It is High pass filter.

$$f_c = 25 \text{ kHz}$$

$$k = 600 \Omega$$

3(28) 46

Design:-

We know that the values of L and C from HPF is

$$L = \frac{k}{4\pi f_c} \quad \& \quad C = \frac{1}{4k\pi f_c}$$


$$L = \frac{600}{4\pi \times 25k}$$

$$L = 1.909 \text{ mH}$$

$$C = \frac{1}{4\pi \times 600 \times 25k}$$


$$C = 5.305 \times 10^{-9} = 0.005305 \mu\text{F}$$

π -section:-

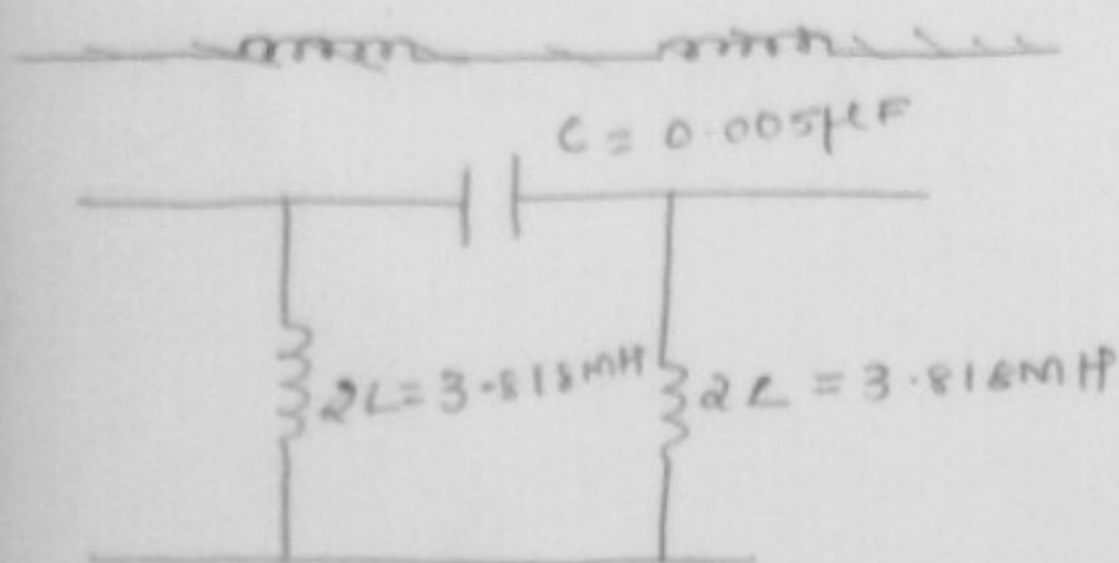

$$Z_1 = \frac{1}{j\omega C}$$

T-section:-

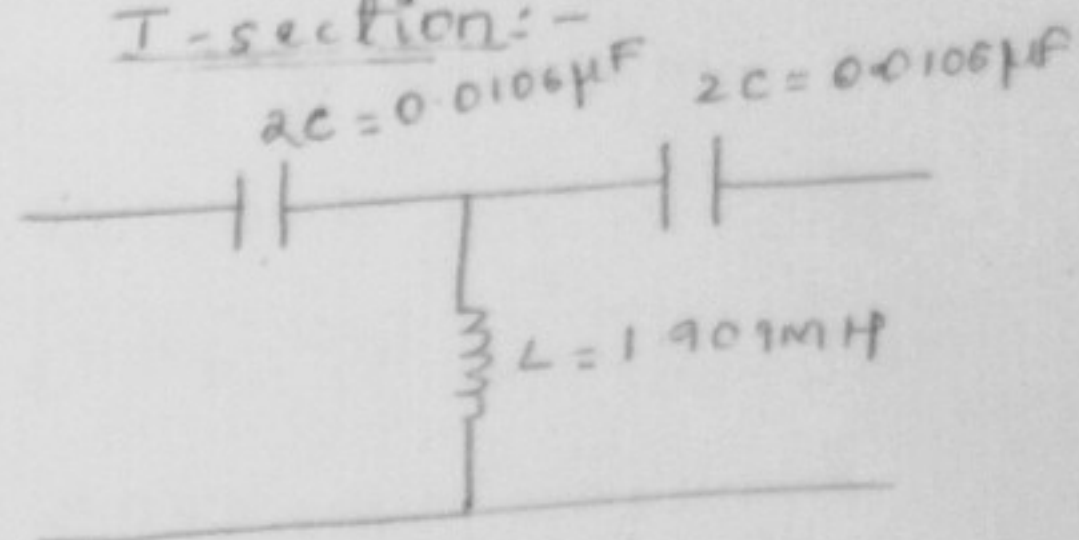

Determination of α , β , Z_0 :-

a) At a frequency of 50 kHz

$$f = 50 \text{ kHz}, f_c = 25 \text{ kHz}$$

$\Rightarrow f > f_c \Rightarrow$ It lies in pass band

$\Rightarrow$ Acc. to pass band,

$$\alpha = 0, \beta = 2 \sin^{-1} \sqrt{\left| \frac{Z_1}{4Z_2} \right|} = 2 \sin^{-1} \left(\frac{f_c}{f} \right) = 2 \sin^{-1} \left(\frac{25}{50} \right) = 2 \sin^{-1} \left(\frac{1}{2} \right)$$

$$\beta = 2 \times 30^\circ$$

$$\beta = 60^\circ$$

$$\Rightarrow Z_{0T} = k \sqrt{1 - \left(\frac{f_c}{f} \right)^2} = k \sqrt{1 - \frac{1}{4}} = 519.615 \Omega$$

$$\Rightarrow Z_{0\pi} = \frac{k}{\sqrt{1 - \left(\frac{f_c}{f} \right)^2}} = \frac{k}{\sqrt{1 - \frac{1}{4}}} = 692.82 \Omega$$

b) At $f = 12.5 \text{ kHz}$

$f < f_c \Rightarrow$ It lies in stop band.

Where $\beta = \pi$, $\alpha = 2 \cosh^{-1} \left(\frac{f_c}{f} \right) = 2 \cosh^{-1} \left(\frac{25}{12.5} \right) = (2.633) \text{ Nepers}$

$$\alpha_{OT} = k \sqrt{1 - \left(\frac{f_c}{f} \right)^2} = j1039.23 \Omega$$

$$\alpha_{OT\pi} = -j346.410 \Omega$$

39:- Design a Band elimination filter, to eliminate the frequencies between 2 kHz and 5 kHz . The characteristic impedance of filter should be 500Ω .

sol:- Given data, It is a Band elimination filter.

$$f_1 = 2 \text{ kHz} \quad \& \quad f_2 = 5 \text{ kHz}$$

$$k = 500 \Omega$$

soln:-

$$\alpha_1 = \frac{k(f_2 - f_1)}{\pi f_1 f_2}$$

$$L_1 = 47.746 \text{ mH}$$

$$C_1 = \frac{1}{4\pi k(f_2 - f_1)}$$

$$C_1 = \frac{0.053 \mu\text{F}}{1} = 0.053 \mu\text{F}$$


$$\alpha_2 = \frac{k}{4\pi(f_2 - f_1)}$$

$$L_2 = 13.26 \text{ mH}$$

$$C_2 = \frac{f_2 - f_1}{\pi k f_1 f_2}$$


$$C_2 = \frac{1.909 \times 10^{-4}}{1.61 \text{ k}} = \frac{0.190}{1.61 \text{ k}} = 0.190 \mu\text{F}$$

Symmetrical T-section BEF:-

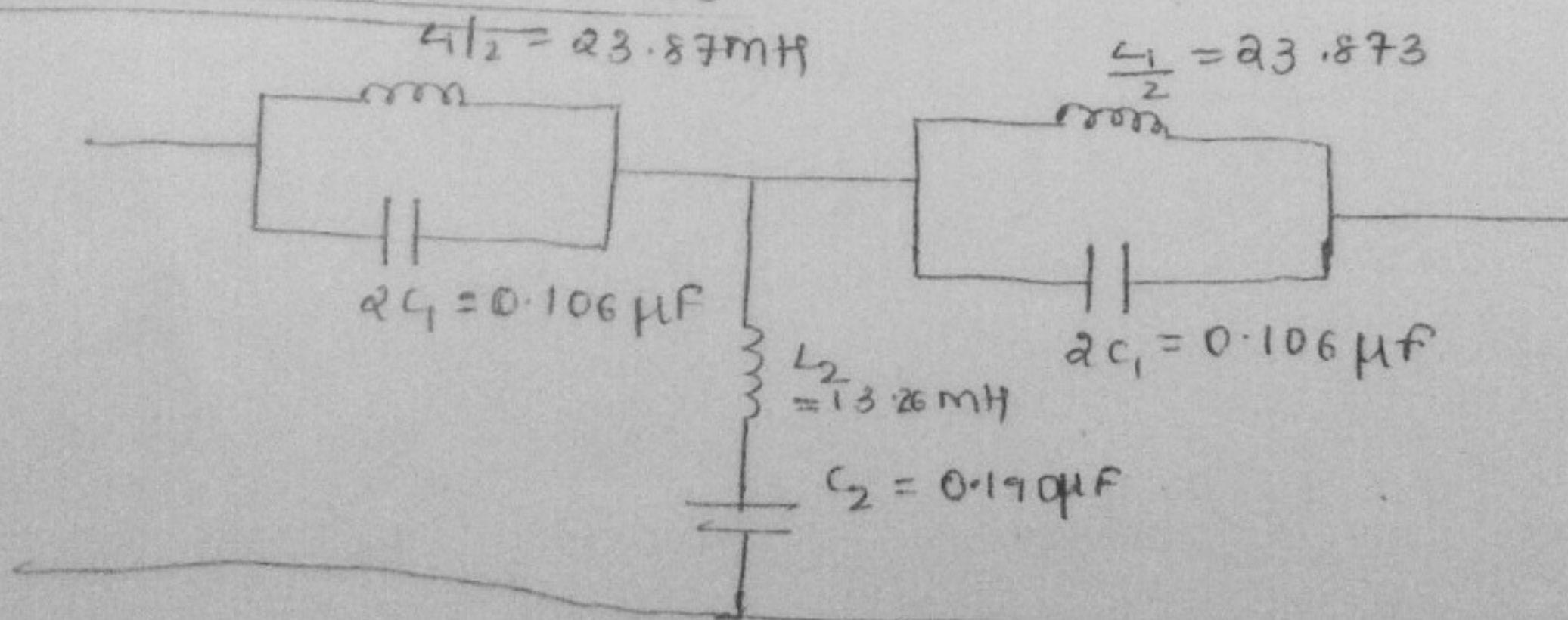

Symmetrical π -section BEF.

3(29) 97

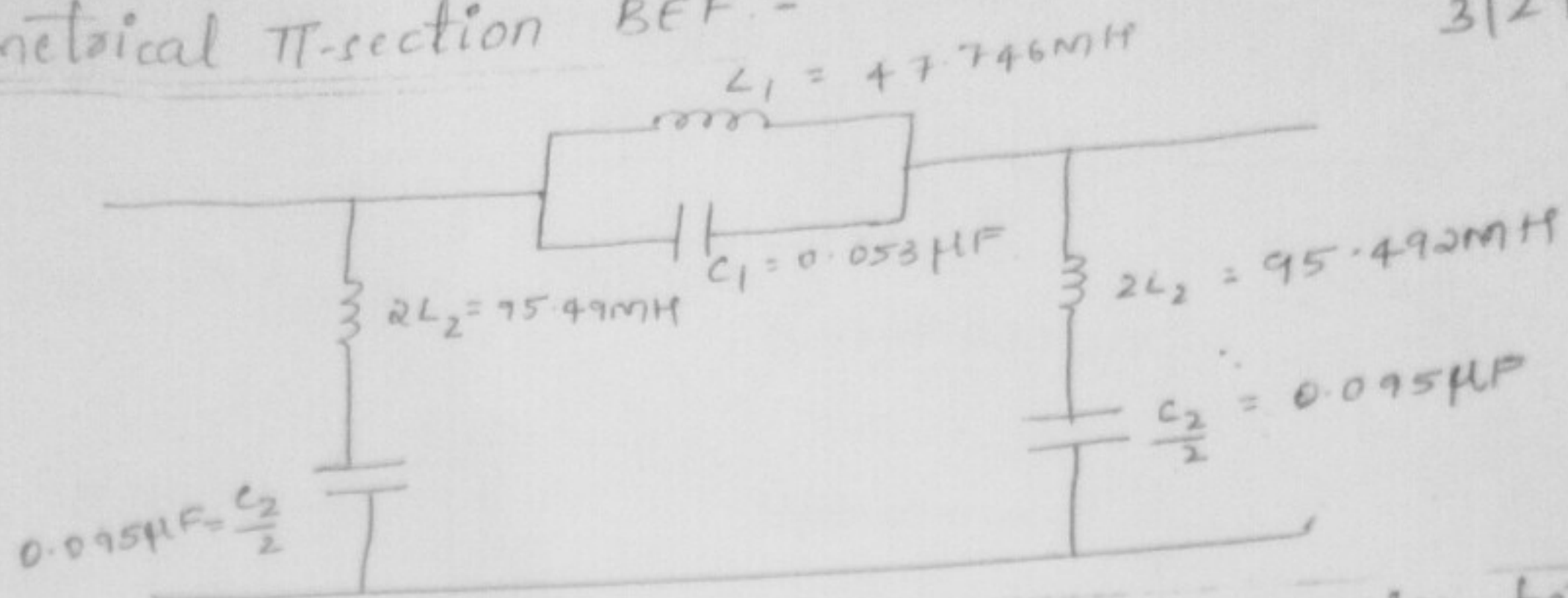

49:- Design a BEF, to eliminate the frequencies between 2 kHz and 4 kHz for a nominal impedance of 600 Ω .
Given data, It is a Band elimination filter
 $f_1 = 2 \text{ kHz}$ & $f_2 = 4 \text{ kHz}$

$$K = 600 \Omega$$

Soln $L_1 = \frac{K(f_2 - f_1)}{\pi f_1 f_2} = 47.746 \text{ mH}$

$$C_1 = \frac{1}{4\pi K(f_2 - f_1)} = \frac{1}{4\pi \times 600 \times 2 \text{ kHz}}$$

$$C_1 = 6.531 \times 10^{-8}$$

$$C_1 = 0.063 \mu\text{F}$$

$$L_2 = \frac{K}{4\pi(f_2 - f_1)} = \frac{600}{4\pi(2 \text{ kHz})}$$


$$L_2 = 23.87 \text{ mH}$$

$$C_2 = \frac{f_2 - f_1}{\pi K f_1 f_2} = \frac{2 \text{ kHz}}{\pi \times 600 \times 8 \text{ kHz}^2}$$

$$C_2 = 1.326 \times 10^{-4} \times 10^{-3}$$


$$C_2 = 1.326 \times 10^{-7} = 0.1326 \mu\text{F}$$

Symmetrical T-section BEF:-

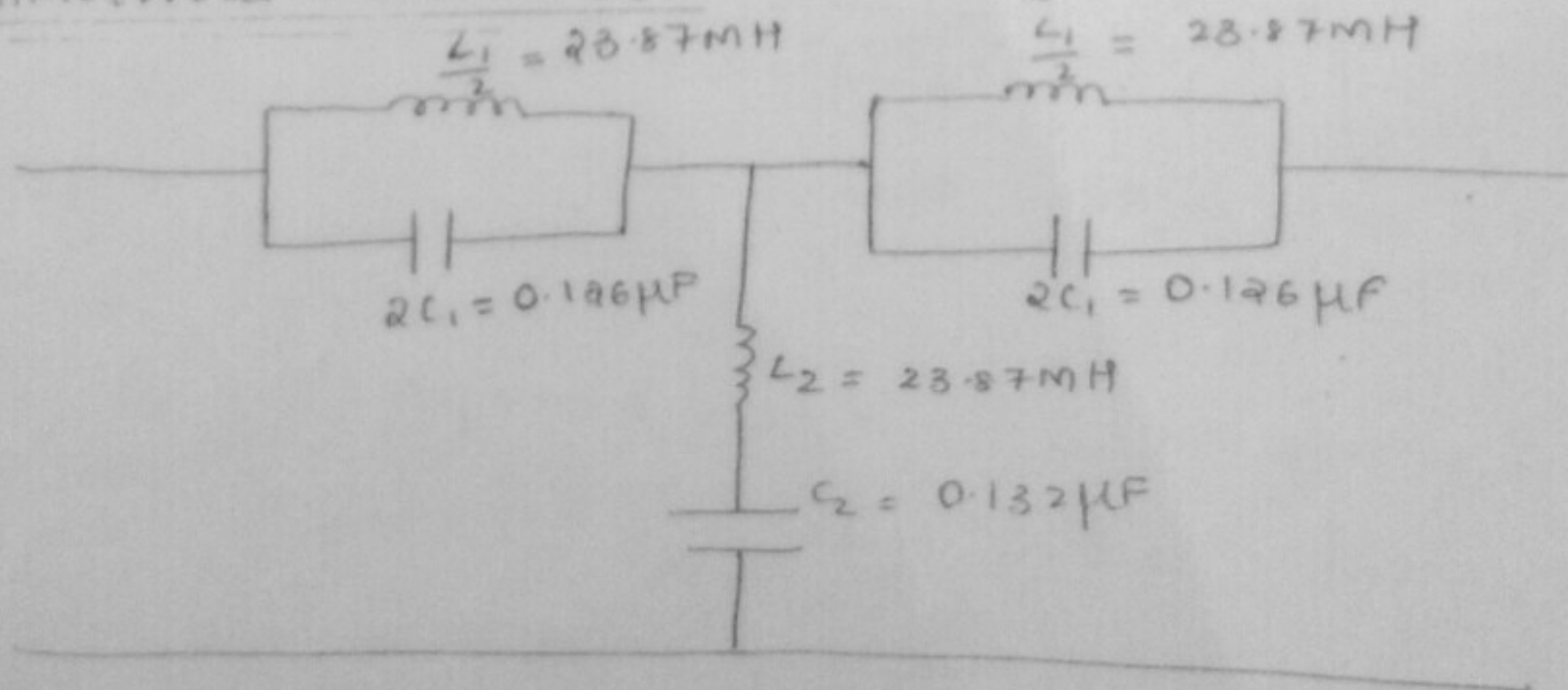

Symmetrical π -section BEF:-

Ques)

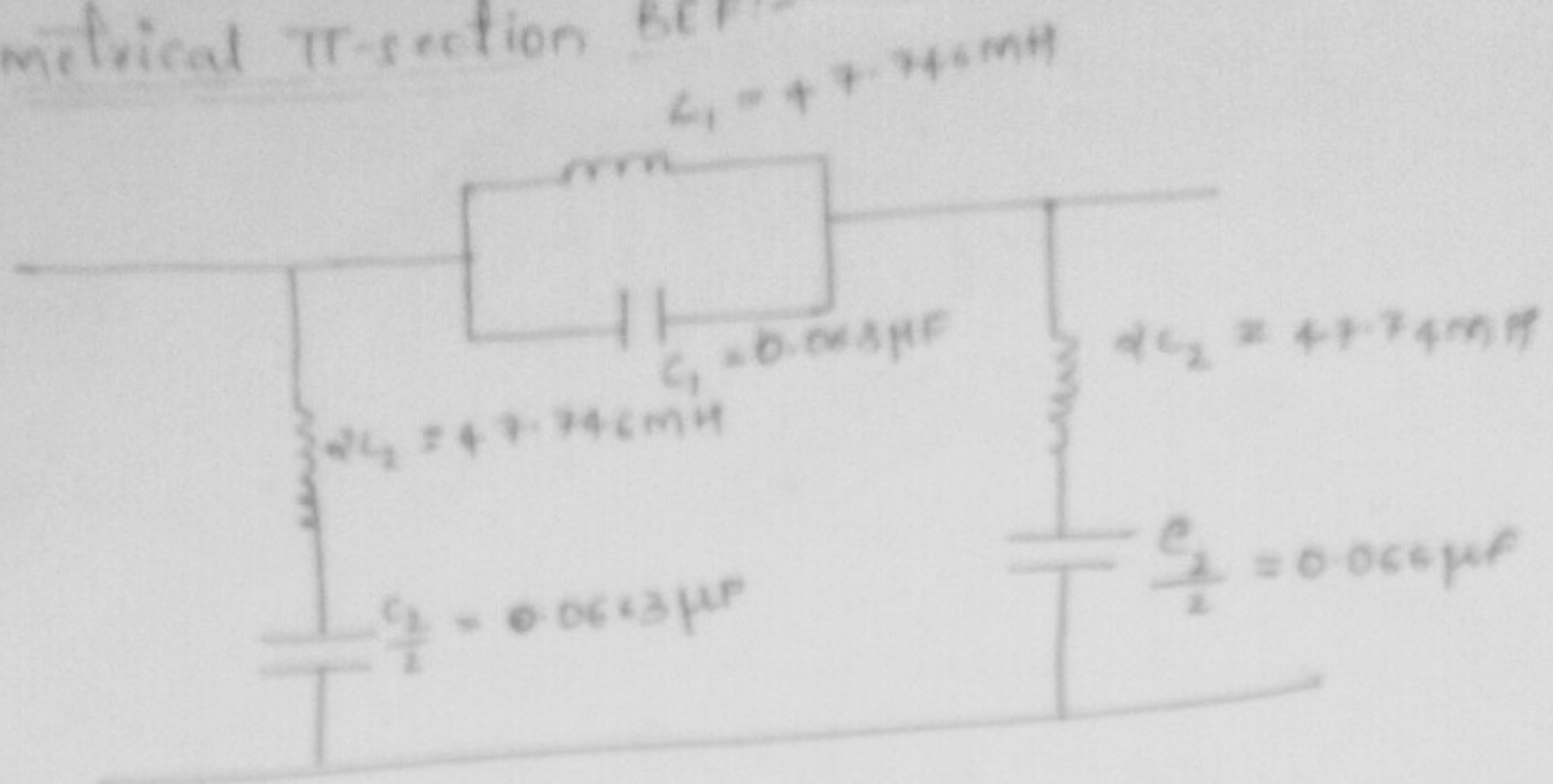

Ques- Design a BEF to eliminate the frequencies between 1kHz and 5kHz for a nominal impedance of 400 Ω .

Ques- Design a m-derived LPP whose cut-off frequency is 20kHz to attain infinite attenuation at a frequency of 24kHz for a nominal impedance of 400 Ω .
Given data, It is a m-derived low pass filter

Ques- cut-off frequency $f_c = 20\text{kHz}$
 $R = 400\Omega$
 $f_c = f_s = 24\text{kHz}$


$$m = \sqrt{1 - \left(\frac{f_c}{f_s}\right)^2} = \sqrt{1 - \left(\frac{20}{24}\right)^2} = 0.5527$$

For a LPP, we know that,

$$L = \frac{R}{\pi f_c} \quad C = \frac{1}{R\pi f_c}$$

$$L = 6.366\text{mH} \quad C = 0.0397\mu\text{F}$$

m-derived T-section of LPP:-

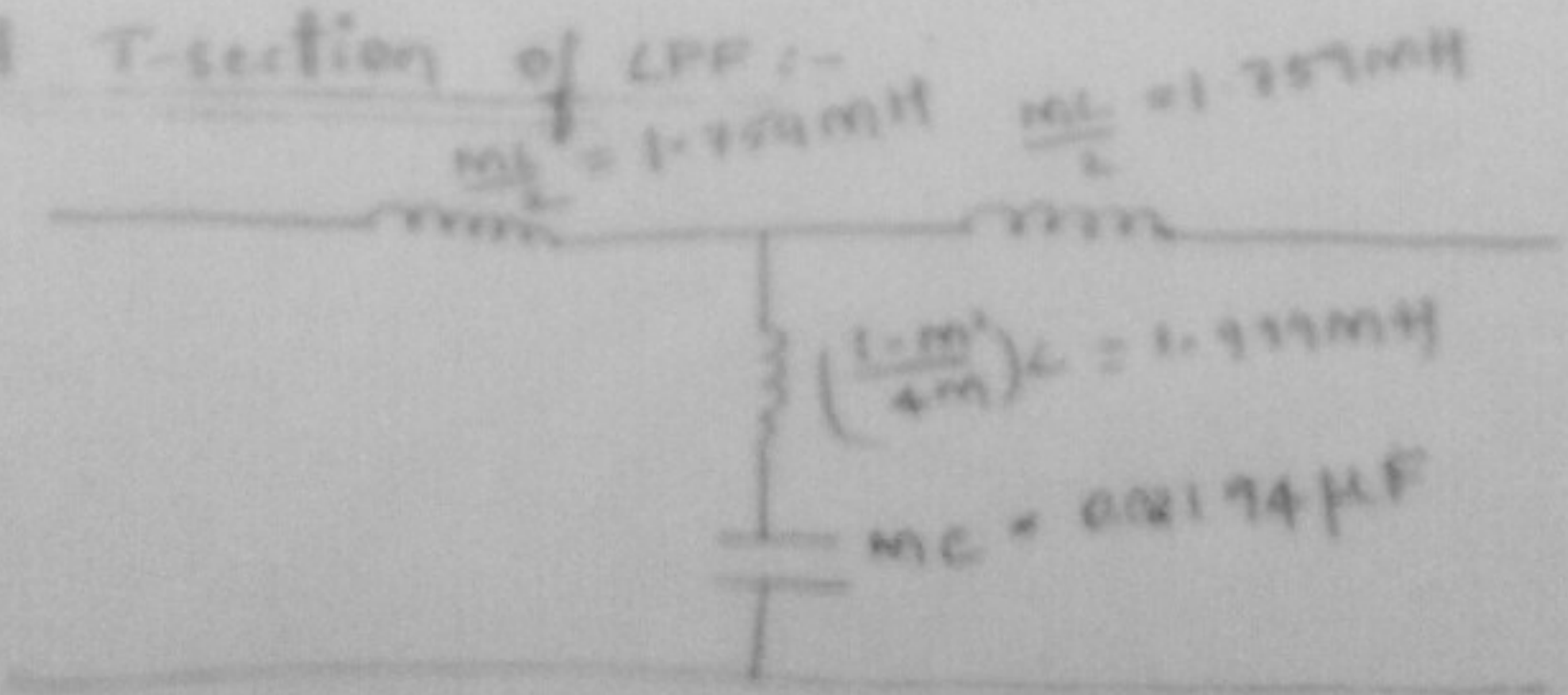

Design a low pass filter (both π and T sections) having a cut-off frequency of 2 kHz to operate with a terminal load resistance of 500Ω . 3(36)

Given data:-

$$f_c = 2\text{ kHz} = 2000\text{ Hz}$$


$$K = 500\Omega$$

we know that

$$K = \sqrt{\frac{L}{C}} = 500\Omega$$

$$L = \frac{K}{\pi f_c} = \frac{500}{\pi \times 2000} = 0.0796\text{ H} \Rightarrow 79.6\text{ mH}$$
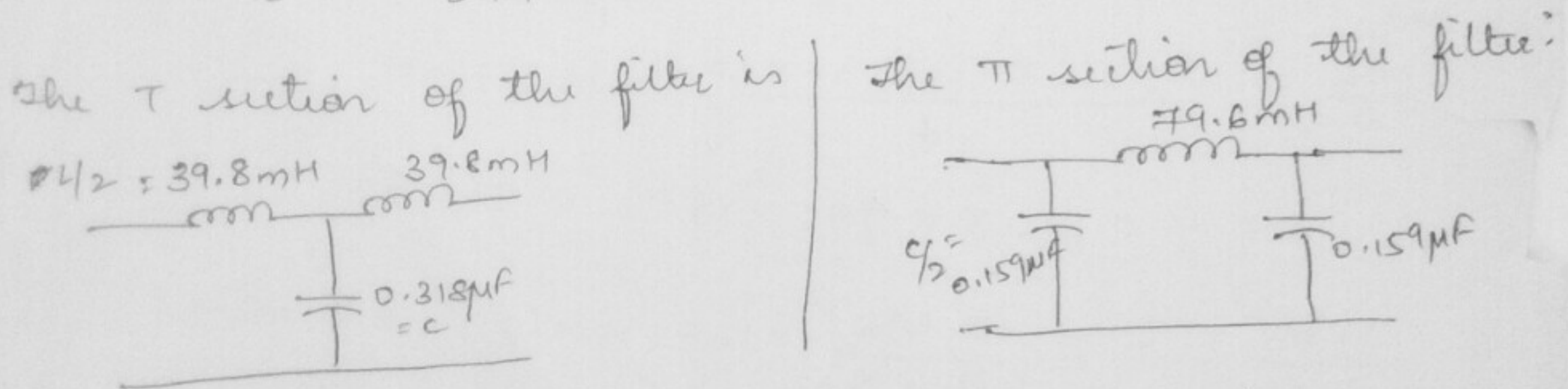
$$C = \frac{1}{\pi f_c K} = \frac{1}{3.14 \times 2000 \times 500} = 3.184 \times 10^{-7} \Rightarrow 0.318\text{ }\mu\text{F}$$



Design a high pass filter having a cut off frequency of 1 kHz with a load resistance of 600Ω .


Given data:-

$$f_c = 1\text{ kHz} = 1000\text{ Hz}$$

$$K = 600\Omega$$

$$L = \frac{K}{4\pi f_c} = \frac{600}{4 \times \pi \times 1000} = 47.74\text{ mH}$$
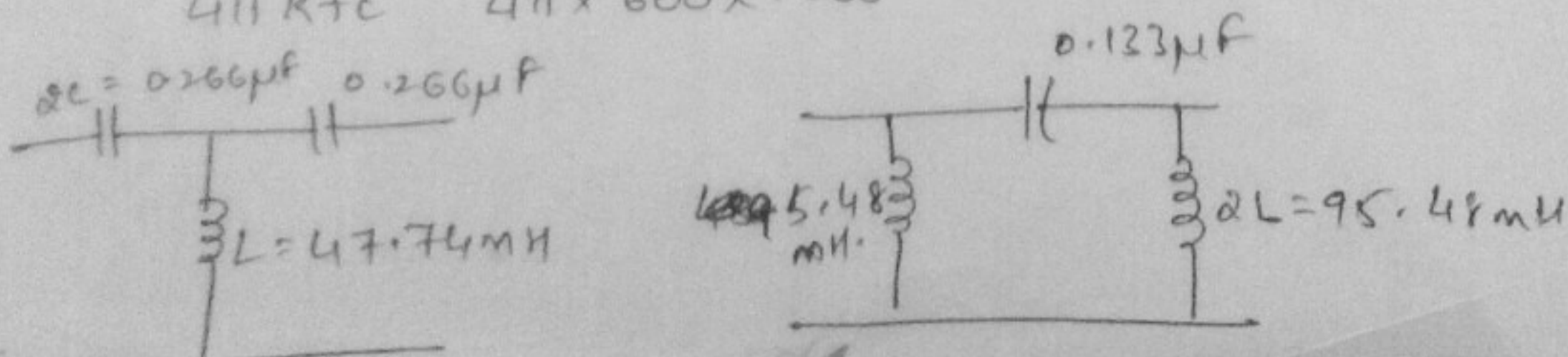
$$C = \frac{1}{4\pi K f_c} = \frac{1}{4\pi \times 600 \times 1000} = 0.133\text{ }\mu\text{F}$$



3) Design a m -derived low pass filter having cut-off f_c of 1 kHz , design the impedance of 400Ω and the resonant freq of 1100 Hz .

Sol $K = 400\Omega$, $f_c = 1\text{ kHz}$, $f_{\infty} = 1100\text{ Hz}$.

$$m = \sqrt{1 - \left(\frac{f_c}{f_{\infty}}\right)^2} = \sqrt{1 - \left(\frac{1000}{1100}\right)^2} = 0.416$$

From ^{const.} k type filter the values of L and C are

$$L = \frac{K}{\pi f_c} = \frac{400}{\pi \times 1000} = 127.32\text{ mH}$$

$$C = \frac{1}{K\pi f_c} = \frac{1}{\pi \times 400 \times 1000} = 0.795\text{ }\mu\text{F}$$

The modified values of L and C for m -derived filter are

$$\frac{mL}{2} = \frac{0.416 \times 127.32 \times 10^{-3}}{2} = 26.48\text{ mH}$$

$$mC = 0.416 \times 0.795 \times 10^{-6} = 0.33\text{ }\mu\text{F}$$

$$\frac{1-m^2}{4m} L = \frac{1 - (0.416)^2}{4(0.416)} \times 127.32 \times 10^{-3} = 63.27\text{ mH}$$

π section elements:-

$$\frac{mC}{2} = \frac{0.416 \times 0.795 \times 10^{-6}}{2} = 0.165\text{ }\mu\text{F}$$

$$\frac{(1-m^2)}{4m} \times C = \frac{1 - (0.416)^2}{4 \times 0.416} \times 0.795 \times 10^{-6} = 0.395\text{ }\mu\text{F}$$

$$mL = 0.416 \times 127.32 \times 10^{-3} = 52.965\text{ mH}$$

m -derived low pass filter are

