

11-12-15

Unit:1 Transient Analysis

(First & Second order circuits)

The transient behaviour is observed in an electrical circuit which has energy storing elements L and C .

Transient state:-

The state where circuit response changes from one steady state to other steady state due to sudden changes in input is called transient state.

Transient time:-

The time taken by the circuit to change from one state to another state is called transient time.

Transient behaviour will be observed under

1) When the circuit contains energy storage elements like inductors, capacitors.

2) When the input of the circuit changes suddenly total response of the circuit.

3) When an input is suddenly applied to a network, the response will undergo transient

nature before it settles to the final value. Hence the total response of the circuit can be categorised into 2 parts:-


(i) Transient (natural) response

(ii) Steady state (forced) response

The transient response will be available for short duration where it dies out when time increases ($t \approx \infty$).

* Total response = Transient response + steady state response
 ↓
 complementary fn

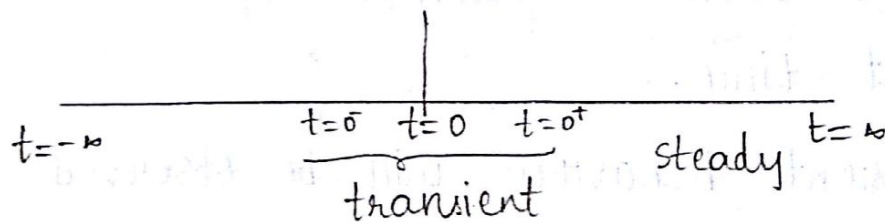Representation of steady state & transient state on time scale:-



Behaviour of inductor & capacitor in steady state and transient state:-



Inductor

1) It stores energy in the form of ^{magnetic} electric field.

Units: Henry

2) voltage across the inductor,

$$V_L = L \cdot \frac{di}{dt}$$

3) Current in an inductor,

$$I = \frac{1}{L} \int v dt$$

4) Under steady state

condition, when $t \rightarrow \infty \rightarrow V=0$, inductor acts as short ckt.

5) Under transient state

(i.e. $t=0^-$, $t=0$, $t=0^+$), $I=0$ it acts as open ckt.

6) Initially charged inductor acts as current source.

Capacitor

1) It stores energy in the form of ^{electric} magnetic field.

Units: Farads

2) Voltage across capacitor,

$$V_C = \frac{1}{C} \int i dt$$

3) Current in capacitor,

$$I = C \frac{dv}{dt}$$

4) Under steady state


condition, when $t \rightarrow \infty \rightarrow I=0$, capacitor acts as open ckt.

5) Under transient state

(i.e. $t=0^-$, $t=0$, $t=0^+$), $V=0$ it acts as short ckt.

6) Initially charged capacitor acts as voltage source.

DC response of series R-L ckt:-

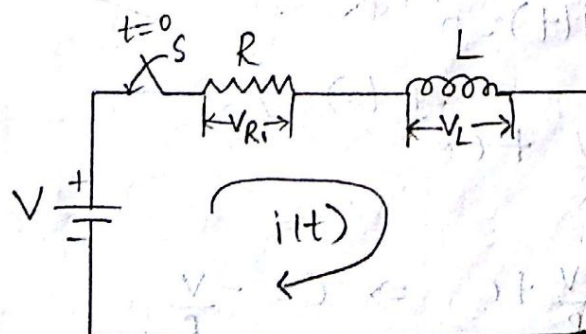

Apply KVL to the circuit,

$$V = V_R + V_L$$

$$V = i(t)R + L \frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} + \frac{R}{L} i(t) = \frac{V}{L}$$

It is in the form of $\frac{dx}{dt} + px = k$

$$x = i(t), \quad p = \frac{R}{L}, \quad k = \frac{V}{L}$$

Sol. is
$$x(t) = e^{-pt} \int k e^{pt} dt + C e^{-pt}$$

$$i(t) = e^{-\frac{R}{L}t} \int \frac{V}{L} e^{+\frac{R}{L}t} dt + C e^{-\frac{R}{L}t}$$

$$i(t) = e^{-\frac{R}{L}t} \cdot \frac{V}{L} \left[\frac{e^{+\frac{R}{L}t}}{+R/L} \right] + C e^{-\frac{R}{L}t}$$

$$i(t) = +e^{-\frac{R}{L}t} \cdot \frac{V}{R} \left[e^{+\frac{R}{L}t} \right] + C e^{-\frac{R}{L}t}$$

$$i(t) = \frac{V}{R} + C e^{-\frac{R}{L}t} \quad \text{--- (1)}$$

Applying initial conditions,

$$t=0, \quad i(t)=0$$

$$0 = \frac{V}{R} + C e^{-\frac{R}{L}(0)}$$

$$0 = \frac{V}{R} + C \Rightarrow C = -\frac{V}{R}$$

$$\therefore \textcircled{1} \Rightarrow i(t) = \frac{V}{R} - \frac{V}{R} e^{-\frac{R}{L}t}$$

$$i(t) = \frac{V}{R} [1 - e^{-\frac{R}{L}t}]$$

$$\boxed{i(t) = \frac{V}{R} [1 - e^{-t/\tau}]}$$

[where $\tau = \frac{L}{R}$]
(time constant)

WKT voltage across resistor V_R ,

$$V_R = i(t) \cdot R$$

$$V_R = V [1 - e^{-t/\tau}]$$

& voltage across inductor V_L ,


$$V_L = L \frac{di(t)}{dt}$$

$$= L \frac{d}{dt} \left[\frac{V}{R} (1 - e^{-t/\tau}) \right]$$

$$= L \cdot \frac{V}{R} \left(-\frac{1}{\tau} e^{-t/\tau} \right)$$

$$= \cancel{L} \cdot \frac{V}{\cancel{R}} \cdot \frac{1}{\cancel{\tau}} e^{-t/\tau} \quad \left(\because \tau = \frac{L}{R} \right)$$

$$V_L = V e^{-t/\tau}$$

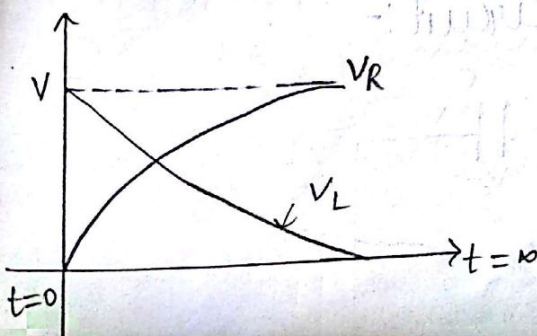

$$\text{Power } P = VI = I^2 R = \frac{V^2}{R}$$

$$P_R = \frac{V_R^2}{R} = \frac{V^2 (1 - e^{-t/\tau})^2}{R}$$


$$P_R = \frac{V^2}{R} (1 + e^{-2t/\tau} - 2e^{-t/\tau})$$

$$P_L = V_L \cdot i(t)$$


$$= V e^{-t/\tau} \cdot \frac{V}{R} (1 - e^{-t/\tau})$$

$$P_L = \frac{V^2}{R} e^{-t/\tau} (1 - e^{-t/\tau})$$
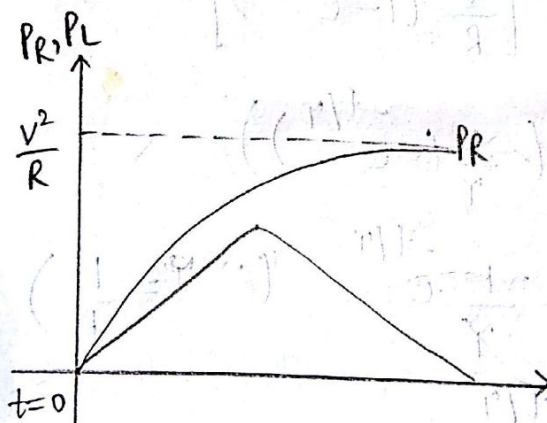
$$P_L = \frac{V^2}{R} (e^{-t/\tau} - e^{-2t/\tau})$$



DC response of series RC circuit:-

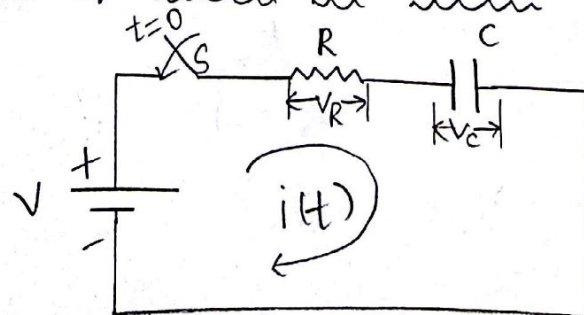

Applying KVL to the ckt,

$$V = V_R + V_C$$

$$V = i(t)R + \frac{1}{C} \int i(t) dt$$

$$0 = R \frac{di(t)}{dt} + \frac{1}{C} i(t) \quad (\because \frac{dv}{dt} = 0)$$

$$\frac{di(t)}{dt} + \frac{1}{RC} i(t) = 0$$

It is in the form of $\frac{dx}{dt} + px = k$

$$x = i(t), \quad p = \frac{1}{RC}, \quad k = 0$$

$$\text{Sol. is } x(t) = e^{-pt} \int k e^{pt} dt + C e^{-pt}$$

$$i(t) = e^{-t/RC} \int 0 \cdot e^{t/RC} dt + C e^{-t/RC}$$

$$i(t) = C e^{-t/RC}$$

$$\boxed{i(t) = C e^{-t/\tau}} \quad \text{--- (1) } (\because \tau = RC) \text{ time constant}$$


Apply initial conditions,

$t=0$, capacitor acts as short ckt

$$V = i(t) \cdot R$$

$$i(t) = \frac{V}{R}$$
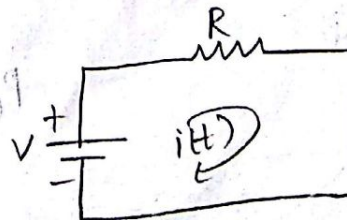
$$\frac{V}{R} = C e^{0/\tau} \Rightarrow C = \frac{V}{R}$$




Sub $C = \frac{V}{R}$ in $i(t)$, we have

$$i(t) = \frac{V}{R} e^{-t/\tau}$$

We know $V_R = i(t)R$; $V_C = V - V_R$ ($V = V_R + V_C$)

$$V_R = V e^{-t/\tau}$$

$$V_C = V(1 - e^{-t/\tau})$$

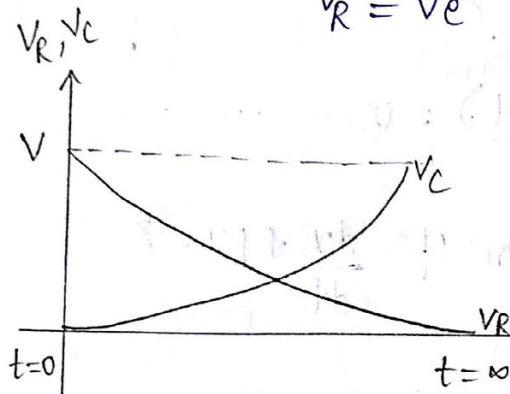

Power $P = VI = \frac{V^2}{R}$


$$P_R = \frac{V_R^2}{R} = \frac{(V e^{-t/\tau})^2}{R}$$

$$P_R = \frac{V^2}{R} e^{-2t/\tau}$$


$$P_C = \frac{V_C^2}{R} = \frac{V^2 (1 - e^{-t/\tau})^2}{R}$$

$$P_C = V_C i(t) = V(1 - e^{-t/\tau}) \cdot \frac{V}{R} e^{-t/\tau}$$
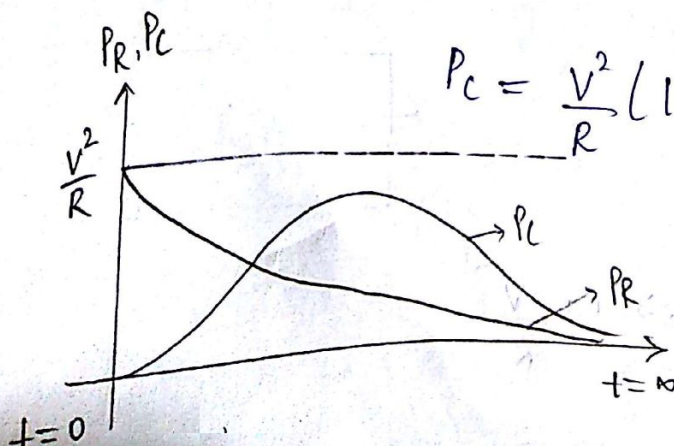
$$P_C = \frac{V^2}{R} (1 - e^{-t/\tau}) e^{-t/\tau}$$



DC response of series RLC ckt:-

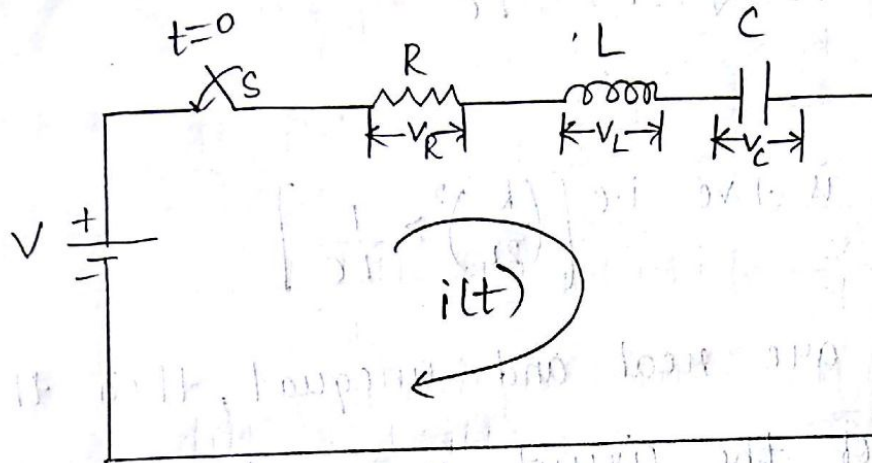

Apply KVL to the ckt,

$$V = V_R + V_L + V_C$$

$$V = i(t)R + L \frac{di(t)}{dt} + \frac{1}{C} \int i(t) dt$$

$$0 = R \frac{di(t)}{dt} + L \frac{d^2 i(t)}{dt^2} + \frac{1}{C} i(t)$$

$$L \frac{d^2 i(t)}{dt^2} + \frac{1}{C} i(t) + R \frac{di(t)}{dt} = 0$$

$$\frac{d^2 i(t)}{dt^2} + \frac{R}{L} \frac{di(t)}{dt} + \frac{1}{LC} i(t) = 0$$

It is in the form of second order diff. equ.

$$\text{i.e. } \left(D^2 + \frac{R}{L} D + \frac{1}{LC} \right) i(t) = 0$$

$$k_1, k_2 = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4\left(\frac{1}{LC}\right)}}{2}$$

$$\Rightarrow \underbrace{-\frac{R}{2L}}_{K_1} \pm \underbrace{\sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}}_{K_2}$$


Case:1) K_2 is +ve i.e. $\left[\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}\right]$

Roots are real and unequal, then the response of the circuit is overdamped.

Sol. of this equation is

$$x(t) = C_1 e^{(K_1+K_2)t} + C_2 e^{(K_1-K_2)t}$$
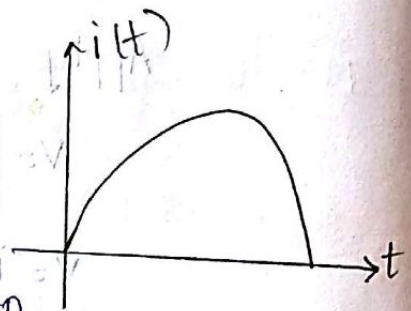
$$\text{i.e. } [D - (K_1+K_2)][D - (K_1-K_2)]i(t) = 0$$




Case:2) K_2 is -ve i.e. $\left[\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}\right]$

Roots are imaginary, response of ckt is underdamped

The roots are $[D - (K_1 + jK_2)][D - (K_1 - jK_2)]i(t) = 0$

Solution for above equ is
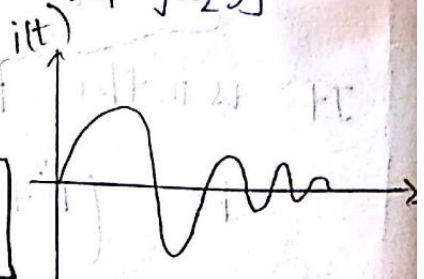
$$x(t) = e^{-K_1 t} (C_1 \cos K_2 t + C_2 \sin K_2 t)$$



Case:3) $K_2 = 0$ i.e. $\left[\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}\right]$


Roots are real and equal, then the response

of the ckt is critically damped

The roots are $D - k_1^2 = 0$


Solution of above eqn is

$$x(t) = e^{k_1 t} (C_1 + C_2 t)$$

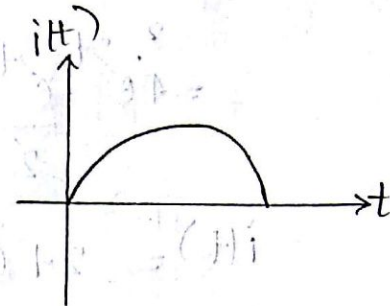

P1.) A series R-L ckt with $R = 30\Omega$, $L = 15H$ has a constant voltage $V = 60V$ applied at $t = 0$. Determine the current I , the voltage across resistor & voltage across inductor.

Sol

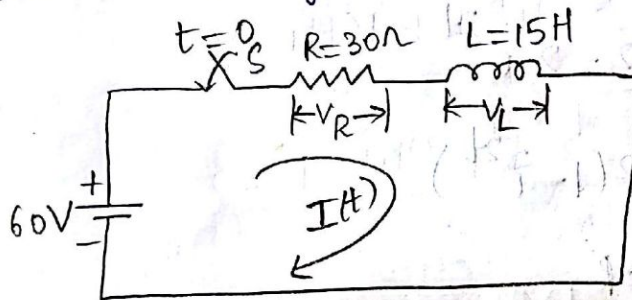

Apply KVL to ckt,

$$V = V_R + V_L$$

$$60 = V_R + V_L$$

$$60 = i(t)R + L \frac{di(t)}{dt}$$

$$60 = i(t)30 + 15 \frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} + 2i(t) = 4 \rightarrow \frac{dx}{dt} + px = k$$

$$x = i(t), \quad p = 2, \quad k = 4$$

$$i(t) = e^{-2t} \int 4e^{2t} dt + Ce^{-2t}$$

$$= Ae^{-2t} \frac{e^{2t}}{2} + Ce^{-2t}$$

$$i(t) = \frac{2}{2} + Ce^{-2t}$$

Apply initial conditions,

$$t=0, i(t)=0$$

$$0 = 2 + C$$

$$C = -2$$

$$\therefore i(t) = 2 - 2e^{-2t}$$

$$i(t) = 2(1 - e^{-2t})$$

$$\text{Now, } V_R = i(t) \cdot R$$

$$V_R = 2(1 - e^{-2t}) \cdot 30$$

$$V_R = 60(1 - e^{-2t})$$


$$V_L = L \frac{di(t)}{dt}$$

$$V_L = 15(-2(-2e^{-2t}))$$

$$V_L = 60e^{-2t}$$

2) A series RC ckt consists of resistor of 10Ω , capacitance of $0.1F$. A constant voltage of $20V$ is applied to ckt at $t=0$. Obtain the current eqn & determine the voltages across resistor & capacitor.

Sol

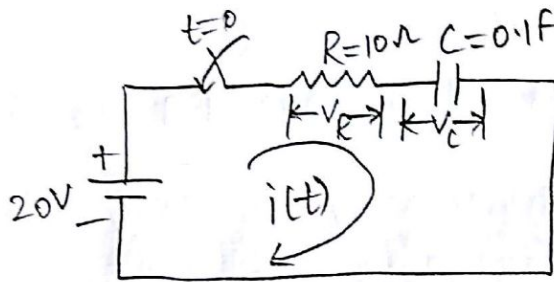

Apply KVL,

$$V = V_R + V_C$$

$$20 = i(t)10 + \frac{1}{0.1} \int i(t) dt$$

$$0 = 10 \frac{di(t)}{dt} + \frac{1}{0.1} i(t)$$

$$\frac{di(t)}{dt} + i(t) = 0$$

$$x = i(t), \quad p = 1, \quad k = 0$$


$$i(t) = e^{-t} \int 0 \cdot e^t dt + C e^{-t}$$

$$i(t) = C e^{-t}$$

Apply initial conditions,

$$V = i(t) \cdot R$$

$$i(t) = \frac{V}{R}$$

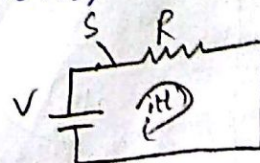

$$\frac{V}{R} = Ce^0$$

$$C = \frac{V}{R} = \frac{20}{10} = 2$$

$$\therefore i(t) = \frac{V}{R} e^{-t}$$

$$V_R = i(t) \cdot R$$

$$= V e^{-t}$$

$$V_R = 20e^{-t}$$

$$\& \quad V_C = \frac{1}{C} \int i(t) dt$$

$$V = V_R + V_C$$

$$V_C = V - V_R$$

$$= \frac{1}{0.1} \int \frac{V}{R} e^{-t} dt$$

$$= 20 - 20e^{-t}$$


$$= \frac{20}{0.1 \times 10} \frac{e^{-t}}{-1}$$

$$V_C = 20(1 - e^{-t})$$

$$V_C = -20e^{-t}$$

3) The ckt shown in fig consists of resistance inductance & capacitance in series with 100V constant source when the switch is closed at $t=0$. Find current transient.

Sol

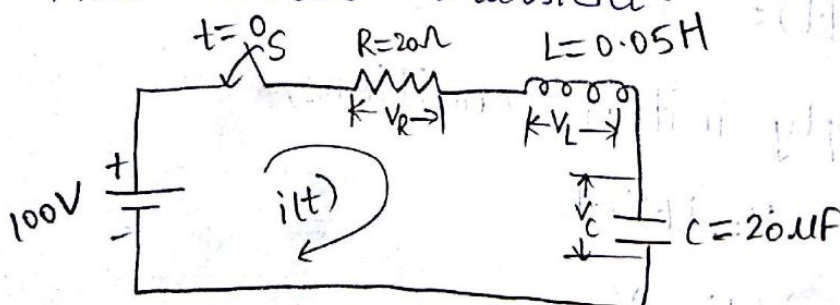

Apply KVL,

$$V = V_R + V_L + V_C$$

$$100 = i(t) \cdot 20 + 0.05 \frac{di(t)}{dt} + \frac{1}{20 \times 10^{-6}} \int i(t) dt$$

$$0 = 20 \frac{di(t)}{dt} + 0.05 \frac{d^2 i(t)}{dt^2} + \frac{1}{2 \times 10^{-5}} i(t)$$

$$\frac{d^2 i(t)}{dt^2} + \frac{10^6}{10^6} i(t) + 400 \frac{di(t)}{dt} = 0$$

$$(D^2 + 400D + 10^6) i(t) = 0$$

$$k_1, k_2 = \frac{-400 \pm \sqrt{(400)^2 - 4 \times 10^6}}{2} = \underbrace{-200}_{k_1} \pm \underbrace{j979.79}_{k_2}$$

$$= -\frac{20}{0.1} \pm \sqrt{\left(\frac{20}{0.1}\right)^2 - \frac{1}{10^{-6}}}$$

$$= \underbrace{-\frac{20}{0.1}}_{k_1} \pm \underbrace{\sqrt{\left(\frac{20}{0.1}\right)^2 - 10^6}}_{k_2}$$

$$\text{Here } \left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$$

$\therefore$ Roots are imaginary

$$\cancel{[D - (-200 + j96 \times 10^4)] [D - (-200 - j96 \times 10^4)] i(t) = 0}$$

$$x(t) = e^{-k_1 t} [C_1 \cos k_2 t + C_2 \sin k_2 t]$$

$$i(t) = e^{200t} [C_1 \cos 979.79t + C_2 \sin 979.79t] \quad \text{--- (1)}$$

Applying initial conditions, $i(t)=0$

$$t=0, V_L = L \frac{di(t)}{dt}$$

$$V_L = 100 \text{ since } V_L = V + V_R \\ = 100 + i(t)R \\ = 100 + 0 \\ V_L = 100$$

$$100 = 0.05 \frac{di(t)}{dt} \Rightarrow \frac{di(t)}{dt} = 2000$$

Sub $t=0$ & $i(t)=0$ in ①

$$C_1 = 0$$

$$\therefore i(t) = e^{200t} [C_2 \sin 979.79t]$$

$$V_L = L \frac{di(t)}{dt}$$

$$V_L = 0.05 \cdot \frac{d}{dt} [e^{200t} (C_2 \sin 979.79t)]$$

$$= 0.05 [200e^{200t} (C_2 \sin 979.79t) + e^{200t} (C_2 \cos 979.79t) \times 979.79]$$

$$V_L = 0.05 [200e^{200t} (C_2 \sin 979.79t) + 979.79e^{200t} (C_2 \cos 979.79t)]$$

V_L at $t=0$


$$V_L = 0 + 48.9895 (C_2)$$

$$\frac{100}{48.9895} = C_2$$

$$C_2 = 2.04$$

$$\therefore i(t) = e^{200t} [2.04 \sin 979.79t]$$

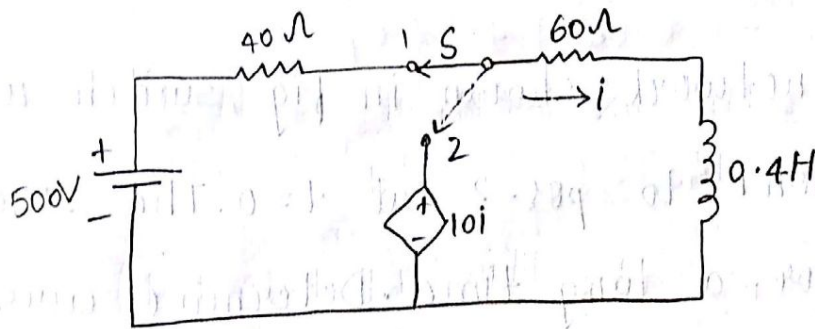4) For the ckt shown in fig, find current eqn when switch is changed from position 1 to pos 2 at $t=0$. The switch is at pos-1 for a long time.



Sol

Apply KVL when switch is at pos-2.

$$10i = 60i + 0.4 \frac{di(t)}{dt}$$

$$\frac{di(t)}{dt} + \frac{50i}{0.4} = 0$$

$$\frac{di(t)}{dt} + 125i = 0$$

$$x = i(t), p = 125, k = 0$$

Sol. is $i(t) = e^{-125t} \int 0 \cdot e^{125t} dt + C e^{-125t}$

$$i(t) = C e^{-125t}$$

inductor doesn't allow sudden changes in the current

$$500 = i(40 + 60)$$

$$i(t) = \frac{500}{100} = 5A$$


$$\text{at } t=0, i(t)=5$$

$$5 = Ce^0$$

$$C = 5$$

$$\therefore i(t) = 5e^{-125t}$$

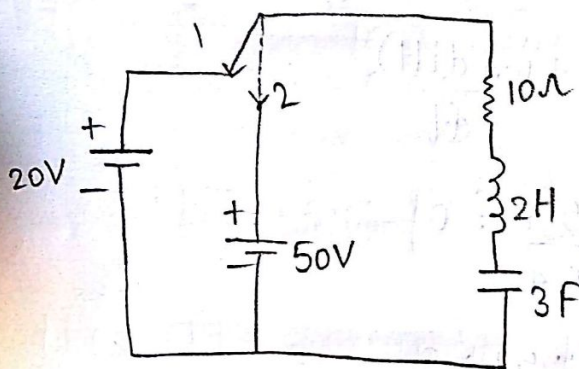5) In the network shown in fig, switch is moved from position 1 to pos-2 at $t=0$. The switch is in pos-1 for a long time. Determine current expression $i(t)$



Sol

Apply KVL when switch is at pos-2,

$$50 = i(t) \cdot 10 + 2 \frac{di(t)}{dt} + \frac{1}{3} \int i(t) dt$$

$$0 = 10 \frac{di(t)}{dt} + 2 \frac{d^2 i(t)}{dt^2} + \frac{i(t)}{3}$$

$$\frac{d^2 i(t)}{dt^2} + 5 \frac{di(t)}{dt} + \frac{i(t)}{6} = 0$$

$$\left(D^2 + 5D + \frac{1}{6} \right) i(t) = 0$$

$$D = \frac{-15 \pm \sqrt{219}}{6}$$

$$= \frac{-5}{2} \pm 2.46$$

$$= \frac{-2.5}{k_1} \pm \frac{2.46}{k_2}$$

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

∴ Roots are real & unequal

$$i(t) = C_1 e^{(-2.5+2.46)t} + C_2 e^{(-2.5-2.46)t} \quad \text{--- ①}$$

Apply initial conditions, $i(t)=0$

$$t=0, \quad V_L = L \frac{di(t)}{dt}$$

$$\frac{50}{20} = 2 \cdot \frac{di(t)}{dt} \Rightarrow \frac{di(t)}{dt} = 1.25$$

Sub $t=0$ & $i(t)=0$ in ①

$$0 = C_1 + C_2$$

$$C_1 = -C_2$$

$$\therefore i(t) = C_1 \left[e^{(-2.5+2.46)t} - e^{(-2.5-2.46)t} \right]$$

$$\frac{di(t)}{dt} = C_1 \left[(-2.5+2.46)e^{(-2.5+2.46)t} - (-2.5-2.46)e^{(-2.5-2.46)t} \right]$$

$$= C_1 \left[-0.04 e^{-0.04t} + 4.96 e^{-4.96t} \right]$$

$$V_L = L \frac{di(t)}{dt}$$

$$50 = 2 C_1 [0.04 e^{-0.04t} + 4.96 e^{-4.96t}]$$

$$\text{at } t=0$$

$$25$$

$$10 = -C_1 0.04 + 4.96 C_1$$

$$25$$

$$10 = 4.92 C_1$$


$$C_1 = \frac{25}{4.92}$$

$$C_1 = 5.08$$

$$\therefore C_2 = -5.08$$

$$\therefore i(t) = 5.08 [e^{-0.04t} - e^{-4.96t}]$$

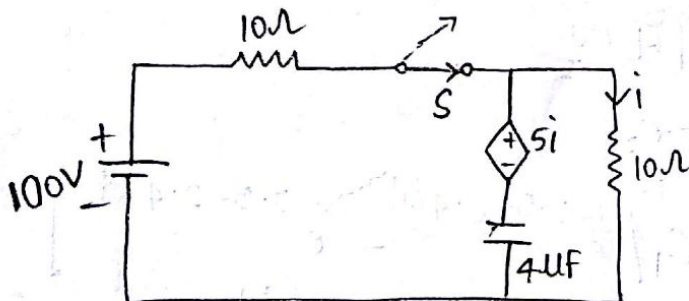6.) For the ckt shown in fig, find current eq when switch is opened at $t=0$



Sol

16-12-15

Laplace transforms:-


LT is a mathematical tool which transfers a function in time domain into a fn in frequency domain. The LT is given by

$$L[f(t)] = \int_{-\infty}^{\infty} f(t)e^{-st} dt$$

Transform impedance elements:-


1) Resistor in t-domain & s-domain:

From ohms law, $v(t) = i(t) \cdot R$

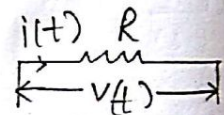

Writing the above eqn in s-domain, we have

$$V(s) = I(s) \cdot R$$

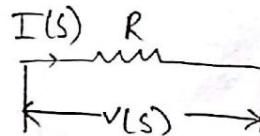

2) Inductor in time domain & freq domain:-

For inductor, $v-i$ char in time domain are



$$V_L = L \frac{di(t)}{dt} ; i(t) = \frac{1}{L} \int v(t) dt + i(0)$$

The corresponding frequency domain relations are given as

$$V(s) = L[sI(s) - I(0)]$$

$$V(s) = LsI(s) - LI(0)$$
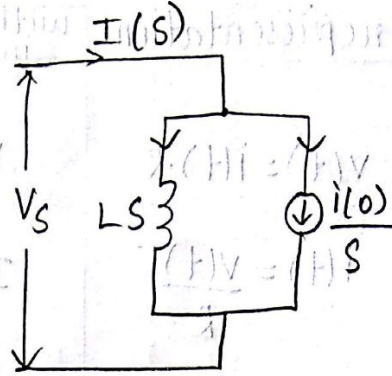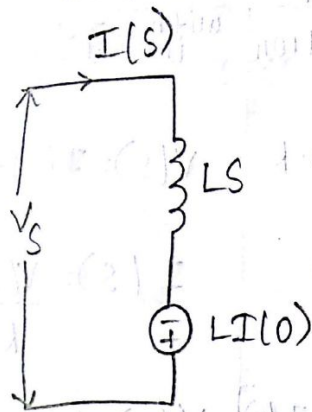
$$I(s) = \frac{1}{Ls} V(s) + \frac{i(0)}{s}$$



3) Capacitor in t-domain & freq domain:-

voltage across capacitor is

$$V_c(t) = \frac{1}{C} \int i(t) dt + V(0)$$



& current is $i(t) = C \frac{dv}{dt}$

The corresponding frequency domain relations are

$$V_c(s) = \frac{1}{Cs} I(s) + \frac{V(0)}{s}$$


$$I(s) = C [s V(s) - V(0)]$$

$$I(s) = Cs V(s) - C V(0)$$

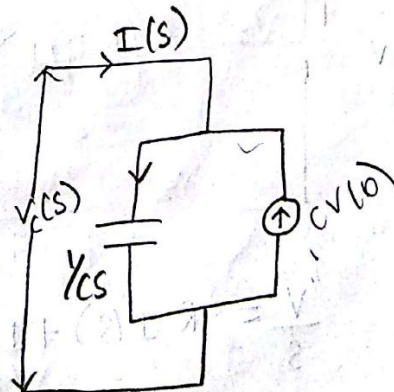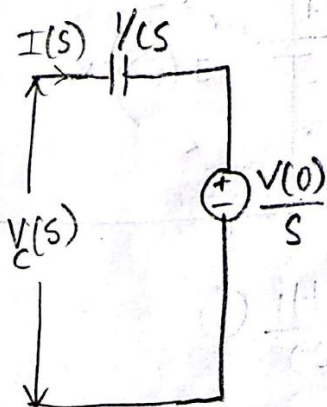

Element	Time domain representation	S-domain representation	
		without zero initial condition	with zero initial condition
Resistor	$v(t) = i(t) \cdot R$ $i(t) = \frac{v(t)}{R}$	$V(s) = I(s) \cdot R$ $I(s) = \frac{V(s)}{R}$	$V(s) = I(s) \cdot R$ $I(s) = \frac{V(s)}{R}$
Inductor	$v_L = L \frac{di(t)}{dt}$ $i(t) = \frac{1}{L} \int v(t) dt + i(0)$	$V_L(s) = L[sI(s) - I(0)]$ $I(s) = \frac{1}{LS} V(s) + \frac{i(0)}{s}$	$V(s) = LS I(s)$ $I(s) = \frac{1}{LS} V(s)$
Capacitor	$V_C = \frac{1}{C} \int i(t) dt + v(0)$ $i(t) = C \frac{dv}{dt}$	$V_C(s) = \frac{1}{Cs} I(s) + \frac{v(0)}{s}$ $I(s) = CsV(s) - Cv(0)$	$V_C(s) = \frac{1}{Cs} I(s)$ $I(s) = CsV(s)$

DC Response of series RL ckt using LT:-

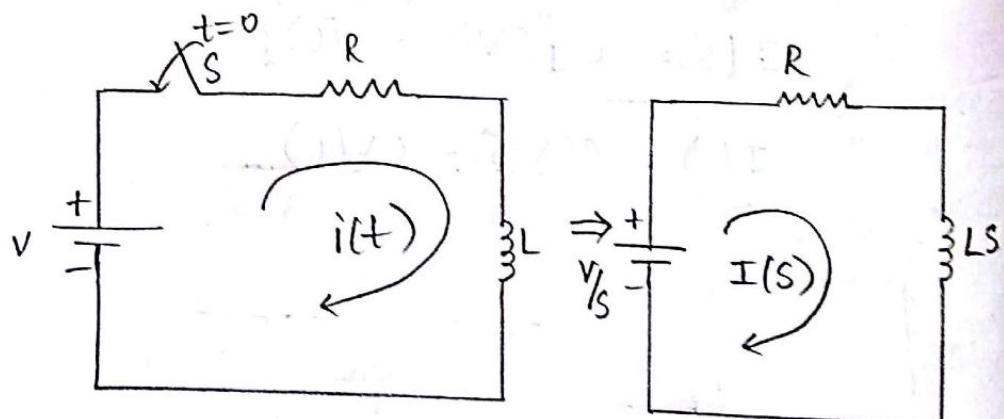

$$\frac{V}{s} = R I(s) + I(s) Ls$$

$$\frac{V}{s} = I(s) (R + Ls)$$

$$I(s) = \frac{V}{s(R+LS)}$$

$$I(s) = \frac{V}{LS \left(s + \frac{R}{L} \right)}$$

$$I(s) = \frac{V/L}{s \left(s + \frac{R}{L} \right)}$$

$$\frac{V/L}{s \left(s + \frac{R}{L} \right)} = \frac{A}{s} + \frac{B}{s + \frac{R}{L}}$$

$$\frac{V}{L} = A \left(s + \frac{R}{L} \right) + B s$$

$$s\text{-coeff} \Rightarrow 0 = A + B$$

$$A = -B$$

$$\text{const} \Rightarrow$$

$$\frac{V}{L} = \frac{A R}{L}$$

$$A = \frac{V}{R} \Rightarrow B = -\frac{V}{R}$$

$$I(s) = \frac{V/R}{s} - \frac{V/R}{s + R/L}$$



$$I(s) = \frac{V}{Rs} + \frac{\left(\frac{V}{L} \right) \left(\frac{1}{s + \frac{R}{L}} \right) A}{R \left(s + \frac{R}{L} \right)}$$

$$i(t) = \frac{V}{R} - \frac{V}{R} e^{-R/L t}$$

$$i(t) = \frac{V}{R} \left[1 - e^{-R/L t} \right] \quad \text{or } \gamma = \frac{L}{R}$$

$$i(t) = \frac{V}{R} \left(1 - e^{-t/\gamma} \right)$$

DC response of series RC ckt using LT:-

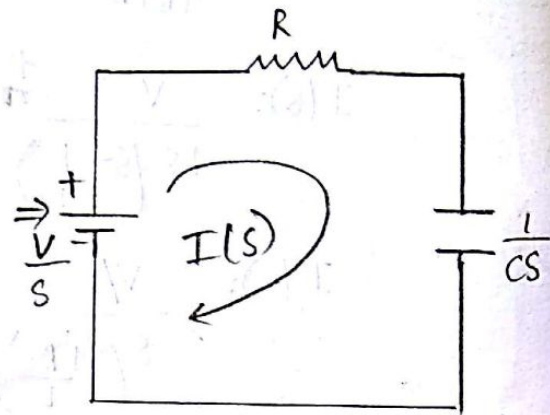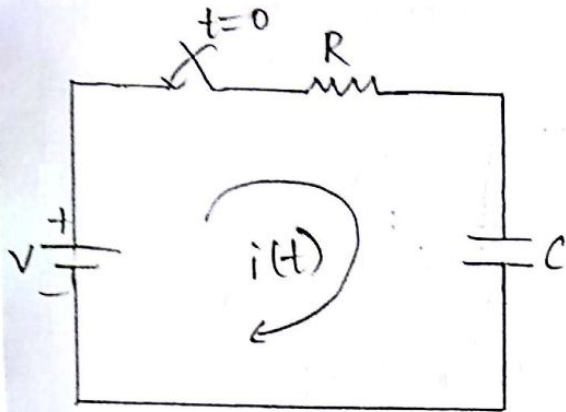

$$\frac{V}{s} = R \cdot I(s) + I(s) \cdot \frac{1}{Cs}$$

$$\frac{V}{s} = I(s) \left(R + \frac{1}{Cs} \right)$$

$$I(s) = \frac{V/s}{R + \frac{1}{Cs}}$$

$$I(s) = \frac{V}{s \left(R + \frac{1}{Cs} \right)} = \frac{V}{sR + \frac{1}{C}} \Rightarrow \frac{V}{R \left(s + \frac{1}{RC} \right)}$$

$$\frac{V}{s \left(R + \frac{1}{Cs} \right)} = \frac{A}{s} + \frac{B}{s + \frac{1}{RC}} \quad \frac{V/R}{s + 1/RC}$$

$$V = A \left(R + \frac{1}{Cs} \right) + BS$$

$$I(s) = \frac{V}{R \left(s + \frac{1}{RC} \right)}$$


$$I(s) = \frac{V/R}{s + \frac{1}{RC}}$$

$$i(t) = \frac{V}{R} e^{-\frac{t}{RC}} \quad \text{or} \quad \tau = RC$$

7-12-15


1) Draw the s-domain ckt for ckt shown in fig.

Assume initial conditions are 0

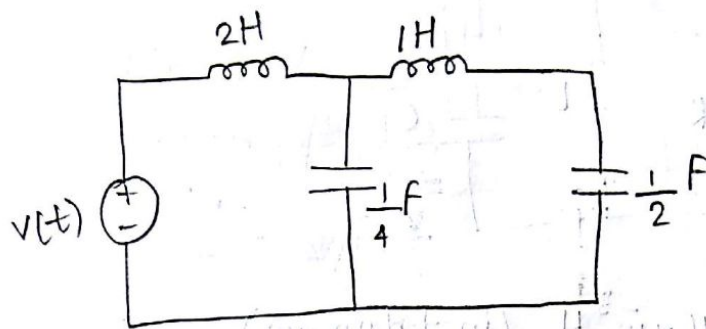


Sol

	Time domain	Freq domain
voltage source	$v(t)$	$v(s)$
Inductor	$L \frac{di(t)}{dt}$	$LS = 2s$
Inductor	$L \frac{di(t)}{dt}$	$LS = 1s$
capacitor	$\frac{1}{C} \int i(t) dt$	$\frac{1}{Cs} = \frac{1}{(\frac{1}{4})s} = \frac{4}{s}$
capacitor	$\frac{1}{C} \int i(t) dt$	$\frac{1}{Cs} = \frac{1}{(\frac{1}{2})s} = \frac{2}{s}$

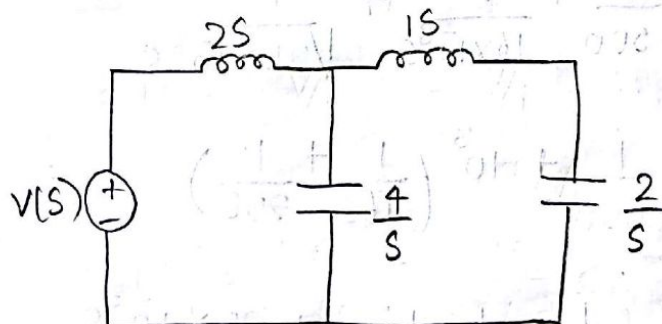

2) A 500Ω resistor, a 16mH inductor and a 25mf capacitor are connected in $||$. Express the admittance of this $||$ combination of the elements as the fn of s .

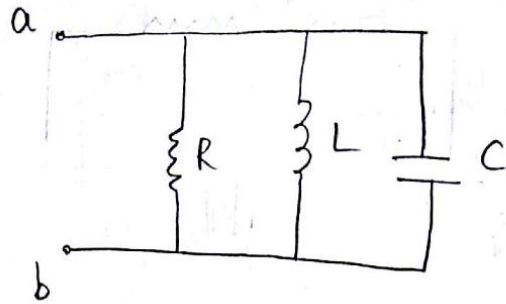Sol $R = 50\Omega$, $L = 16\text{mH}$, $C = 25\text{mF}$



$$L = 16 \times 10^{-3} \text{ H (in t domain)}$$

$$= 16 \times 10^{-3} \text{ S (in freq-domain)}$$

$$C = 25 \times 10^{-3} \text{ F (in t)}$$

$$= \frac{1}{25 \times 10^{-3} \text{ S (in s)}}$$

$$Y(s) = \frac{1}{Z(s)}$$

$$= \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3}$$

$$= \frac{1}{500} + \frac{1}{16 \times 10^{-3} \text{ S}} + \frac{1}{1/25 \times 10^{-3} \text{ S}}$$


$$= \frac{1}{500} + 10^3 \left(\frac{1}{16 \text{ S}} + \frac{1}{25 \text{ S}} \right)$$

$$= \frac{1}{500} + \frac{1}{16 \times 10^{-3} \text{ S}} + 25 \times 10^{-3} \text{ S}$$

$$= 2 \times 10^{-3} + \frac{6 \times 10^5}{\text{S}} + 25 \times 10^{-3} \text{ S}$$


$$= (2 \times 10^{-3} \text{ S} + 6 \times 10^5 + 25 \times 10^{-3} \text{ S}^2) / \text{S}$$

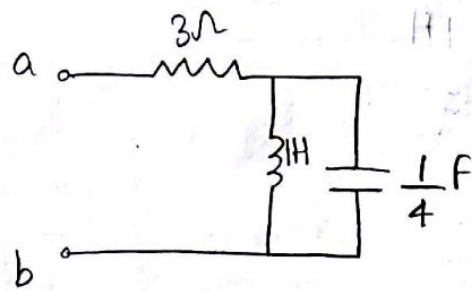3) Transform the ckt shown to the s-domain & determine the laplace impedance.



Sol

s-domain $\Rightarrow$

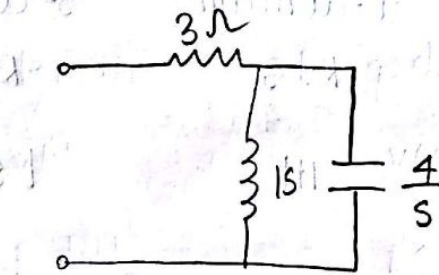


$$1/s \parallel \frac{4}{s} = \frac{4}{1s + \frac{4}{s}} = \frac{4s}{s^2 + 4}$$

3 ohm series with $\frac{4s}{s^2 + 4}$


$$= 3 + \frac{4s}{s^2 + 4}$$

$$= \frac{4s + 3s^2 + 12}{s^2 + 4}$$

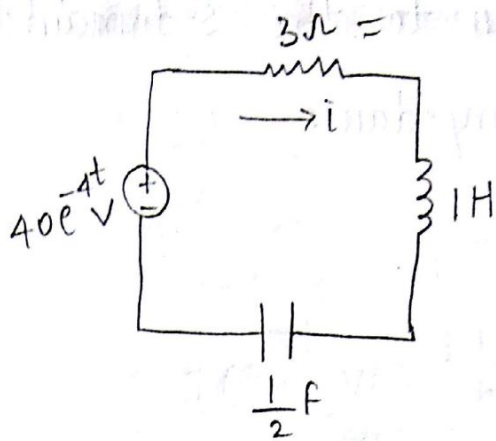4) Determine the current i if the ckt is driven by a voltage source as shown in fig. The initial value of the voltage across the capacitor & the initial current through the inductor are ^{both} zero.



	t-domain	s-domain
Resistor	$R=3$	$R=3$
Inductor	$1H$	$Ls - \underline{Li(0)} = 1s$
Capacitor	$\frac{1}{2}F$	$\frac{1}{Cs} + \frac{v(0)}{\underline{\frac{s}{0}}} = \frac{2}{s}$
voltage source	$40e^{-4t}$	$\frac{40}{s+4}$

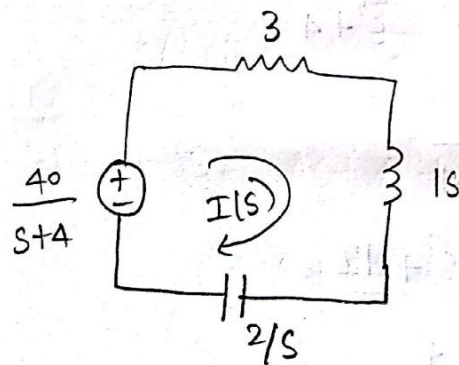

$$I(s) = \frac{V(s)}{Z(s)}$$

$$Z(s) = 3 + 1s + \frac{2}{s}$$

$$Z(s) = \frac{s^2 + 3s + 2}{s}$$

$$\therefore I(s) = \frac{40s}{(s+4)(s^2 + 3s + 2)}$$

$$40s = A(s^2 + 3s + 2) + \dots$$

$$I(s) = \frac{40s}{(s+4)(s+1)(s+2)}$$

$$\frac{40s}{(s+4)(s+1)(s+2)} = \frac{A}{s+4} + \frac{B}{s+1} + \frac{C}{s+2}$$

$$40s = A(s+1)(s+2) + B(s+4)(s+2) + C(s+4)(s+1)$$

$$s^2 \text{ coeff} \Rightarrow 0 = A + B + C$$

$$s \text{ coeff} \Rightarrow 40 = 3A + 6B + 5C$$

$$\text{const} \Rightarrow 0 = 2A + 8B + 4C$$

$$A = -\frac{80}{3}, B = -\frac{40}{3}, C = 40$$


$$I(s) = \frac{-80}{3(s+4)} - \frac{40}{3(s+1)} + \frac{40}{s+2}$$

$\rightarrow$ ILT

$$i(t) = -\frac{80}{3}e^{-4t} - \frac{40}{3}e^{-t} + 40e^{-2t}$$

5) Determine the current i for $t \geq 0$ if initial current $i(0) = 1$ for the ckt shown in fig.

Sol

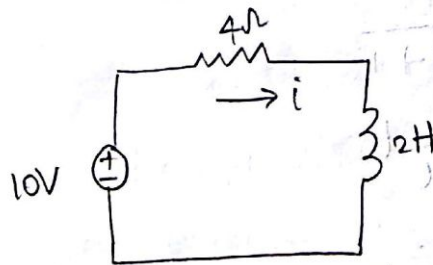

t -domain

s -domain


resistor

4

inductor

2

$$\frac{4}{2s-2} = 2(s-1)$$

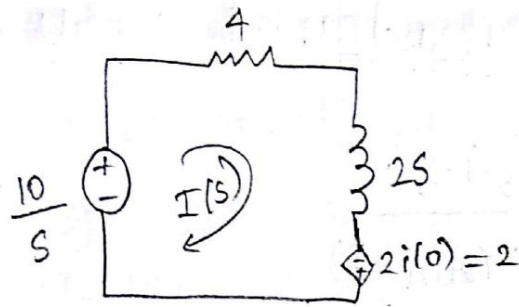

$$I(s) = \frac{V(s)}{Z(s)}$$

$$= \frac{10/s}{4+2s-2}$$

$$= \frac{10}{s(2+2s)}$$

$$I(s) = \frac{10}{2s^2+2s}$$

$$\frac{10}{s} = 4I(s) + 2sI(s) + 2$$

$$\frac{10}{s} + 2 = (4+2s)I(s)$$

$$I(s) = \frac{\frac{10}{s} + 2}{4+2s}$$

$$= \frac{10+2s}{2s^2+4s}$$

$$= \frac{10+2s}{2s^2+4s}$$

$$= \frac{5}{s^2+2s} = \frac{5}{s(s+2)}$$

$$\frac{5}{s(s+2)} = \frac{A}{s} + \frac{B}{s+2} = \frac{5+s}{s^2+2s}$$

$$5 = As + A + Bs$$

$$0 = A + B$$


$$5 = A$$

$$B = -5$$

$$I(s) = \frac{5}{s} - \frac{5}{s+1}$$

$$i(t) = 5 - 5e^{-t}$$

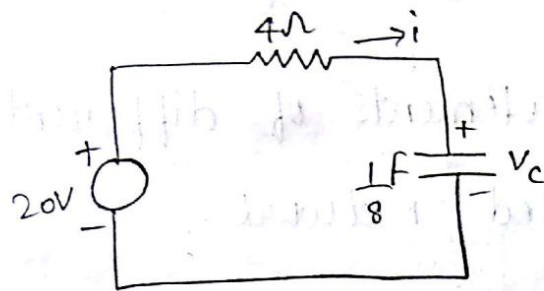6) Determine current i for $t \geq 0$ if $V_C(0) = 4V$ for ckt shown in fig.



Sol

$$R = 4$$

$$C = \frac{8}{s} + \frac{4}{s} ; V = \frac{20}{s}$$

Apply KVL to ckt,

$$\frac{20}{s} = 4I(s) + \left(\frac{8}{s} + \frac{4}{s}\right)I(s) = \frac{8}{s}I(s) + \frac{4}{s}I(s)$$

$$\frac{20}{s} = \left(4 + \frac{12}{s}\right)I(s) \quad \frac{20}{s} - \frac{4}{s} = \left(\frac{4s+12}{s}\right)I(s)$$

$$I(s) = \frac{20/s}{(4s+12)/s} = \frac{5/8}{s+3} \quad I(s) = \frac{16/s}{4s+8}$$

$$\frac{5s}{s+3} \neq \frac{A}{s+3}$$

$$I(s) = \frac{4}{s+2}$$

$$I(s) = \frac{5}{s+3}$$

$$i(t) = 4e^{-2t}$$

Apply ILT,

$$i(t) = 5e^{-3t}$$