

# UNIT - I SINGLE STAGE AMPLIFIERS

1-①

## Classification of Amplifiers:

- A circuit that increases the amplitude of the given input signal is an amplifier.
- A small ac signal fed to the amplifier is obtained as a larger ac signal of the same frequency at the output.
- Amplifiers constitute an essential part of radio, television and other communication circuits.
- In discrete circuits BJT's and FET's are commonly used as amplifying elements. Depending on the nature and level of amplification and impedance matching requirements different types of amplifiers can be considered.
- Amplifiers can be classified as follows,

### ① Based on active devices

- (a) BJT amplifier
- (b) FET amplifier

### ② Based on transistor Configuration

- (a) CE amplifier
- (b) CB "
- (c) CC "
- (d) CS "
- (e) CD "

### ③ Based on type of load impedance

- (a) Untuned amplifier
- (b) Tuned amplifier

### ④ Based on frequency range.

- Audio freq. (AF) :  $40 - 20\text{KHz}$
- Radio freq. (RF) :  $20\text{KHz} - 1\text{MHz}$
- Video freq. (VF) :  $5 - 8\text{ MHz}$
- Very Low freq. (VLF) :  $10 - 30\text{ KHz}$
- Low freq. (LF) :  $30 - 300\text{ KHz}$
- Medium freq. (MF) :  $300 - 3000\text{ KHz}$
- High freq. (HF) :  $3 - 30\text{ MHz}$
- Very High freq. (VHF) :  $30 - 300\text{ MHz}$
- Ultra High freq. (UHF) :  $300 - 3000\text{ MHz}$
- Super High freq. (SHF) :  $3000 - 30,000\text{ MHz}$

- (5) Based on no. of stages
- (a) Single stage amplifiers
  - (b) Multistage amplifiers
- (6) Based on method of Coupling
- (a) Direct Coupled (DC) amplifier
  - (b) Resistance Capacitor (RC) Coupled amplifier
  - (c) Inductor Capacitor (LC) Coupled amplifier
  - (d) Transformer Coupled amplifier
- (7) Based on primary function
- (a) Small Signal amplifiers
  - (b) Large signal amplifiers (Power amplifiers)
- (8) Based on Q - point
- (a) class A amplifier
  - (b) class B "
  - (c) class AB "
  - (d) class C "
- (9) Based on bandwidth
- (a) Narrow band amplifier
  - (b) Wide band amplifier
- Distortion in amplifiers :
- An amplifier should produce an output waveform which does not differ from the input signal waveform in any respect except amplitude i.e. the output is an amplified signal of the input.
- An ideal amplifier will amplify a signal without changing its wave shape at all frequencies. Such an amplifier faithfully amplifies the signal and we say it has a good fidelity. Such an amplifier is called Hi-Fi (High Fidelity) amplifier.

- In practice, it is highly impossible to construct an ideal amplifier whose output waveform is an exact replica of the input signal waveform because of the nonlinearity of the characteristics of an active device.
- The output differs from the input either in its waveform or frequency content. The difference between the output waveform and the input waveform in an amplifier is called distortion.
- Distortions are classified into three types. These may exist separately or simultaneously in amplifiers, they are




- ① Amplitude (Non-Linear) / Harmonic distortion
- ② Frequency distortion
- ③ Phase distortion

### Harmonic distortion:

- Harmonic distortion occurs when the device is operated in non-linear part of the dynamic transfer characteristics. Since the output frequencies are produced in the output which are not present in the input signal. This harmonic distortion is also called as amplitude distortion.
- The component of frequency at the output same as the input signal is called the fundamental frequency.
- The frequency components which are integral multiples of fundamental frequency are called harmonics.
- Intermodulation distortion is also a type of non-linear distortion which occurs when the input signal consists of more than one frequency.
- If an input signal consists two frequencies  $f_1$  and  $f_2$ , then the output will contain their harmonics i.e.  $(f_1, 2f_1, 3f_1, \dots)$  and  $(f_2, 2f_2, 3f_2, \dots)$ .
- In addition there will be components  $(f_1 + f_2)$  and  $(f_1 - f_2)$  and also the sum and differences of the harmonics.
- These sum and difference frequencies are called intermodulation frequencies which are undesirable because they subtract from the original intelligence.
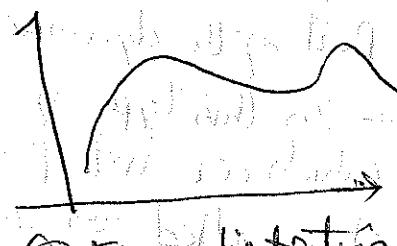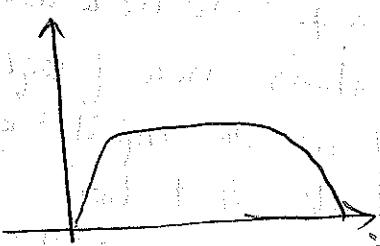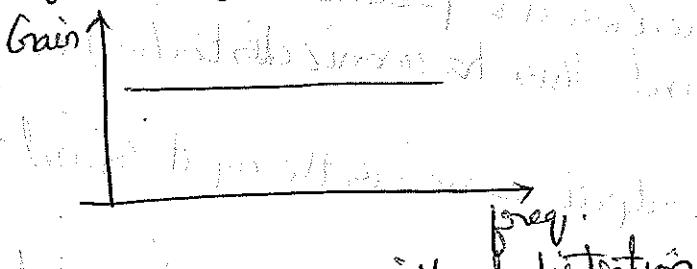
## Frequency distortion:

- Frequency distortion results when the signal components of different frequencies are amplified differently. This distortion is due to the various frequency dependent reactances (both Capacitive and Inductive) associated with the circuit or the active device itself.
- In case of audio signals, the frequency distortion leads to a change in the quality of sound, because all the different frequencies have different amplitudes.
- Here in the design of untuned or wideband amplifiers, the amplifier should provide the same gain for all the frequencies so that all the frequencies will have the same relative amplitudes in the output.
- If the frequency-response characteristic is not flat over the range of frequencies under consideration, the circuit is said to have frequency distortion.



④ freq. response without distortion  
for Ideal amplifiers

⑤ freq. response with  
distortion in RC Coupled  
amplifiers

⑥ freq. distortion  
in transformer  
coupled amplifier

## Phase distortion:

- Phase distortion results from unequal phase shifts of signals of different frequencies. This distortion is due to the fact that the phase angle of the complex gain  $A$  depends upon frequency.
- Phase distortion is said to occur if the phase relationship between the various frequency components making up the signal waveform is not the same in the output as in the input. It means that the time of transmission or the delay introduced by the amplifier is different for various frequencies. The reactive components of the circuit are responsible for causing this type of distortion.

→ This distortion is not important in audio amplifiers as ears are not capable of distinguishing the relative phases of different frequency components. But this distortion is objectionable in video amplifiers used in television.

### Equivalent simplified Hybrid Model:

→ For a transistor amplifier the detailed calculations of all four parameters

→ ~~AV, AI, RI, RO~~ are determined using exact h-model.

→ But in most practical cases it is better to calculate above mentioned parameters using approximate h-model rather than cumbersome exact h-model.

→ This is because of the fact that the transistor parameters are unstable, varies with temperature, ageing and so on.

→ Here even with exact analysis one is not assured of obtaining the values of parameters accurately. So approximations may be allowed within tolerable limits.

→ Of the four parameters, two parameters  $h_{ie}$  and  $h_{fe}$  are sufficient for the approximate analysis of low frequency circuits provided that the load resistance is small enough to satisfy the condition  $h_{re}R_L \leq 0.1$ .

→ The simplified equivalent h-model of transistor is shown in figure.

→ This simplified model can be used for all the transistor configurations by grounding the approximate node. Connect signal source between the input node and ground, load in between the output node and ground.

→ The error in calculating various parameters  $A_I$ ,  $A_V$ ,  $R_I$  and  $R_O$  for all the configurations will be less than 10%.

CC	CB
$h_{rc} = h_{ie}$	$h_{ib} = h_{ie} / (1 + h_{fe})$
$h_{oc} = 1$	$h_{eb} = \frac{h_{ie} h_{oc}}{1 + h_{fe}} - h_{re}$
$h_{ic} = - (1 + h_{fe})$	$h_{fb} = \frac{-h_{re}}{1 + h_{fe}}$
$h_{oe} = h_{re}$	$h_{ob} = \frac{h_{re}}{1 + h_{fe}}$

Analysis of CE using Simplified h-model:

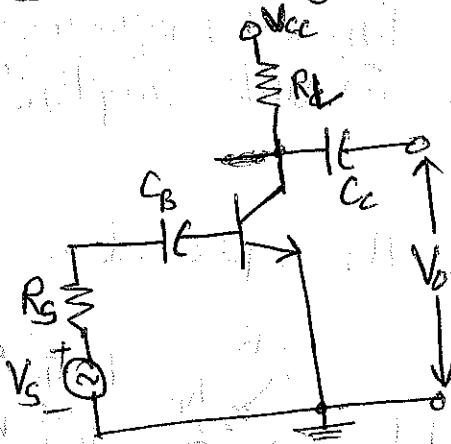


Fig (a) CE Amplifier Circuit

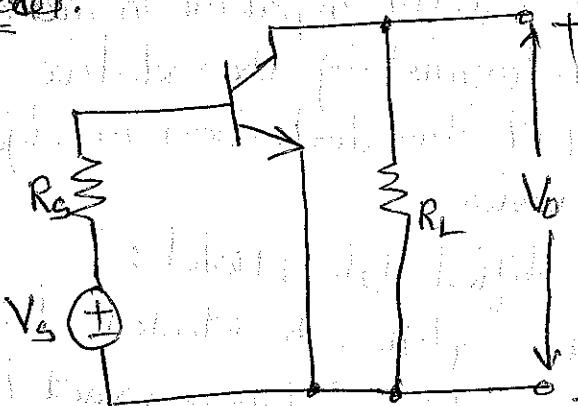


Fig (b) AC equivalent of CE amplifier

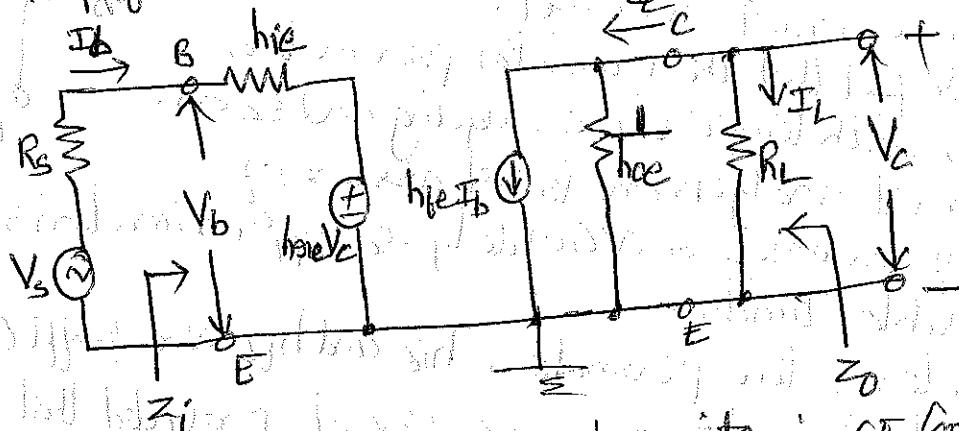


Fig (c) Exact h-parameter model of transistor in CE Configuration.

In figure (c)  $\frac{1}{hoe}$  and  $R_L$  are in parallel. Thus the parallel combination of these two resistances produces a resistance value, which is approximately equal to the load value i.e.  $R_L$ .

Hence the term  $\frac{1}{hoe}$  can be neglected if  $\frac{1}{hoe} \gg R_L$  i.e.,  $hoe \ll 1$ . In the absence of  $hoe$ , the Collector Current  $I_c$  value is obtained by,

$$I_c = h_{fe} I_b$$

Then the magnitude of Voltage generated in emitter circuit is given by,

$$hoe |V_e| = hoe I_c R_L = hoe h_{fe} I_b R_L$$

But  $hoe \cdot h_{fe} \approx 0.01$ , when the load resistance  $R_L$  is too large, the above voltage can be neglected in comparison with the voltage across  $h_{ie}$  i.e.  $h_{ie} \cdot I_b$ . The approximate equivalent circuit can be obtained by neglecting the parameters  $hoe$  and  $hoe$  such that the load resistance  $R_L$  is very small.

Current gain ( $A_I$ ): The general expression for current gain of CE is,

$A_I = \frac{-h_{fe}}{1+h_{oe}R_L}$  but here  $R_L \ll \text{load}$

$$\therefore A_I \approx -h_{fe}$$

Input Impedance ( $Z_i$ ): The general expression for input impedance of CE configuration is given by,

$$Z_i = h_{ie} + h_{oe} A_I R_L$$

The above equation can also be written as,

$$Z_i = h_{ie} \left[ 1 - \frac{h_{oe} h_{fe} (A_I) h_{oe} R_L}{h_{ie} h_{oe} h_{fe}} \right]$$

By using the typical values of h-parameters, we have

$$\frac{h_{oe} h_{fe}}{h_{ie} h_{oe}} \approx 0.5 \quad \text{and} \quad |A_I| = h_{fe}$$

$$\therefore Z_i = h_{ie} \left[ 1 - \frac{0.5 h_{fe} R_L}{h_{fe}} \right] =$$

$$\text{But } h_{oe} R_L \ll 0.1 \quad \therefore Z_i = h_{ie}.$$

Voltage gain ( $A_V$ ): The general expression for voltage gain of CE configuration is given by,

$$A_V = \frac{A_I R_L}{Z_i} = \frac{-h_{fe} R_L}{h_{ie}}$$

Output Impedance ( $Z_o$ ):

It is the ratio of  $V_o$  to  $I_C$  with  $V_s = 0$  and  $R_L$  excluded. The simplified circuit has infinite output impedance because with  $V_s = 0$  and external voltage source applied at the output, it is found that  $I_B = 0$  and hence  $I_C = 0$ . So  $Z_o = \infty$ .

→ with the load resistance  $R_L$  included the output resistance  $R_o$  calculated using approximate model increases but not more than 10%.

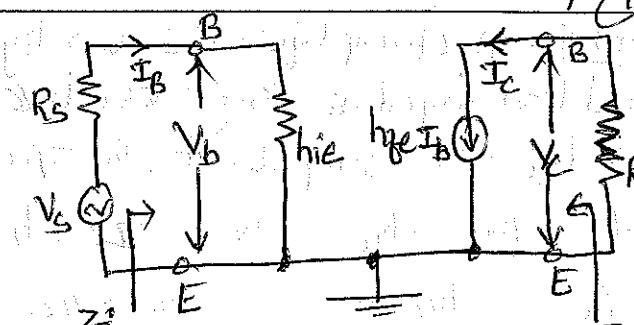



Fig ① Simplified h-model of CE amplifier

Prob ①: A CE amplifier is driven by a voltage source of internal resistance  $R_i = 800\Omega$  and load impedance is a resistance  $R_L = 1000\Omega$ . The h-parameters are  $h_{ie} = 1k\Omega$  and  $h_{fe} = 50$ . Compute  $A_I$ ,  $A_V$ ,  $Z_i$  and  $Z_o$  using approximate analysis.

Sol ①:  $A_I = -h_{fe} = -50$ ,  $Z_i = h_{ie} = 1k\Omega$ ,  $R_o = \infty$

$$A_V = -\frac{h_{fe} R_L}{R_i} = -\frac{50 \times 1000}{1000} = -50$$

CE Amplifier with fixed bias:

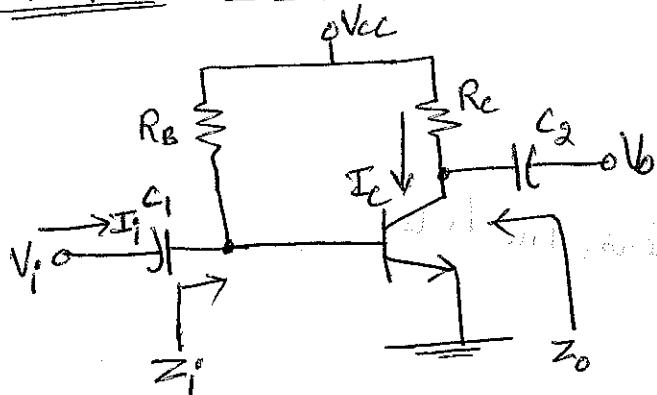

Fig(A) CE fixed bias Configuration

Input Impedance:

$$Z_i = R_B // h_{ie}$$

If  $R_B \gg h_{ie}$ ,

$$\text{then } Z_i = h_{ie}$$

Output Impedance:

It is the impedance determined with  $V_i = 0$ , with  $V_i = 0$ ,  $I_b = 0$  and  $h_{fe} I_b = 0$  indicating an open circuit equivalent for the Current Source.

$$\text{Here } Z_o = R_L = (R_L)$$


$$\text{Voltage gain: } A_V = \frac{V_o}{V_i}$$

$$I_o = h_{fe} I_b \Rightarrow V_o = h_{fe} I_b R_L$$


Assuming  $R_B \gg h_{ie}$   $I_o \approx I_b$  and  $V_i = I_b h_{ie}$ .

$$\therefore A_V = \frac{-h_{fe} I_b R_L}{I_b h_{ie}} = -\frac{h_{fe} R_L}{h_{ie}}$$

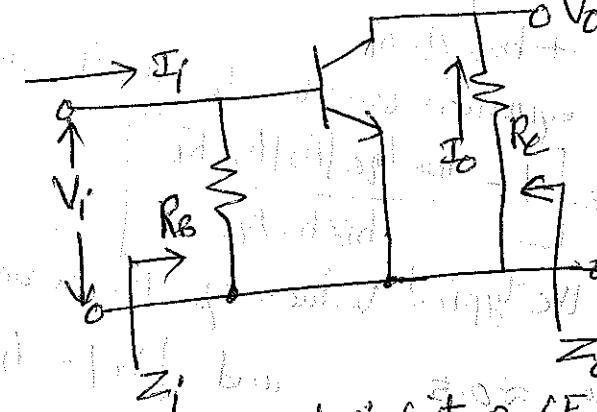As  $h_{fe} > h_{ie}$  are positive  $\rightarrow A_V$  is negative. The negative sign indicates a  $180^\circ$  phase shift between input and output signals.



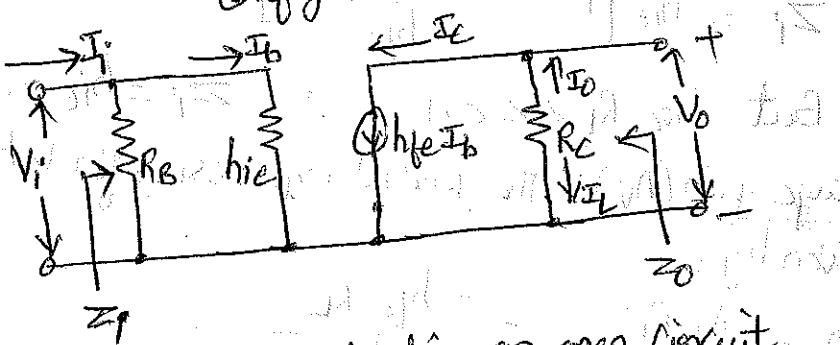Fig(B) AC equivalent Circuit of CE fixed bias Configuration



Current gain:  $A_I = \frac{I_L}{I_i} = \frac{-I_o}{I_i} \approx -\frac{h_{fe} I_b}{I_b} \approx -h_{fe}$

The sign of  $A_I$  will be positive if  $A_I$  is defined as the ratio of  $I_o$  to  $I_i$ .

Prob C: Determine  $Z_i$ ,  $Z_o$ ,  $A_V$  &  $A_I$  for CE amplifier shown in figure.  $h_{fe} = 60$ ,  $h_{ie} = 500 \Omega$ .

Soln:  $R_B = 220k\Omega \gg h_{ie} = 500 \Omega$


$$\therefore Z_{in} = h_{ie} = 500 \Omega$$

$$Z_o = R_C = 5.1k\Omega$$


$$A_V = \frac{-h_{fe} R_C}{h_{ie}} = \frac{-60(5.1 \times 10^3)}{500} = -612$$

$$A_I = -h_{fe} = -60$$

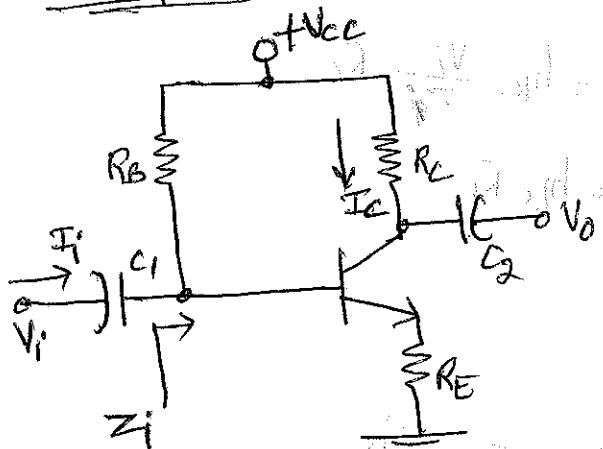
CE Amplifier with unbypassed emitter resistor ( $R_E$ ): (A)



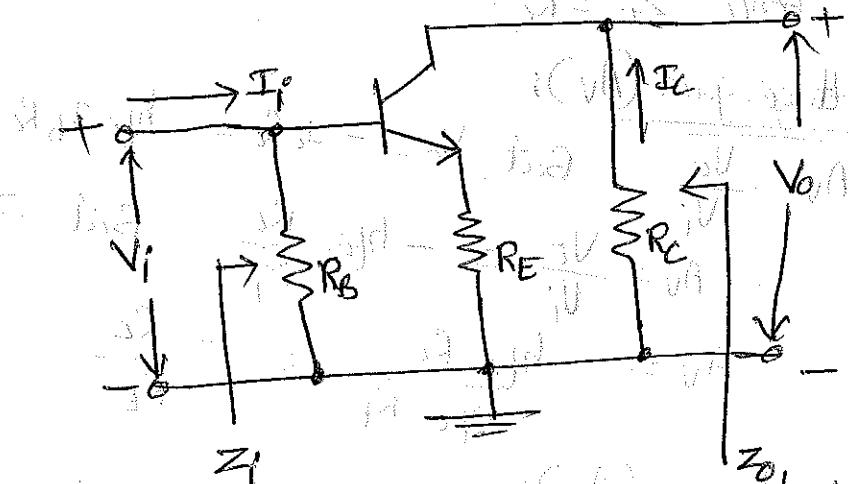Fig(A): CE Amplifier with unbypassed emitter resistor



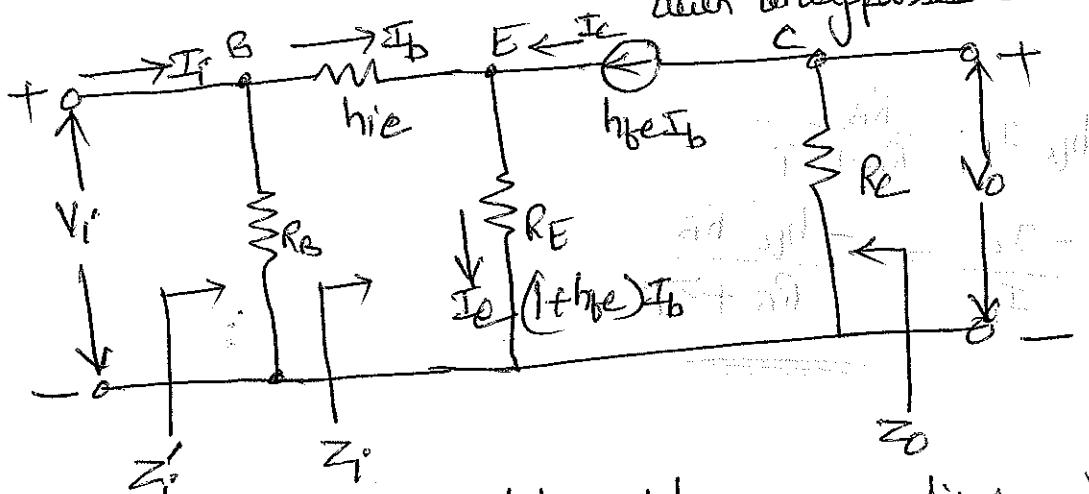Fig(B) An equivalent circuit for CE amplifier with unbypassed emitter resistor



Fig(C) Approximate small signal h-model of CE amplifier with unbypassed emitter resistor.

Input Impedance ( $Z_i$ ):

$$I_e = I_b + h_{fe} I_b = (1+h_{fe}) I_b$$

$$V_i = I_b h_{ie} + (1+h_{fe}) I_b \cdot R_E$$

$$Z_i = \frac{V_i}{I_b} = h_{ie} + (1+h_{fe}) R_E$$

As  $h_{fe} \gg 1$  then  $Z_i = h_{ie} + h_{fe} R_E$

But  $h_{fe} R_E \gg h_{ie}$  leading to  $Z_i = h_{fe} R_E$ .

$$Z_f = R_B // Z_i$$

Output impedance ( $Z_o$ ):

with  $V_i = 0$ ,  $I_b = 0$ ,  $h_{fe} I_b = 0$  indicating open circuit for Current Source

Hence  $Z_o = R_C$ .

Voltage gain ( $A_V$ ):

$$A_V = \frac{V_o}{V_i} \text{ But } V_o = -I_e R_C = -h_{fe} I_b R_C = -h_{fe} \frac{V_i}{Z_i} R_C$$

$$\therefore A_V = \frac{V_o}{V_i} = -h_{fe} \frac{R_C}{Z_i} \text{ But } Z_i \approx h_{fe} R_E$$

$$\therefore A_V = -\frac{h_{fe} \cdot R_C}{h_{fe} \cdot R_E} \approx -\frac{R_C}{R_E}$$

Current gain ( $A_I$ ):

$$A_I = \frac{-I_C}{I_i} \text{ But } I_e = h_{fe} I_b \text{ where } I_b = I_i \cdot \frac{R_B}{R_B + Z_i}$$

$$\therefore I_C = h_{fe} I_i \cdot \frac{R_B}{R_B + Z_i}$$

$$\therefore A_I = \frac{-I_C}{I_i} = \frac{-h_{fe} R_B}{R_B + Z_i}$$

Based on other configurations, load and biasing, current gain  $\beta$  & voltage settings.

Prob(1): Determine  $Z_i$ ,  $Z_o$ ,  $A_V$  and  $A_{VI}$  for CE amplifier shown.

$$h_{ie} = 1k\Omega \quad h_{fe} = 50$$

$$\text{Sol(1)}: Z_i = h_{fe} R_E = 50 \times 330 = 16.5 k\Omega$$


$$Z_i' = R_B \parallel Z_i = 20k \parallel 16.5k = 9.04 k\Omega$$

$$Z_o = R_C = 5k\Omega$$

$$A_V = -\frac{R_C}{R_E} = -\frac{5k}{330} = -15.15$$

$$A_{VI} = -\frac{h_{fe} R_B}{R_B + h_{fe} R_E} = -\frac{50 \times 20 \times 10^3}{20 \times 10^3 + 50 \times 330} = -27.39$$

CE Amplifier with Voltage Divider bias:

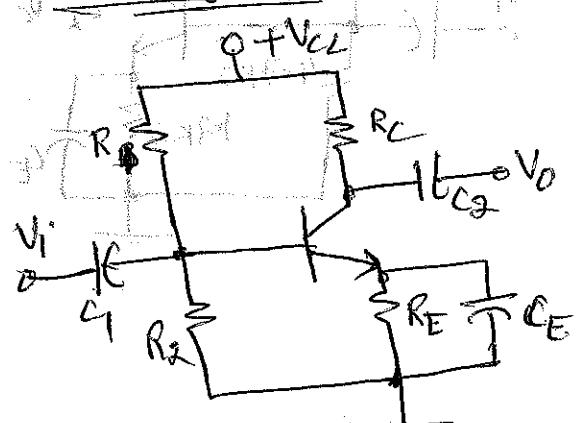

Fig(1) CE Amplifier with Voltage divider bias.

Voltage gain:  $V_o = -I_C R_C = -h_{fe} I_B R_C$


$$A_V = \frac{V_o}{V_i} \quad V_i = I_B [R_1 \parallel R_2] \parallel h_{ie}$$

$$V_i = I_B h_{ie} \quad \text{(neglecting } R_1 \parallel R_2)$$


$$V_i = h_{ie} I_B \quad \{ I_B = I_C \}$$

$$\therefore A_V = \frac{-h_{fe} I_B R_C}{h_{ie} I_B}$$

$$A_V = -\frac{h_{fe} R_C}{h_{ie}}$$

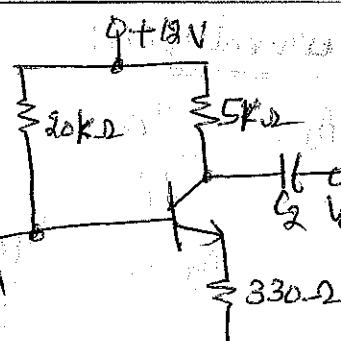

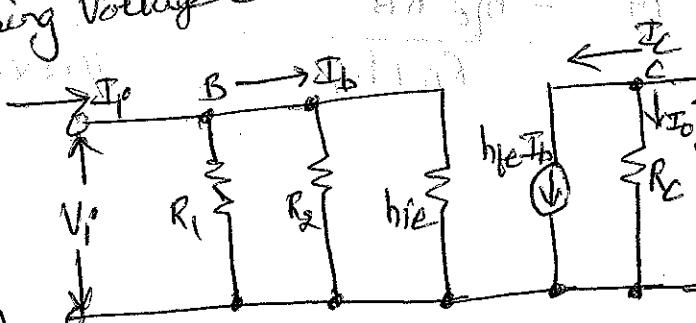Fig(2): AC equivalent circuit for CE amplifier using Voltage divider bias.



Fig(3) Simplified hybrid model of CE amplifier with Voltage divider bias.

Current gains:

$$I_o = h_{fe} I_b \quad ; \quad I_b = I_i \frac{R_B}{R_B + h_{ie}} \quad ; \quad R_o = R_1 \parallel R_2$$

$$A_I = \frac{I_o}{I_i}$$

$$\therefore A_I = - \frac{h_{fe} I_i \left( \frac{R_B}{R_B + h_{ie}} \right)}{I_i} = - h_{fe} \frac{R_B}{R_B + h_{ie}}$$

Input Impedance:  $Z_i = R_B \parallel h_{ie}$  where  $R_B = R_1 \parallel R_2$

Output Impedance:  $Z_o = R_C$

Prob 1: Determine  $Z_i, Z_o, A_V$  and  $A_I$  of CE amplifier

shown in figure with  $h_{ie} = 3.2k\Omega$  &  $h_{fe} = 100$

$$\text{Sol: } Z_i = R_B \parallel h_{ie} \quad ; \quad R_B = R_1 \parallel R_2 = 40k \parallel 4.7k$$


$$= 4.2k \parallel 3.2k$$

$$Z_i = 1.82k\Omega$$

$$Z_o = R_C = 4k\Omega$$

$$A_V = -h_{fe} \frac{R_C}{R_E} = -100 \times \frac{4 \times 10^3}{1.2 \times 10^3} = -125$$
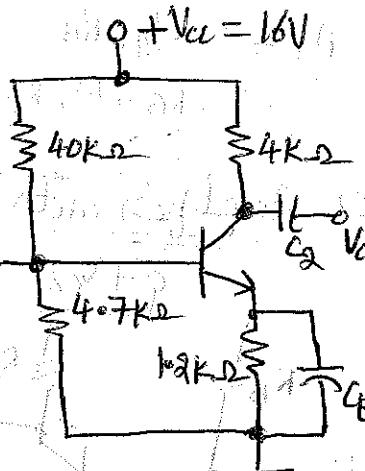
$$A_I = - \frac{h_{fe} R_B}{R_B + h_{ie}} = - \frac{100 \times 4.2 \times 10^3}{4.2 \times 10^3 + 3.2 \times 10^3} = -56.76$$



Analysis of CB Configuration using approximate model:

Current gain:

$$A_I = -\frac{I_C}{I_E} = -\frac{h_{FE} I_B}{I_E} = \frac{-h_{FE} I_B}{-(h_{FE} I_B + I_B)} = \frac{h_{FE}}{1+h_{FE}}$$

$$A_I = -h_{FE}$$

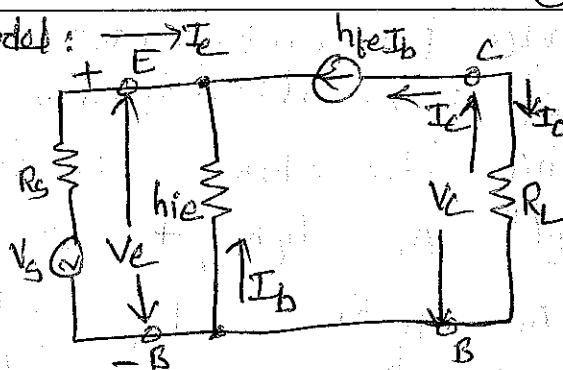


Fig: Simplified hybrid model of CB Circuit.

Input Resistance:

$$R_I = \frac{V_{BE}}{I_E} = \frac{-I_B h_{IE}}{I_E} = \frac{h_{IE}}{1+h_{FE}} = h_{IB}$$

Voltage gain:

$$A_V = \frac{V_C}{V_S} = \frac{-h_{FE} I_B R_L}{-h_{IE} I_B} = \frac{h_{FE} R_L}{h_{IE}}$$



Output Impedance:

$$R_O = \frac{V_C}{I_E} \text{ with } V_S = 0 \Rightarrow R_L = \infty$$

But with  $V_S = 0$ ,  $I_E = 0 \Rightarrow I_B = 0$

Prob ①: A CB amplifier as shown in figure has  $R_S = 600\Omega$ ,  $R_E = 5.6K\Omega$ ,  $R_C = 5.6K\Omega$ ,  $R_L = 39K\Omega$ ,  $h_{IE} = 1K\Omega$ ,  $h_{FE} = 85$  and  $h_{OE} = 2\mu A/V$ . Calculate  $R_I$ ,  $R_O$ ,  $A_V$  &  $A_I$ .

Soln:

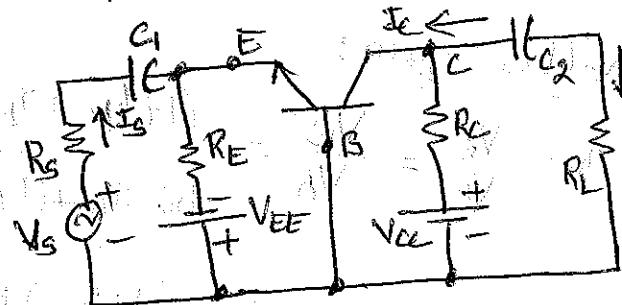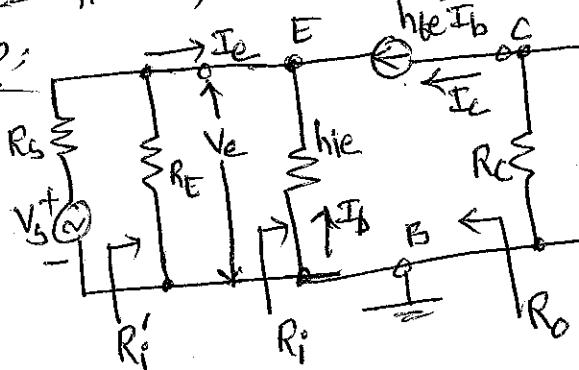

$$h_{OE} \times (R_C || R_L) = 2 \times 10^{-6} \times (5.6K) || (39K) = 9.79 \times 10^{-3} \quad \text{(so use approximate analysis.)}$$

$$A_V = \frac{h_{FE} R_L'}{h_{IE}} = \frac{85 \times (5.6K || 39K)}{1K} = 416.2$$

$$A_I = \frac{h_{FE}}{1+h_{FE}} = \frac{85}{1+85} = 0.928$$

$$R_I = \frac{h_{IE}}{1+h_{FE}} = \frac{1000}{1+85} = 11.627 \Omega$$

$$R_I' = R_I || R_E = 11.627 || 5.6K = 11.6 \Omega$$

$$R_O = \infty$$

$$R_O' = R_O || R_C || R_L = \infty || 5.6K || 39K = 4.89K$$

Prob(2): For a c-e transistor amplifier driven by a voltage source of internal resistance  $R_S = 1200\Omega$  and load impedance is a resistor  $R_L = 1000\Omega$ . The h-parameters are  $h_{ib} = 22.2$  &  $h_{fb} = -0.98$ . Compute  $R_i$ ,  $R_o$ ,  $A_i$  &  $A_v$  using approximate analysis.

Sol'n:  $A_i = -h_{fb} = +0.98 \quad R_i = h_{ib} = 22.2 \quad R_o = \infty$

$$A_v = \frac{h_{fe} R_L}{h_{ie}} \quad h_{fe} = \frac{-h_{fb}}{1+h_{fb}} = \frac{-(-0.98)}{1-0.98} = 49$$

$$\therefore h_{ib} = \frac{h_{ie}}{1+h_{fe}} \Rightarrow h_{ie} = h_{ib}(1+h_{fe}) = 22(1+49) = 1100 \Omega$$

$$\therefore A_v = \frac{49 \times 1000}{1100} = 44.54$$

Analysis of CE Configuration using the approximate model:

Current gain:

$$A_i = \frac{I_e}{I_b} = \frac{(1+h_{fe}) I_b}{I_b} = 1+h_{fe}$$

Input Resistance:

$$R_i = \frac{V_b}{I_b} \text{ But } V_b = h_{ie} I_b + (1+h_{fe}) I_b R_L$$

$$\therefore R_i = h_{ie} + (1+h_{fe}) R_L$$


Voltage gain:

$$A_v = \frac{V_e}{V_b} = \frac{V_e}{V_b} = \frac{(1+h_{fe}) I_b R_L}{h_{ie} I_b + (1+h_{fe}) I_b R_L}$$

$$= \frac{(1+h_{fe}) R_L}{h_{ie} + (1+h_{fe}) R_L}$$

$$= \frac{h_{ie} + (1+h_{fe}) R_L - h_{ie}}{h_{ie} + (1+h_{fe}) R_L}$$
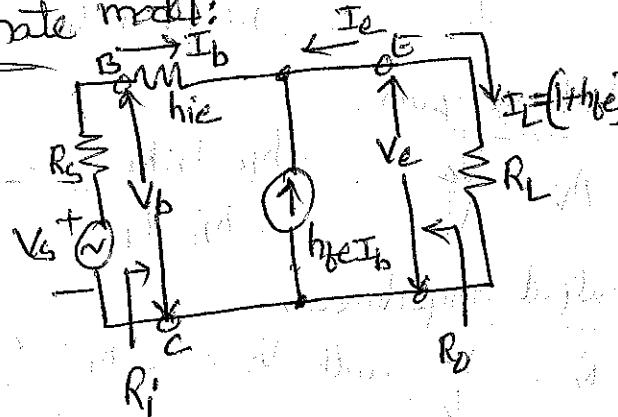
$$A_v = 1 - \frac{h_{ie}}{h_{ie} + (1+h_{fe}) R_L} = 1 - \frac{h_{ie}}{R_i}$$



output Impedance:

output admittance  $Y_o = \frac{\text{short circuit current in output terminals}}{\text{open circuit voltage between output terminals}}$

short circuit current in output terminals  $= (1+hfe) I_b = \frac{(1+hfe) V_s}{h_{ie} + R_s}$

open circuit voltage between output terminals  $= V_s$

$$\therefore Y_o = \frac{1+hfe}{h_{ie} + R_s} \Rightarrow Z_o = \frac{1}{Y_o} = \frac{h_{ie} + R_s}{1+hfe}$$

prob ①: A voltage source of internal resistance  $R_s = 900\Omega$  drives a CC amplifier using load resistance  $R_L = 2000\Omega$ . The CE parameters are  $h_{ie} = 1200\Omega$  &  $h_{fe} = 60$ . Compute  $A_i$ ,  $A_v$ ,  $R_i$  and  $R_o$  using approximate analysis.

Sol<sup>n</sup>:  $A_i = 1+hfe = 1+60 = 61$

$$R_i = h_{ie} + (1+hfe) R_L = 1200 + 61 \times 2000 = 123.2k\Omega$$

$$A_v = 1 - \frac{h_{ie}}{R_i} = 1 - \frac{1200}{123.2 \times 10^3} = 0.9903$$



$$Y_o = \frac{1+hfe}{h_{ie} + R_s} = \frac{1+60}{1200 + 900} = 0.029 \text{ V}$$

$$R_o = 34.43 \Omega$$

prob ②: A CC circuit has the following components  $R_1 = 27k\Omega$ ,  $R_2 = 27k\Omega$ ,  $R_E = 5.6k\Omega$ ,  $R_L = 47k\Omega$ ,  $R_s = 600\Omega$ . The h-parameters are  $h_{ie} = 1k\Omega$ ,  $h_{fe} = 85$  &  $h_{oc} = 2\text{mA/V}$ .

Calculate  $A_i$ ,  $R_i$ ,  $R_o$  &  $A_v$ .

Sol<sup>n</sup>:

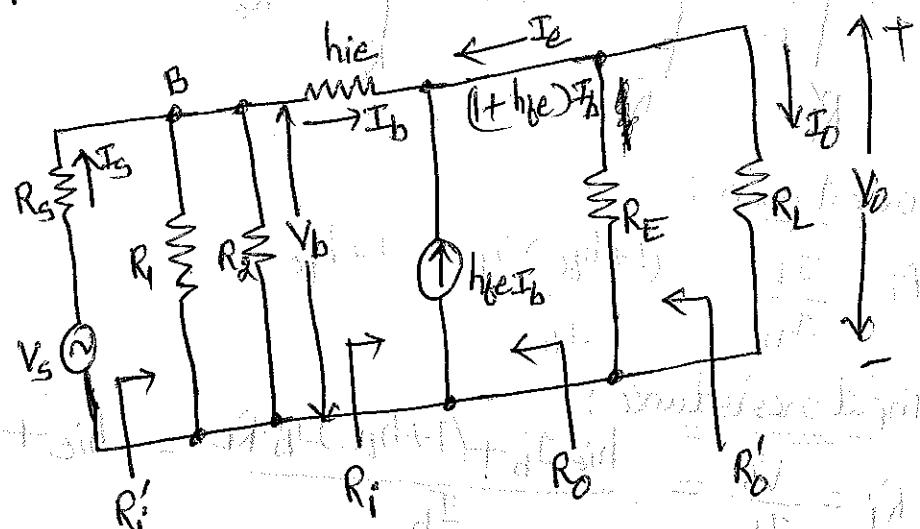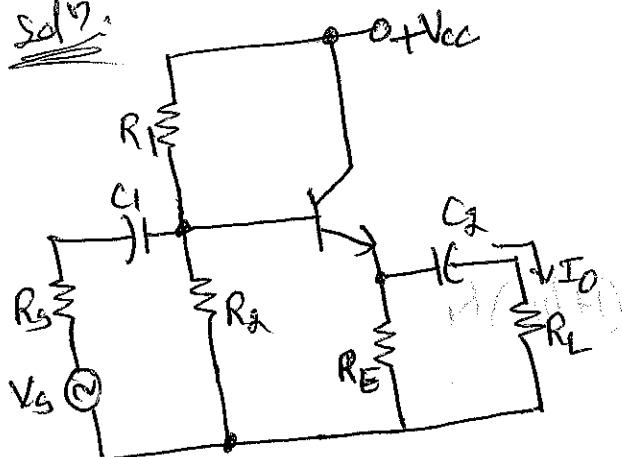

$$h_{oe} \times R'_L = 2 \times 10^{-6} \times (5.6k \parallel 47k) = 0.01 < 0.1 \text{ thus we use approximate h-model}$$

$$A_i = 1 + h_{fe} = 1 + 85 = 86$$

$$R_i = h_{ie} + (1 + h_{fe}) R_L' = h_{ie} + (1 + h_{fe})(R_E \parallel R_L)$$

$$R_i = 1k + (1+85) (5.6k \parallel 47k) = 431.33k\Omega$$



$$R'_i = R_i \parallel R_1 \parallel R_2 = 431.33k \parallel 27k \parallel 27k = 13.09k\Omega$$

$$AV = 1 - \frac{h_{ie}}{R_i} = 1 - \frac{1k}{431.33k} = 0.997$$

$$R_o = \frac{h_{re} + R'_o}{1 + h_{fe}} = \frac{h_{re} + (R_E \parallel R_2 \parallel R_L)}{1 + h_{fe}} = \frac{1k + (27k \parallel 27k \parallel 600)}{1 + 85} = 18.3\Omega$$

$$R'_o = R_o \parallel R_E \parallel R_L = 18.3 \parallel 5.6k \parallel 47k = 18.23\Omega$$

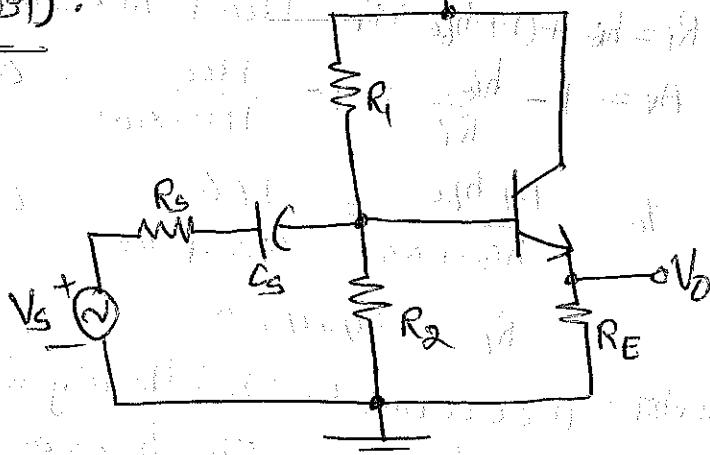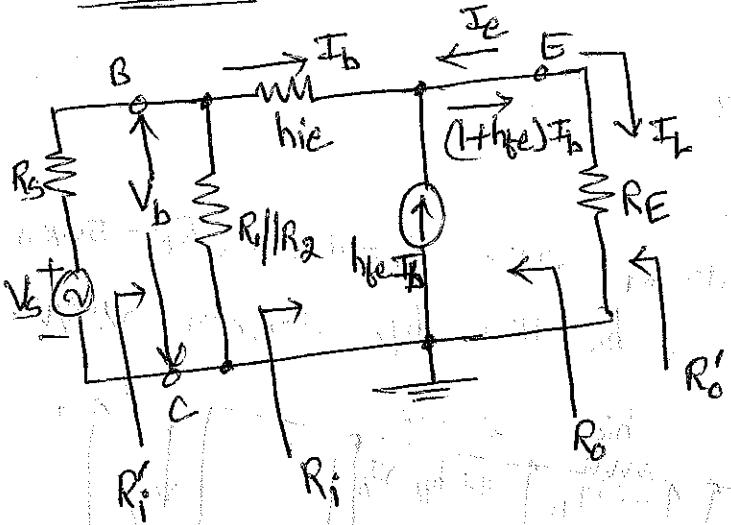Emitter Follower (Common Collector Amplifier):



Current gain:

$$A_i = \frac{I_L}{I_B} = \frac{(1 + h_{fe}) I_B}{I_B} = 1 + h_{fe}$$

Input resistance:

$$R_i = \frac{V_B}{I_B} = \frac{h_{ie} I_B + (1 + h_{fe}) I_B \cdot R_L}{I_B} = h_{ie} + (1 + h_{fe}) R_L$$

$$R'_i = R_i \parallel R_1 \parallel R_2$$

Voltage gain:

$$A_v = \frac{V_o}{V_i} = \frac{A_i R_L}{R_i}$$

$$A_i = 1 + h_{fe}$$

$$R_i = h_{ie} + (1 + h_{fe}) R_L = h_{ie} + A_i R_L$$

$$\Rightarrow \frac{R_i - h_{ie}}{R_L} = A_i$$

$$\therefore A_v = \frac{R_i - h_{ie}}{R_i} = 1 - \frac{h_{ie}}{R_i}$$

Output admittance:

$$Y_o = h_{oc} - \frac{h_{fc} h_{oc}}{h_{ic} + R'_s}$$

$$\text{where } R'_s = R_s \parallel R_i \parallel R_L$$

Neglecting  $h_{oc}$  and assuming  $h_{oc} \approx 1$ ,  $h_{fc} = -(A + h_{fe})$  we get,

$$Y_o = \frac{1 + h_{fe}}{h_{ie} + R'_s} \quad \left\{ \because h_{ic} = h_{ie} \right\}$$

$$\therefore R_o = \frac{h_{ie} + R'_s}{1 + h_{fe}}$$

$$R'_o = R_o \parallel R_E$$

Prob ①: for the emitter follower shown in figure

$$R_s = 500\Omega, R_i = R_2 = 50k\Omega, R_L = 2k\Omega$$

$$h_{fe} = 100 \text{ and } h_{ie} = 1.1k\Omega. \text{ Find } R_i, R_o, A_i, A_v.$$

Soln:

$$R_i = h_{ie} + (1 + h_{fe}) R_L = 1.1 \times 10^3 + (1 + 100) \times 2 \times 10^3 = 203.1k\Omega$$


$$R'_i = R_i \parallel R_1 \parallel R_2 = 203.1k \parallel 50k \parallel 50k = 22.26k\Omega$$

$$R_o = \frac{h_{ie} + R'_s}{1 + h_{fe}} = \frac{1.1 \times 10^3 + (500 \parallel 50k \parallel 50k)}{1 + 100} = 15.74\Omega$$

$$R'_o = R_o \parallel R_L = 15.74 \parallel 2k = 15.62\Omega$$



$$A_i = 1 + h_{fe} = 1 + 100 = 101$$
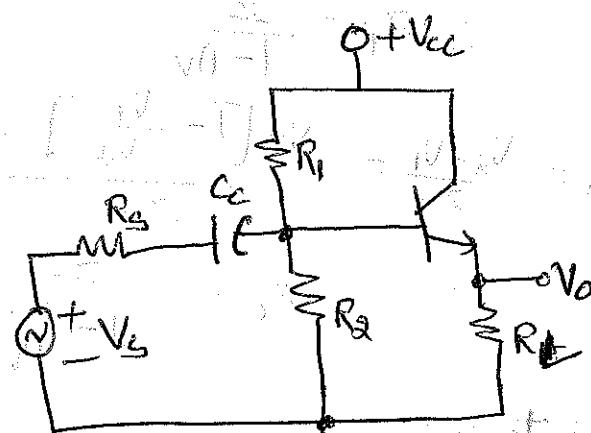
$$A_v = 1 - \frac{h_{ie}}{R_i} = 1 - \frac{1.1 \times 10^3}{203.1 \times 10^3} = 0.9946$$


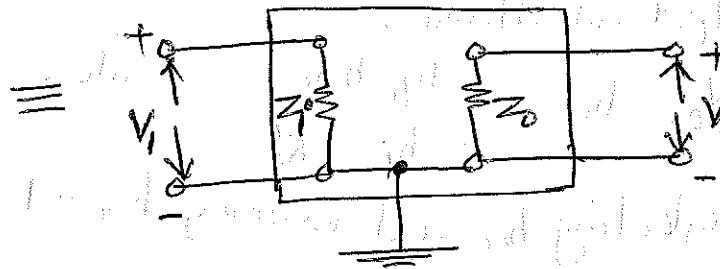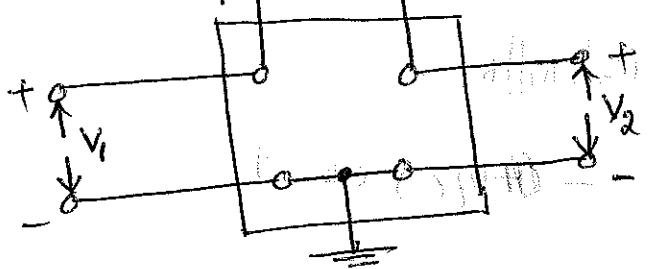
### Miller's Theorem :

→ Miller's theorem states that if an impedance 'z' is connected between input and output terminals of a network which provides a voltage gain 'Av', an equivalent circuit that gives the same effect can be drawn by removing 'z' and connecting an impedance  $Z_i = \frac{z}{1-Av}$  across the input and  $Z_o = \frac{z}{1-\frac{1}{Av}} = \frac{z Av}{Av-1}$  across the output.



Proof:

$$I_1 = \frac{V_1 - V_2}{z} = V_1 \left[ 1 - \frac{V_2}{V_1} \right] = \frac{V_1 (1-Av)}{z} = \frac{V_1}{z/(1-Av)} = \frac{V_1}{Z_i}$$

$$\therefore Z_i = \frac{z}{1-Av}$$

$$I_2 = \frac{V_2 - V_1}{z} = \frac{V_2 \left[ 1 - \frac{V_1}{V_2} \right]}{z} = \frac{V_2 \left[ 1 - \frac{1}{Av} \right]}{z} = \frac{V_2}{z \left( 1 - \frac{1}{Av} \right)} = \frac{V_2}{Z_o}$$

$$\therefore Z_o = \frac{z}{1 - \frac{1}{Av}} = \frac{z Av}{Av-1}$$

### Advantages:

→ Using Miller's theorem, complex circuit can be easily simplified.

### Disadvantages:

→ This theorem will be useful in making calculations only if it is possible to find the value of  $Av$  by some independent means.

$$\Delta HPPD = \frac{V_{out}(t)}{V_{in}(t)} = 1 + \frac{R_f}{R_s} = 1 + \frac{1}{10} = 1.1 = V_A$$

### Miller Effect Capacitance:

- In inverting amplifiers, the capacitive element  $C_f$  is connected between input and output terminals of the active device i.e.  $X_{Cf} = \frac{1}{j\omega C_f}$ .
- The large capacitors will control the low frequency response due to their low reactance levels.
- Therefore, the Miller effect input capacitance  $C_{Mi}$  is derived as,

$$Z_i = \frac{Z}{1-A}$$

$$\text{i.e. } \frac{1}{j\omega C_{Mi}} = \frac{1}{j\omega C_f(1-A)}$$

$$\text{Therefore, } C_{Mi} = (1-A)C_f$$

- Hence it is evident that in any inverting amplifier the input capacitance will be increased by a Miller effect capacitance sensitive to the gain of the amplifier and the interelectrode capacitance  $C_f$  between the input and output terminals of the active device.

- The Miller output capacitance  $C_{Mo}$  is derived as,

$$Z_o = \frac{Z}{1-\frac{1}{A}}$$


$$\text{i.e. } \frac{1}{j\omega C_{Mo}} = \frac{1}{j\omega C_f(1-\frac{1}{A})}$$

$$\text{Therefore, } C_{Mo} = (1-\frac{1}{A})C_f$$

$$\text{If } A \gg 1 \text{ then } C_{Mo} = C_f$$
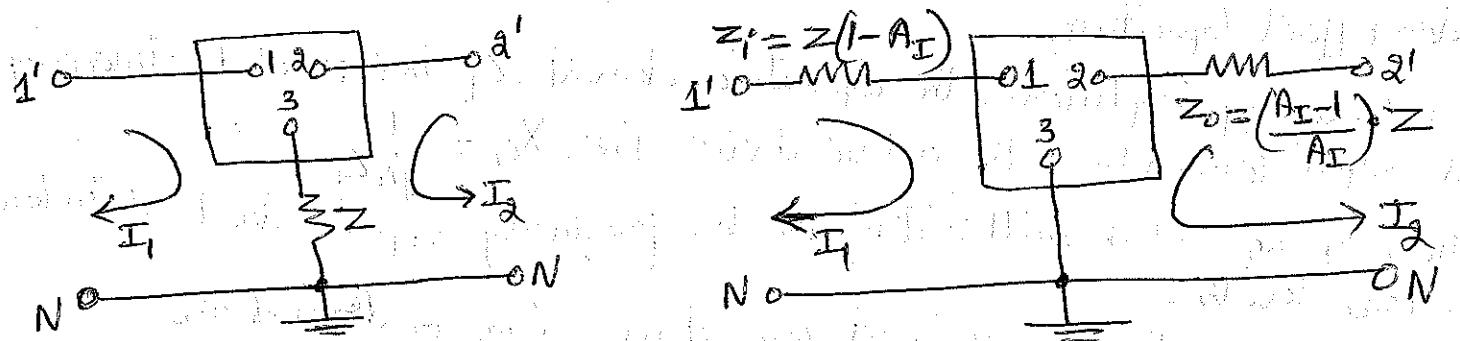
### Dual of Miller's theorem:

- Dual of Miller's theorem states that if an impedance  $Z$  connected as shunt element between input and output terminals can be replaced by an impedance  $Z_i = Z(1-\frac{1}{A_I})$  at the input side and  $Z_o = Z(1-\frac{1}{A_I}) = \frac{Z(A_I-1)}{A_I}$  at the output side where the current ratio  $A_I = -\frac{I_2}{I_1}$ .



Proof:

Voltage across  $z_1$  is  $V_1 = I_1 z_1$

Voltage drop across  $z$  is  $(I_1 + I_2)z$

$$V_1 = I_1 z_1 = (I_1 + I_2)z \Rightarrow z_1 = \left(1 + \frac{I_2}{I_1}\right)z = (1 - A_1)z.$$

Also Voltage across  $z_0$  is  $V_2 = I_2 z_0$

$$\therefore I_2 z_0 = (I_1 + I_2)z$$

$$\Rightarrow z_0 = \left(1 + \frac{I_1}{I_2}\right)z = \left(1 - \frac{1}{A_1}\right)z = \underline{\underline{\left(\frac{A_1 - 1}{A_1}\right)z}}.$$

prob①: Common-emitter amplifier with collector to base bias is as shown in figure. The h-parameters are,


$h_{ie} = 1.1K$ ,  $h_{fe} = 50$ ,  $h_{oe} = 25 \times 10^{-6} A/V$ ,  $h_{ce} = 2.5 \times 10^{-4}$ .

Soln: Calculate  $R_i$ ,  $A_1$ ,  $A_v$ ,  $R_o$ .


$$h_{ce} \cdot (R_L / R_F) = 2.5 \times 10^{-6} (10k / 200k) = 0.138$$

which is greater than 0.1 so we use exact analysis

h-parameter equivalent circuit is,

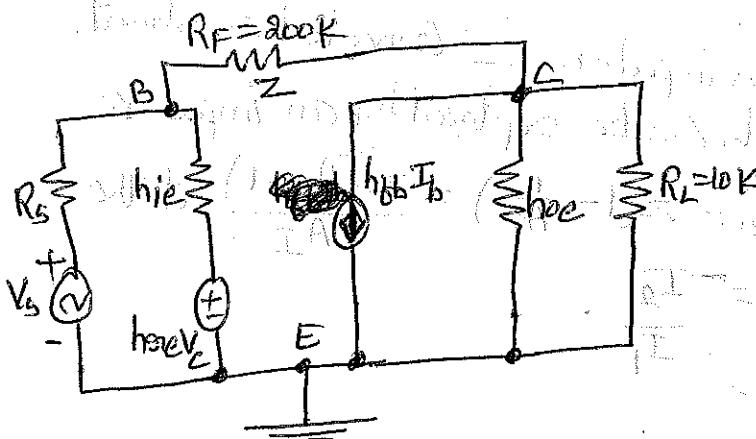

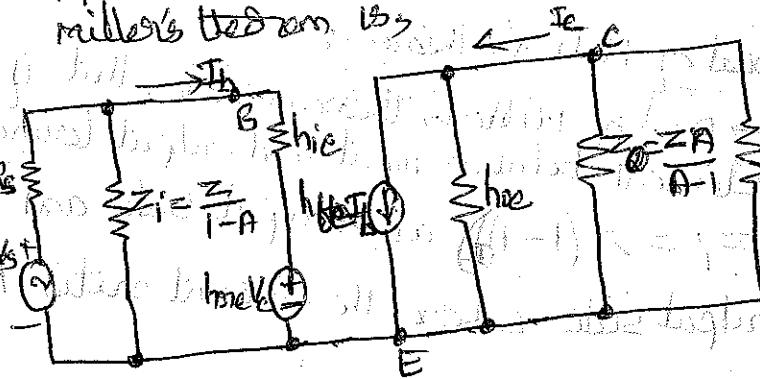h-parameter equivalent circuit using Miller's theorem is,



$$Z_0 = \frac{Z \cdot A}{A-1} \quad \text{If } A \gg 1 \text{ then } Z_0 = Z = 200\text{ k}\Omega$$

$$A_i' = -\frac{h_{fe}}{1 + h_{fe} R_L} \quad \text{where } R_L' = R_L \parallel Z_0 = 10k \parallel 200k = 9.52k\Omega$$

$$A_i = \frac{-50}{1 + 25 \times 10^{-6} \times 9.52 \times 10^3} = -40.3$$

$$R_p = h_{ie} + h_{oe} A_i R_L' = 1.1 \times 10^3 + 9.5 \times 10^{-4} \times 9.52 \times 10^3 \times (-40.3) = 1004 \Omega$$

$$A_V = \frac{A_i R_L'}{R_i} = \frac{-40.3 \times 9.52 \times 10^3}{1004} = -382.13$$

$\therefore A_V > 1$  is justified

$$\therefore Z_i = \frac{Z}{1-A} = \frac{200 \times 10^3}{1+382.13} = 5.22 \Omega$$

$$R_i' = R_i \parallel Z_i = 1004 \parallel 5.22 = 343.44 \Omega$$



Analysis of Common Emitter amplifier with an Emitter resistance using dual of Miller theorem

→ whenever the gain provided by a single stage amplifier is not sufficient, it is necessary to cascade the no. of stages of the amplifier.



→ In such situations it becomes important to stabilize the voltage amplification of each stage because instability of the first stage is amplified in the second stage and it is further amplified in the next. This is not desired.

→ The simple and effective way to obtain voltage gain stabilization is to add an emitter resistance  $R_E$  to a CE stage as shown in figure. The presence of emitter resistance has no. of better effects on the amplifier performance.

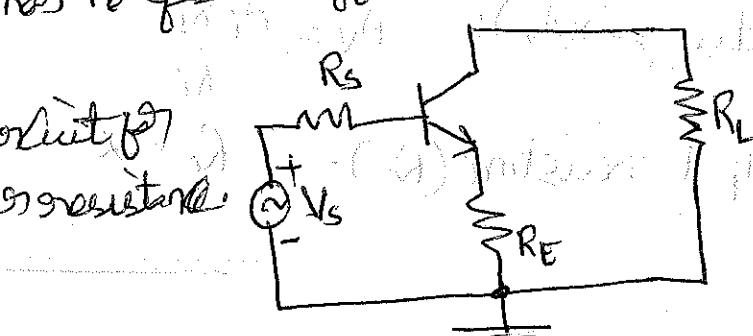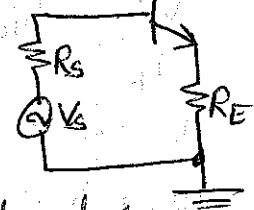→ Figure shows an ac equivalent circuit for CE circuit with unbypassed emitter resistance.



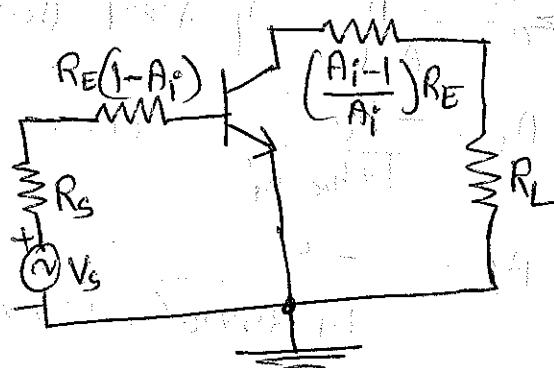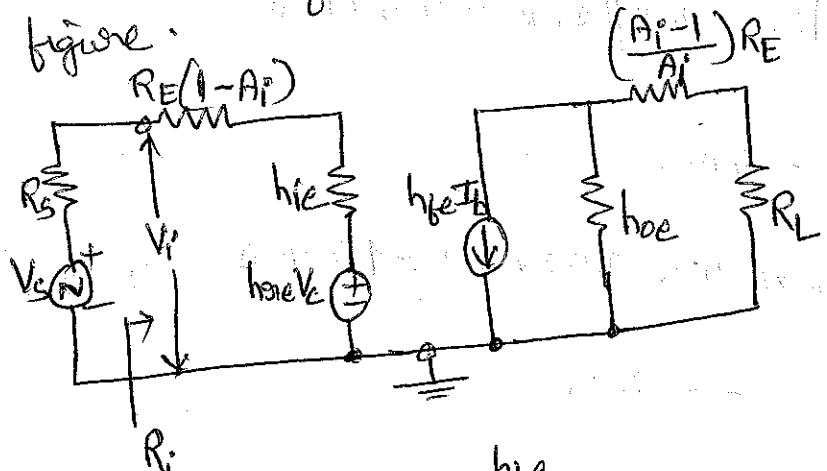→ To make the analysis of CE amplifier with  $R_E$  we use dual of Miller's theorem as shown in figure.



$$\text{Current gain: } A_i = \frac{-h_{fe}}{1 + h_{oe} R_L} = \frac{-h_{fe}}{1 + h_{oe} [R_L + \left(\frac{A_i - 1}{A_i}\right) R_E]}$$

$$A_i + A_i h_{oe} R_L + A_i h_{oe} R_E - h_{oe} R_E = -h_{fe}$$

$$A_i [1 + h_{oe} (R_L + R_E)] = h_{oe} R_E - h_{fe}$$

$$A_i = \frac{h_{oe} R_E - h_{fe}}{1 + h_{oe} (R_L + R_E)}$$

Input Resistance ( $R_i$ ):


$$R_i = \frac{V_i}{I_b} = h_{ie} + h_{oe} A_i R_L'$$

From the figure the resistance  $R_E(1-A_i)$  is in series with  $h_{ie}$  and  $R_L'$  is in parallel with  $h_{oe}$ .


$$R_L + \left(\frac{A_i - 1}{A_i}\right) R_E$$

$$\therefore R_i = (1 - A_i) R_E + h_{ie} + h_{oe} A_i R_L'$$

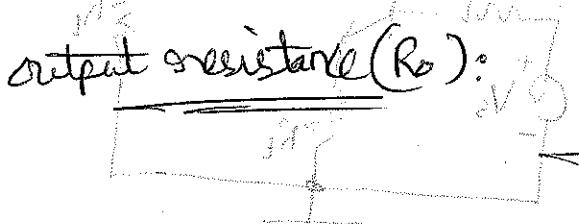Voltage gain ( $A_v$ ):  $A_v = \frac{A_i R_L'}{R_i}$



$$Ro = \frac{V_{out}}{I_{out}}$$

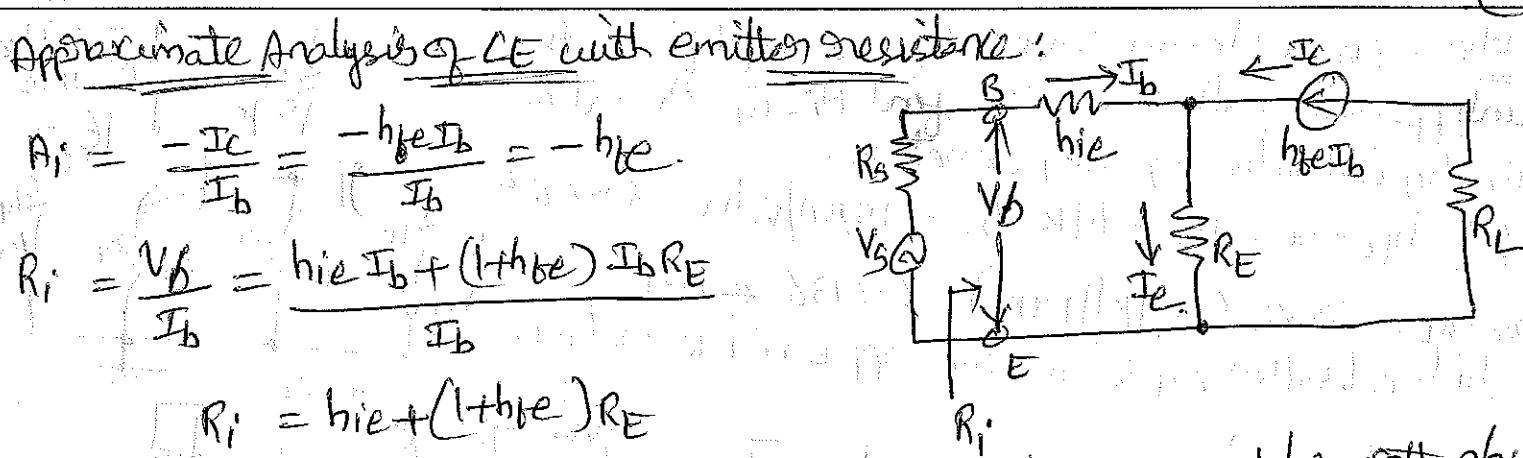

The input resistance due to factor  $(1+h_{fe})R_E$  may be very much larger than  $h_{ie}$ . Hence an emitter resistance greatly increases the input resistance.

$$A_v = \frac{A_i R_L}{R_i} = \frac{-h_{fe} R_L}{h_{ie} + (1+h_{fe})R_E}$$

Output Resistance ( $R_o$ ): It is the resistance of an amplifier without output resistance ( $R_o$ ). It is defined as a ratio of output Voltage  $V_o$  to output Current with  $V_s=0$ .

$$\therefore R_o = \frac{V_o}{I_o} \quad | V_s = 0$$

When  $V_s = 0$ , the current through the input loop  $I_b = 0$ , hence  $I_c$  and  $I_E$  both are zero. Therefore  $R_o = \infty$ .

The output resistance  $R'_o$  of the stage taking the load into account is given as,  $R'_o = R_o // R_L = \infty // R_L = R_L$ .

---

Prob 0: figure shows a single stage CE amplifier with unbypassed emitter resistor, find  $A_i$ ,  $R_i$ ,  $A_v$  and  $R_o$ . use typical values of h-parameter.

Soln:  $h_{fe} = 50$ ,  $h_{ie} = 1.1K$ ,  $h_{oe} = 25 \mu A/V$ ,  $h_{me} = 2.5 \times 10^{-4}$

$$h_{oe} \cdot R_E = 25 \times 10^{-6} \times (1K || 1.2K) = 0.0136$$

which is less than 0.1 so we use approximate analysis.

$$A_i = -h_{fe} = -50$$



$$R_i = \frac{V_i}{I_b} = h_{ie} + (1+h_{fe}) R_E \\ = 1.1K + (1+50) \times 270$$

$$R_i = 14.87K$$

$$A_v = \frac{A_i R_L}{R_o} = \frac{-50 \times (1.2K || 1K)}{14.87K} = -1.834$$

$$R_i' = R_i || R_1 || R_2 = 14.87K || 2K || 50K = 1.7K$$

$$R_o' = R_o || R_C || R_L = \infty || 1K || 1.2K = 545.45 \Omega$$

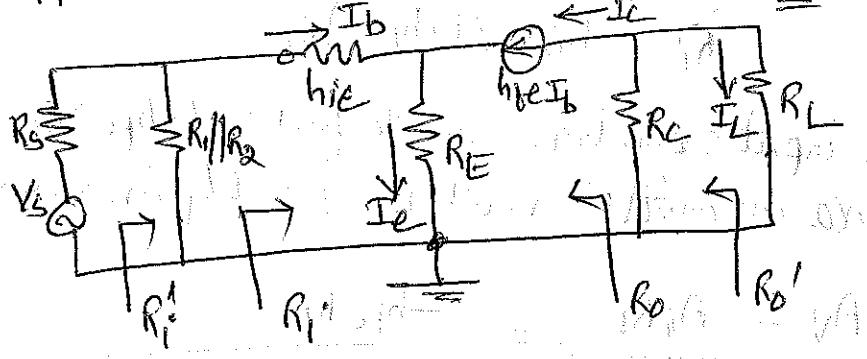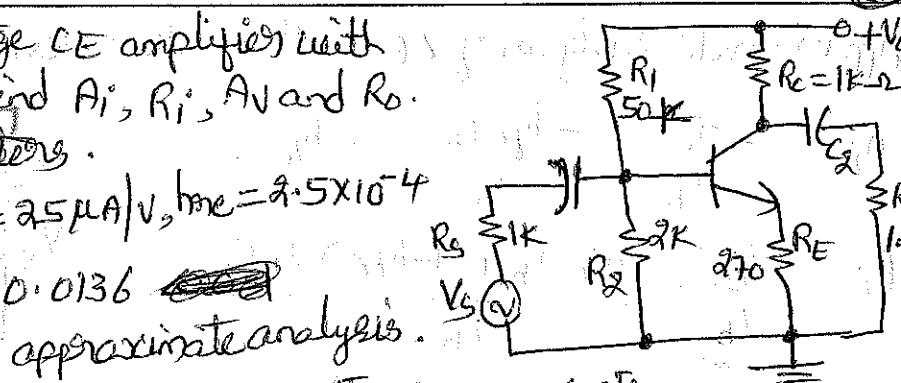

## 1/

### Design of Single Stage RC Coupled Amplifier using BJT












- A single stage RC Coupled CE amplifier can be employed as a small signal amplifier but a circuit with two cascaded stage gives large amplification.
- The design of resistor values involves application of ohm's law after selecting suitable Voltage and Current levels throughout the Circuit.
- The design of capacitor values are based on the lower cut-off frequency of the circuit and the resistance which is in series with the capacitor.
- In this circuit, the biasing is provided by three resistors  $R_1$ ,  $R_2$  and  $R_E$ . The resistors  $R_1$  and  $R_2$  act as a potential divider giving a fixed voltage to the base.
- If the collector current increases due to change in temperature or change in  $I_E$ , then the emitter current  $I_E$  also increases, reducing the voltage difference between base and emitter  $V_{BE}$ .
- Due to reduction in  $V_{BE}$ ,  $I_B$  and hence  $I_C$  also reduces. Negative feedback acts in emitter bias circuit.
- This reduction in collector current  $I_C$  compensated for the original change in

$I_C$ :

#### Design of $R_C$ and $R_E$ :

- The design of single stage RC Coupled amplifier is based on the specifications like Supply Voltage, minimum voltage gain, frequency response, source impedance and load impedance.
  - The circuit has no provision for negative feedback because of bypass capacitor  $C_E$  and hence it is designed to achieve the largest possible gain. The voltage gain of a CE amplifier circuit is given by,
- $$A_V = \frac{-h_{FE} (R_C // R_L)}{h_{IE}}$$
- since  $A_V$  is directly proportional to  $R_C // R_L$ , the design for large voltage gain requires selection of the largest possible collector resistance.
  - But a large value of  $R_C$  needs the collector current to be small for satisfactory operation of transistor.

$g + V_{CO}$

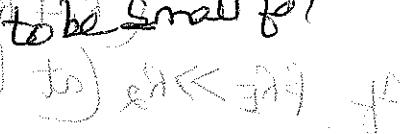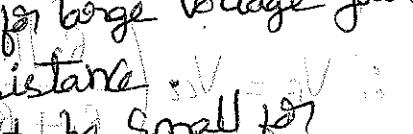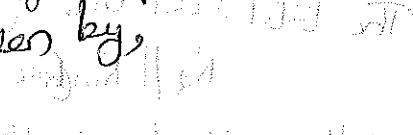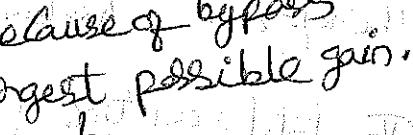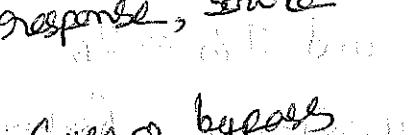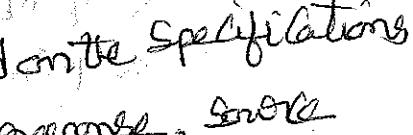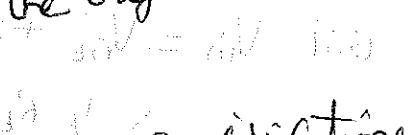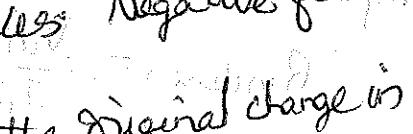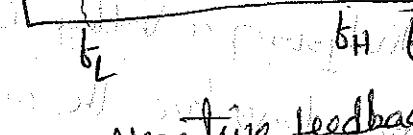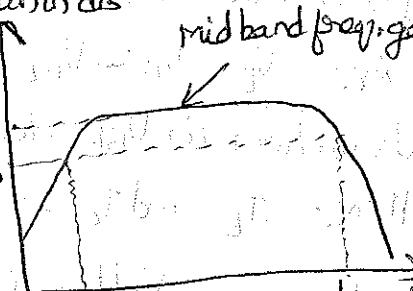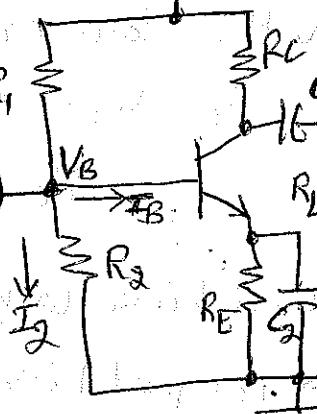

→ The value of collector resistance  $R_C$  can be determined by applying Kirchhoff's Voltage law around the collector-emitter circuit.

$$\text{i.e. } V_{CE} = I_C R_C + V_{CE} + V_E$$

$$\Rightarrow R_C = \frac{V_{CE} - V_E}{I_C} \quad \text{where } V_E = I_E R_E \Rightarrow R_E = \frac{V_E}{I_E} \approx \frac{V_E}{I_C}$$

To achieve larger value of  $R_C$ , let us assume  $V_{CE} = \frac{V_{CC}}{2}$  and  $V_E = \frac{V_{CC}}{10}$ .

→ For good bias stability, the emitter resistor voltage drop  $V_E$  should be greater than the base-emitter voltage  $V_{BE}$  i.e.  $V_E > V_{BE}$ .

Since  $V_E = V_B - V_{BE}$ , the emitter voltage  $V_E$  will be slightly affected by the variation in  $V_{BE}$  due to change in temperature.

Hence  $I_E$  and  $I_C$  remain stable at  $\frac{V_E}{R_E} = \frac{V_E}{I_E}$ .

Analysis of a Voltage Divider Bias Circuit:

By ohm's law the input resistance at the transistor base is

$$R_{in(base)} = \frac{V_{in}}{I_{in}}$$

$$\text{But } V_{in} = V_{BE} + I_E R_E = V_B$$

since  $V_{BE} \ll I_E R_E$

$$\approx I_E R_E$$

$$\text{since } I_E \approx I_C = \beta I_B$$

$$\approx \beta I_B R_E$$

$$\text{and } I_{in} = I_B$$

$$R_{in(base)} = \frac{V_{in}}{I_{in}} = \frac{\beta I_B R_E}{I_B} \approx \beta R_E$$

Therefore,  $R_{in(base)} = \frac{V_{in}}{I_{in}} = \frac{\beta I_B R_E}{I_B} \approx \beta R_E$

The total resistance from base to ground is,  $R_2 \parallel R_{in(base)}$

$$R_2 \parallel R_{in(base)} \approx R_2 \parallel \beta R_E$$

A voltage divider is formed by  $R_1$  and the resistance from base to ground,  $\beta R_E$  in parallel with  $R_2$ .

$$\therefore V_B = V_{CC} \left( \frac{R_2 \parallel \beta R_E}{R_1 + R_2 \parallel \beta R_E} \right)$$

If  $\beta R_E \gg R_2$  (at least 10 times greater), then it results in

$$V_B = V_{CC} \left( \frac{R_2}{R_1 + R_2} \right)$$

### Design of Bias Resistors:

The Voltage divider Current  $I_2$  is selected as  $\frac{I_C}{10}$  which results in good bias stability and high input resistance.

Hence the bias resistors are calculated as,

$$R_2 = \frac{V_B}{I_2} \text{ and } R_1 = \frac{V_{CC} - V_B}{I_2} \text{ where } V_B = V_E + V_{BE} \quad (8) \quad V_B = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC}$$

### Design of Bypass and Coupling Capacitors:

Always the bypass capacitor across the emitter resistor is used to filter the signal variations at the emitter with respect to ground.

Therefore the reactance offered by this capacitor should be low for high frequencies but high for dc and nearby low frequencies.

$$X_{CE} = \frac{1}{2\pi f C_E}$$

where  $X_{CE}$  should be high for dc and very low frequency signals and low for high frequencies.

$$C_E = \frac{1}{2\pi f X_{CE}}$$

where  $C_E$  should be high for high frequencies starting from 100Hz.

Therefore  $X_{CE}$  can be fixed at one-tenth of  $R_E$ .

All capacitors should be selected to have the smallest possible capacitance value mainly to minimize the physical size of the circuit.

Each capacitor has its highest impedance at the lowest operating frequency and it is calculated based on the lower cut-off frequency.

The bypass capacitor  $C_E$  is normally the largest capacitor in the circuit.

The Voltage gain for CE circuit with unbypassed emitter resistance given by,

$$A_V = \frac{-h_{FE}(R_L || R_E)}{h_{IE} + R_E(1+h_{FE})}$$

By including the bypass capacitor in parallel with  $R_E$  the Voltage gain is given by,

$$-h_{FE}(R_L || R_E)$$

$$A_V = \frac{-h_{FE}(R_L || R_E)}{h_{IE} + (1+h_{FE})(R_E || X_{CE})}$$

Normally  $R_E > X_{CE}$  so  $R_E$  can be neglected and also  $X_{CE}$  is capacitive reactance.

$$\text{Hence, } |AV| = \frac{+h_{fe}(R_C/R_L)}{\sqrt{h_{ie}^2 + [(1+h_{fe})X_{CE}]^2}}$$

$$\text{when } h_{ie} = (1+h_{fe})X_{CE}$$

$$|AV| = \frac{+h_{fe}(R_C/R_L)}{h_{ie}\sqrt{1^2 + 1^2}} = \frac{A_{Vm}}{(\sqrt{2})}$$

where  $A_{Vm}$  is the mid frequency gain.

Therefore at lower cut-off frequency  $f_L$ ,

$$h_{ie} = (1+h_{fe})X_{CE}$$

$$\text{Hence, } X_{CE} = \frac{h_{ie}}{1+h_{fe}} = h_{ib}$$

$$\therefore C_E = \frac{1}{2\pi f_L X_{CE}} = \frac{1}{2\pi f_L h_{ib}}$$

→ The Coupling Capacitors  $C_1$  and  $C_2$  have negligible effect on the frequency response of the amplifier circuit and to minimize the effects of these capacitors, the reactance of each coupling capacitor is selected to be approximately equal to one-tenth of the impedance in series with it at the lower cut-off frequency  $f_L$ .

→ These capacitances can be determined from the equations given by,

$$C_1 = \frac{1}{2\pi f_L X_1} \text{ where } X_1 = \frac{Z_i}{10} = \frac{(R_i // R_L // h_{ie})}{10}$$

$$\text{and } C_2 = \frac{1}{2\pi f_L X_2} \text{ where } X_2 = \frac{Z_o}{10} = \frac{R_o // R_L}{10}$$

$$\text{imp. input } \frac{(s+D)j\omega + j\omega}{(s+D)j\omega - j\omega}$$

$$(s+D)j\omega -$$

$$(s+D)(s+D)j\omega + sD$$

prob 0: Design a single stage RC Coupled BJT amplifier circuit. Assume that  $V_{CC} = 10V$ ,  $I_C = 4mA$ ,  $h_{FE} = 100$ ,  $h_{ie} = 1K\Omega$ ,  $R_L = 100k\Omega$  and  $f_L \leq 100$  Hz.

Soln: ① To determine  $R_1$ ,  $R_2$ ,  $R_E$  &  $R_E$ :

$$V_E = \frac{V_{CC}}{10} = \frac{10}{10} = 1V, V_{CE} = \frac{V_{CC}}{2} = 5V$$

$$R_E = \frac{V_{CE} - V_{CE} - V_E}{I_C} = \frac{10 - 5 - 1}{4 \times 10^{-3}} = 1K\Omega$$

$$V_E = I_E R_E \approx I_C R_E$$

$$\therefore R_E = \frac{V_E}{I_C} = \frac{1}{4 \times 10^{-3}} = 250\Omega$$

$$V_B = V_{BE} + V_E = 0.7 + 1 = 1.7V$$

$$V_B = \left( \frac{R_2}{R_1 + R_2} \right) V_{CC} \Rightarrow \frac{R_2}{R_1 + R_2} = \frac{V_B}{V_{CC}} = \frac{1.7}{10} = 0.17$$

$$R_2 = 0.17(R_1 + R_2)$$

$$5.88 R_2 = R_1 + R_2$$

$$4.88 R_2 = R_1 \Rightarrow R_1 = 19.52 K\Omega \approx 20 K\Omega$$

The value of  $R_2$  can be selected to satisfy  $R_E > R_2$ . Hence  $R_2$  is selected as  $2K\Omega$ . Therefore  $R_1 = 9.76 K\Omega \approx 10 K\Omega$ .

② To determine the bypass capacitor  $C_E$ :

$$X_{LE} = \frac{h_{ie}}{1+h_{fe}} = \frac{1 \times 10^3}{1+100} = 9.9$$

$$C_E = \frac{1}{2\pi f_L X_{LE}} = \frac{1}{2\pi \times 100 \times 9.9} = \frac{1}{6217.2} = 160.8 \mu F$$

③ To determine coupling capacitors  $C_1$  and  $C_2$ :

$$X_{C_1} = \frac{Z_i}{10} = \frac{R_1 || R_2 || h_{ie}}{10} = 246.154$$

$$C_1 = \frac{1}{2\pi f_L X_{C_1}} = 6.47 \mu F$$

$$X_{C_1} = \frac{R_1 || R_2 || h_{ie}}{10} = \frac{3.3K || 1K}{10} = \frac{767.1}{10} = 76.71$$

$$C_1 = \frac{1}{2\pi f_L X_{C_1}} = \frac{1}{2 \times 10^{-5} \times 76.71} = 0.2 \mu F$$

$$X_C2 = \frac{Z_0}{10} = \frac{R_C || R_L}{10} = 99.00$$

$$C_2 = \frac{1}{2\pi f_L X_{C2}} = 0.1602 \mu F$$

Conversion formulae for hybrid parameters:

CC	CB
$h_{ie} = h_{ic}$	$h_{ib} = \frac{h_{ie}}{1+h_{fe}}$
$h_{oc} = 1$	$h_{ob} = \frac{h_{ie}h_{oe}}{1+h_{fe}} - h_{oe}$
$h_{fc} = - (1+h_{fe})$	$h_{fb} = \frac{-h_{fe}}{1+h_{fe}}$
$h_{ac} = h_{oe}$	$h_{ob} = \frac{h_{oe}}{1+h_{fe}}$

# UNIT - I JNTUH Previous Question Papers Solved.

1-16

- 1) The hybrid parameters for a transistor used in CE Configuration are  $h_{ie} = 1K\Omega$ ,  $h_{fe} = 150$ ,  $h_{oe} = 25 \times 10^{-6}$ . The transistor has a load resistance of  $10K\Omega$  in the collector and is supplied from a signal source of resistance  $5K\Omega$ . Compute the values of input impedance, output impedance, current gain and voltage gain.

Dec' 2013 7

Sol:

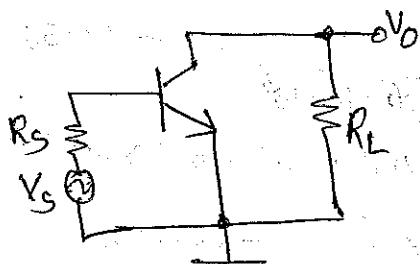
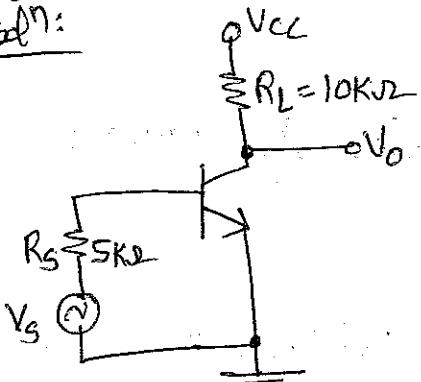


Fig: AC equivalent ckt.

$$A_i = \frac{I_o}{I_i} = -\frac{h_{fe} I_b}{I_b} = -h_{fe} = -150$$

$$R_o = \infty \quad \left\{ \begin{array}{l} V_s = 0, I_b = 0, I_c = 0 \\ \Rightarrow R_o = \frac{V_o}{I_c} = \infty \end{array} \right.$$

$$R_i = \frac{V_i}{I_i} = \frac{h_{ie} I_b}{I_b} = h_{ie} = 1K\Omega$$

$$A_v = \frac{V_o}{V_i} = -\frac{h_{fe} I_b R_L}{h_{ie} I_b} = -\frac{h_{fe} R_L}{h_{ie}} = -\frac{150 \times 10 \times 10^3}{1 \times 10^3} = -1500$$

- a) For the Circuit shown in figure estimate  $A_i$ ,  $A_v$ ,  $R_i$  &  $R_o$  using reasonable approximations. The h-parameters for the transistor are given as  $h_{fe} = 100$ ,  $h_{ie} = 2K\Omega$ ,  $h_{oe}$  is negligible  $\Rightarrow h_{oe} = 10^{-5} \text{ mhos}$ .

Sol:

$$h_{oe} \times R'_L = h_{oe} (R_C || R_L) = 10^{-5} \times (2K || 1K) = 0.666 \times 10^{-2} < 0.1$$

so use approximate analysis.


$$A_i = -h_{fe} \frac{R_A}{R_B + h_{ie}}, \quad R_B = R_1 || R_2 = 100K || 100 = 99.9\Omega$$

$$A_i = -\frac{100 \times 99.9}{99.9 + 2 \times 10^3} = -4.76$$

$$R_i = R_A || h_{ie} = (99.9 || 2K) \Omega = 95.14 \Omega$$

$$A_v = -\frac{h_{fe} (R_C || R_L)}{h_{ie}} = -\frac{100 \times (2K || 1K)}{2 \times 10^3} = -33.3$$

$$R_o = \infty$$

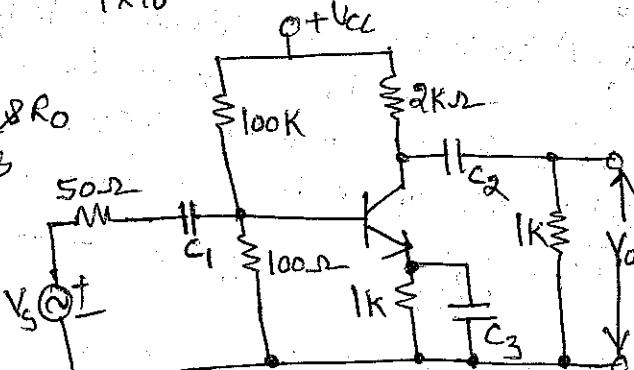

May' 2012 8M

- 3) Draw the circuit diagram of Emitter follower, and derive the equation for  $A_v$  &  $A_i$ .

May' 2012 7M

- 4) Draw the simplified hybrid model for the CC Circuit and derive expressions for  $R_i$ ,  $R_o$ ,  $A_v$  and  $A_i$ .

May' 2012 8M

5) State and prove dual of Miller's theorem. [May'2012] 7M

6) For a CE amplifier calculate  $A_v$ ,  $R_i$ ,  $R_o$  and  $A_i$  if  $R_L = 10k\Omega$ ,  $h_{ie} = 1.1k\Omega$ ,  $h_{oe} = 2.5 \times 10^{-4}$ ,  $h_{fe} = 50$  and  $h_{fb} = 24 \mu A/V$ . [May'2012] 8M

Soln:  $h_{oe} \times R_L = 24 \times 10^{-6} \times 10 \times 10^3 = 0.24 > 0.1$   
So use exact analysis.

$$A_i = \frac{-h_{fe}}{1+h_{oe}R_L} = \frac{-50}{1+24 \times 10^{-6} \times 10 \times 10^3} = -40.32$$

$$R_i = h_{ie} + h_{oe} A_i R_L = 1.1 \times 10^3 + 2.5 \times 10^{-4} \times (-40.32) \times 10 \times 10^3 = 999.2 \Omega$$

$$A_v = \frac{A_i R_L}{R_i} = \frac{-40.32 \times 10 \times 10^3}{999.2} = -403.52$$

$$Y_o = h_{oe} - \frac{h_{fe} h_{oe}}{h_{ie} + R_o} = 24 \times 10^{-6} - \frac{50 \times 2.5 \times 10^{-4}}{1.1 \times 10^3 + 0} = 12.64 \times 10^{-6}$$

$$R_o = \frac{1}{Y_o} = 79.11 k\Omega$$

7) Draw the CE amplifier with unbypassed emitter resistance and derive expressions for  $R_i \propto A_v$ .

8) A transistor in CB circuit has the following set of h-parameters  $h_{ib} = 20 \Omega$ ,  $h_{fb} = -0.98$ ,  $h_{mb} = 3 \times 10^{-4}$ ,  $h_{ob} = 0.5 \mu A/V$ . Find the values of  $R_i$ ,  $R_o$ ,  $A_i$  &  $A_v$  if  $R_s = 600 \Omega$  and  $R_L = 1.5 k\Omega$ . [Jan'2012] 8M

Soln: Use approximate analysis.

$$A_i = \frac{h_{fe}}{1+h_{fe}} = -h_{fb} = -(-0.98) = 0.98$$


$$R_o = \infty$$

$$R_i = h_{ie} = h_{ib} = 20 \Omega$$

$$A_v = \frac{A_i R_L}{R_i} = \frac{0.98 \times 1.5 \times 10^3}{20} = 73.5$$

9) Consider an emitter follower and show that as  $R_e \rightarrow \infty$ ,  $R_i = h_{ie} + \frac{1+h_{fe}}{h_{oe}}$ . [Jan'2012] 7M

Soln:

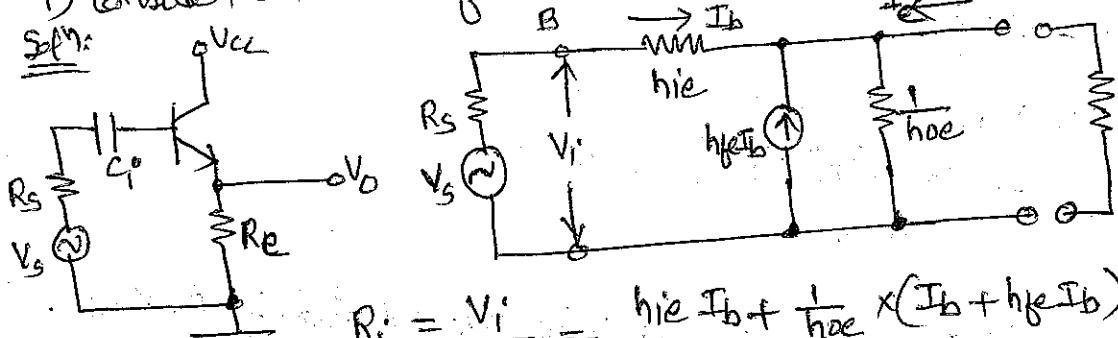

$$R_i = \frac{V_i}{I_i} = \frac{h_{ie} I_b + \frac{1}{h_{oe}} \times (I_b + h_{fe} I_b)}{I_b}$$

$$R_i = h_{ie} + \frac{(1+h_{fe})}{h_{oe}}$$

10) State Miller's theorem and its dual. [Jan'2012] 8M.

11) For the Circuit shown in figure estimate  $A_V$  and  $R_i$ . Assume  $\frac{1}{h_{oe}}$  is large compared with load seen by the transistor. All capacitors have negligible reactance at the test frequency,  $h_{ie} = 1K\Omega$ ,  $h_{fe} = 99$  and  $h_{re}$  is negligible.

$$\text{Solt: } R_i = (R_1 || R_2) + h_{ie} = (60K || 30K) + 1K = 21K\Omega$$

$$A_V = \frac{A_i Z_L}{Z_i} \quad A_i = -h_{fe} = -99$$

$$Z_L = R_C || R_L = (5K || 20K) \Omega = 4K\Omega$$

$$Z_i = R_i$$

$$\therefore A_V = \frac{-99 \times 4 \times 10^3}{21 \times 10^3} = -18.86$$


11) For the CB amplifier circuit shown, compute  $R_i$  and  $R_o$  if  $C_1$  is

(a) Connected (b) Not Connected.

The  $h$ -parameters are  $h_{ie} = 2.1K\Omega$ ,  $h_{fe} = 81$ ,  $h_{oe} = 1.66 \mu\text{mho}$ ,  $h_{re}$  negligible.


$$\text{Solt: } h_{oe} \times R'_i = h_{oe} \times (R_C || R_L) = 1.66 \times 10^{-6} \times (2.2K || 12K) \\ = 3.08 \times 10^{-3} < 0.1$$

[Jan'2012] 8M

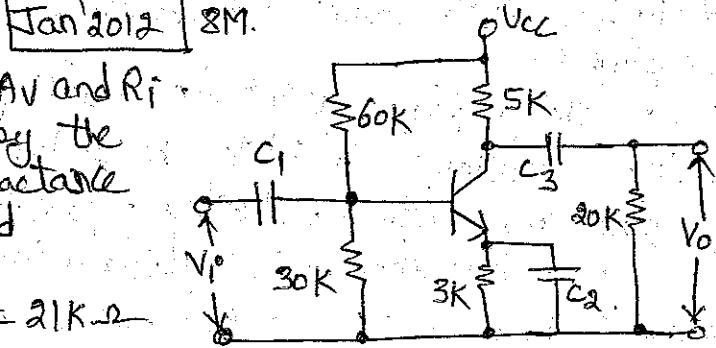

So we use approximate analysis.

(a)  $C_1$  is connected:

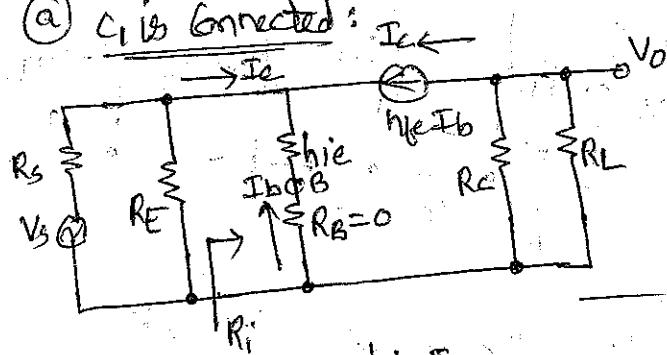


$$R_i = \frac{V_i}{I_i}; \quad V_i = -h_{ie} I_b \\ I_i = I_e \\ I_i = -(1+hfe) I_b$$

$$R_i = \frac{-h_{ie} I_b}{-(1+hfe) I_b}$$

$$R_i = \frac{h_{ie}}{1+hfe} = \frac{2.1 \times 10^3}{1+81}$$

$$R_i = 25.6 \Omega$$

(b)  $C_1$  is not connected:

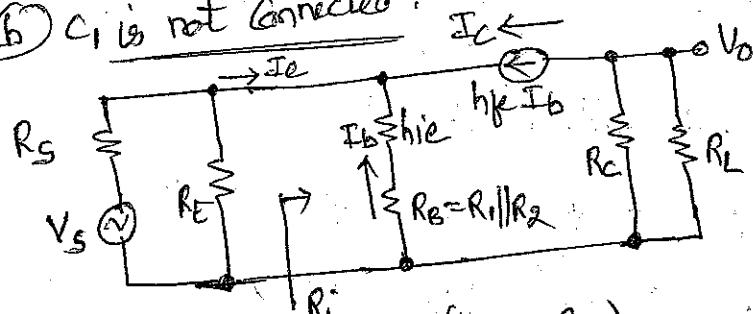

$$R_i = \frac{V_i}{I_i}; \quad V_i = -I_b(h_{ie} + R_B) \\ I_i = I_e = -(1+hfe) I_b \\ \therefore R_i = \frac{-I_b(h_{ie} + R_B)}{-(1+hfe) I_b} = \frac{h_{ie} + (R_B || R_L)}{1+hfe}$$

$$\therefore R_i = \frac{2.1 \times 10^3 + (60K || 10K)}{1+81}$$

$$R_i = 135.4 \Omega$$

$R_o = \infty$  in both the cases.


12) Reason out the causes and results of phase & frequency distortions in transistor amplifiers.

13) For the amplifier circuit shown with partially unbypassed emitter resistance, calculate the Voltage gain with  $R_4$  in place and with  $R_4$  shorted. Consider  $h_{ie} = 1.1K\Omega$ ,  $h_{fe} = 100$ ,  $h_{oe}$  &  $h_{ce}$  are negligibly small.

Assume  $R_i = 100K\Omega$  &  $R_o = 22K\Omega$ .

Sol'n:

Case(i) with  $R_4$  in place

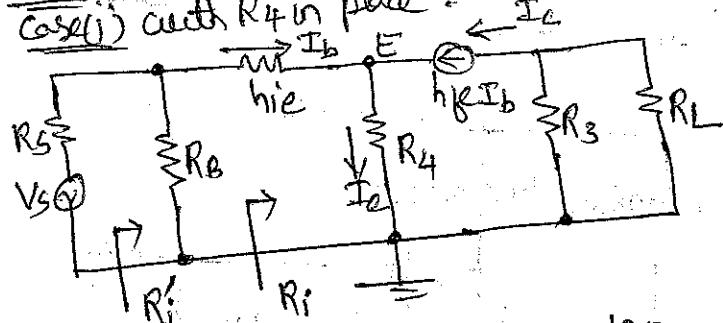

$$A_i = \frac{-h_{fe} I_b}{I_b} = -h_{fe} = -100$$

$$R_i = h_{ie} I_b + R_4 (1+h_{fe}) I_b = h_{ie} + (1+h_{fe}) R_4 = 1.1 \times 10^3 + (1+100) \times 82 = 9.382 K\Omega$$

$$A_v = \frac{A_i Z_L}{Z_i} \quad Z_L = R_3 // R_L = 1K // 10K = 909.09 \Omega$$

$$A_v = \frac{-100 \times 909.09}{6.1 \times 10^3} = -14.9$$

Case(ii) with  $R_4$  shorted

$$A_i = \frac{-h_{fe} I_b}{I_b} = -h_{fe} = -100$$

$$R_i = h_{ie} I_b = h_{ie} = 1.1K\Omega$$


$$Z_L = R_3 // R_L = 909.09 \Omega$$

$$Z_i = R_i // R_1 // R_2 = (1.1K // 100K // 22K) \Omega = 1.036 K\Omega$$


$$A_v = \frac{-100 \times 909.09}{1.036 \times 10^3} = -87.74$$

14). Analyse what the output voltage should be if the dc power supply given to a CE amplifier is shorted to ground.

May'2011 6M

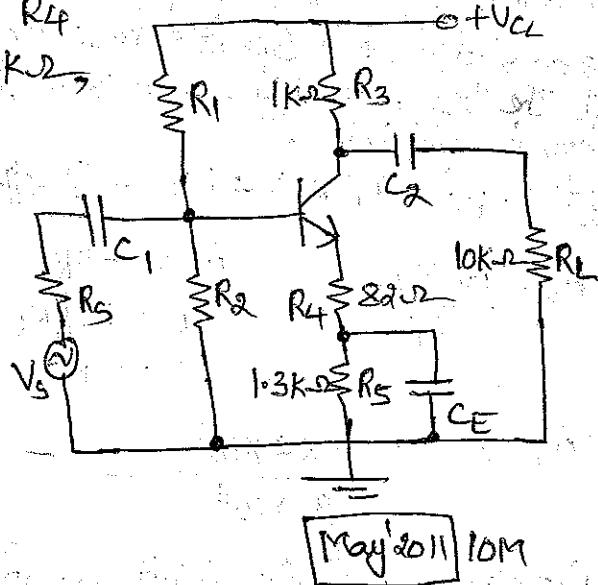

May'2011 10M

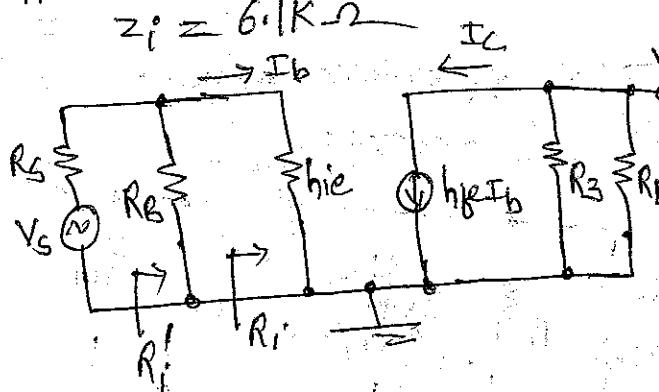

May'2011 5M

1-8

15) For the CE amplifier shown determine the peak-to-peak output voltage for sinusoidal input voltage of 30mV peak-to-peak.

Assume  $C_1, C_2$  and  $C_3$  are large enough to act as short circuit at the input frequency. Consider  $h_{ie} = 1.1K\Omega$  &  $h_{fe} = 100$ .


$$\text{Soln: } A_V = \frac{V_o}{V_i} \Rightarrow V_o = A_V \cdot V_i$$

$$A_V = -\frac{h_{fe} Z_L}{Z_i} ; \quad Z_L = R_C // R_L = 2.2K // 1.2K = 1.86K\Omega$$

$$Z_i = h_{ie} // R_1 // R_2 = 1.1K // 90K // 10K = 980.2\Omega$$

$$A_V = -\frac{100 \times 1.86 \times 10^3}{980.2} = -189.7$$

$$V_o = |A_V| \cdot V_i = 189.7 \times 30 \times 10^{-3} = 5.691 \text{ V peak-to-peak.}$$

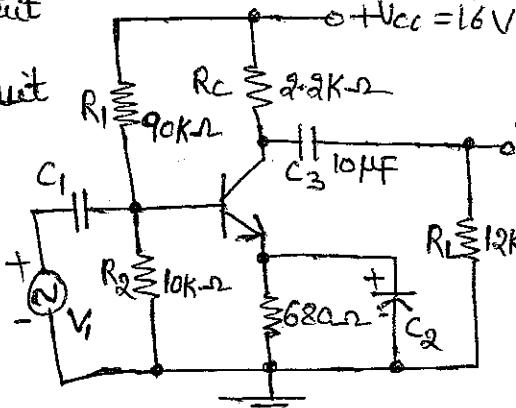

May'2011 7M

16) State Miller's theorem. Specify its relevance in the analysis of a BJT amplifier. May'2011 4

17) Write expressions for  $A_V$  and  $R_i$  of a CE amplifier. May'2011 4M

18) Draw the circuit diagram of a CC amplifier along with its equivalent circuit. May'2011 7

Derive expressions for  $A_V$  and  $R_i$ . May'2011 4M

19) What is meant by small signal for analysing a BJT based amplifier? May'2011 4M

What is non-linear distortion? List the causes for this type of distortion in amplifiers. May'2011 4

