

II B.Tech I Semester Examinations, May/June 2012

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) Draw the circuit diagram of discrete-component regenerative comparator.
(b) Draw the transfer characteristic showing hysteresis. [16]
2. (a) What is meant by linear wave shaping
(b) A pulse of amplitude 5V and duration $20\mu\text{sec}$ is applied to high pass RC circuit having $R=10\text{K}\Omega$ and $C=1000\text{pf}$. calculate the output amplitude and sketch the o/p wave form.
(c) Draw the response of low pass RC circuit for ramp i/p signal. [2+10+4]
3. (a) In a current sweep circuit, explain how linearity correction is made through adjustment of driving waveform.
(b) Write the basic mechanism of transistor television sweep circuit. [16]
4. (a) For the circuit shown in figure 1 an input voltage V_i linearly from 0 to 150V is applied. Sketch the output waveform V_o to the same time scale. Assume ideal diodes.

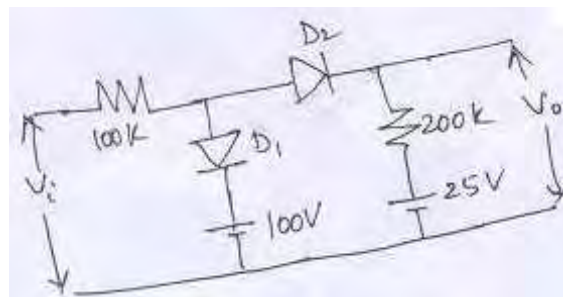


Figure 1

- (b) What is meant by a d.c restoration circuit and explain? [12+4]
5. (a) Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
(b) Draw the output waveform X for the given inputs shown in figure 2.

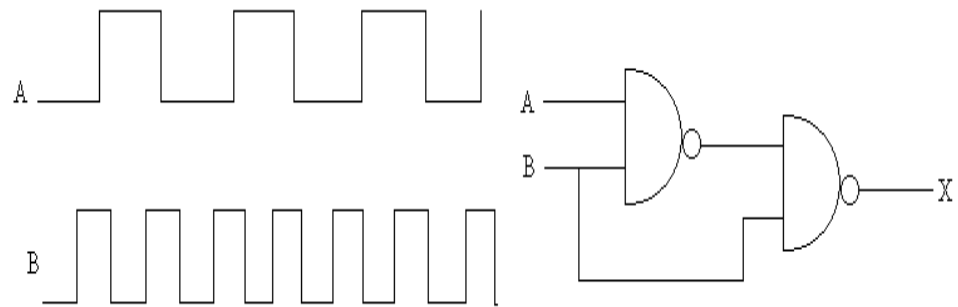


Figure 2

6. (a) What are the applications of sampling gates?
 (b) What are the advantages and disadvantages of unidirectional diode gate?
 (c) Discuss the operation of the four diode bi-directional sampling gate. [4+4+8]
7. (a) With the help of a circuit diagram and waveforms explain frequency division of monostable multivibrator with pulse signals.
 (b) A symmetrical astable multivibrator using germanium transistors and operating from a 10V collector supply voltage has a free period of $1000 \mu\text{sec}$. Triggering pulses whose spacing is $750 \mu\text{sec}$ are applied to one base through a small capacitor from a high impedance source. Find the minimum triggering pulse amplitude required to achieve 1 : 1 synchronization. Assume typical junction voltage of the transistor and that the timing portion of the base waveform is linear. [16]
8. (a) Explain the reverse recovery of a semiconductor diode. How does the recovery time place a limitation on the diode speed?
 (b) Write short notes on the switching times of a transistor. [8+8]

II B.Tech I Semester Examinations, May/June 2012

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- In a current sweep circuit, explain how linearity correction is made through adjustment of driving waveform.
 - Write the basic mechanism of transistor television sweep circuit. [16]
- What is meant by linear wave shaping
 - A pulse of amplitude 5V and duration $20\mu\text{sec}$ is applied to high pass RC circuit having $R=10\text{K}\Omega$ and $C=1000\text{pf}$. calculate the output amplitude and sketch the o/p wave form.
 - Draw the response of low pass RC circuit for ramp i/p signal. [2+10+4]
- Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
 - Draw the output waveform X for the given inputs shown in figure 3.

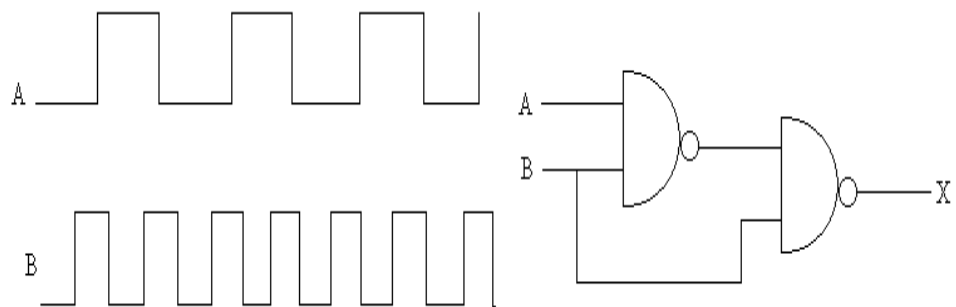


Figure 3

- Explain the reverse recovery of a semiconductor diode. How does the recovery time place a limitation on the diode speed? [8+8]
 - Write short notes on the switching times of a transistor. [8+8]
- Draw the circuit diagram of discrete-component regenerative comparator.
 - Draw the transfer characteristic showing hysteresis. [16]
- What are the applications of sampling gates?
 - What are the advantages and disadvantages of unidirectional diode gate?
 - Discuss the operation of the four diode bi-directional sampling gate. [4+4+8]

7. (a) With the help of a circuit diagram and waveforms explain frequency division of monostable multivibrator with pulse signals.
- (b) A symmetrical astable multivibrator using germanium transistors and operating from a 10V collector supply voltage has a free period of 1000 μsec . Triggering pulses whose spacing is 750 μsec are applied to one base through a small capacitor from a high impedance source. Find the minimum triggering pulse amplitude required to achieve 1 : 1 synchronization. Assume typical junction voltage of the transistor and that the timing portion of the base waveform is linear. [16]
8. (a) For the circuit shown in figure 4 an input voltage V_i linearly from 0 to 150V is applied. Sketch the output waveform V_o to the same time scale. Assume ideal diodes.

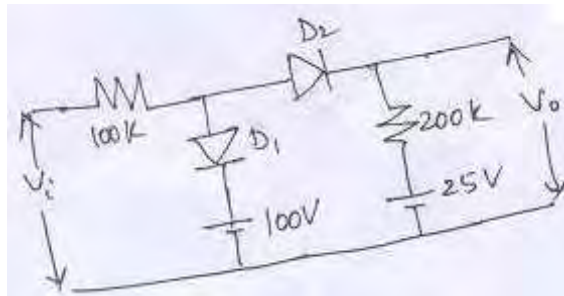


Figure 4

- (b) What is meant by a d.c restoration circuit and explain? [12+4]

II B.Tech I Semester Examinations, May/June 2012

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

1. (a) What are the applications of sampling gates?
(b) What are the advantages and disadvantages of unidirectional diode gate?
(c) Discuss the operation of the four diode bi-directional sampling gate. [4+4+8]
2. (a) What is meant by linear wave shaping
(b) A pulse of amplitude 5V and duration $20\mu\text{sec}$ is applied to high pass RC circuit having $R=10\text{K}\Omega$ and $C=1000\text{pf}$. calculate the output amplitude and sketch the o/p wave form.
(c) Draw the response of low pass RC circuit for ramp i/p signal. [2+10+4]
3. (a) Draw the circuit diagram of discrete-component regenerative comparator.
(b) Draw the transfer characteristic showing hysteresis. [16]
4. (a) In a current sweep circuit, explain how linearity correction is made through adjustment of driving waveform.
(b) Write the basic mechanism of transistor television sweep circuit. [16]
5. (a) Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
(b) Draw the output waveform X for the given inputs shown in figure 5.

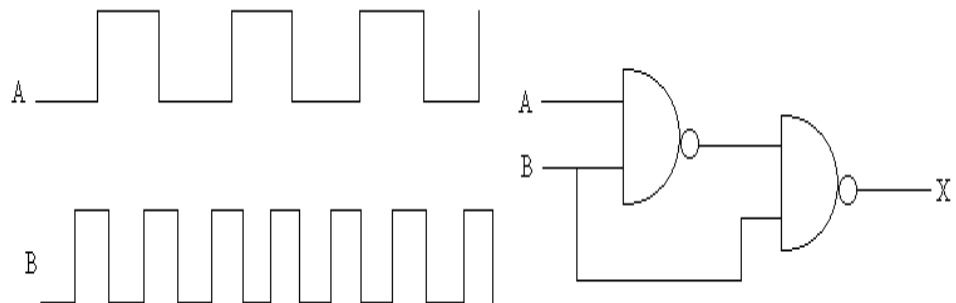


Figure 5

6. (a) With the help of a circuit diagram and waveforms explain frequency division of monostable multivibrator with pulse signals.

- (b) A symmetrical astable multivibrator using germanium transistors and operating from a 10V collector supply voltage has a free period of $1000 \mu\text{sec}$. Triggering pulses whose spacing is $750 \mu\text{sec}$ are applied to one base through a small capacitor from a high impedance source. Find the minimum triggering pulse amplitude required to achieve 1 : 1 synchronization. Assume typical junction voltage of the transistor and that the timing portion of the base waveform is linear. [16]
7. (a) For the circuit shown in figure 6 an input voltage V_i linearly from 0 to 150V is applied. Sketch the output waveform V_o to the same time scale. Assume ideal diodes.

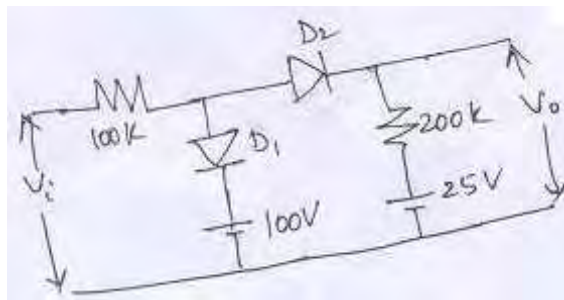


Figure 6

- (b) What is meant by a d.c restoration circuit and explain? [12+4]
8. (a) Explain the reverse recovery of a semi conductor diode. How does the recovery time place a limitation on the diode speed?
- (b) Write short notes on the switching times of a transistor. [8+8]

II B.Tech I Semester Examinations, May/June 2012

PULSE AND DIGITAL CIRCUITS

Common to Electronics And Instrumentation Engineering, Electrical And
Electronics Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions
All Questions carry equal marks

- What are the applications of sampling gates?
 - What are the advantages and disadvantages of unidirectional diode gate?
 - Discuss the operation of the four diode bi-directional sampling gate. [4+4+8]
- Draw the circuit diagram of diode-transistor logic NOR gate and explain its operation.
 - Draw the output waveform X for the given inputs shown in figure 7.

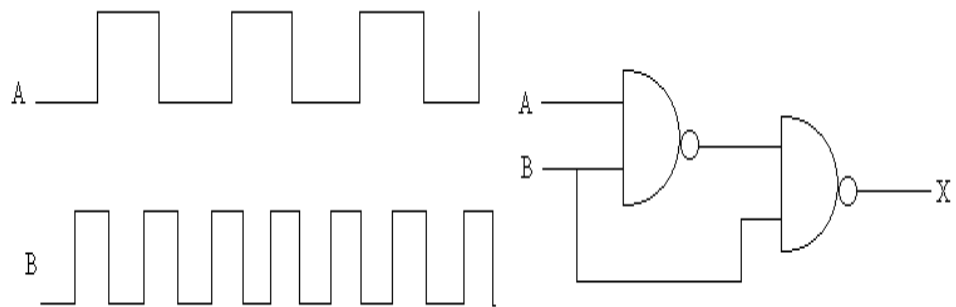


Figure 7

- What is meant by linear wave shaping
 - A pulse of amplitude 5V and duration $20\mu\text{sec}$ is applied to high pass RC circuit having $R = 10\text{K}\Omega$ and $C = 1000\text{pf}$. calculate the output amplitude and sketch the o/p wave form.
 - Draw the response of low pass RC circuit for ramp i/p signal. [2+10+4]
- In a current sweep circuit, explain how linearity correction is made through adjustment of driving waveform.
 - Write the basic mechanism of transistor television sweep circuit. [16]
- For the circuit shown in figure 8 an input voltage V_i linearly from 0 to 150V is applied. Sketch the output waveform V_o to the same time scale. Assume ideal diodes.

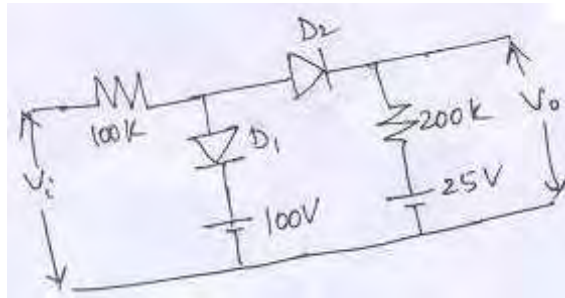


Figure 8

- (b) What is meant by a d.c restoration circuit and explain? [12+4]
6. (a) With the help of a circuit diagram and waveforms explain frequency division of monostable multivibrator with pulse signals.
- (b) A symmetrical astable multivibrator using germanium transistors and operating from a 10V collector supply voltage has a free period of 1000 μsec . Triggering pulses whose spacing is 750 μsec are applied to one base through a small capacitor from a high impedance source. Find the minimum triggering pulse amplitude required to achieve 1 : 1 synchronization. Assume typical junction voltage of the transistor and that the timing portion of the base waveform is linear. [16]
7. (a) Explain the reverse recovery of a semiconductor diode. How does the recovery time place a limitation on the diode speed?
- (b) Write short notes on the switching times of a transistor. [8+8]
8. (a) Draw the circuit diagram of discrete-component regenerative comparator.
- (b) Draw the transfer characteristic showing hysteresis. [16]
