

## II B.Tech II Semester Examinations, April/May 2012

## LINEAR IC APPLICATIONS

## Electronics And Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage and Gain band width product.
- (b) What are the differences between the inverting and non-inverting terminals? What do you mean by the term “virtual ground”? [10+6]
2. (a) Design a second order IGMF band pass filter with the following specifications:  $f_0 = 500\text{Hz}$ , Gain at resonance = -5 and band width = 50Hz. Use the circuit shown in Figure 3. Assume necessary data.
- (b) Explain the operation of a RC phase shift oscillator and obtain the frequency of oscillation. [6+10]

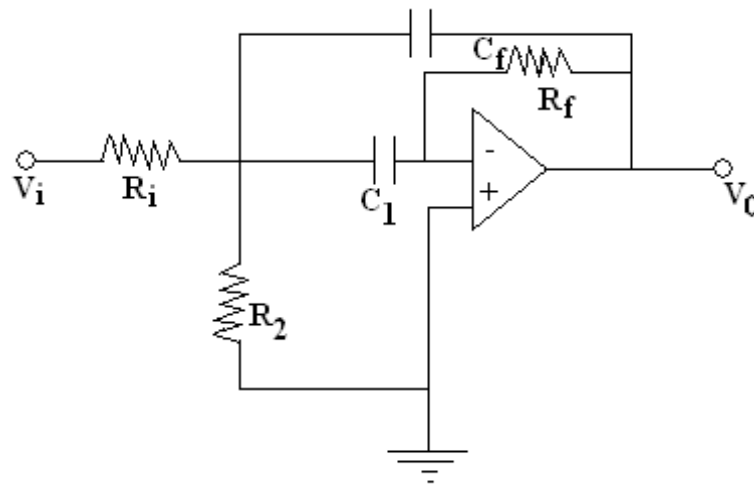


Figure 3

3. In some measurements it is necessary to sense current from a transducer and convert it into voltage. For a three op - amp realization of a current input instrumentation amplifier, derive the expression for  $V_o$ . [16]
4. What are the basic blocks of analog multiplexer? Explain how the data selection process is performed using it. [16]
5. (a) Design a logarithmic amplifier for positive input voltages in the range 5mV to 50V.
- (b) With suitable circuit diagram explain the operation of a triangular wave generator using a comparator and an integrator. [8+8]
6. Describe any two applications of 555 timer in

Code No: 07A40402

**R07**

**Set No. 2**

- (a) Astable multivibrator configuration
  - (b) Monostable multivibrator configuration. [8+8]
7. (a) Draw the circuit of a R-2R ladder type DAC for 4 bits and derive expression for output voltage.
- (b) Sketch the Analog output voltage for the given digital code.
  - (c) Compare R - 2R and Weighted resistor types of DACs. [8+4+4]
8. (a) An op - amp has a slew rate of  $2V/\mu s$ . What is the maximum frequency of an output sinusoid of peak value 5 V at which the distortion sets in due to the slew rate limitation?
- (b) What are the characteristics of an ideal op - amp? Explain. [8+8]

\*\*\*\*\*

**II B.Tech II Semester Examinations, April/May 2012****LINEAR IC APPLICATIONS****Electronics And Instrumentation Engineering****Time: 3 hours****Max Marks: 80****Answer any FIVE Questions****All Questions carry equal marks**

\*\*\*\*\*

1. In some measurements it is necessary to sense current from a transducer and convert it into voltage. For a three op - amp realization of a current input instrumentation amplifier, derive the expression for  $V_o$ . [16]
2. (a) Design a logarithmic amplifier for positive input voltages in the range 5mV to 50V.  
(b) With suitable circuit diagram explain the operation of a triangular wave generator using a comparator and an integrator. [8+8]
3. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage and Gain band width product.  
(b) What are the differences between the inverting and non-inverting terminals? What do you mean by the term "virtual ground"? [10+6]
4. What are the basic blocks of analog multiplexer? Explain how the data selection process is performed using it. [16]
5. Describe any two applications of 555 timer in
  - (a) Astable multivibrator configuration
  - (b) Monostable multivibrator configuration. [8+8]
6. (a) Draw the circuit of a R-2R ladder type DAC for 4 bits and derive expression for output voltage.  
(b) Sketch the Analog output voltage for the given digital code.  
(c) Compare R - 2R and Weighted resistor types of DACs. [8+4+4]
7. (a) Design a second order IGMF band pass filter with the following specifications:  $f_o = 500\text{Hz}$ , Gain at resonance = -5 and band width = 50Hz. Use the circuit shown in Figure 3. Assume necessary data.  
(b) Explain the operation of a RC phase shift oscillator and obtain the frequency of oscillation. [6+10]

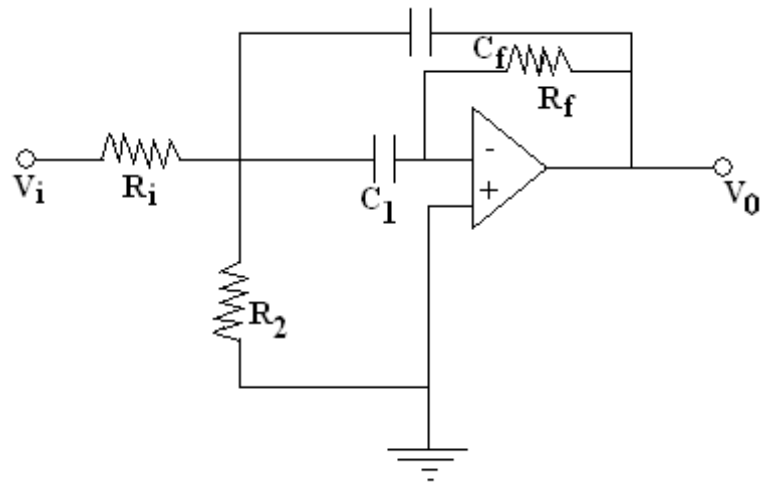


Figure 3

8. (a) An op - amp has a slew rate of  $2V/\mu s$ . What is the maximum frequency of an output sinusoid of peak value 5 V at which the distortion sets in due to the slew rate limitation?
- (b) What are the characteristics of an ideal op - amp? Explain. [8+8]

\*\*\*\*\*

## II B.Tech II Semester Examinations, April/May 2012

## LINEAR IC APPLICATIONS

## Electronics And Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) An op - amp has a slew rate of  $2V/\mu s$ . What is the maximum frequency of an output sinusoid of peak value 5 V at which the distortion sets in due to the slew rate limitation?
- (b) What are the characteristics of an ideal op - amp? Explain. [8+8]
2. (a) Design a second order IGMF band pass filter with the following specifications:  $f_0 = 500\text{Hz}$ , Gain at resonance = -5 and band width = 50Hz. Use the circuit shown in Figure 3. Assume necessary data.
- (b) Explain the operation of a RC phase shift oscillator and obtain the frequency of oscillation. [6+10]

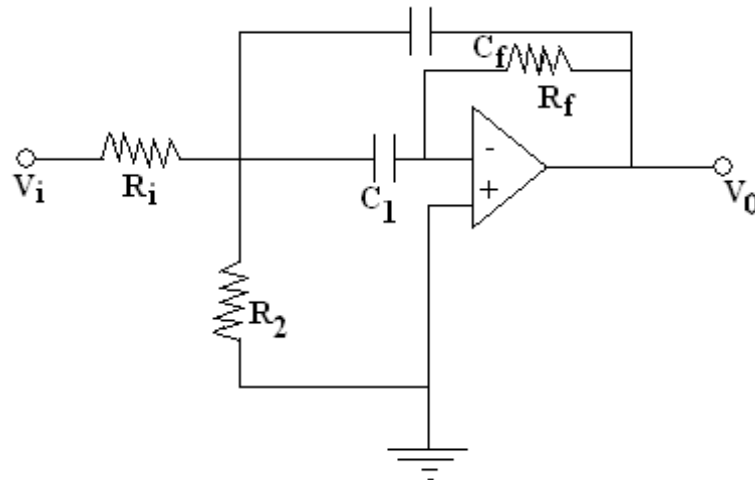


Figure 3

3. Describe any two applications of 555 timer in
  - (a) Astable multivibrator configuration
  - (b) Monostable multivibrator configuration. [8+8]
4. In some measurements it is necessary to sense current from a transducer and convert it into voltage. For a three op - amp realization of a current input instrumentation amplifier, derive the expression for  $V_o$ . [16]
5. (a) Draw the circuit of a R-2R ladder type DAC for 4 bits and derive expression for output voltage.
- (b) Sketch the Analog output voltage for the given digital code.

- (c) Compare R - 2R and Weighted resistor types of DACs. [8+4+4]
6. (a) Design a logarithmic amplifier for positive input voltages in the range 5mV to 50V.
- (b) With suitable circuit diagram explain the operation of a triangular wave generator using a comparator and an integrator. [8+8]
7. What are the basic blocks of analog multiplexer? Explain how the data selection process is performed using it. [16]
8. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage and Gain band width product.
- (b) What are the differences between the inverting and non-inverting terminals? What do you mean by the term "virtual ground"? [10+6]

\*\*\*\*\*

## II B.Tech II Semester Examinations, April/May 2012

## LINEAR IC APPLICATIONS

## Electronics And Instrumentation Engineering

Time: 3 hours

Max Marks: 80

Answer any FIVE Questions  
All Questions carry equal marks

\*\*\*\*\*

1. (a) Define the terms: SVRR, CMRR, input bias current, input offset voltage and Gain band width product.  
(b) What are the differences between the inverting and non-inverting terminals? What do you mean by the term “virtual ground”? [10+6]
2. (a) An op - amp has a slew rate of  $2V/\mu s$ . What is the maximum frequency of an output sinusoid of peak value 5 V at which the distortion sets in due to the slew rate limitation?  
(b) What are the characteristics of an ideal op - amp? Explain. [8+8]
3. (a) Design a second order IGMF band pass filter with the following specifications:  $f_0 = 500\text{Hz}$ , Gain at resonance = -5 and band width = 50Hz. Use the circuit shown in Figure 3. Assume necessary data.  
(b) Explain the operation of a RC phase shift oscillator and obtain the frequency of oscillation. [6+10]

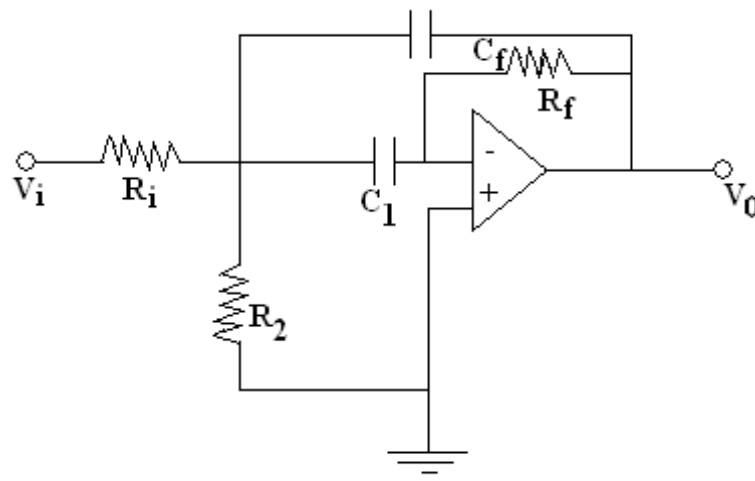


Figure 3

4. Describe any two applications of 555 timer in
  - (a) Astable multivibrator configuration
  - (b) Monostable multivibrator configuration. [8+8]
5. (a) Design a logarithmic amplifier for positive input voltages in the range 5mV to 50V.

- (b) With suitable circuit diagram explain the operation of a triangular wave generator using a comparator and an integrator. [8+8]
6. In some measurements it is necessary to sense current from a transducer and convert it into voltage. For a three op - amp realization of a current input instrumentation amplifier, derive the expression for  $V_o$ . [16]
7. What are the basic blocks of an analog multiplexer? Explain how the data selection process is performed using it. [16]
8. (a) Draw the circuit of an R-2R ladder type DAC for 4 bits and derive an expression for output voltage.
- (b) Sketch the analog output voltage for the given digital code.
- (c) Compare R - 2R and Weighted resistor types of DACs. [8+4+4]

\*\*\*\*\*