

Code No: 113BR

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B.Tech II Year I Semester Examinations, December-2014

BASIC ELECTRICAL ENGINEERING

(Common to CSE, IT)

Time: 3 Hours

Max. Marks: 75

**Note:** This question paper contains two parts A and B.  
 Part A is compulsory which carries 25 marks. Answer all questions in Part A.  
 Part B consists of 5 Units. Answer any one full question from each unit.  
 Each question carries 10 marks and may have a, b, c as sub questions.

**Part- A****(25 Marks)**

- 1.a) State and explain KCL and KVL. [2M]
- b) State and explain Norton's theorem. [3M]
- c) Define RMS and Average value of an alternating quantity. [2M]
- d) A coil has a resistance of  $4 \Omega$  and an inductance of  $9.55 \text{ mH}$ . Calculate (i) the reactance, (ii) the impedance, and (iii) the current taken from a  $240 \text{ V}$ ,  $50 \text{ Hz}$  supply. [3M]
- e) Why rating of the transformer is given in KVA? Explain. [2M]
- f) Draw and explain the phasor diagram of single phase transformer on no load. [3M]
- g) Explain the principle of DC motor operation. [2M]
- h) Write the similarities between transformer and induction motor. [3M]
- i) What are the different types torques acting on the moving system of measuring instrument? [2M]
- j) Explain how the deflecting torque provided in a moving system of a measuring instrument? [3M]

**Part-B****(50 Marks)**

- 2.a) For the circuit shown in Figure 1, calculate the current  $I$  and voltage  $V_{ab}$  when  
 i)  $R_x = 0 \Omega$     ii)  $R_x = 15 \text{ K}\Omega$     iii)  $R_x = \infty \Omega$ .

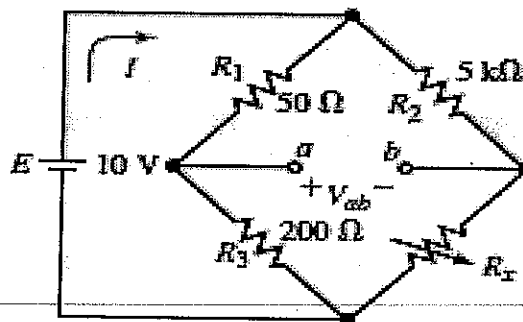


Figure 1

- b) For the arrangement shown in Figure 2 find:  
 i) the equivalent capacitance of the circuit and  
 ii) the voltage across a  $4.5 \mu\text{F}$  capacitor.

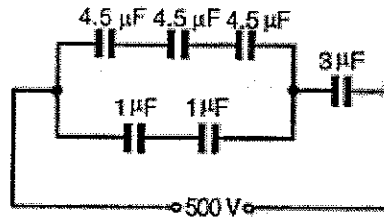


Figure 2

OR

- 3.a) Find the value of  $R_L$  for maximum power transfer in the circuit shown in Figure 3. Find the maximum power.

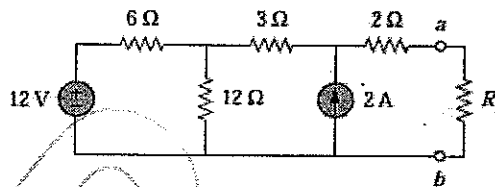


Figure 3

- b) State and explain thevenin's theorem with an example.
- 4.a) Calculate:  
 i) The admittance  $Y$   
 ii) The conductance  $G$  and  
 iii) Susceptance  $B$  of a circuit consisting of a resistor of  $10 \Omega$  in series with an inductor of  $0.3 \text{ H}$ , when the frequency is  $50 \text{ Hz}$ .
- b) A resistance of  $10 \text{ Ohms}$ , an inductive reactance of  $5 \text{ Ohms}$ , and a capacitive reactance of  $10 \text{ Ohms}$  are connected in parallel with each other across a supply of  $230 \angle 45^\circ \text{ Volts}$ . Calculate  
 i) Impedance and admittance of each branch  
 ii) Current in each branch  
 iii) Total current drawn from the supply  
 iv) Draw the phasor diagram.

OR

- 5.a) A  $20 \Omega$  resistance and  $30 \text{ mH}$  inductance are connected in series and the circuit is fed from a  $220 \text{ V}$ ,  $50 \text{ Hz}$  AC supply. Find  
 i) Reactance across the inductance, impedance, admittance, current  
 ii) Voltage across the resistance  
 iii) Voltage across the inductance  
 iv) Real, reactive and active powers  
 v) Power factor
- b) The waveform shown in Figure 4 is a half-wave rectified sine wave. Find the rms value and the amount of average power dissipated in a  $10 \Omega$  resistor.

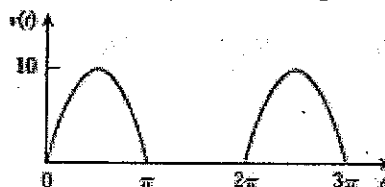


Figure 4

- 6.a) Explain the working principle of single phase transformer.
- b) A 5 KVA single-phase transformer has a turns ratio of 10:1 and is fed from a 2.5 kV supply. Neglecting losses, determine:
- the full-load secondary current
  - the minimum load resistance which can be connected across the secondary winding to give full load KVA
  - the primary current at full load KVA.

**OR**

- 7.a) Enumerate the various losses in a transformer. How can these losses be minimized?
- b) A 2400 V/400 V single-phase transformer takes a no load current of 0.5 A and the core loss is 400 W. Determine the values of the magnetizing and core loss components of the no load current. Draw to scale the no-load phasor diagram for the transformer.

- 8.a) Based on the type of excitation classify the DC generators.
- b) A 4-pole armature of a d.c. machine has 1000 conductors and a flux per pole of 20 mWb. Determine the e.m.f. generated when running at 600 rev/min when the armature is:
- wave-wound
  - lap-wound.

**OR**

- 9.a) Explain the working principle of three phase induction motor.
- b) A 3-phase, 60 Hz induction motor has 2 poles. If the slip is 2% at a certain load, determine:
- the synchronous speed
  - the speed of the rotor and
  - the frequency of the induced e.m.f.'s in the rotor.

10. With the help of a neat sketch explain the construction and operation of PMMC instrument.

**OR**

- 11.a) Discuss the classification of electrical instruments.
- b) Explain the significance of controlling torque and damping torque relevant to the operation of indicating instrument.

---oo0oo---

