

**MASSACHUSETTS INSTITUTE OF TECHNOLOGY**  
**Department of Electrical Engineering and Computer Sciences**

**Analysis and Design of Digital Integrated Circuits (6.374) - Fall 2003 Quiz #1**  
Prof. Anantha Chandrakasan

**Student Name:** \_\_\_\_\_

Problem 1 (30 Points): \_\_\_\_\_

Problem 2 (24 Points): \_\_\_\_\_

Problem 3 (18 Points): \_\_\_\_\_

Problem 4 (28 Points): \_\_\_\_\_

Total (100 Points): \_\_\_\_\_

Use the following device parameters unless otherwise specified:


Parameter	NMOS	PMOS
$V_{T0}$	0.4 V	-0.4V
$K' = \mu C_{ox}$	$75 \mu A/V^2$	$-25 \mu A/V^2$
$V_{DSAT}$	0.5V	-0.75V
$\gamma$	$0.3V^{1/2}$	$-0.3V^{1/2}$
$ 2\phi $	0.6V	0.6V
$\lambda$	0	0

**Also assume that all NMOS device bulks are connected to 0V and PMOS well terminals are connected to  $V_{DD}$ .**

**STATE ANY ASSUMPTIONS YOU MAKE IN SOLVING PROBLEMS and SHOW YOUR WORK.** Points might be taken off if you don't explain how you arrived at your answer.

**There are 13 pages in total**

 **Problem 1: Driver Circuit:** Consider the following circuit driving a capacitive load of 1pF.



(a) Assuming that *In* swings from rail-to-rail (0 to 2.5V), what is the swing on the node *Out*? (2 points)

(b) At the switching threshold  $V_M = 1.75\text{V}$ , what is the mode of operation for  $M_1$  and  $M_2$ . Show your work (4 points)


(c) Assuming  $(W/L)_2 = 25\mu\text{m}/0.25\mu\text{m}$ , determine  $(W/L)_1$  such that  $V_M = 1.75\text{V}$ . **(6 points)**

(d) Assuming  $(W/L)_2 = 25\mu\text{m}/0.25\mu\text{m}$ , determine the low-to-high propagation delay using the method of equivalent RC. Assume that the input switches from 2.5V to 0V with a zero fall time (**8 points**)

(e) Assuming that the input switches at a clock frequency of 100MHz with a swing of 0 to  $V_{DD}$  (with zero rise and fall times) what is the average power dissipation of this circuit? Show your work **(10 points)**.

**Problem 2: Pass Transistor Logic**

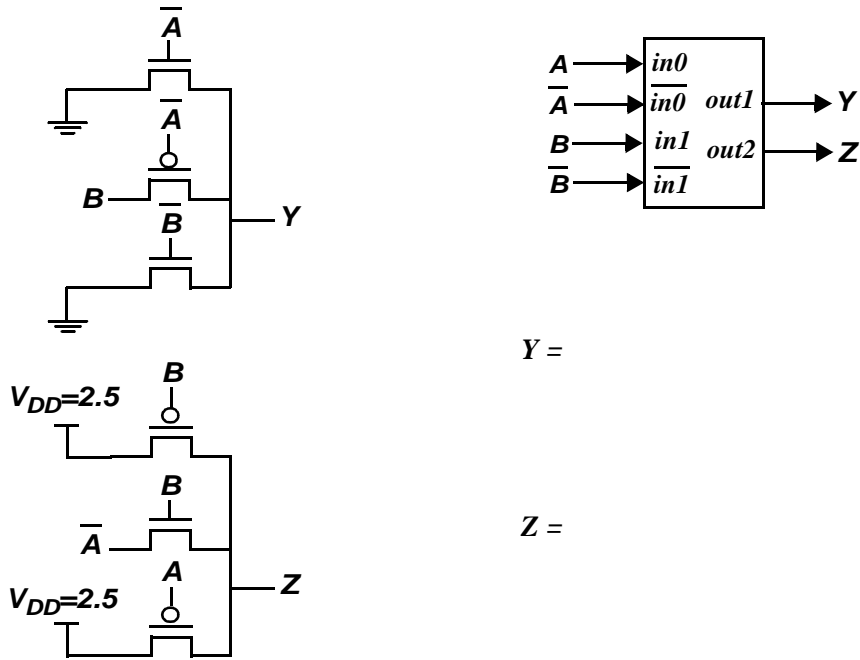
(a) Consider the following circuit implemented using NMOS and PMOS pass transistors. Assume that the inputs and their complements ( $A, \bar{A}, B, \bar{B}$ ) swing rail-to-rail (0 to  $V_{DD}$ ). What is the function implemented by the two circuits. (6 points)



$Y =$


$Z =$

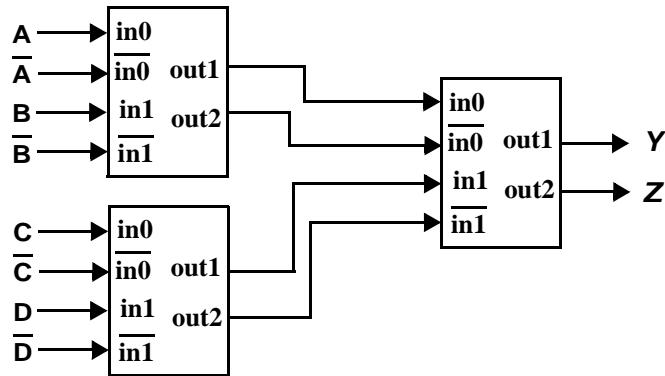(b) Assuming that the primary inputs ( $A, B, C, D$ ) and their complements are have rail-to-rail swing (0 to  $V_{DD}$ ), what is the voltage swing on outputs  $Y$  and  $Z$ ? (4 points)



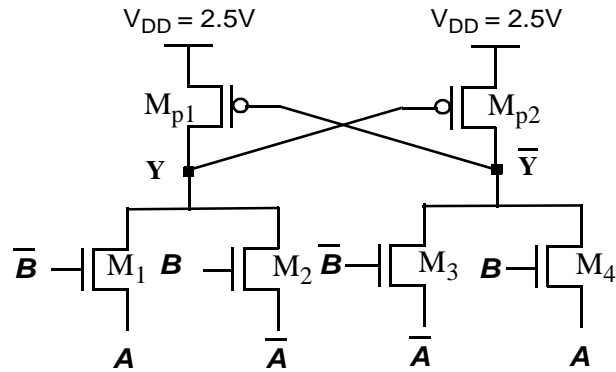(c) Using the same style of logic in part 2(a) (i.e., using NMOS, PMOS pass transistors connected to signal or  $V_{DD}$ /GND), create the minimal transistor implementation of the OR/NOR function. Your implementation should have the same swing as the circuits in 2(a) **(6 points)**

Consider the following cross-coupled complementary pass-gate logic




(d) What is the logic function  $Y$  implemented by the above gate? What is the voltage swing on nodes  $Y$  and  $\bar{Y}$ ? **(4 points)**

(e) Assume that  $A$ ,  $\bar{A}$ ,  $B$ ,  $\bar{B}$  are from ideal voltage sources and have a rail-to-rail swing (0 to  $V_{DD}$ ). Also assume (just for this part) that there is no body effect ( $\gamma = 0$ ) and ignore sub-threshold conduction. Is this a ratioed circuit? Explain. **(4 points)**.




**Problem 3: Dynamic Logic**

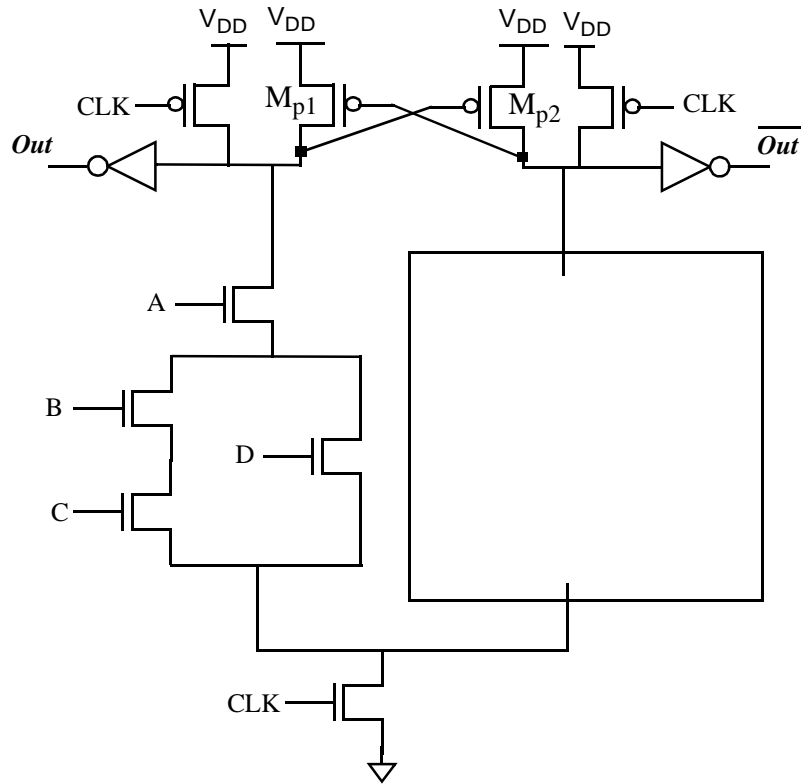(a) Complete the circuit schematic of the DCVSL gate below (6 points)




(b) What is the function of  $M_{p1}$  and  $M_{p2}$ ? Is this a ratioed circuit? (4 points)

 (c) Consider the following function  $Y = A + B + C$  implemented using a cascade of two 2-input DOMINO OR gates. Assume that  $p_{(A=1)} = 0.1$ ,  $p_{(B=1)} = 0.2$ ,  $p_{(C=1)} = 0.5$ . Determine the order of inputs to minimize power dissipation (show numerical analysis). Explain. Fill in the empty boxes with the appropriate inputs. **(8 points)**






 (b) Assuming  $SLEEP = 0$  (Active mode), compute the total leakage when  $A=0, B=0$ ? **A numerical result is expected.** Draw all the contributing leakage paths on the figure below (10 points)



 (c) Assuming  $SLEEP = 1$  (Sleep mode) and  $A=0, B=1$ . In the Sleep mode, ideally, the leakage should be small and be set by high-threshold devices. Unfortunately, this is not always the case for distributed sleep devices as shown below. Identify (**but do not compute**) any leakage path(s) from  $V_{DD}$  to ground which are determined by low-threshold devices (i.e., not cut-off by high-threshold devices). (**8 points**)



(d) For the same assumption of part (c), what do you expect the leakage through device M9 to be:

- (1) 10pA
- (2) 1nA
- (3)  $\gg 1nA$

Briefly explain why (**6 points**)