

# Lab 1 - Revisited

- Display signals on scope
- Measure the time, frequency, voltage visually and with the scope
- *Voltage measurement\**
- *Build simple circuits on a protoboard.\**
  
- Oscilloscope demo

# RMS Voltage

- 0-5v square wave (50%) duty cycle has a rms value of  $5 / \sqrt{2} = 3.54\text{v}$
- 5v peak-peak square wave (-2.5v to +2.5v 50% duty cycle) has a rms value of 2.5v




# General Conventions

- Wire coding
  - red: positive or signal source
  - black: ground or common reference point
- Circuit flow, signal flow left to right
- Higher voltage on top, ground negative voltage on bottom

# Lab Hints & Cautions


- Current measure must be taken in series – not parallel.
- There are tools for most situations: wire strippers, de-soldering tool, etc..
- Power ratings of components must not be exceeded
- Polarity of electrolytic capacitors must be observed.

# Lab 1 Circuits

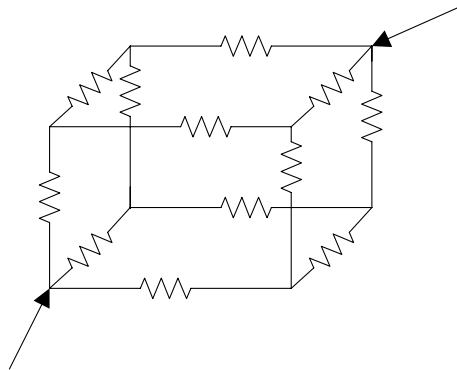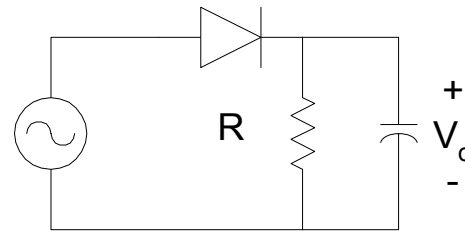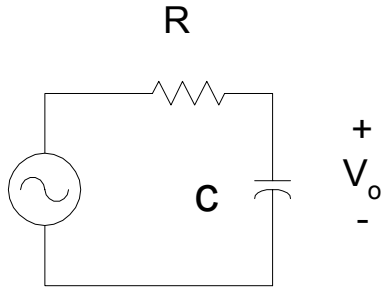

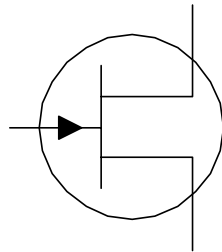
# Field Effect Transistors (FET)

- MOSFET: Metal Oxide Semiconductor FET
- JFET: Junction FET
- FETs are voltage controlled device with very high input impedance (little current)





N channel JFET

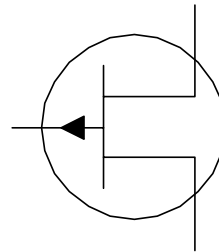

P channel JFET

# Simple Model of MOSFET

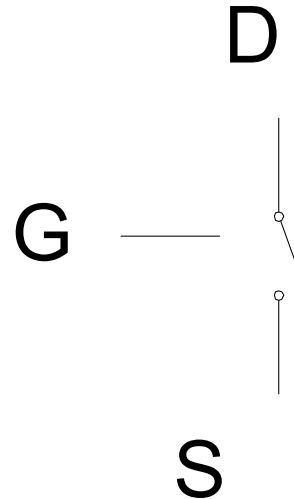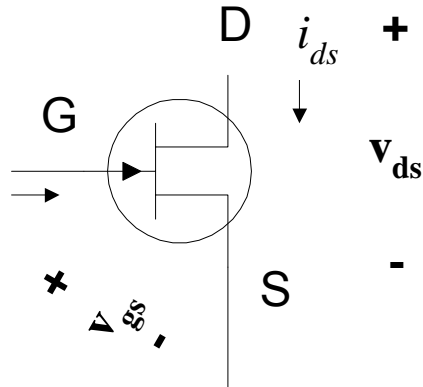

**OFF**

$$V_{gs} < V_t$$



**ON**

$$V_{gs} \geq V_t$$


MOSFET made VSLI  
(microprocessors and  
memories) possible.

Very high input resistance

Voltage controlled device

~25 V max operating


# Bipolar Junction Transistors

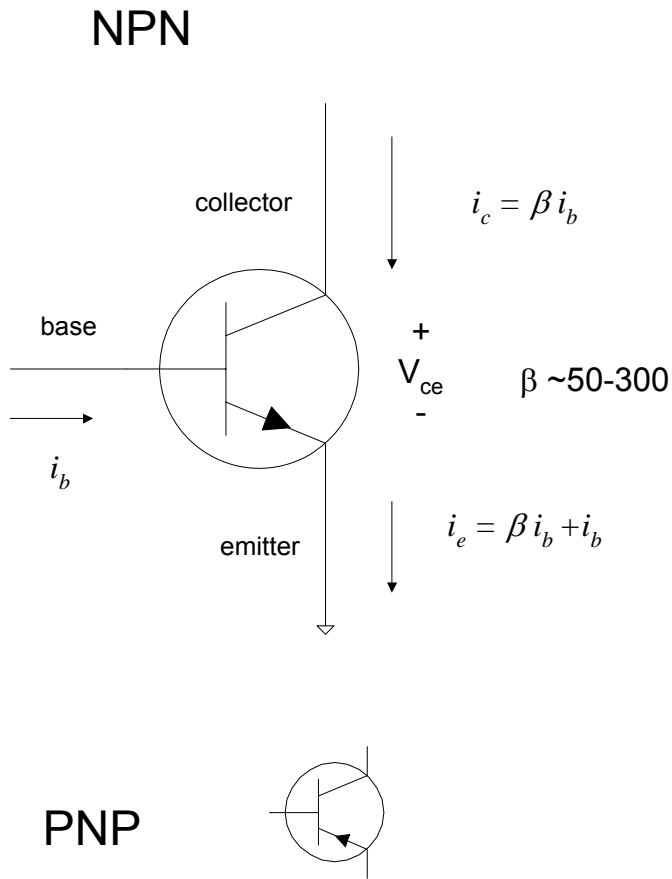

- BJT can operate in a linear mode (amplifier) or can operate as a digital switch.
- Current controlled device
- Two families: npn and pnp.
- BJT's are current controlled devices
- NPN – 2N2222
- PNP – 2N2907
- $V_{CE} \sim 30V$ , 500 mw power



# BJT Switching Models

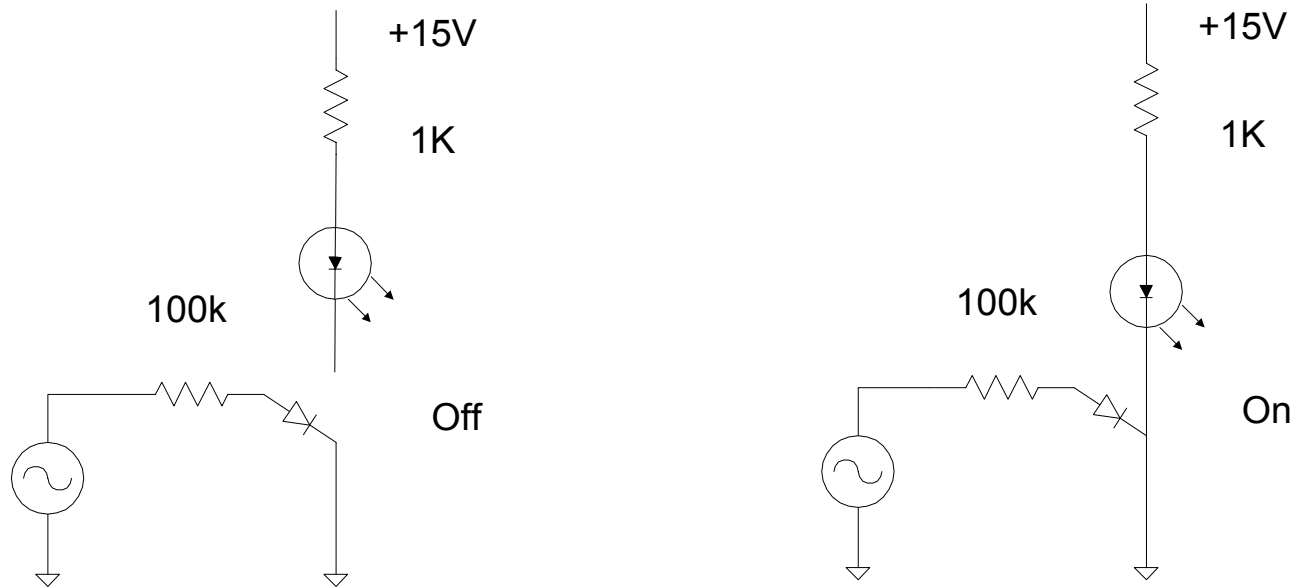


# Light Emitting Diode

- LED's are pn junction devices which emit light. The frequency of the light is determined by a combination of gallium, arsenic and phosphorus.
- Red, yellow and green LED's are in the lab
- Diodes have polarity
- Typical forward current 10-20ma
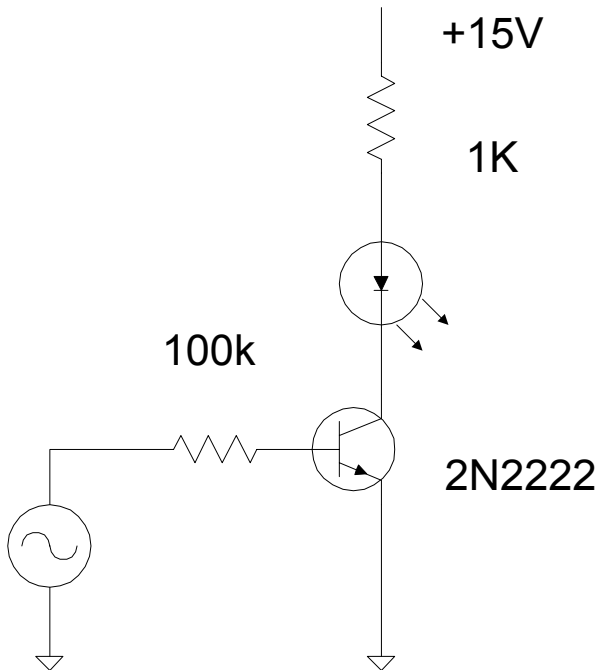
# Lab Exercise

- Wire up protoboard.
- Turn on function generator and using a ramp signal try to get a pulsing light




# Optical Isolators

## Pin Configurations (Top View)


TLP731

- 1: Anode
- 2: Cathode
- 3: NC
- 4: Emitter
- 5: Collector
- 6: Base

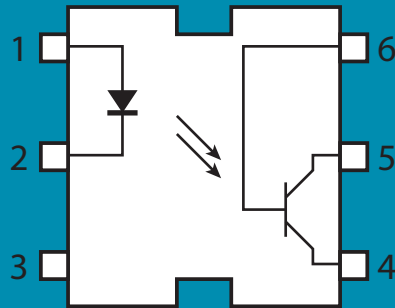

TLP732

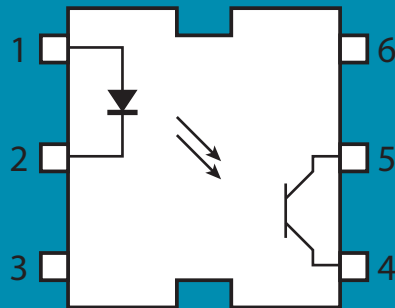- 1: Anode
- 2: Cathode
- 3: NC
- 4: Emitter
- 5: Collector
- 6: Base





- Optical Isolators are used to transmit information optically without physical contact.
- Single package with LED and photosensor (BJT, thyristor, etc.)
- Isolation up to 4000 Vrms

Figure by MIT OpenCourseWare.

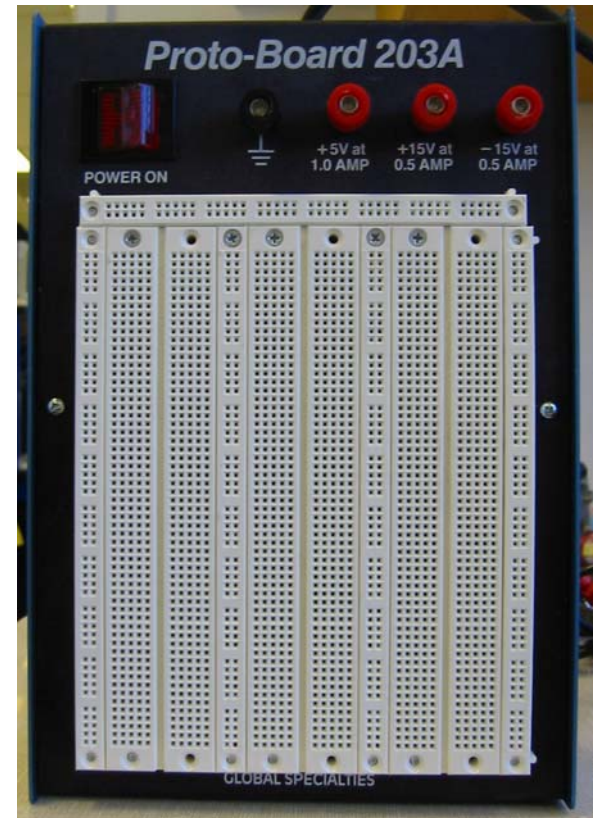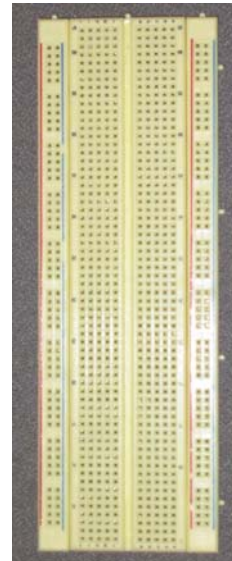
# Proto-Board

- +5v, +15v, -15v available
- Pins within row or column connected
- Use bypass capacitors liberally



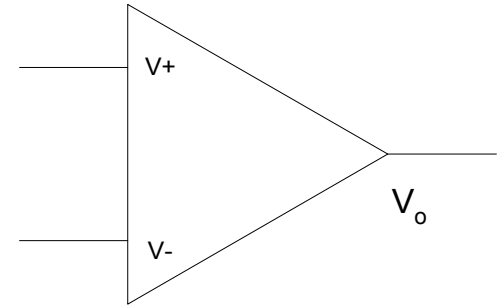
# Op-Amps

- Active device:  $V_o = A(V_+ - V_-)$ ; note that it is the difference of the input voltage!
- $A$ =open loop gain  $\sim 10^5 - 10^6$
- Most applications use negative feedback.
- Comparator: no feedback
- Active device requires power. No shown for simplicity.
- Classics op-amps: 741, 357  $\sim$  \$0.20




# 741 Circuit

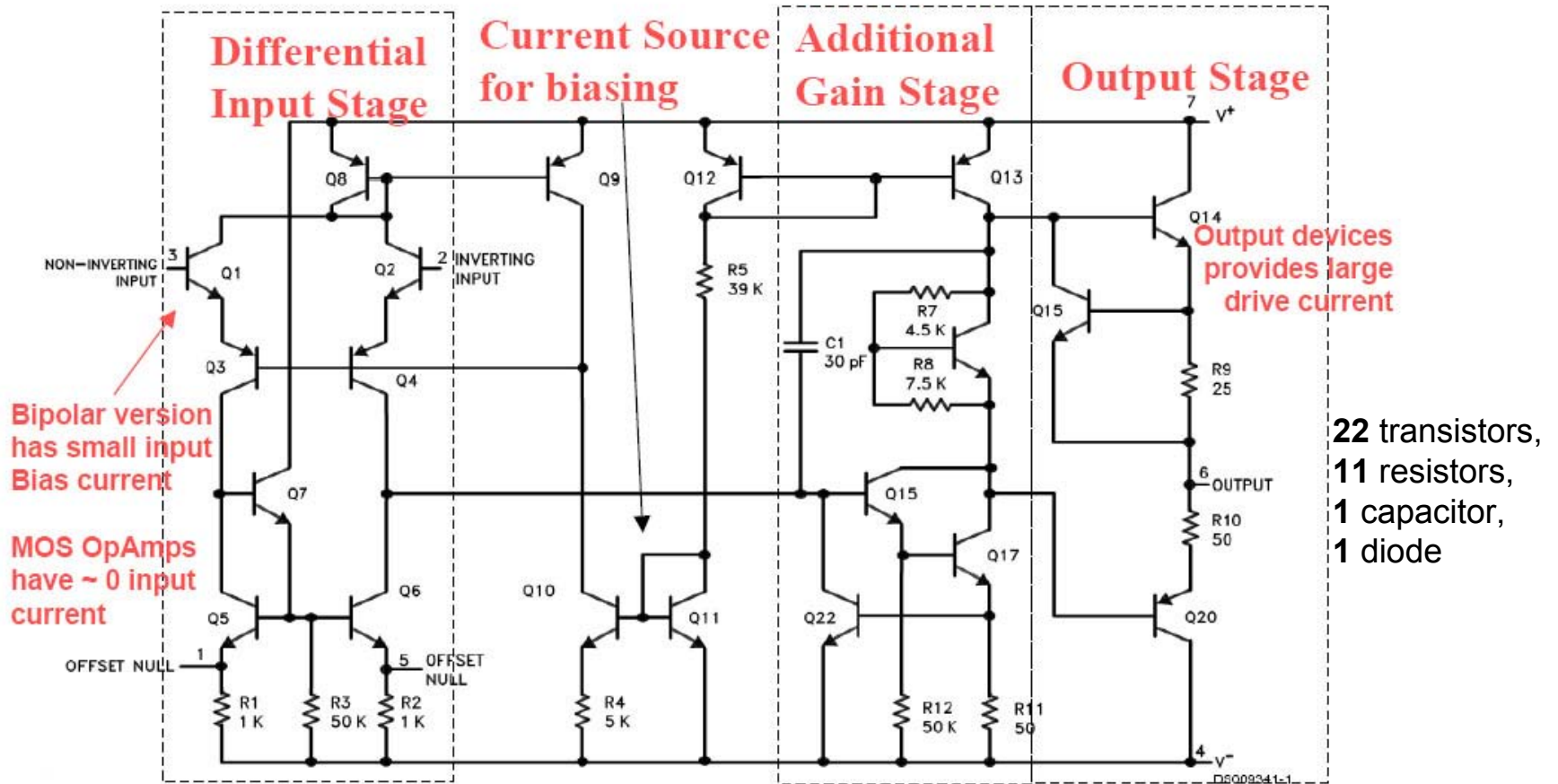

Reprinted with permission of National Semiconductor Corporation.

# 356 JFET Input Op-amp

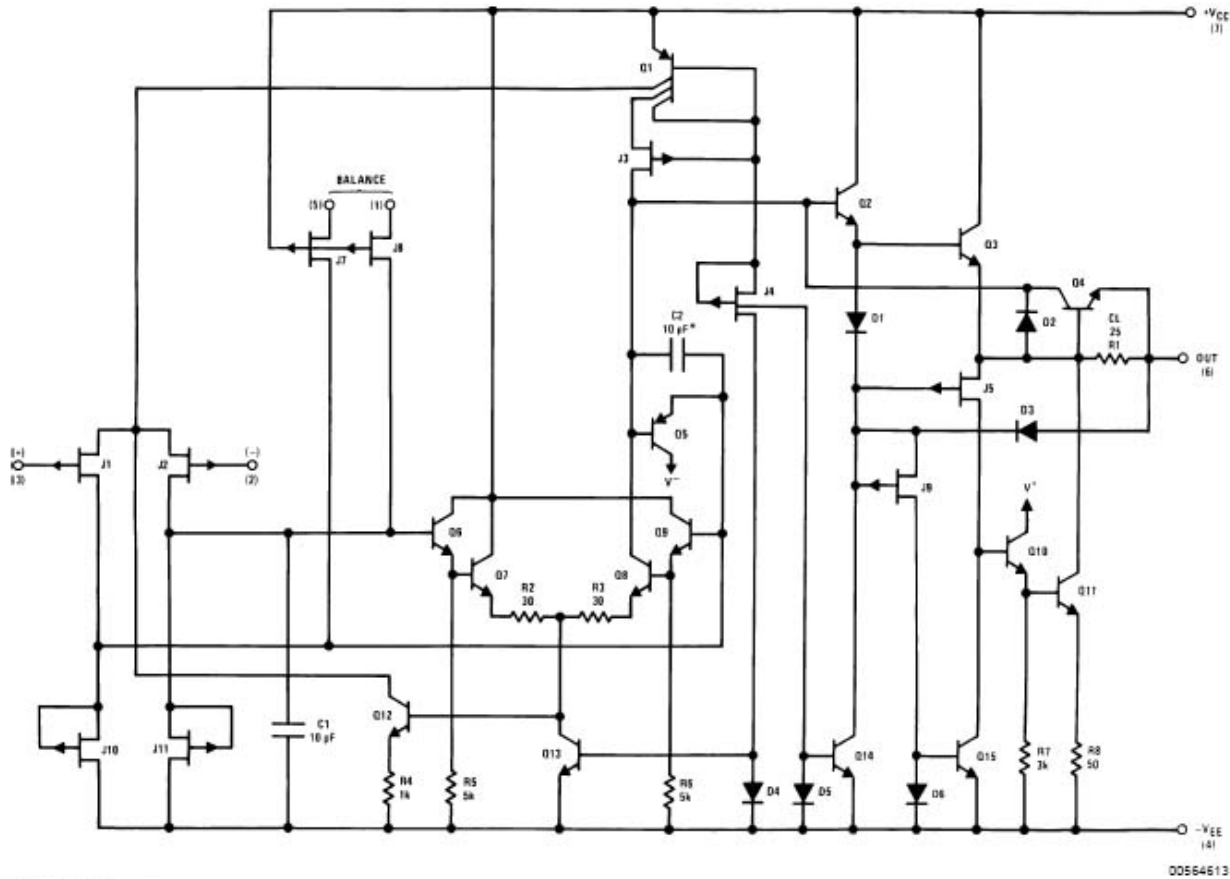

\*C = 3pF in LF357 series.

Reprinted with permission of National Semiconductor Corporation.



# 741 Op Amp Max Ratings

## MAXIMUM RATINGS

Rating	Symbol	Value	Unit
Power Supply Voltage	$V_{CC}, V_{EE}$	$\pm 18$	Vdc
Input Differential Voltage	$V_{ID}$	$\pm 30$	V
Input Common Mode Voltage (Note 1.)	$V_{ICM}$	$\pm 15$	V
Output Short Circuit Duration (Note 2.)	$t_{SC}$	Continuous	–
Operating Ambient Temperature Range	$T_A$	0 to +70	°C
Storage Temperature Range	$T_{stg}$	–55 to +125	°C

1. For supply voltages less than +15 V, the absolute maximum input voltage is equal to the supply voltage.
2. Supply voltage equal to or less than 15 V.

Reprinted with permission of National Semiconductor Corporation.

# 741 Electrical Characteristics

ELECTRICAL CHARACTERISTICS ( $V_{CC} = +15\text{ V}$ ,  $V_{EE} = -15\text{ V}$ ,  $T_A = 25^\circ\text{C}$ , unless otherwise noted.)

Characteristic	Symbol	Min	Typ	Max	Unit
Input Offset Voltage ( $R_S \leq 10\text{ k}$ )	$V_{IO}$	–	2.0	6.0	mV
Input Offset Current	$I_{IO}$	–	20	200	nA
Input Bias Current	$I_{IB}$	–	80	500	nA
Input Resistance	$r_i$	0.3	2.0	–	M $\Omega$
Input Capacitance	$C_i$	–	1.4	–	pF
Offset Voltage Adjustment Range	$V_{IOR}$	–	$\pm 15$	–	mV
Common Mode Input Voltage Range	$V_{ICR}$	$\pm 12$	$\pm 13$	–	V
Large Signal Voltage Gain ( $V_O = \pm 10\text{ V}$ , $R_L \geq 2.0\text{ k}$ )	$A_{VOL}$	20	200	–	V/mV
Output Resistance	$r_o$	–	75	–	$\Omega$
Common Mode Rejection ( $R_S \leq 10\text{ k}$ )	CMR	70	90	–	dB
Supply Voltage Rejection ( $R_S \leq 10\text{ k}$ )	PSR	75	–	–	dB
Output Voltage Swing ( $R_L \geq 10\text{ k}$ ) ( $R_L \geq 2.0\text{ k}$ )	$V_O$	$\pm 12$ $\pm 10$	$\pm 14$ $\pm 13$	– –	V
Output Short Circuit Current	$I_{SC}$	–	20	–	mA
Supply Current	$I_D$	–	1.7	2.8	mA
Power Consumption	$P_C$	–	50	85	mW
Transient Response (Unity Gain, Noninverting)					
( $V_i = 20\text{ mV}$ , $R_L \geq 2.0\text{ k}$ , $C_L \leq 100\text{ pF}$ ) Rise Time	$t_{TLH}$	–	0.3	–	$\mu\text{s}$
( $V_i = 20\text{ mV}$ , $R_L \geq 2.0\text{ k}$ , $C_L \leq 100\text{ pF}$ ) Overshoot	os	–	15	–	%
( $V_i = 10\text{ V}$ , $R_L \geq 2.0\text{ k}$ , $C_L \leq 100\text{ pF}$ ) Slew Rate	SR	–	0.5	–	V/ $\mu\text{s}$

Reprinted with permission of National Semiconductor Corporation.

# Decibel (dB)


$$dB = 20 \log \left( \frac{V_o}{V_i} \right)$$

$$dB = 10 \log \left( \frac{P_o}{P_i} \right)$$

$$\log_{10}(2) = .301$$

3 dB point = ?

# 741 Open Loop Frequency Gain

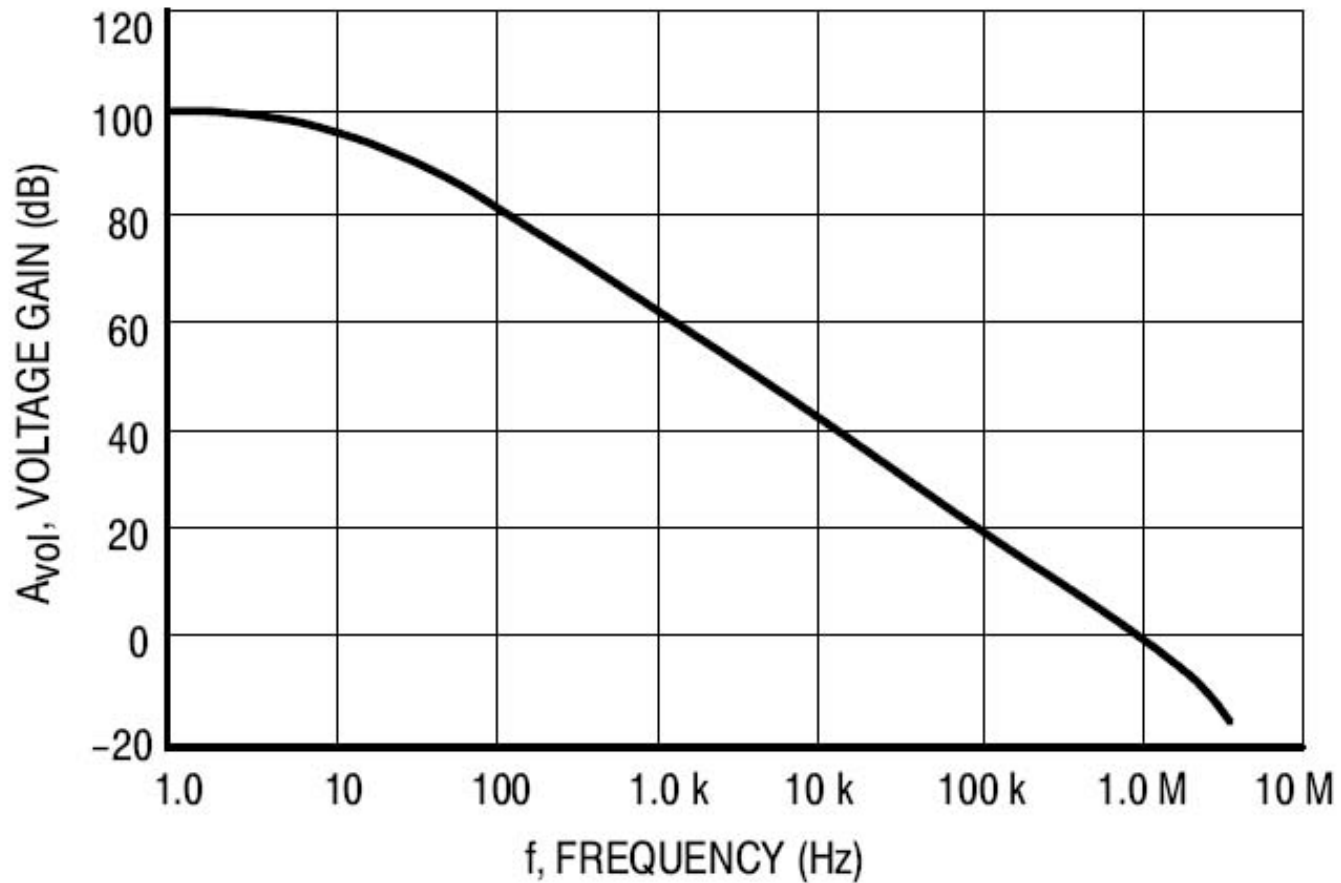


# 741 vs 356 Comparison

	<b>741</b>	<b>356</b>
Input device	BJT	JFET
Input bias current	0.5uA	0.0001uA
Input resistance	0.3 MΩ	10 <sup>6</sup> MΩ
Slew rate*	0.5 v/us	7.5 v/us
Gain Bandwidth product	1 Mhz	5 Mhz
Output short circuit duration	Continuous	continuous
Identical pin out		

\* comparators have >50 v/us slew rate

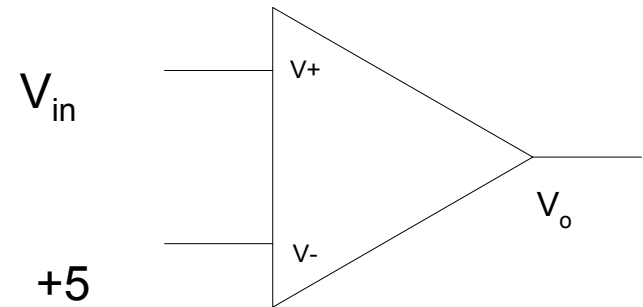
# Comparator Operation

- Supply voltage = +15V, -15V
- $V_- = +5\text{ V}$
- For  $V_{in} = +4$ ,  $V_o = ?$
- For  $V_{in} = +5.1$ ,  $V_o = ?$
- Comparators are design for fast response time and high slew rate.



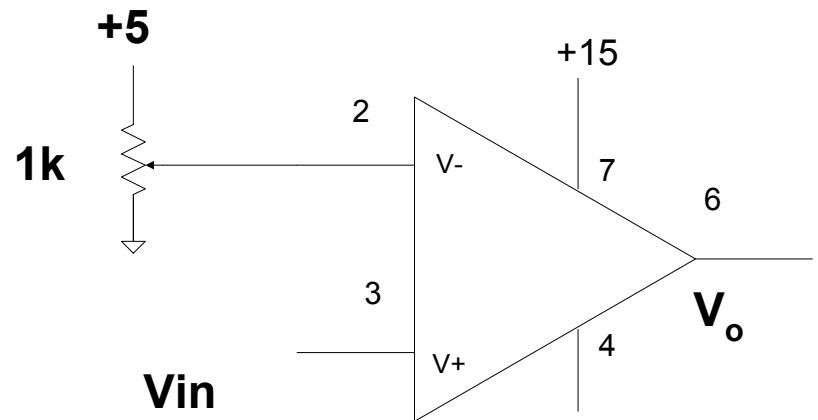
# Lab Exercise - Comparator

- Wire up a comparator on the proto-board using 741 op-amp. Be sure to supply power and ground.
- Turn on function generator using a ramp. Display both the input and the output on an oscilloscope. Describe what is happening.
- What is the maximum output voltage (the plus rail)?
- What is the minimum output voltage (negative rail)?



# Lab Exercise - Oscillator

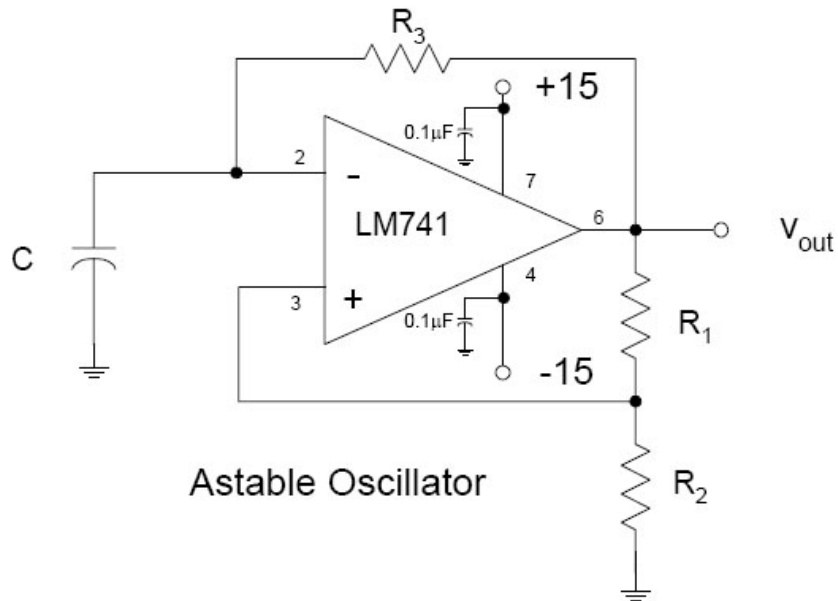


- Wire up a comparator on the proto-board using 741 op-amp. Be sure to supply power and ground.
- $R_1=10k$ ,  $R_2=4.7k$ ,  $R_3=10K$ ,  $C=.33\mu f$
- Display  $V_{in}$  and  $V_{out}$  on the scope. Describe what is happening. Set  $R_3=4.7k$ . Predict what happens to the frequency.



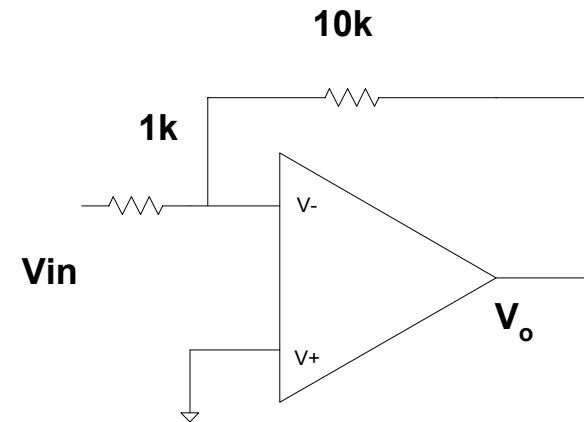
# Lab Exercise – Inverting amplifier

- Wire up a comparator on the proto-board using 741 op-amp. Be sure to supply power and ground. Find the pin #
- Turn on function generator using a ramp. Display both the input and the output on an oscilloscope. How is the output related to the input?
- What is the peak output voltage?
- What is the minimum output voltage?
- What at frequency does the gain start to drop below ten?




# Negative Feedback

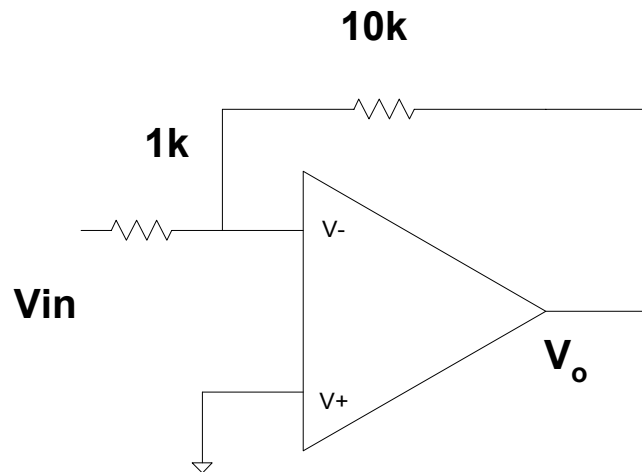


- Take product with 100,000 gain and reduce it to 10?

# Lab Exercise – Integrator

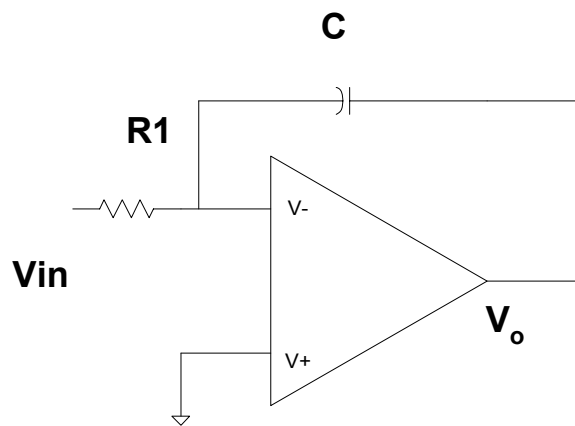

- Op-amps are frequently used as integrators. Wire up an integrator on the proto-board using a 741 op-amp. Be sure to supply power and ground.  $R1=47K$ ,  $C=0.1\mu f$
- Input a square wave to the integrator. What is the minimum frequency for which the integrator integrates? Display both the input and the output on an oscilloscope.
- Notice that for a square wave, the output voltage is proportional to the “on” time.

# Lab Exercise - Schmitt Trigger

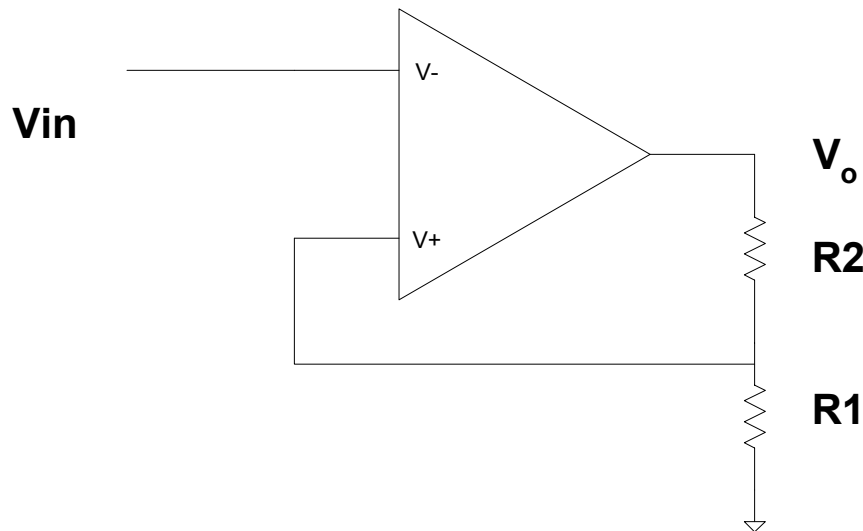

- Schmitt trigger have different triggers points for rising edge and falling edge.
- Can be used to reduce false triggering
- This is NOT a negative feedback circuit.



# Current Source

- Household application: battery charger (car, laptop, mp3 players)
- Differential amplifier current source
- Ramp waveform generator
- High Speed DA converter using capacitors
- Simple circuit: 2N5459 Nchannel JFET


$I_{DSS}$  = current with  $V_{GS}=0$

$V_P$  = pinchoff voltage
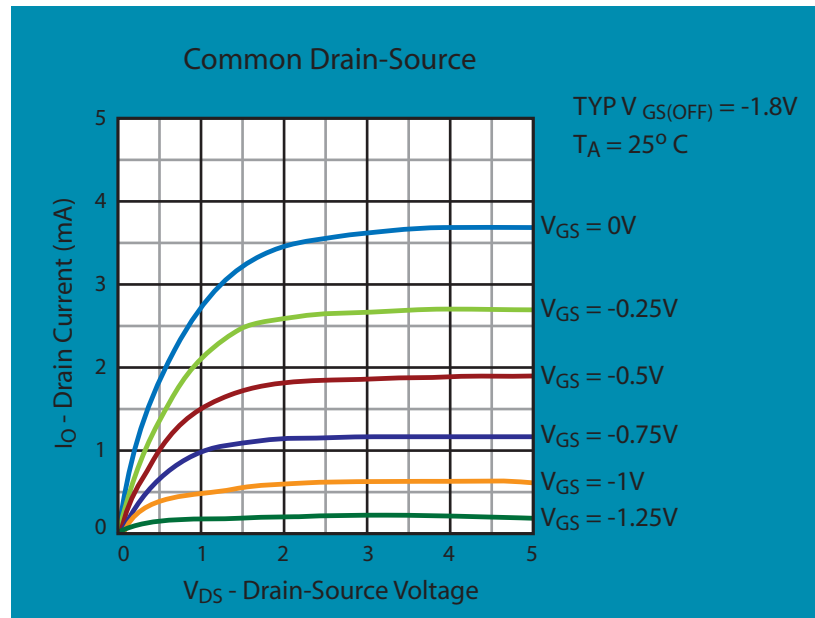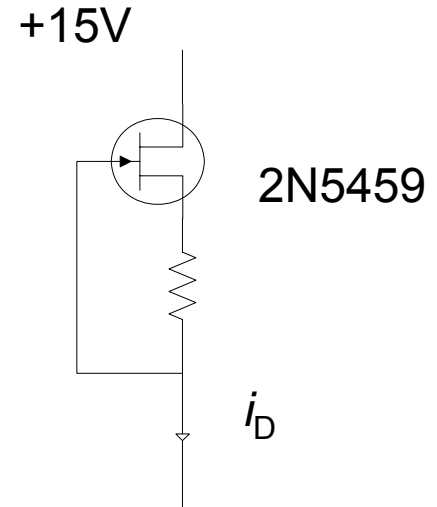
$$i_D = I_{DSS} \left( 1 - \frac{v_{GS}}{V_P} \right)^2$$



# Voltage Control Current Source\*

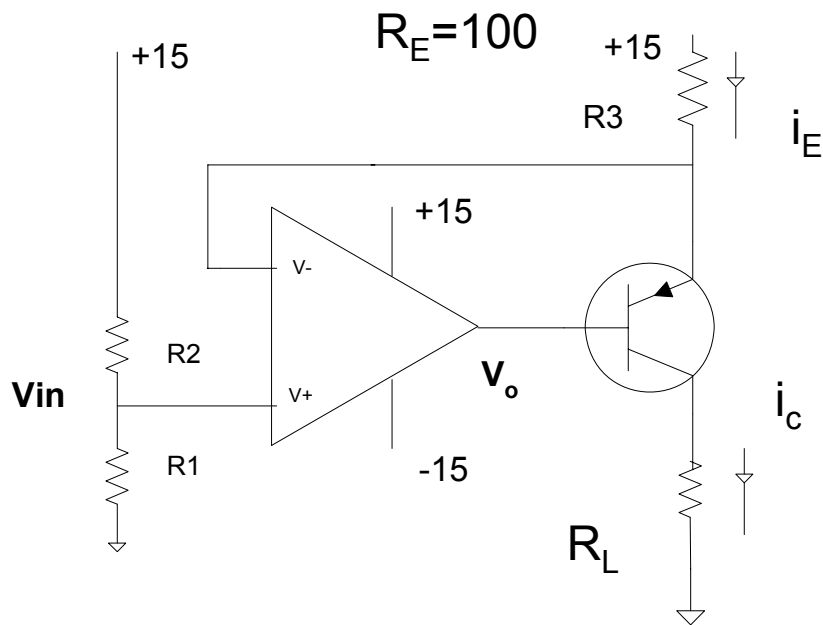

- Feedback forces  $V_+ = V_-$ .
- $R_E = 100$ ,  $\beta_F = 100$ ,  $V_{in} = 5$
- $i_E \sim i_C$
- $R_1 = 10k$ ,  $R_2 = 4.7k$ ,  
 $R_3 = 10K$ ,  $C = .33\mu f$
- $R_1$ ,  $R_2$  can be replaced with a pot.

# Lecture 2 Summary

- BJT, MOSFET
- Op Amp circuits
  - Comparator
  - Oscillator
  - Schmitt trigger
  - Current Source