
 
 




# Lab 3 Revisited

- Zener diodes

 


# Lab 3 Revisited


- Voltage regulators
- 555 timers

  
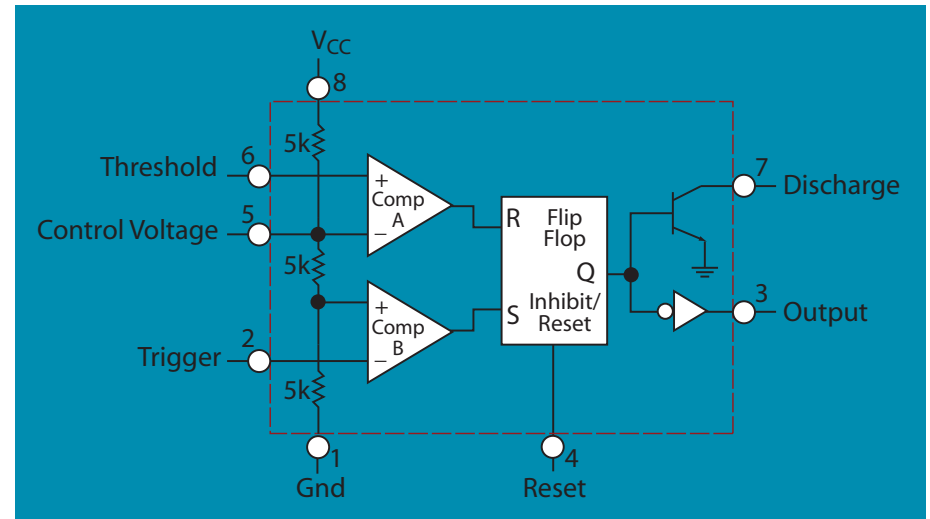
$$V_c = V_s \left( 1 - e^{-\frac{t}{RC}} \right)$$



# Closet Light Timer

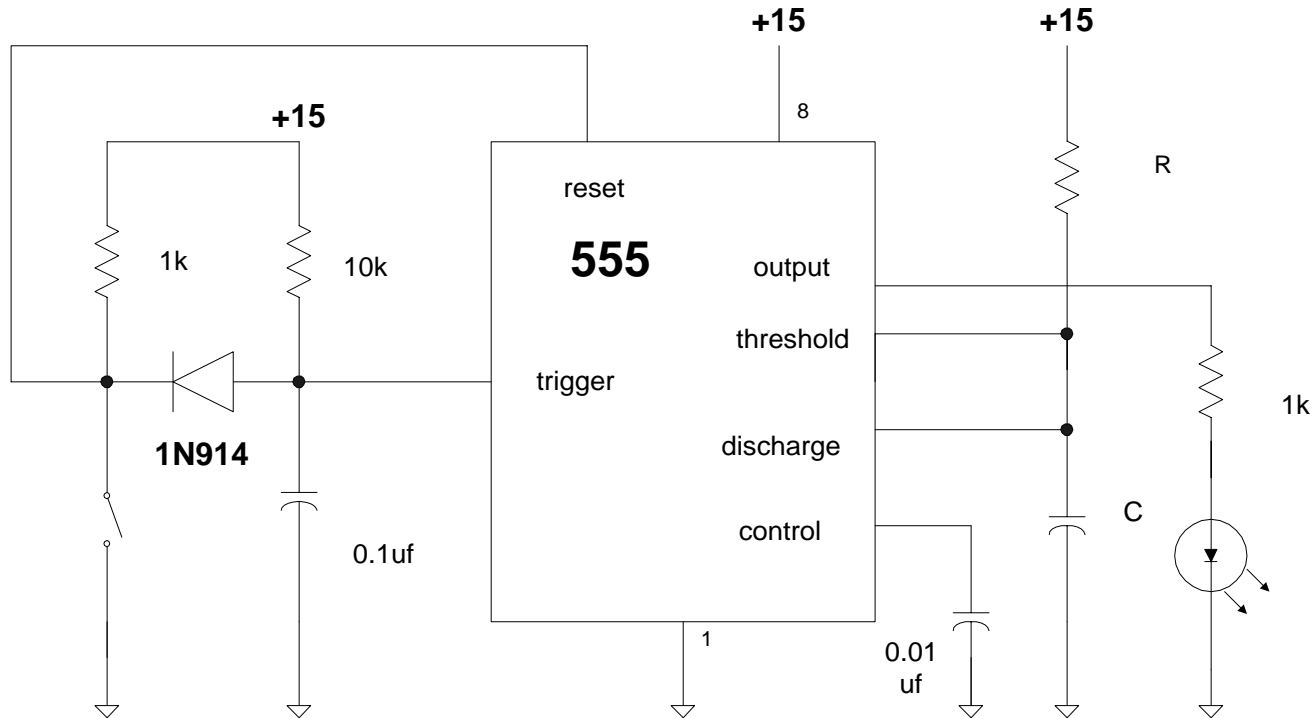


# Digital Circuits

- Real world analog signals have noise – unavoidable.
- Digital circuits offers better noise immunity.
- Use voltage to represent “0” and “1”
  - Avoid forbidden voltage zone.
  - Make standards tighter for output than for inputs.
- Data (HCMOS family): 0 (low), 1 (high)
  - Input voltage low: **0.0 – 0.7v**
  - Input voltage high: **>2.0V**
  - Output low: **<0.4v**
  - Output high: **>3.98v**
 
# Digital Circuits

HCMOS 1 (high)

- **Output high:  $>3.98\text{v}$**
- Input voltage high:  $>2.0\text{V}$




HCMOS 0 (low)

- **Output low:  $<0.4\text{v}$**
- Input voltage low:  $0.0 - 0.7\text{v}$
 
# Power Requirements

- The following power supplies are common for analog and digital circuits:
  - +5v for digital circuits,
  - +15v, -15v for analog,
  - 5v, +12v, -12v also used
  - +3.3
- Other voltages generally derived.



# Boolean Algebra

$$A B = A \& B$$

$$\overline{A} = \text{Inverse of } A$$

$$\overline{A B} = \text{Inverse of } [A\&B]$$

DeMorgan's Law

$$\overline{A B} = \overline{A} + \overline{B}$$

$$\overline{A + B} = \overline{A} \& \overline{B}$$




# Digital System Implementation

- Start with AND, OR, NOR, NAND gates and add more complex building blocks: registers, counters, shift registers, multiplexers. Wire up design. High manufacturing cost, low fix costs. **Examples 74LS, 74HC series IC**
- For volume production, move to PALs, FPGAs, ASICs. Low manufacturing cost, high fix costs.

# Basic Gates

**Gate**                      **Symbol**                      **Truth-Table**                      **Expression**

NAND

 

X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

$$Z = \overline{X \cdot Y}$$

Circle indicates inversion


AND



X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

$$Z = X \cdot Y$$

NOR

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

$$Z = \overline{X + Y}$$

OR




X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1

$$Z = X + Y$$

# 74LS00 NAND Gate

Dual-In-Line Package

 


This device contains four independent gates each of which performs the logic NAND function.

Figure by MIT OpenCourseWare, adapted from the National Semiconductor 54LS00 datasheet.

# 74LS02 NOR Gate

Dual-In-Line Package

 


This device contains four independent gates each of which performs the logic NOR function.

Figure by MIT OpenCourseWare, adapted from the National Semiconductor 54LS02 datasheet.

# 74LS08 AND Gate

Dual-In-Line Package

 


This device contains four independent gates each of which performs the logic AND function.

Figure by MIT OpenCourseWare, adapted from the National Semiconductor 54LS08 datasheet.

# 74LS151

## 8-1 Multiplexer

Dual-in-line Package

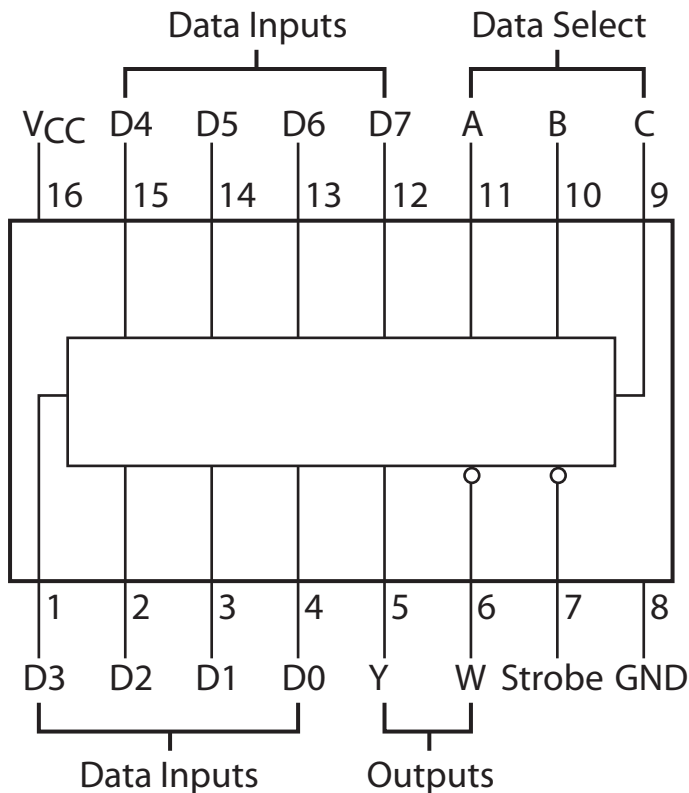


Inputs				Outputs	
Select			Strobe S	Y	W
C	B	A			
X	X	X	H	L	$\overline{D0}$
L	L	L	L	D0	$\overline{D1}$
L	L	H	L	D1	$\overline{D2}$
L	H	L	L	D2	$\overline{D3}$
L	H	H	L	D3	$\overline{D4}$
H	L	L	L	D4	$\overline{D5}$
H	L	H	L	D5	$\overline{D6}$
H	H	L	L	D6	$\overline{D7}$
H	H	H	L	D7	

H = High Level, L = Low Level, X = Don't Care  
 $\overline{D0}, \overline{D1} \text{--} \overline{D7}$  = Level of the Respective D Input


Figures by MIT OpenCourseWare.
 
# Building Logic

- From basic gates, we can build other functions: Exclusive OR Gate



X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

 

# 74LS86 Exclusive OR


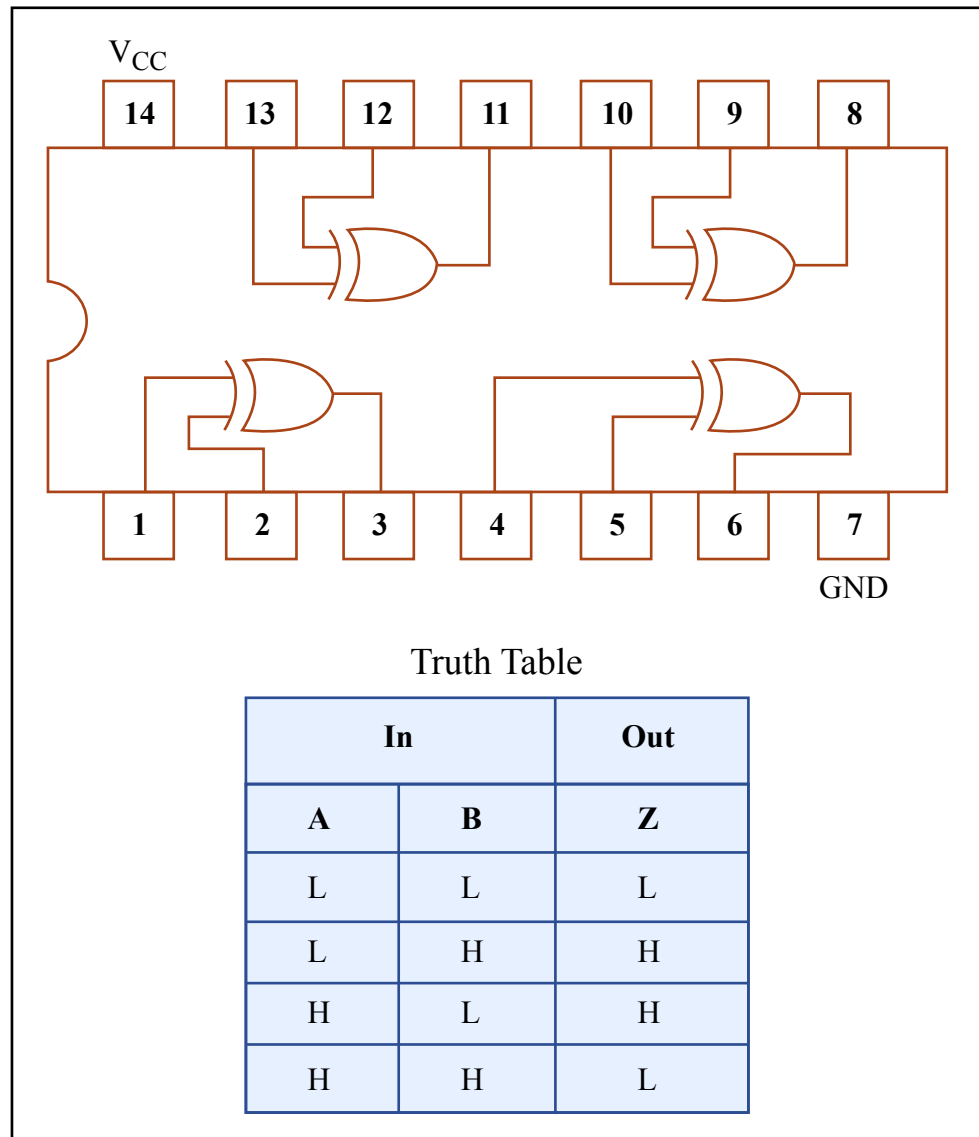


Figure by MIT OpenCourseWare, based on Motorola datasheet.

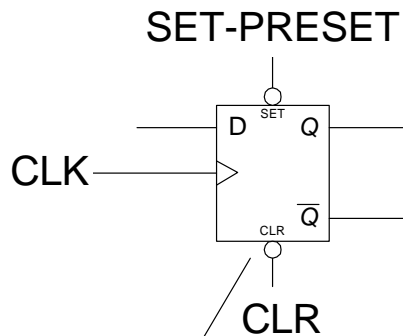

# 74LS74 D Flip Flop

Note both Q and Qbar



circle indicates inversion (active low)

Inputs				Outputs	
PR	CLR	CLK	D	Q	$\bar{Q}$
L	H	X	X	H	L
H	L	X	X	L	H
L	L	X	X	H*	H*
H	H	↑	H	H	L
H	H	↑	L	L	H
H	H	L	X	Q <sub>0</sub>	$\bar{Q}$ <sub>0</sub>

H = High Logic Level


X = Either Low or High Logic Level

L = Low Logic Level

↑ = Positive-going Transition

\* = This configuration is nonstable; that is, it will not persist when either the preset and/or clear inputs return to their inactive (high) level.

 
Reprinted with permission of National Semiconductor Corporation.




# Counters

- Ripple carry
  - Previous stage used to clock next bit;

B <sub>1</sub>	B <sub>0</sub>
0	0
0	1
1	0
1	1

 

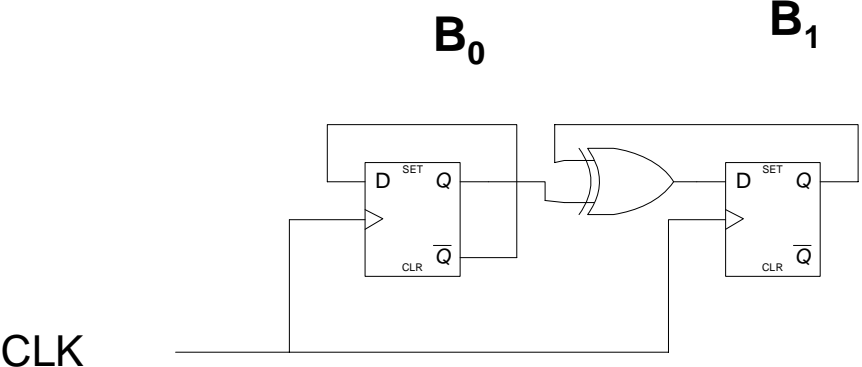- Synchronous
  - Same clock used for each bit




**Power connections not shown**

# Building a Synchronous Counter



- All bits clock on the same clock signal.
- Next count based on current count.

Power connections not shown

$B_1$	$B_0$	$B_1$ Next
0	0	0
0	1	1
1	0	1
1	1	0

 


# Shift Register

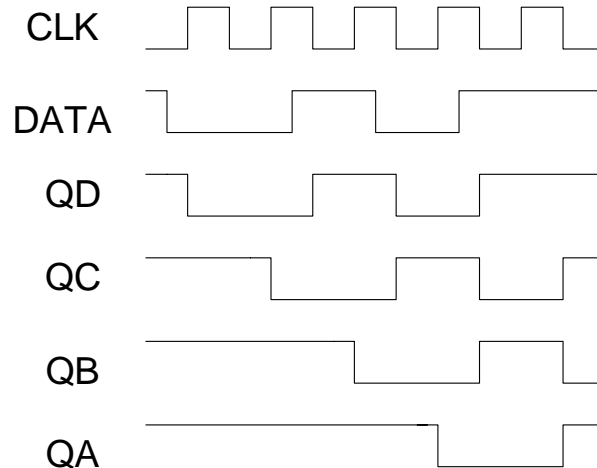 

Converts serial data to parallel data or parallel data to serial data.

# 74LS175 4 Bit Shift Register

74LS175

 

Clock and  $\overline{\text{Clear}}$  are common for all FF. The D FF will store the state of their individual D inputs on the LOW to HIGH Clock transition, causing the individual Q and  $\overline{Q}$  to follow.

A LOW input on the  $\overline{\text{Clear}}$  will force all Q outputs LOW and  $\overline{Q}$  outputs HIGH independent of Clock or Data inputs.


# Binary Numbers

- MSB – Most Significant Bit
- LSB – Least Significant Bit
- Let's build an adder:  
 $A+B=S$  where  
 $A, B, S$  are  $m$  bits wide:  
 $A: A_m A_{m-1} \dots A_1 A_0$

Dec	Binary	Hex		Dec	Binary	Hex
0	0000	0		8	1000	8
1	0001	1		9	1001	9
2	0010	2		10	1010	A
3	0011	3		11	1011	B
4	0100	4		12	1100	C
5	0101	5		13	1101	D
6	0110	6		14	1110	E
7	0111	7		15	1111	F

# Binary Adder – $m^{\text{th}}$ bit

$C_{in}$	A	B	Sum	$C_{out}$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

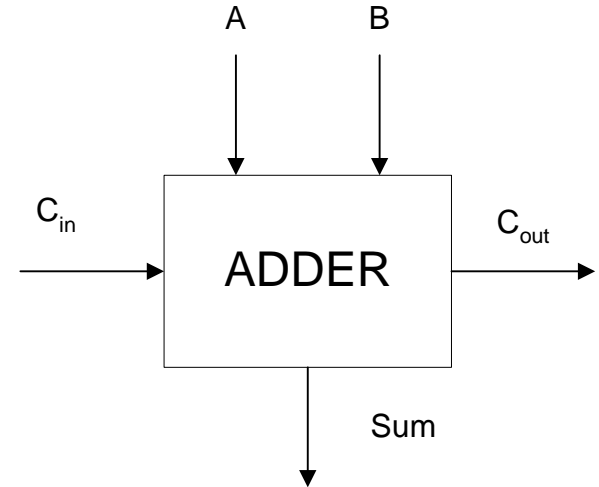

Sum =

$C_{out}$  =

# Signed Numbers – Twos Complement



- Positive Number:  
MSB=0
- Negative Number:  
MSB=1
- 4 Bit example
- Simple addition & subtraction
- Most common notation

MSB			LSB	Decimal
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	-8
1	0	0	1	-7
1	0	1	0	-6
1	0	1	1	-5
1	1	0	0	-4
1	1	0	1	-3
1	1	1	0	-2
1	1	1	1	-1



  
# Propagation Delays

- All digital logic have propagation delay
- Typical discrete logic gate propagation delay  $\sim 10\text{ns}$




# Lab Exercise Ring Oscillator

 

.


# Lab Exercise

## 4 Bit Counter – Logic Analyzer

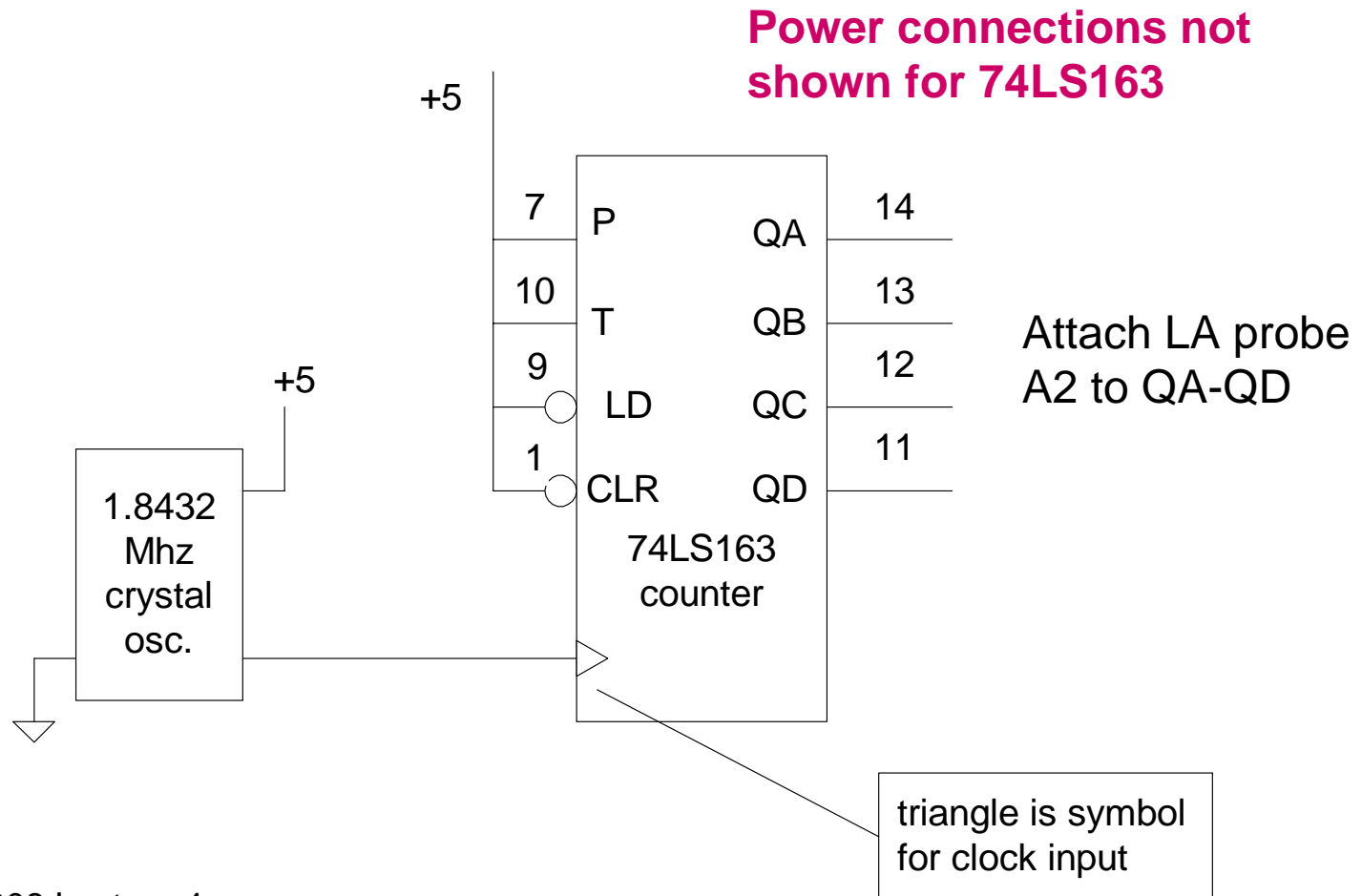


# Lab Exercise

## Ramp Generator

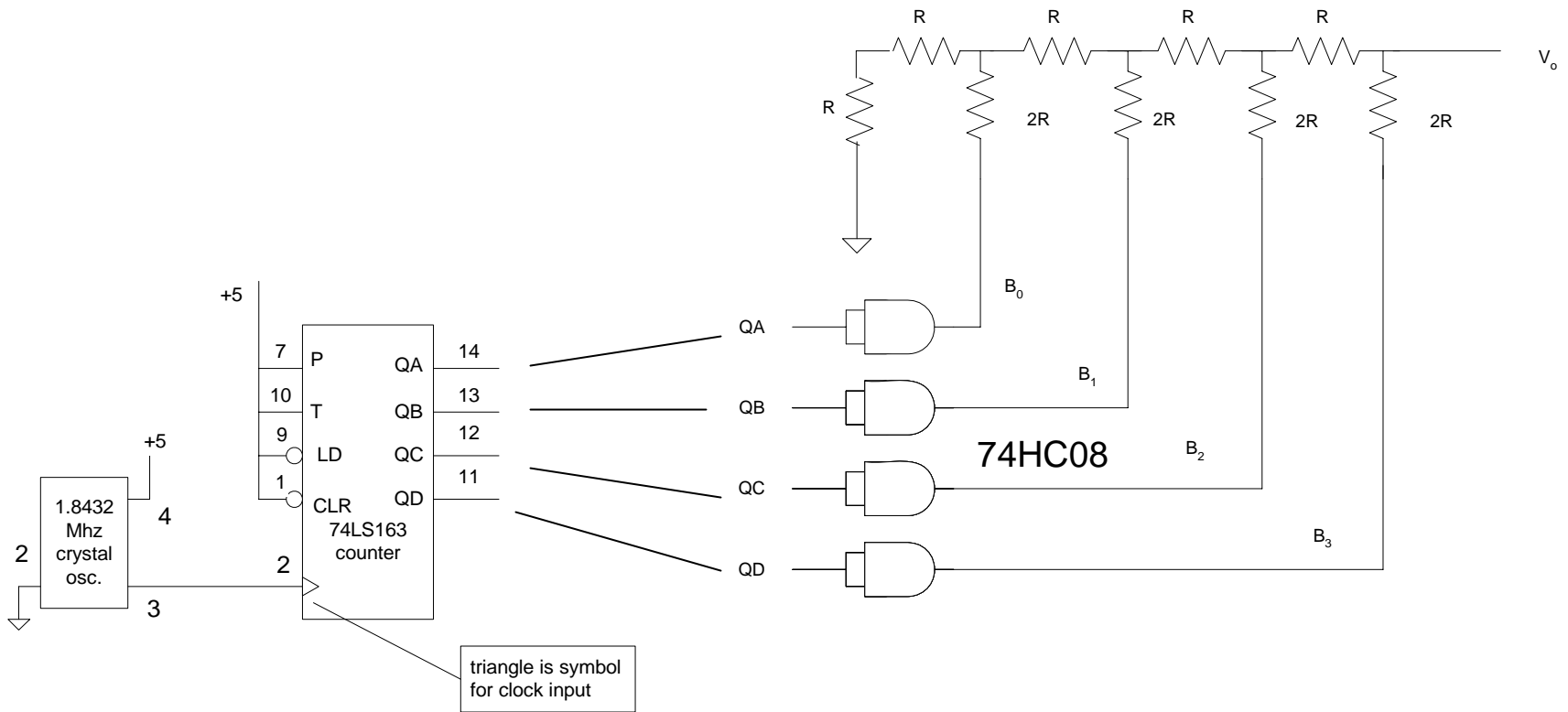


# RAMP Generator Output

 

24 Jan 2007  
16:09:07
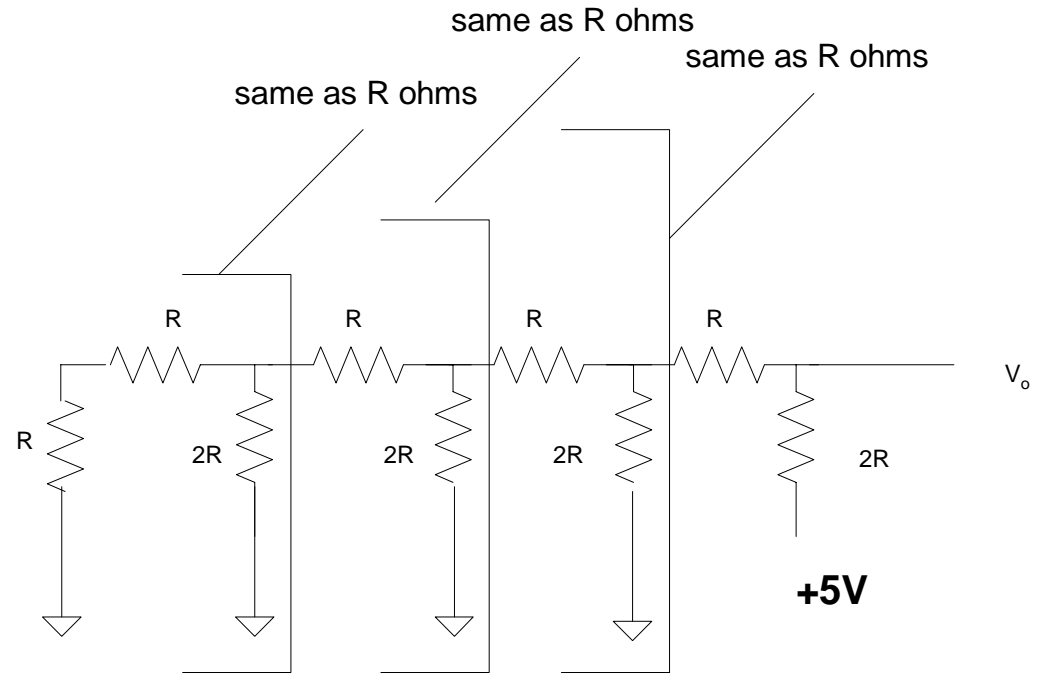
# R-2R Theory

- For linear circuits, superposition applies. Calculate contribute of bit  $n$  by setting all other inputs to zero.
- Equivalent resistance looking left or right is  $R$  ohms!
- Use Thevenin equivalent to show division by  $2^n$



# DA Summary


- Output from digital to analog conversion are discrete levels.
- More bits means better resolution.
- An example of DA conversion
  - Current audio CD's have 16 bit resolution or 65,536 possible output levels
  - New DVD audio samples at 192 khz with 24 bit resolution or  $2^{24} = 16,777,216$

# Analog to Digital Conversion (ADC)

- Successive approximate conversion steps
  - Scale the input to 0-3 volts (example)
  - Sample and hold the input
  - Internally generate and start ramp and compare
- Flash Compare
  - Compare voltage to one of  $2^n$  possible voltage levels. 8 bit ADC would have 255 comparators.
- Note that by definition, ADC have quantizing errors (number of bits resolution)



# Successive Approximation AD

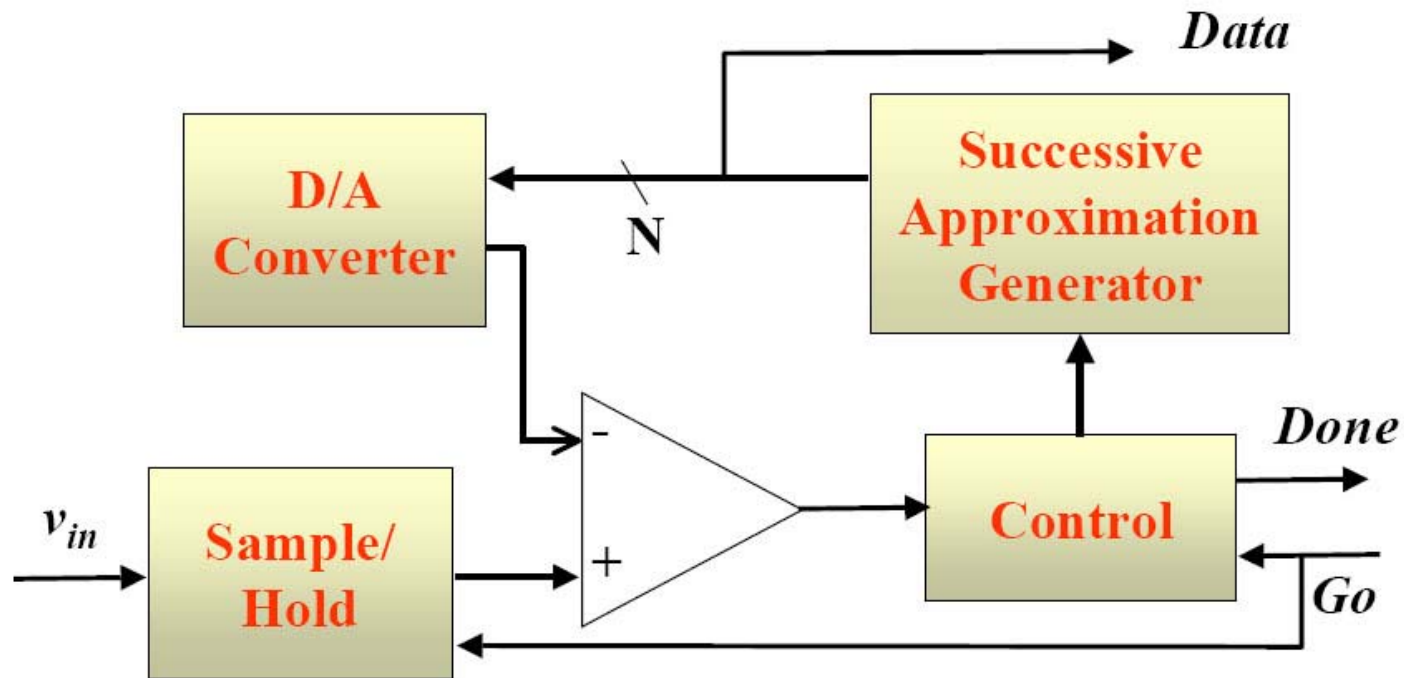

Serial conversion takes a time equal to  $N(t_{D/A} + t_{comp})$

# AD7871



LC<sup>2</sup>MOS  
Complete 14-Bit, Sampling ADCs

## AD7871/AD7872


### FEATURES

- Complete Monolithic 14-Bit ADC
- 2s Complement Coding
- Parallel, Byte and Serial Digital Interface
- 80 dB SNR at 10 kHz Input Frequency
- 57 ns Data Access Time
- Low Power—50 mW typ
- 83 kSPS Throughput Rate
- 16-Lead SOIC (AD7872)

### APPLICATIONS

- Digital Signal Processing
- High Speed Modems
- Speech Recognition and Synthesis
- Spectrum Analysis
- DSP Servo Control



### FUNCTIONAL BLOCK DIAGRAMS

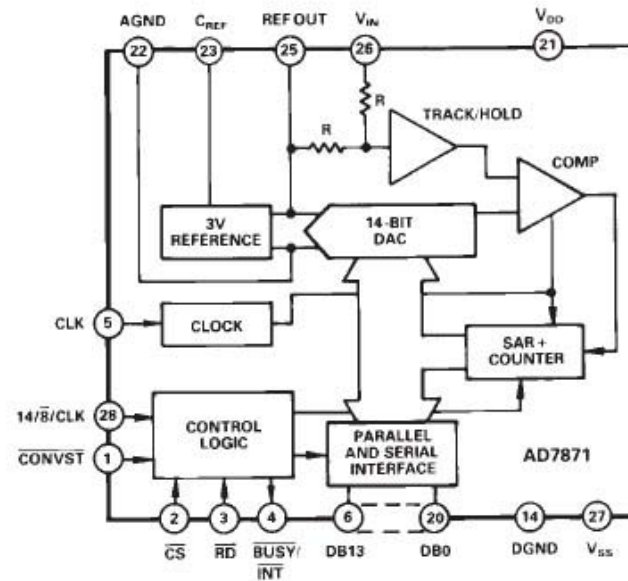

Courtesy of Analog Devices. Used with permission.

  
# Switch Bounce

- All mechanical switches have “switch bounce”



23 Jan 2007  
15:14:01

# Debounce Circuit

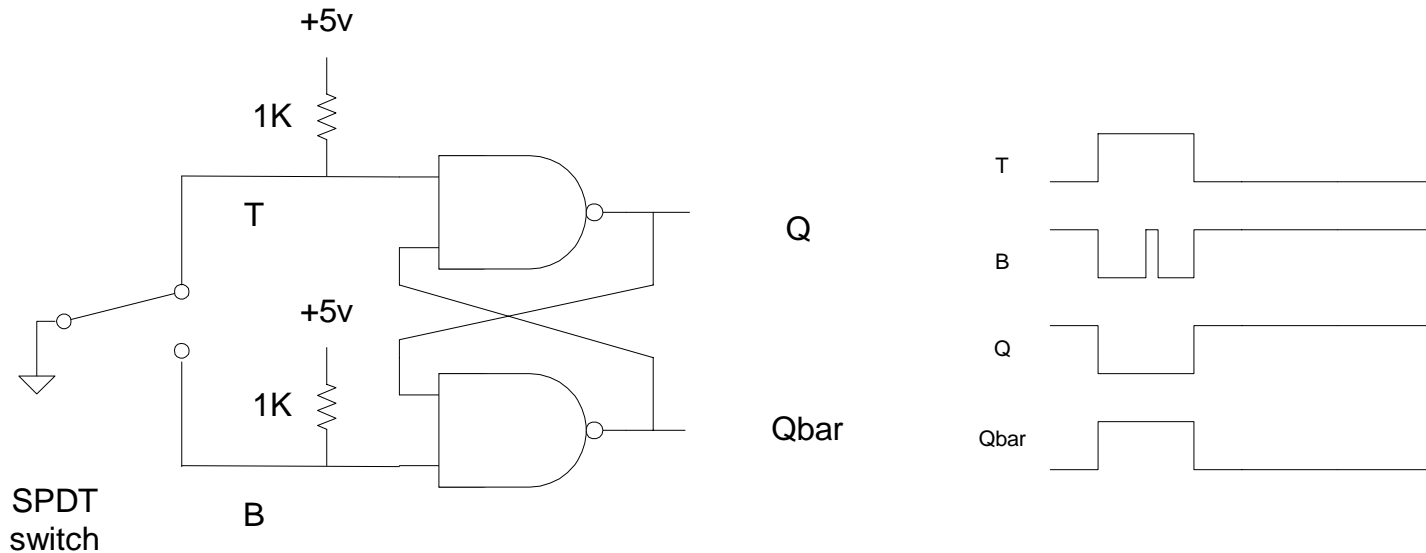

Requires SPDT switch

# Lab 4

- Use last three aisles on the left at the end of the 6.111 lab
- Pick up IC's and tools from LA's.
- Return IC's and tools to LA's at the end of the lab

# Lab 5

- Design, build and keep the electronics for a digital lock.
- Unlock key based on sequence of 0, 1.

