


Massachusetts Institute of Technology  
Department of Nuclear Science and Engineering  
Department of Electrical Engineering and Computer Science

22.071/6.071 - Introduction to Electronics, Signals and Measurement  
Spring 2006

Homework 8  
Due 4/19/06


Problem 1.

The input signal  $V_s$  is a sinusoid with an amplitude of 10 Volts and a frequency of 1kHz. Determine the output waveform  $V_o$  (shape and relevant values)

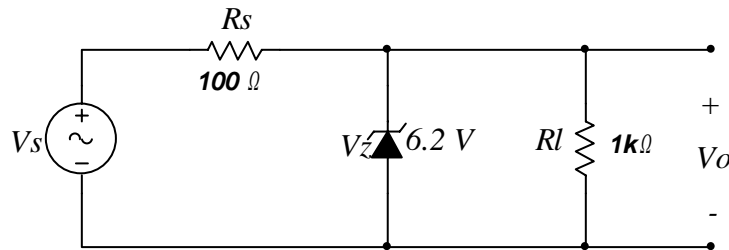

Problem 2.


For this circuit  $C=47\mu\text{F}$ ,  $R=20\text{k}\Omega$  and the on resistance of the diode is  $30\Omega$ . Determine the charge and discharge times of the capacitor.

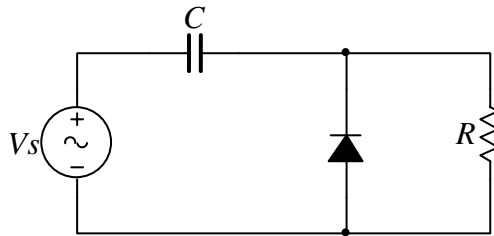

Problem 3.


The input signal  $V_i$  is a sinusoid with an amplitude of 20 Volts. For the diode assume  $V_g=0$  Volts. All resistors are equal to  $10k\Omega$ .

Determine the output signal  $V_o$ . Does the frequency of  $V_i$  matter?

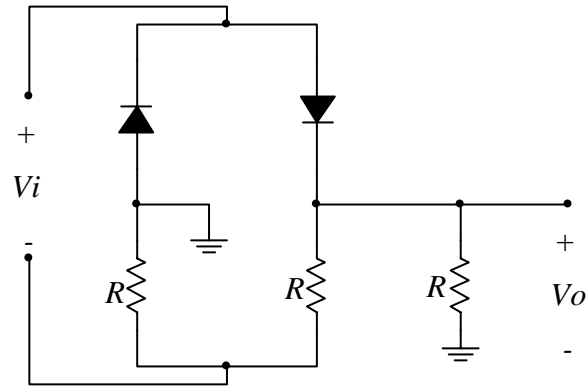

Problem 4.

For the following circuit,

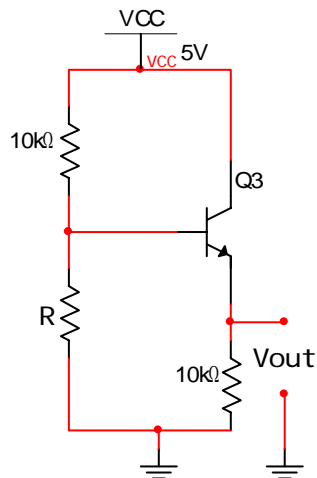

Determine the value of resistor  $R$  so that  $V_{out} = 2V$