

**Tutorial #7**

1. Design Project Discussion
  - (a) Where should you start? From the input? Or from the output?
  - (b) What does Stage 1 do? What is the input? What is the output? What should nodes N1, N2, and N3 look like?
  - (c) What does Stage 2 do? What is an XOR gate?
  - (d) What does Stage 3 do? What is a buffer?

MIT OpenCourseWare  
<http://ocw.mit.edu>

6.012 Microelectronic Devices and Circuits  
Spring 2009

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.